

1. For  $A = \begin{bmatrix} 1 & \tan x \\ -\tan x & 1 \end{bmatrix}$ , the determinant of  $A^T A^{-1}$  is

A.  $\sec^2 x$  B.  $\cos 4x$   
C. 1 D. 0

Answer ||| A

Solution ||| Correct option is (A).

$$A = \begin{bmatrix} 1 & \tan x \\ -\tan x & 1 \end{bmatrix}$$

$$A^T = \begin{bmatrix} 1 & -\tan x \\ \tan x & 1 \end{bmatrix}$$

$$|A| = 1 + \tan^2 x = \sec^2 x$$

$$A^{-1} = \frac{1}{|A|} \begin{bmatrix} 1 & -\tan x \\ \tan x & 1 \end{bmatrix}$$

$$A^T A^{-1} = \frac{1}{|A|} \begin{bmatrix} 1 & -\tan x \\ \tan x & 1 \end{bmatrix} \begin{bmatrix} 1 & -\tan x \\ \tan x & 1 \end{bmatrix}$$

$$= \frac{1}{\sec^2 x} \begin{bmatrix} 1 - \tan^2 x & -2 \tan x \\ 2 \tan x & 1 - \tan^2 x \end{bmatrix}$$

$$|A^T A^{-1}| = \frac{1}{\sec^2 x} [(1 - \tan^2 x)^2 + 4 \tan^2 x]$$

$$= \frac{1}{\sec^2 x} [1 + \tan^4 x - 2 \tan^2 x + 4 \tan^2 x]$$

$$= \frac{1}{\sec^2 x} [1 - \tan^4 x + 2 \tan^2 x]$$

$$= \frac{1}{\sec^2 x} [(1 - \tan^2 x)^2]$$

$$= \frac{[\sec^2 x]^2}{\sec^2 x} = \sec^2 x$$

2. The contour on the x-y plane, where the partial derivative of  $x^2 + y^2$  with respect to y is equal to the partial derivative of  $6y + 4x$  with respect to x, is

A.  $y = 2$  B.  $x = 2$   
C.  $x + y = 4$  D.  $x - y = 0$

Answer ||| A

Solution ||| Correct option is (A).

Given

Partial derivative of  $(x^2 + y^2)$  with respect to y  
= partial derivative of  $(6y + 4x)$  with respect to x  
 $0 + 2y = 0 + 4$

$$\text{So, } 2y = 4$$

$$y = 2$$

3. If C is a circle of radius r with centre  $z_0$ , in the complex z-plane and if n is a non-zero integer, then

$$\oint_C \frac{dz}{(z - z_0)^{n+1}}$$

A.  $2\pi nj$  B. 0  
C.  $\frac{nj}{2\pi}$  D.  $2\pi n$

Answer ||| B

Solution ||| Correct option is (B).

By the residue theorem,

$$\oint_C \frac{f(z)}{(z - z_0)^{n+1}} dz = 2\pi j \times (\text{residue at that point})$$

$$\text{where Residue} = \lim_{z \rightarrow z_0} \frac{1}{n!} \frac{d^n f(z)}{dz^n}$$

From given question  $f(z) = 1$

So, residue = 0

$$\text{Hence, } \oint_C \frac{dz}{(z - z_0)^{n+1}} = 0$$

4. Consider the function  $g(t) = e^{-t} \sin(2\pi t) u(t)$  where  $u(t)$  is the unit step function. The area under  $g(t)$  is \_\_\_\_\_

A. 2.5 B. 2 C. 0.155 D. 1.45

Answer ||| C

Solution ||| Correct answer is 0.155

Given  $g(t) = e^{-t} \sin(2\pi t) u(t)$

Taking the Laplace transform

$$G(s) = \frac{2\pi}{(3+1)^2 + (2\pi)^2}$$

From definition of Laplace transform

$$G(s) = \int_{-\infty}^{\infty} g(t) e^{-st} dt$$

So,  $G(0) = \int_{-\infty}^{\infty} g(t) dt = \text{area under the curve } g(t)$

(taking  $s = 0$ )

$$G(0) = \frac{2\pi}{1 + (2\pi)^2} = 0.155$$

5. The value of  $\sum_{n=0}^{\infty} n \left(\frac{1}{2}\right)^n$  is \_\_\_\_\_.

A. 2 B. 6 C. 8 D. 4

Answer ||| A

Solution |||

$$\text{Let } \sum_{n=0}^{\infty} n \left(\frac{1}{2}\right)^n$$

$$= 0 + 1 \cdot \left(\frac{1}{2}\right)^1 + 2 \cdot \left(\frac{1}{2}\right)^2 + 3 \cdot \left(\frac{1}{2}\right)^3 \dots (i)$$

Multiply equation (1) by 1/2

$$\frac{S}{2} = \left(\frac{1}{2}\right)^2 + 2 \left(\frac{1}{2}\right)^3 + 3 \left(\frac{1}{2}\right)^4 \dots (ii)$$

Subtracting equation (2) from (1)


$$S - \frac{S}{2} = \frac{1}{2} + \left(\frac{1}{2}\right)^2 (2-1) + \left(\frac{1}{2}\right)^3 (3-2)$$

$$\frac{S}{2} = \frac{1}{2} + \left(\frac{1}{2}\right)^2 + \left(\frac{1}{2}\right)^3 + \left(\frac{1}{2}\right)^4 \dots (\text{sum of GP} = \frac{a}{1-r})$$

$$\frac{S}{2} = \frac{\frac{1}{2}}{1 - \frac{1}{2}} = 1$$

$$\text{Hence, } S = 2$$

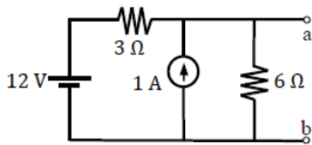6. For the circuit shown in the figure, the Thevenin equivalent voltage (in Volts) across terminals a-b is \_\_\_\_\_




A. 45 B. 50 C. 10 D. 30

Answer ||| C

Solution ||| Correct answer is 10.

Given circuit is

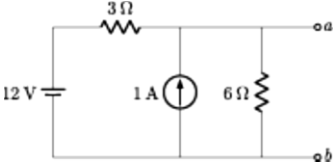


Apply KCL at node A,

$$1A = \frac{12 - V_A}{3} + \frac{V_A}{6}$$

$$1 = \frac{12 - V_A}{3} + \frac{V_A}{6}$$

$$V_A = 10V$$

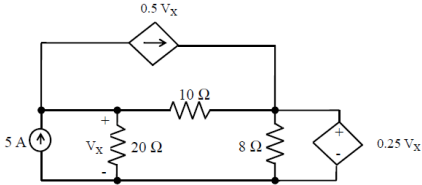
7. In the circuit shown, the voltage  $V_x$  (in Volts) is \_\_\_\_\_



A. 4 B. 8 C. 10 D. 20

Answer ||| B

Solution ||| Correct answer is 8.

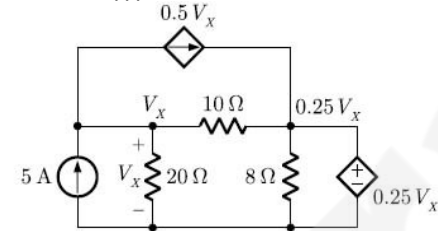


Applying KCL at node  $V_x$ ,

$$\frac{V_x}{20} + \frac{V_x - 0.25V_x}{10} + 0.5V_x = 5$$

$$V_x \left( \frac{1}{20} + \frac{0.75}{10} + 0.5 \right) = 5$$

$$V_x = 8V$$

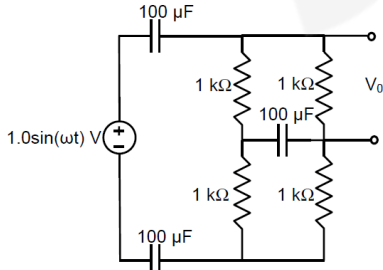8. At very high frequencies, the peak output voltage  $V_0$  (in Volts) is \_\_\_\_\_.



A. 0.5 B. 0.333 C. 1.5 D. 5


Answer ||| A

Solution ||| Correct answer is 0.5

At very high frequencies capacitors acts short circuit

because  $Z_C = \frac{1}{j\omega C}$  and at  $\omega \rightarrow \infty$ ,  $Z_C \rightarrow 0$

So, the circuit reduces to

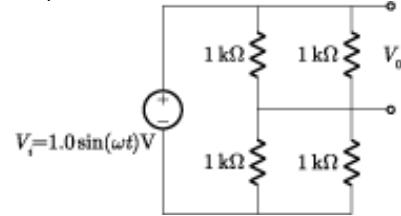

By voltage division rule,

$$V_0 = \left( \frac{1K}{1K + 1K} \right) V_i$$

$$V_0 = \frac{V_i}{2} = \frac{1.0 \sin \omega t}{2}$$

At peak voltage,  $\sin \omega t = 1$

Hence,  $V_0 = 0.5V$

9. Which one of the following process is preferred to form the gate dielectric ( $\text{SiO}_2$ ) of MOSFETs?

- A. Sputtering
- B. Molecular beam epitaxy
- C. Wet oxidation
- D. Dry oxidation

Answer ||| D

Solution ||| Correct option is (D).

Dry oxidation is better than wet oxidation, so dry oxidation is always preferred.

10. If the base width in a bipolar junction transistor is doubled, which one of the following statements will be TRUE?


- A. Current gain will increase
- B. Unity gain frequency will increase
- C. Emitter-base junction capacitance will increase
- D. Early voltage will increase

Answer ||| D

Solution ||| Correct option is (D).

On increasing the base width slope of the  $I_C$  vs  $V_{CE}$  curve decreases due to less  $(I_C)$ . Hence, decrease in slope means increase in early effect. So, early voltage will increase.

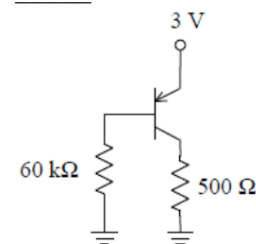11. In the circuit shown in the figure, the BJT has a current gain ( $\beta$ ) of 50. For an emitter-base voltage  $V_{EB} = 600 \text{ mV}$ , the emitter-collector voltage  $V_{EC}$  (in Volts) is \_\_\_\_\_.



A. 2.5 B. 2 C. 3 D. 5

Answer ||| B

Solution ||| Correct answer is 2.

$$V_{EB} = 0.6V (= 50) \quad (\beta = 50)$$

$$V_E - V_B = 0.6V$$

$$V_E = 3V \text{ (given)}$$

$$\text{So, } 3 - V_B = 0.6V$$

$$V_B = 2.44$$

$$I_B = \frac{V_B}{60k}$$

$$= \frac{2.4}{60} \text{ mA}$$

$$I_C = \beta I_B$$

$$= 50 \times \left( \frac{2.4}{60} \right) \text{ mA}$$

$$= \left( \frac{2.4}{60} \right) 5 \text{ mA}$$


$$V_C = (500\Omega) \left( \frac{2.4}{60} \right) (5) \times 10^{-3} V$$

$$= 1V$$

$$\text{Hence, } V_{EC} = V_E - V_C = 3 - 1 = 2V$$

$$= 2V$$

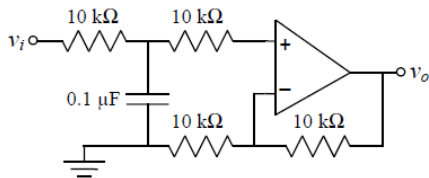12. In the circuit using an ideal opamp, the 3-dB cut-off frequency (in Hz) is \_\_\_\_\_.



A. 159.23 B. 158.25 C. 165.55 D. 151.22

Answer ||| A


Solution ||| Correct answer is 159.23

$$f_{3dB} = \frac{1}{2\pi RC} \quad (R = 10 \text{ k and } C = 0.1 \mu F)$$

$$= \frac{1}{2\pi (10) \times 10^3 \times 0.1 \times 10^{-6}}$$

$$= 159.23$$

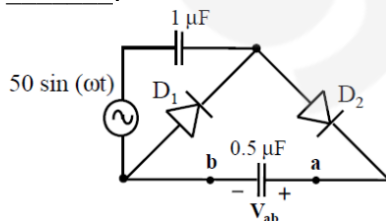13. In the circuit shown, assume that diodes  $D_1$  and  $D_2$  are ideal. In the steady state condition, the average voltage  $V_{ab}$  (in Volts) across the  $0.5 \mu F$  capacitor is \_\_\_\_\_.



A. 200 B. 300 C. 100 D. 400

Answer ||| C

Solution ||| Correct answer is 100.

For positive half cycle, diode  $D_2$  will be ON. So, peak voltage at point  $a$  is


$$V_a = 50V$$

For negative half cycle, diode  $D_1$  will be ON. So, peak voltage at point  $b$  is

$$V_b = -50V$$

$$\text{Hence } V_{ab} = V_a - V_b \\ = 50 - (-50) = 100V$$

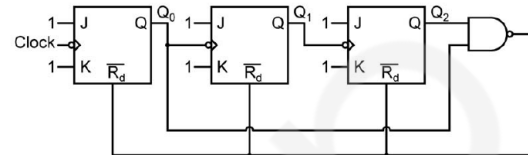14. The circuit shown consists of J-K flip-flops, each with an active low asynchronous reset ( $\overline{R_d}$  input). The counter corresponding to this circuit is



- A. a modulo-5 binary up counter
- B. a modulo-6 binary down counter
- C. a modulo-5 binary down counter
- D. a modulo-6 binary up counter

Answer ||| A

Solution ||| Correct option is (A).


From the figure, it can be seen it is basic modulo UP counter configuration because clock is negative edge triggering.

At Modulo-5

1 0 1

For this state, all the 3 flip flops will be set to initial condition.

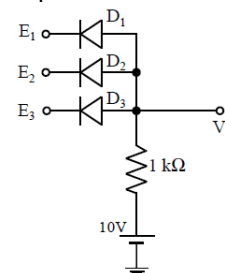15. In the circuit shown diodes  $D_1$ ,  $D_2$  and  $D_3$  are ideal, and the inputs  $E_1$ ,  $E_2$  and  $E_3$  are "0 V" for logic '0' and "10 V" for logic '1'. What logic gate does the circuit represent?



- A. 3-input OR gate
- B. 3-input NOR gate
- C. 3-input AND gate
- D. 3-input XOR gate

Answer ||| C

Solution ||| Correct option is (C).

If any of the inputs from  $E_1$ ,  $E_2$ ,  $E_3$  is logic 0 (means 0V) then the corresponding diode will be "ON" resulting in 0V at the output and only when all the inputs are logic 1 (means  $V_{DD}$ ) then  $V_o$  (output voltage) will be high, hence, resulting into 3 input AND-gate. Truth table for the logic circuit is shown below.

| $E_1$ | $E_2$ | $E_3$ | $V_0$ |
|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     |
| 0     | 0     | 1     | 0     |
| 0     | 1     | 0     | 0     |
| 0     | 1     | 1     | 0     |
| 1     | 0     | 0     | 0     |
| 1     | 0     | 1     | 0     |
| 1     | 1     | 0     | 0     |
| 1     | 1     | 1     | 1     |

16. Which one of the following 8085 microprocessor programs correctly calculates the product of two 8-bit numbers stored in register B and C?

- |            |            |
|------------|------------|
| MVI A, 00H | MVI A, 00H |
| JNZ LOOP   | CMP C      |
| CMP C      | LOOP DCR B |
| LOOP DCR B | JNZ LOOP   |
| HLT        | HLT        |
- 
- |            |            |
|------------|------------|
| MVI A, 00H | MVI A, 00H |
| LOOP ADD C | ADD C      |
| DCR B      | JNZ LOOP   |
| JNZ LOOP   | LOOP INR B |
| HLT        | HLT        |

Answer ||| C

Solution ||| Correct option is (C).

We check the given options.

The codes given in option (C), executes the following instructions

MVI A 00H (loading the accumulator with 00H)  
 LOOP ADD C (adding the contents of C to accumulator and store it to accumulator)  
 DCR B (Decrementing the content of registers B)  
 JNZ LOOP  
 HLT

Hence, decreasing the number in B as many-time as adding the another number C will result in product of two numbers till value in registers B is zero.

17. The impulse response of an LTI system can be obtained by

- A. differentiating the unit ramp response  
 B. differentiating the unit step response  
 C. integrating the unit ramp response  
 D. integrating the unit step response

Answer ||| B

Solution ||| Correct option is (B).

By property from LTI systems

$$h(t) = \frac{d(s(t))}{dt}$$

$h(t)$  = impulse response

$s(t)$  = step response

18. Consider a four-point moving average filter defined by the equation  $y[n] = \sum_{i=0}^3 \alpha_i x[n-i]$ . The condition on

the filter coefficients that results in a null at zero frequency is

- A.  $\alpha_1 = \alpha_2 = 0; \alpha_0 = -\alpha_3$   
 B.  $\alpha_1 = \alpha_2 = 1; \alpha_0 = -\alpha_3$   
 C.  $\alpha_0 = \alpha_3 = 0; \alpha_1 = \alpha_2$   
 D.  $\alpha_1 = \alpha_2 = 0; \alpha_0 = \alpha_3$

Answer ||| A

Solution ||| Correct option is (A).

$$\text{Given } y[n] = \sum_{i=0}^3 \alpha_i x[n-i]$$

Taking the DTFT (Discrete time fourier transform),

$$Y(e^{j\Omega}) = \alpha_0 X(e^{j\Omega}) + \alpha_1 (e^{j\Omega})^{-1} X(e^{j\Omega}) + \alpha_2 (e^{j\Omega})^{-2} X(e^{j\Omega}) + \alpha_3 (e^{j\Omega})^{-3} X(e^{j\Omega})$$

$$Y(e^{j\Omega}) = (\alpha_0 + \alpha_1 e^{-j\Omega} + \alpha_2 e^{-j2\Omega} + \alpha_3 e^{-j3\Omega}) X(e^{j\Omega})$$

$$\text{or } \frac{Y(e^{j\Omega})}{X(e^{j\Omega})} = H(e^{j\Omega}) = \alpha_0 + \alpha_1 (e^{j\Omega})^{-1} + \alpha_2 (e^{j\Omega})^{-2} + \alpha_3 (e^{j\Omega})^{-3}$$

At zero frequency, put  $\Omega = 0$


$$H(e^{j0}) = \alpha_0 + \alpha_1 + \alpha_2 + \alpha_3$$

It should be null.

For  $H(e^{j0}) = 0$ , only condition required is

$$\alpha_1 = \alpha_2 = 0; \alpha_0 = -\alpha_3$$

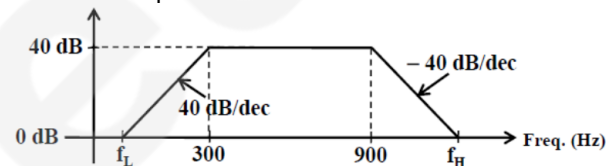19. Consider the Bode plot shown in the figure. Assume that all the poles and zeros are real-valued.



The value of  $f_H - f_L$  (in Hz) is \_\_\_\_\_.

- A. 8050 B. 7060  
 C. 8060 D. 8970

Answer ||| D

Solution ||| Correct answer is 8970.

For  $f_L$ , equating the slope,

$$40 = \frac{40 - 0}{\log_{10}(300) - \log_{10}(f_L)}$$

$$= \log_{10} \left( \frac{300}{f_L} \right) = 1$$

$$= \frac{300}{f_L} = 10$$

$$f_L = 30 \text{ Hz}$$

For  $f_H$ , equating the slope

$$-40 = \frac{0 - 40}{\log_{10} f_H - \left( \frac{\log}{900} \right)}$$

$$\log_{10} \left( \frac{f_H}{900} \right) = 1$$

$$f_H = 900 \times 10 = 9000$$

$$\text{Hence, } f_H - f_L = 9000 - 30 = 8970 \text{ Hz}$$

20. The phase margin (in degrees) of the system  $G(s) =$

$$\frac{10}{s(s+10)} \text{ is } \underline{\hspace{2cm}}.$$

- A.  $25^\circ$  B.  $84.28^\circ$  C.  $82.84^\circ$  D.  $90^\circ$

Answer ||| B

Solution ||| Correct answer is  $84.28^\circ$ .

To find PM, we need to find gain cross over frequency  $\omega_g$

At  $\omega = \omega_g$ ,

$$|G(s)| = 1$$

$$\text{So, } \left| \frac{10}{\omega_g \sqrt{\omega_g^2 + 100}} \right| = 1$$

$$10 = \omega_g \sqrt{\omega_g^2 + 100}$$

Squaring both side,

$$100 = \omega_g^2 (\omega_g^2 + 100)$$

$$100 = \omega_g^4 + 100\omega_g^2$$

$$\omega_g^4 + 100\omega_g^2 - 100 = 0$$

Accepted value,  $\omega_g^2 = 3.98$

$$\omega_g \approx 2 \text{ rad/sec}$$

Hence,  $PM = 180^\circ + \angle G(j\omega)$

$$= 180^\circ - 90^\circ - \tan^{-1} \left( \frac{\omega_g}{10} \right)$$

$$= 90^\circ - \tan^{-1} \left( \frac{2}{10} \right) = 84.28^\circ$$

21. The transfer function of a first-order controller is given as

$$G_C(s) = \frac{K(s+a)}{s+b}$$


Where K, a and b are positive real numbers. The condition for this controller to act as a phase lead compensator is

- A.  $a < b$  B.  $a > b$   
C.  $K < ab$  D.  $K > ab$

Answer ||| A

Solution ||| Correct option is (A).

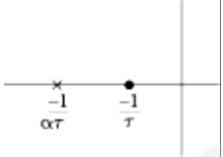The pole zero plot of lead compensator is shown below.



By comparing it to the given problem, we get

$$\frac{1}{\tau} = a$$

$$\frac{1}{\alpha\tau} = b$$

$$\text{So, } \frac{a}{b} = \alpha$$

For lead compensator,  
 $\alpha < 1$

$$\frac{a}{b} < 1$$

$$a < b$$

22. The modulation scheme commonly used for transmission from GSM mobile terminals is

- A. 4-QAM

B. 16-PSK

C. Walsh-Hadamard orthogonal codes

D. Gaussian Minimum Shift Keying (GMSK)

Answer ||| D

Solution ||| Correct option is (D).

Gaussian Minimum Shift Keying (GMSK) is used for GSM mobile terminals.

23. A message signal  $m(t) = A_m \sin(2\pi f_m t)$  is used to modulate the phase of a carrier  $A_c \cos(2\pi f_c t)$  to get the modulated signal  $y(t) = A_c \cos(2\pi f_c t + m(t))$ . The bandwidth of  $y(t)$

A. depends on  $A_m$  but not on  $f_m$

B. depends on  $f_m$  but not on  $A_m$

C. depends on both  $A_m$  and  $f_m$

D. does not depend on  $A_m$  or  $f_m$

Answer ||| C

Solution ||| Correct option is (C).

Bandwidth of PM signal is given by

$$B = 2(\Delta f + f_m)$$

So, it depends upon  $f_m$  and

$$\Delta f = \frac{k_f m_p}{2\pi}$$

( $m_p = A_m$  = message signal amplitude)

24. The directivity of an antenna array can be increased by adding more antenna elements, as a larger number of elements

A. improves the radiation efficiency

B. increases the effective area of the antenna

C. results in a better impedance matching

D. allows more power to be transmitted by the antenna

Answer ||| B


Solution ||| As per antenna array concept,


$$D \propto \frac{4\pi}{\lambda^2} Ae$$


$$D \uparrow \Rightarrow Ae \uparrow$$


Therefore, the directivity of an antenna array can be increased by increasing the effective area of the antenna.


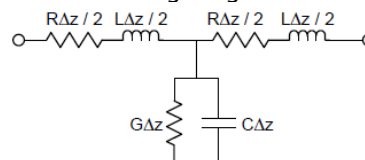
25. A coaxial cable is made of two brass conductors. The spacing between the conductors is filled with Teflon ( $\epsilon_r = 2.1$ ,  $\tan \delta = 0$ ). Which one of the following circuits can represent the lumped element model of a small piece of this cable having length  $\Delta z$ ?



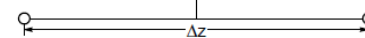A. 

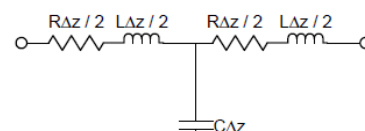

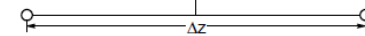B. 

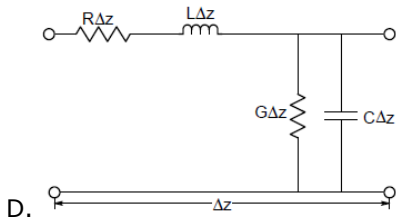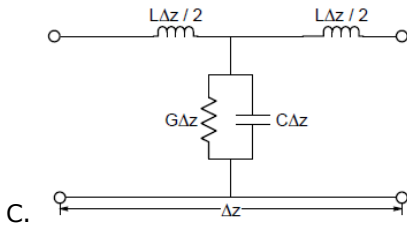

Answer ||| B

Solution ||| Correct option is (B).

Given that

$$\tan \delta = 0$$

$$\tan \delta = \text{loss tangent} = \frac{\sigma}{\omega \epsilon} = 0$$

So,  $\sigma = 0$

Hence, conductivity is

$$G = 0$$

26. The Newton-Raphson method used to solve the equation  $f(x) = x^3 - 5x^2 + 6x - 8 = 0$ . Taking the initial guess as  $x = 5$ , is \_\_\_\_\_.

A. 4.3 B. 2 C. 15 D. 15

Answer ||| A

Solution ||| Correct answer is 4.29

$$f(x) = x^3 - 5x^2 + 6x - 8$$

$$x_0 = 5 \text{ (initial point)}$$

$$f'(x) = 3x^2 - 10x + 6$$

By Newton-Raphson method,

$$x_1 = x_0 - \frac{f(x_0)}{f'(x_0)} = 5 - \frac{f(5)}{f'(5)}$$

$$\text{So, } f(5) = (5)^3 - 5(5)^2 + 6(5) - 8 = 22$$

$$f'(5) = 3(5)^2 - 10(5) + 6 = 31$$

$$\text{So, } x_1 = 5 - \frac{22}{31} = 5 - 0.7097 = 4.2903$$

27. A fair die with faces  $\{1, 2, 3, 4, 5, 6\}$  is thrown repeatedly till '3' is observed for the first time. Let  $X$  denote the number of times the die is thrown. The expected value of  $X$  is \_\_\_\_\_.

A. 4 B. 2X C. 6 D. 12

Answer ||| C

Solution ||| Correct answer is 6.

We have

$$\text{Probability of getting 3} = \frac{1}{6}$$

$$\text{Probability of not getting 3} = 1 - \frac{1}{6} = \frac{5}{6}$$

Now, the random variable  $X$  represents the number of throws required for getting 3. So,

$$X = 1, P(x = 1) = \frac{1}{6}$$

$$X = 2, P(x = 2) = \frac{5}{6} \times \frac{1}{6}$$

$$X = 3, P(x = 3) = \frac{5}{6} \times \frac{5}{6} \times \frac{1}{6}$$

$$X = 4, P(x = 4) = \frac{5}{6} \times \frac{5}{6} \times \frac{5}{6} \times \frac{1}{6}$$

$$E[X] = \sum xP(x)$$

$$= (1)\left(\frac{1}{6}\right) + (2)\left(\frac{5}{6}\right)\left(\frac{1}{6}\right) + 3\left(\frac{5}{6}\right)^2\left(\frac{1}{6}\right) + 4\left(\frac{5}{6}\right)^3\left(\frac{1}{6}\right) \dots$$

$$= \frac{1}{6} \left[ 1 + 2\left(\frac{5}{6}\right) + 3\left(\frac{5}{6}\right)^2 + 4\left(\frac{5}{6}\right)^3 \dots \right]$$

Let

$$S = 1 + 2\left(\frac{5}{6}\right) + 3\left(\frac{5}{6}\right)^2 + 4\left(\frac{5}{6}\right)^3$$

$$\left(\frac{5}{6}\right)S = \frac{5}{6} + 2\left(\frac{5}{6}\right)^2 + 3\left(\frac{5}{6}\right)^3 + 4\left(\frac{5}{6}\right)^4$$

Equation (1) - (2),

$$S - \frac{5}{6}S = 1 + \left(\frac{5}{6}\right)(2-1) + \left(\frac{5}{6}\right)^2(3-2) + \left(\frac{5}{6}\right)^3(4-3) \dots$$

$$\frac{5}{6}S = 1 + \frac{5}{6} + \left(\frac{5}{6}\right)^2 + \left(\frac{5}{6}\right)^3 \dots$$

$$\frac{5}{6}S = \frac{1}{1 - \frac{5}{6}} = 6 \text{ or } S = 36$$

Hence, the expected value of  $X$  is

$$E[X] = \frac{36}{6} = 6$$

28. Consider the differential equation

$$\frac{d^2x(t)}{dt^2} + 3\frac{dx(t)}{dt} + 2x(t) = 0.$$

Given  $x(0) = 20$  and  $x(1) = 10/e$ , where  $e = 2.718$ , the value of  $x(2)$  is \_\_\_\_\_.

A. 0 B. 2.55 C. 1.2 D. 0.856

Answer ||| D

Solution ||| Correct answer is 0.856

$$\text{Given, } \frac{d^2x(t)}{dt^2} + 3\frac{dx(t)}{dt} + 2x(t) = 0$$

$$\text{where } x(0) = 20, x(1) = \frac{10}{e}, e = 2.718$$

This is homogeneous equation. So particular solution is zero. We obtain auxiliary equation as

$$m^2 + 3m + 2 = 0$$

$$m = -1, -2$$

$$x(t) = Ae^{-t} + Be^{-2t}$$

$$x(0) = A + B = 20 \dots (1)$$

$$x(1) = Ae^{-1} + Be^{-2} = \frac{10}{e} \dots (2)$$

Solving equations (1) and (2),



$$A = \left( \frac{10e - 20}{e - 1} \right), B = \frac{10e}{e - 1}$$

$$x(t) = \left( \frac{10e - 20}{e - 1} \right) e^{-t} + \left( \frac{10e}{e - 1} \right) e^{-2t}$$

Put  $t = 2$

$$x(2) = \left( \frac{10e - 20}{e - 1} \right) e^{-2} + \left( \frac{10e}{e - 1} \right) e^{-4}$$

$$x(2) = 0.8556$$

29. A vector field  $D = 2\rho^2 a_\rho + z a_z$  exists inside a cylindrical region enclosed by the surfaces  $\rho = 1$ ,  $z = 0$  and  $z = 5$ . Let  $S$  be the surface bounding this cylindrical

region. The surface integral of this field on  $S$  is \_\_\_\_\_.

A. 56.33 B. 80.5 C. 78.00 D. 78.52

Answer ||| D

Solution ||| Correct answer is 78.52

Given vector field,

$$D = 2\rho^2 a_\rho + z a_z$$

By using divergence theorem

$$\oint_V (\nabla \cdot D) dV = \oint_S D \cdot d\mathbf{s}$$

$$\nabla \cdot D = \frac{1}{\rho} \frac{\partial}{\partial \rho} (\rho D_\rho) + \frac{1}{\rho} \frac{\partial D_\phi}{\partial \phi} + \frac{\partial D_z}{\partial z}$$


$$= \frac{1}{\rho} \frac{\partial}{\partial \rho} (\rho 2\rho^2) + 0 + 1$$

$$= \frac{1}{\rho} (2) (3) \rho^2 + 1 = 6\rho + 1$$

$$\int_V (\nabla \cdot D) dV = \int_{\rho=0}^1 \int_{\phi=0}^{2\pi} \int_{z=0}^5 (6\rho + 1) (\rho) d\rho d\phi dz$$

$$= 78.52$$

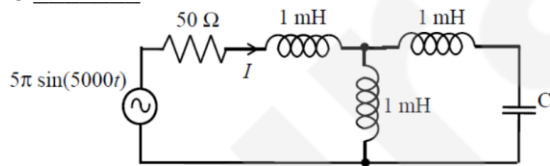30. In the circuit shown, the current  $I$  flowing through the  $50 \Omega$  resistor will be zero if the value of capacitor  $C$  (in  $\mu F$ ) is \_\_\_\_\_.




A. 10 B. 20 C. 30 D. 50

Answer ||| B

Solution ||| Correct answer is 20.

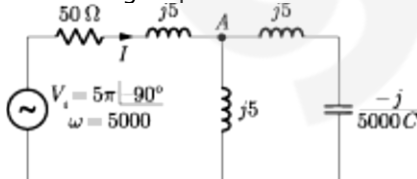Converting to phasor domain for AC analysis



If current  $I = 0$ ,

Voltage at node  $A$  = input voltage


Applying KCL at node  $A$ ,

$$\frac{V_i}{j5} + \frac{V_i}{j\left(5 - \frac{1}{5000C}\right)} = 0$$

$$\text{or } \frac{1}{j5} + \frac{-1}{j\left(5 - \frac{1}{5000C}\right)}$$

For value of  $C$ , we solve above equation. Hence,  
 $C = 20 \mu F$

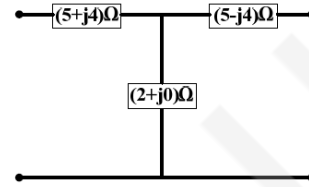31. The ABCD parameters of the following 2-port network are



$$\text{A. } \begin{bmatrix} 3.5 + j2 & 20.5 \\ 20.5 & 3.5 - j2 \end{bmatrix} \quad \text{B. } \begin{bmatrix} 3.5 + j2 & 30.5 \\ 0.5 & 3.5 - j2 \end{bmatrix}$$

$$\text{C. } \begin{bmatrix} 10 & 2 + j0 \\ 2 + j0 & 10 \end{bmatrix} \quad \text{D. } \begin{bmatrix} 7 + j4 & 0.5 \\ 30.5 & 7 - j4 \end{bmatrix}$$


Answer ||| B

Solution ||| Correct option is (B).

ABCD parameters are defined as

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$
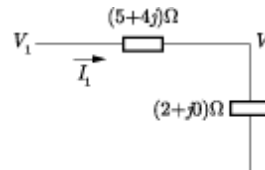
$$\begin{bmatrix} 3.5 + j2 & 30.5 \\ 0.5 & 3.5 - j2 \end{bmatrix} \quad \begin{matrix} V_1 = A V_2 - B I_2 \\ I_1 = C V_2 - D I_2 \end{matrix}$$



From the circuit,

$$A = \frac{V_1}{V_2}$$

$$V_2 = \frac{2}{7 + 4j} V_1$$

$$\frac{V_1}{V_2} = A = \frac{7 + 4j}{2} = 3.5 + 2j$$

$$\frac{I_1}{V_2} = C$$

$$I_1 = \frac{V_1}{7 + 4j}$$

$$V_2 = \left( \frac{2}{7 + 4j} \right) V_1$$

$$V_2 = \left( \frac{2}{7 + 4j} \right) (I_1)(7 + 4j)$$

$$\frac{I_1}{V_2} = 0.5 = C$$

Similarly, we may obtain other parameters. The value of parameter C satisfies the option B. only. So, the ABCD parameters are

$$\begin{bmatrix} 3.5 + j2 & 30.5 \\ 0.5 & 3.5 - j2 \end{bmatrix}$$

32. A network is described by the state model as

$$x_1 = 2x_1 - x_2 + 3u$$

$$x_2 = -4x_2 - u$$

$$y = 3x_1 - 2x_2$$

The transfer function  $H(s) \left( = \frac{Y(s)}{U(s)} \right)$  is.

A.  $\frac{11s+35}{(s-2)(s+4)}$  B.  $\frac{11s-35}{(s-2)(s+4)}$

C.  $\frac{11s+38}{(s-2)(s+4)}$  D.  $\frac{11s-38}{(s-2)(s+4)}$

Answer ||| A

Solution |||

Correct option is (A).

$$x_1 = 2x_1 - x_2 + 3u$$

$$x_2 = -4x_2 - u$$

$$y = 3x_1 - 2x_2$$

Where  $X = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$ ,  $U =$  Input vector

In matrix form,

$$\begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} 2 & -1 \\ 0 & -1 \end{bmatrix} X + \begin{bmatrix} 3 \\ -1 \end{bmatrix} U$$

$$Y = [3 \ -2] \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

$$\text{So, } A = \begin{bmatrix} 2 & -1 \\ 0 & -1 \end{bmatrix}, B = \begin{bmatrix} 3 \\ -1 \end{bmatrix}, C = [3 \ -2], D = 0$$

$$H(s) = C(sI - A)^{-1} B + D$$

Here,  $D = 0$ . So,


$$H(s) = C(sI - A)^{-1} B$$

$$= [3 \ -2] \begin{bmatrix} s-2 & 1 \\ 0 & s+4 \end{bmatrix}^{-1} \begin{bmatrix} 3 \\ -1 \end{bmatrix}$$

$$= [3 \ -2] \frac{1}{(s^2 + 2s - 8)} \begin{bmatrix} s+4 & -1 \\ 0 & s-2 \end{bmatrix} \begin{bmatrix} 3 \\ -1 \end{bmatrix}$$

$$= \frac{11s + 35}{(s-2)(s+4)}$$

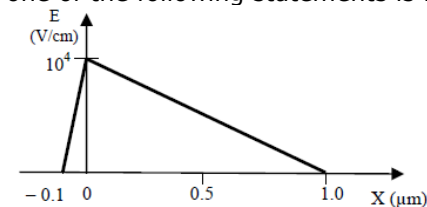33. The electric field profile in the depletion region of a p-n junction in equilibrium is shown in the figure. Which one of the following statements is **NOT TRUE**?



A. The left side of the junction is n-type and the right side is p-type

B. Both the n-type and p-type depletion regions are uniformly doped

C. The potential difference across the depletion region is 700 mV

D. If the p-type region has a doping concentration of  $10^{15} \text{ cm}^{-3}$ , then the doping concentration in the n-type region will be  $10^{16} \text{ cm}^{-3}$ .


Answer ||| C

Solution ||| Correct option is (C).

We know that the electric field is the negative gradient of electric potential, i.e.

$$E = -\frac{dV}{dx}$$

$$\text{Or } V = -\int E dx$$

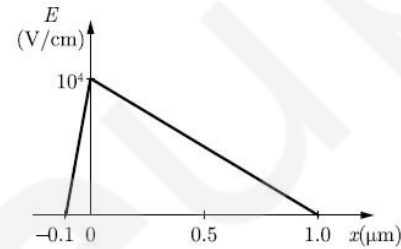

Area under the curve given in figure will give the built in potential as

$$\begin{aligned} U_{bi} &= \frac{1}{2} (0.1) \times 10^4 \text{ V/cm} + \frac{1}{2} \times 1 \text{ cm} \times 10^4 \text{ V/cm} \\ &= \frac{1}{2} (0.1) \times 10^{-6} \times 10^4 \times 100 + \frac{1}{2} \times 10^{-4} \times 10^4 \text{ V/cm} \\ &= 0.55 \text{ V} \end{aligned}$$

In option C. it is given as 700 mV, so it is not true.

34. The current in an enhancement mode NMOS transistor biased in saturation mode was measured to be 1 mA at a drain-source voltage of 5 V. When the drain-source voltage was increased to 6V while keeping gate-source voltage same, the drain current increased to 1.02 mA. Assume that drain to source saturation voltage is much smaller than the applied drain-source voltage. The channel length modulation parameter  $\lambda$  (in  $\text{V}^{-1}$ ) is \_\_\_\_.

A. 0.002 B. 0.022 C. 0.4 D. 0.033

Answer ||| B

Solution ||| Correct answer is 0.022

Given transistor is in saturation region, and

Current = 1 mA at  $V_{DS} = 5 \text{ V}$

Current = 1.02 mA at  $V_{DS} = 6 \text{ V}$

Assuming  $V_G$  constant, current in saturation region is

$$I_D = \frac{k}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$$I_{D1} = (1 + \lambda V_{DS1})$$

$$I_{D2} = (1 + \lambda V_{DS2})$$

$$\text{So, } \frac{1.02 \text{ mA}}{1 \text{ mA}} = \frac{(1 + \lambda V_{DS2})}{(1 + \lambda V_{DS1})}$$

$$1.02 = \frac{1 + 6\lambda}{1 + 5\lambda}$$

$$\lambda = 0.022 \text{ V}^{-1}$$

35. An npn BJT having reverse saturation current  $I_s = 10^{-15} \text{ A}$  is biased in the forward active region with  $V_{BE} = 700$



mV. The thermal voltage ( $V_T$ ) is 25 mV and the current gain ( $\beta$ ) may vary from 50 to 150 due to manufacturing variations. The maximum emitter current (in  $\mu A$ ) is \_\_\_\_.

A. 655 B. 1555 C. 1475.5 D. 100

Answer ||| C

Solution ||| Correct answer is 1475.5

Collector current is given by

$$I_C = I_S \exp \left[ \frac{V_{BE}}{V_T} \right] = 10^{15} A \exp \left[ \frac{700 mV}{25 mV} \right]$$

$$= 10^{-15} A \exp [28]$$

Also, we may define

$$I_C = \beta I_B$$

$$\text{or } I_B = \frac{I_C}{\beta}$$

$$\text{and } I_E = (\beta + 1) I_B$$

So, for maximum  $I_E$ ,  $I_B$  and  $\beta$  should be maximum.


Therefore, we obtain

$$I_E = (\beta + 1) I_B = \frac{(\beta + 1) I_C}{\beta}$$

$$I_E = \frac{\beta + 1}{\beta} (I_C) = \frac{(\beta + 1)}{\beta} (10^{-15} A) \exp (28)$$

Here, we will take  $\beta = 50$  for maximum  $I_E$ . Hence,  
 $I_E = 1475.51 A$

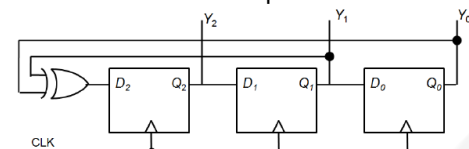36. A three bit pseudo random number generator is shown. Initially the value of output  $Y \equiv Y_2 Y_1 Y_0$  is set to 111. The value of output  $Y$  after three clock cycles is



A. 000 B. 001 C. 010 D. 100

Answer ||| D

Solution ||| Correct option is (D).

For D-flip flop

$$Q(t + 1) = D(t)$$

or next state = input

So, we may write

$$Q_2(t + 1) = Q_1(t) + Q_0(t)$$


$$Q_1(t + 1) = Q_2(t)$$

$$Q_0(t + 1) = Q_1(t)$$

The resulting output is illustrated in the truth table below.

|                       | $Q_2$ | $Q_1$ | $Q_0$ |
|-----------------------|-------|-------|-------|
| Given initial         | 1     | 1     | 1     |
| 1 <sup>st</sup> clock | 0     | 1     | 1     |
| 2 <sup>nd</sup> clock | 0     | 0     | 1     |
| 3 <sup>rd</sup> clock | 1     | 0     | 0     |

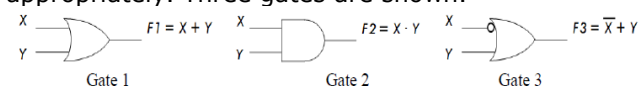37. A universal logic gate can implement any Boolean function by connecting sufficient number of them appropriately. Three gates are shown.



Which one of the following statements is TRUE?

A. Gate 1 is a universal gate

B. Gate 2 is a universal gate

C. Gate 3 is a universal gate


D. None of the gates shown is a universal gate

Answer ||| C

Solution ||| Correct option is (C).

In general, the only universal gates are NAND and NOR gates but none of the given question is NAND/NOR gate. However, we must observe the given Gate 3. All the Boolean function can be implemented by using the gate. Hence it is a universal gate.

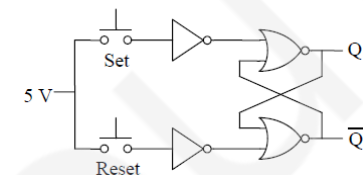38. An SR latch is implemented using TTL gates as shown in the figure. The set and reset pulse inputs are provided using the push-button switches. It is observed that the circuit fails to work as desired. The SR latch can be made functional by changing



A. NOR gates to NAND gates

B. inverters to buffers

C. NOR gates to NAND gates and inverters to buffers

D. 5 V to ground

Answer ||| D

Solution ||| Correct option is (D).


SR latch truth table is shown below.

| S | R | Q           |
|---|---|-------------|
| 0 | 0 | hold        |
| 0 | 1 | reset       |
| 1 | 0 | Set         |
| 1 | 1 | Not Defined |

The above truth table can be obtained from the given circuit, if we change 5 V to ground.

39. In the circuit shown, assume that the opamp is ideal. If the gain ( $v_0 / v_{in}$ ) is -12, the value of R (in  $k\Omega$ ) is


\_\_\_\_\_.

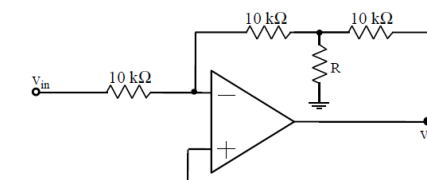

A. 1 B. 16 C. 15 D. 2

Answer ||| A

Solution ||| Correct answer is 1.

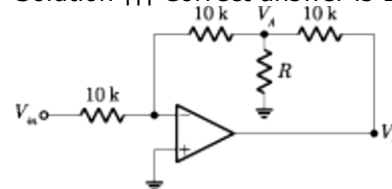

Given

$$\frac{V_0}{V_{in}} = -12$$

$$\frac{V_{in} - 0}{10k} = \frac{0 - V_A}{10k}$$

At node A

$$\frac{V_A - 0}{10k} + \frac{V_A}{R} + \frac{V_A - V_0}{10k} = 0$$

$$V_{in} = -V_A$$

Or  $V_A = -V_{in}$

Substituting equation (2) in (1), we have


$$\frac{-V_{in}}{10k} - \frac{V_{in}}{R} + \frac{-V_{in} - V_0}{10k} = 0 \text{ and } V_0 = -12 V_{in}$$

$$\frac{-V_{in}}{10k} - \frac{V_{in}}{R} + \frac{(-V_{in} + 12V_{in})}{10k} = 0$$

Solving above equation, we get

$$R = 1k$$

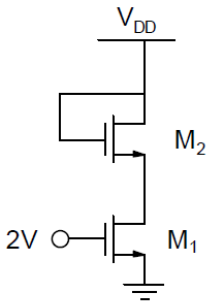40. In the circuit shown, both the enhancement mode NMO transistors have the following characteristics:  $k_n = \mu_n C_{ox} (W/L) = 1 \text{ mA/V}^2$ ;  $V_{TN} = 1\text{V}$ . Assume that the channel length modulation parameter  $\lambda$  is zero and body is shorted to source. The minimum supply voltage  $V_{DD}$  (in volts) needed to ensure that transistor  $M_1$  operates in saturation mode of operation is \_\_\_\_\_.



A. 1 B. 2 C. 3 D. 4

Answer ||| C

Solution ||| correct answer is 3.

For  $M_1$  to be in saturation,

$$V_{DS1} > V_{GS1} - V_{TN}$$

$$V_{D1} > 2 - 1$$

$$V_{D1} > 1$$

For minimum value  $V_{D1} = 1 \text{ V}$

$$\text{So, } I_{D1} = \frac{1 \text{ mA/V}^2}{2} (V_{us} - V_{TN})^2$$

$$= \frac{1 \text{ mA/V}^2}{2} (2 - 1)^2 = \frac{1 \text{ mA}}{2} (1)$$

$$I_{D1} = 0.5 \text{ mA}$$

Now, for  $M_2$

$$V_{DS2} V_{GS2} - V_{TN} \text{ will hold}$$

Since,  $V_G = V_D$

So, it will always be in saturation. Therefore

$$I_{D2} = \frac{1}{2} (k) (V_{GS} - V_{TN})^2$$

$$\text{Now, } I_{D1} = I_{D2}$$

(current in series connected components)


$$0.5 \text{ mA} = (1 \text{ mA/V}^2) \frac{1}{2} (V_{DD} - 1 - 1)^2$$

$$(V_{DD} - 2)^2 = 1$$

$$V_{DD} = 3 \text{ V}$$

This is the minimum required value.

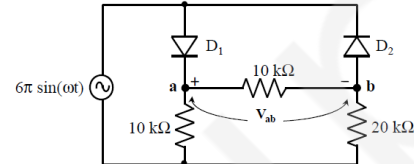41. In the circuit shown, assume that the diodes  $D_1$  and  $D_2$  are ideal. The average value of voltage  $V_{ab}$  (in volts), across terminals 'a' and 'b' is \_\_\_\_\_.



A. 2 Volts B. 3 Volts C. 6 Volts D. 5 Volts

Answer ||| D

Solution ||| Correct answer is 5.

In positive half-cycle ( $D_1 = \text{ON}, D_2 = \text{OFF}$ ), we have

$$V_{ab} = \frac{6\pi}{3} \sin \omega t = 2\pi \sin \omega t$$

Again, in Negative half-cycle ( $D_1 = \text{OFF}, D_2 = \text{ON}$ ), we have

$$V_{ab} = \frac{6\pi}{3} \sin \omega t = 3\pi \sin \omega t$$

Hence, the average of  $V_{ab}$  is

$$= \frac{2\pi}{\pi} + \frac{3\pi}{\pi} = 5 \text{ volts}$$

42. Suppose  $x[n]$  is an absolutely summable discrete-time signal. Its z-transform is a rational function with two poles and two zeroes. The poles are at  $z = \pm 2j$ . Which one of the following statements is TRUE for the signal  $x[n]$ ?

A. It is a finite duration signal

B. It is a causal signal

C. It is a non-causal signal


D. It is a periodic signal

Answer ||| C

Solution ||| Correct option is (C).


Given sequence is absolutely summable, so its Fourier transform (DTFT) exists.

Now, the poles are located below.

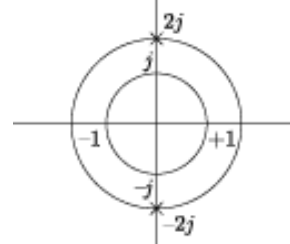

Here, ROC is inside the circle including unit circle. Hence, it is a non-causal system.

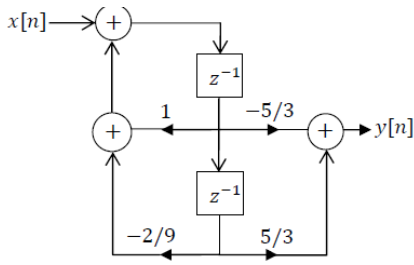43. A realization of a stable discrete time system is shown in the figure. If the system is excited by a unit step sequence input  $x[n]$ , the response  $y[n]$  is




- A.  $4\left(-\frac{1}{3}\right)^n u[n] - 5\left(-\frac{2}{3}\right)^n u[n]$   
 B.  $5\left(-\frac{2}{3}\right)^n u[n] - 3\left(-\frac{1}{3}\right)^n u[n]$   
 C.  $5\left(\frac{1}{3}\right)^n u[n] - 5\left(-\frac{2}{3}\right)^n u[n]$   
 D.  $5\left(\frac{2}{3}\right)^n u[n] - 5\left(-\frac{1}{3}\right)^n u[n]$

Answer ||| C

Solution ||| Correct option is (C).

We redraw the given system as

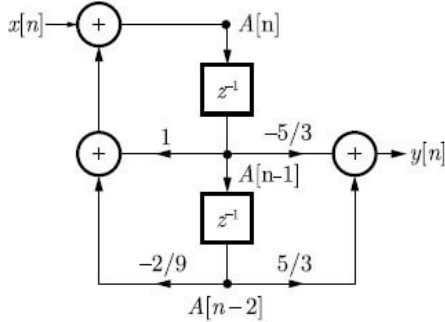

From the circuit, we have

$$A[n] = x[n] + A[n-1] - \frac{2}{9}A[n-2]$$

$$A(z) \times \left[1 - z^{-1} + \frac{2}{9}z^{-2}\right] = X(z) \quad \dots(i)$$

$$\frac{A(z)}{X(z)} = \frac{1}{1 - z^{-1} + \frac{2}{9}z^{-2}} \quad \dots(1)$$

Again,

$$Y[n] = -\frac{5}{3}A[n-1] + \frac{5}{3}A[n-2]$$

$$Y[z] = \left[-\frac{5}{3}z^{-1} + \frac{5}{3}z^{-2}\right]A(z)$$

$$\frac{Y(z)}{A(z)} = \frac{-5}{3}z^{-1} + \frac{5}{3}z^{-2} \quad \dots(2)$$

Multiplying equations (1) and (2),

$$\frac{Y(z)}{X(z)} = \frac{-\frac{5}{3}z^{-1} + \frac{5}{3}z^{-2}}{1 - z^{-1} + \frac{2}{9}z^{-2}}$$

For unit step response,

$$X(z) = \frac{1}{1 - z^{-1}}$$

$$\text{So, } Y(z) = \frac{-\frac{5}{3}z^{-1}[1 - z^{-1}]}{1 - z^{-1} + \frac{2}{9}z^{-2}} \times \frac{1}{1 - z^{-1}}$$

$$= \frac{5}{1 - \frac{1}{3}z^{-1}} - \frac{5}{1 - \frac{2}{3}z^{-1}}$$

$$\text{Hence, } y[n] = 5\left(\frac{1}{3}\right)^n u[n] - 5\left(\frac{2}{3}\right)^n u[n]$$

44. Let

$$\tilde{x}[n] = 1 + \cos\left(\frac{\pi n}{8}\right)$$

be a periodic signal period 16. Its DFS coefficients are defined by

$$a_k = \frac{1}{16} \sum_{n=0}^{15} \tilde{x}[n] \exp\left(-j\frac{\pi}{8}kn\right)$$

for all k. The value of the coefficient  $a_{31}$  is \_\_\_\_\_.

- A. 0.5 B. 3 C. 2.5 D. 5

Answer ||| A

Solution ||| Correct answer is 0.5

Given

$$x[n] = 1 + \cos\left(\frac{\pi n}{8}\right), \text{ with } N = 16$$

$$x[n] = 1 + \frac{1}{2}e^{j\frac{2\pi n}{16}} + \frac{1}{2}e^{j\frac{2\pi n}{16}}$$

$$a_1 = a_{-1} = \frac{1}{2}, a_0 = 1$$

For discrete series,

$$\text{So, } a_k = a_{k+N} \\ a_{31} = 0.5$$

45. Consider a continuous-time signal defined as

$$x(t) = \left(\frac{\sin(\pi t/2)}{(\pi t/2)}\right) * \sum_{n=-\infty}^{\infty} \delta(t - 10n)$$

Where '\*' denotes the convolution operation and t is in seconds. The Nyquist sampling rate In samples/sec) for x(t) is \_\_\_\_\_.

- A. 2.3 B. 3.3 C. 5.2 D. 0.4

Answer ||| D


Solution ||| Correct answer is 0.4

$$x(t) = \left(\frac{\sin\left(\frac{\pi t}{2}\right)}{\left(\frac{\pi t}{2}\right)}\right) * \sum_{n=-\infty}^{\infty} \delta(t - 10n)$$

Time domain convolution = frequency domain multiplication so, we obtain


$$\sum_{n=-\infty}^{\infty} \delta(t - 10n) \leftrightarrow \frac{1}{10} \sum_{n=-\infty}^{\infty} \delta(f - kf_s)$$

$$f_s = \frac{1}{T_s} = 0.1$$

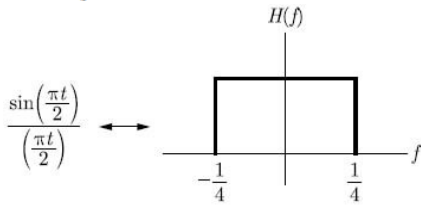

Thus, the multiplication will result in maximum frequency of 0.2. Hence,  
Nyquist rate =  $2 f_m = 2(0.2) = 0.4$  sample/sec

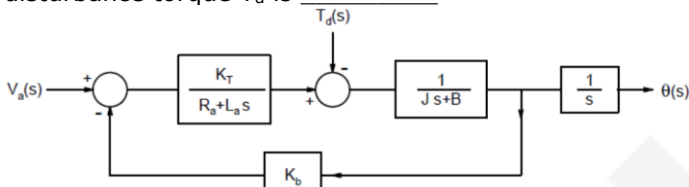46. The position control of a DC servo-motor is given in the figure. The values of the parameters are  $K_T = 1$  N-m/A,  $R_a = 1\Omega$ ,  $L_a = 0.1$  H,  $J = 5$  kg-m<sup>2</sup>,  $B = 1$  N-m/(rad/sec) and  $K_b = 1$  V/(rad/sec). The steady-state position response (in radians) due to unit impulse disturbance torque  $T_d$  is \_\_\_\_\_



A. 2.5 B. 0.5 C. -5 D. 4.5

Answer ||| B

Solution ||| Correct answer is 0.5

To find the response due to  $T_d(s)$ , we will use superposition making input  $V_a(s) = 0$  and finding

$$\text{Transfer function} = \frac{Q(s)}{T_d(s)}$$

$$T_d(s) = 1 \text{ (unit impulse response)}$$

$$\text{So, } \theta(s) = \frac{\left( \frac{1}{Js + B} \right)}{\left[ 1 + \left( \frac{1}{Js + B} \right) \left( \frac{K + Kb}{Ra + La s} \right) \right]} \times \frac{1}{s}$$


$$= \frac{1}{s \left[ (Js + B) \frac{K + Kb}{Ra + La s} \right]}$$

For steady state response,

$$\lim_{s \rightarrow 0} s \theta(s) = \frac{1}{(Js + B) + \frac{K + Kb}{Ra + La s}}$$

$$= \frac{1}{B + \frac{K + Kb}{Ra}} = \frac{1}{1 + \frac{1}{1}} = \frac{1}{2} = 0.5$$

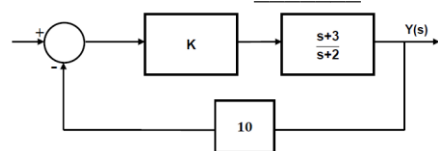47. For the system shown in the figure,  $s = -2.75$  lies on the root locus if  $K$  is \_\_\_\_\_.



A. 0.5 B. -0.5 C. 0.3 D. -0.3

Answer ||| C

Solution ||| Correct answer is 0.3

The open loop transfer function is

$$G(s) H(s) = \frac{K(s+3)(10)}{(s+2)}$$

At point  $s = -2.75$ ,

$$|G(s) H(s)| = 1$$

$$\left| \frac{K(s+3)}{(s+2)} 10 \right| = 1 \quad (\text{point lie on root locus})$$

$$\text{Hence, } K = \frac{0.75 \left( \frac{1}{10} \right)}{0.25 \left( \frac{1}{10} \right)} = \frac{3}{10} = 0.3$$

48. The characteristic equation of an LTI system is given by  $F(s) = s^5 + 2s^4 + 3s^3 + 6s^2 - 4s - 8 = 0$ . The number of roots that lie strictly in the left half s-plane is \_\_\_\_\_.

A. 2 B. 5 C. 3 D. 30

Answer ||| A

Solution ||| Correct answer is 2.

Given characteristic equation,

$$F(s) = s^5 + 2s^4 + 3s^3 + 6s^2 - 4s - 8 = 0$$

Applying the Routh stability criterion,

$$s^5 \quad 1 \quad 3 \quad -4$$

$$s^4 \quad 2 \quad 6 \quad -8$$

$$s^3 \quad 0 \quad 0 \quad 0$$

$$s^2$$

$$s^1$$

$$s^0$$

It contains complete zero row, so we obtain the auxiliary equation as  $2s^4 + 6s^2 - 8 = 0$

$$\text{Put } x = s^2,$$

$$2x^2 + 6x - 8 = 0$$

$$x = 1, -4$$

$$\text{So, } s^2 = 1 \text{ or } s = \pm 1$$

$$\text{and } s^2 = -4 \text{ or } s = \pm 2j$$

Hence, one root  $s = -1$  lies on left side. Taking

differential of auxiliary equation,  $8s^3 + 12s = 0$

Now, the Routh array is redrawn as

$$s^5 \quad 1 \quad 3 \quad -4$$

$$s^4 \quad 2 \quad 6 \quad -8$$

$$s^3 \quad 8 \quad 12 \quad 0$$

$$s^2 \quad 3 \quad -8 \quad 0$$

$$s^1 \quad -9.33 \quad 0$$

$$s^0 \quad 0$$

Since, there is only one sign change in the first column of Routh array, so one pole lie in R.H.P and two poles lie on imaginary axis. Hence, the remaining two poles lies in L.H.P.

49. Two sequences  $x_1[n]$  and  $x_2[n]$  have the same energy. Suppose  $x_1[n] = \alpha 0.5^n u[n]$ , where  $\alpha$  is a positive real number and  $u[n]$  is the unit step sequence. Assume

$$x_2[n] = \begin{cases} \sqrt{1.5} & \text{for } n = 0, 1 \\ 0 & \text{otherwise.} \end{cases}$$

Then the value of  $\alpha$  is \_\_\_\_\_.

A. 2 B. 1.5 C. 2.5 D. 14

Answer ||| B

Solution ||| Correct answer is 1.5

$$x_1[n] = -(0.5)^n u[n]$$

Energy of signal  $x_1[n]$  is

$$\begin{aligned} &= \sum_{n=-\infty}^{\infty} x_1^2[n] \\ &= \sum_{n=0}^{\infty} \alpha^2 (0.5)^{2n} \\ &= \alpha^2 \sum_{n=0}^{\infty} \left(\frac{1}{2}\right)^{2n} \\ &= \alpha^2 \left[1 + \frac{1}{4} + \frac{1}{16} + \dots\right] \\ &= \alpha^2 \left[\frac{1}{1 - \frac{1}{4}}\right] \\ &= \frac{4}{3} \alpha^2 \end{aligned}$$

$$\text{Again, } x_2[n] = \{\sqrt{1.5}, \sqrt{1.5}, 0, 0, \dots\}$$

So, energy of signal  $x_2[n]$  is

$$\begin{aligned} &= (\sqrt{1.5})^2 + (1.5)^2 \\ &= 1.5 + 1.5 = 3 \end{aligned}$$

Given that

Energy of signal  $x_1[n] = \text{Energy of signal } x_2[n]$

$$\frac{4}{3} \alpha^2 = 3$$

$$\alpha^2 = \frac{9}{4}$$

$$\alpha = \frac{+3}{2} = \pm 1.5$$

Since  $\alpha$  is a positive real number, so we have

$$\alpha = 1.5$$

50. The variance of the random variable  $X$  with

probability density function  $f(x) = \frac{1}{2} |x| e^{-|x|}$  is \_\_\_\_\_.

A. 6 B. 12 C. 5 D. 15

Answer ||| A

Solution |||

Correct answer is 6.

$$\text{Given } f(x) = \frac{1}{2} |x| e^{-|x|}$$

By definition, variance is

$$V(X) = E[X^2] - \{E[X]\}^2$$

$$E[X] = \int_{-\infty}^{\infty} x f_{\infty}(x) = \int_{-\infty}^{\infty} x \frac{1}{2} |x| e^{-|x|} dx$$

Since it is an odd function, we get

$$E[X] = 0$$

$$\begin{aligned} E[X^2] &= \int_{-\infty}^{\infty} x^2 f(x) = \int_{-\infty}^{\infty} \frac{1}{2} x^2 |x| e^{-|x|} dx \\ &= \int_{-\infty}^{\infty} x^3 e^{-x} dx = 6 \end{aligned}$$

$$\text{Hence, } V(x) = 6 - (0)^2 = 6$$

51. The complex envelope of the bandpass signal, centered about Hz, is

$$\begin{aligned} \text{A. } &\left(\frac{\sin(\pi t/5)}{\pi t/5}\right) e^{j\frac{\pi}{4}} \quad \text{B. } \left(\frac{\sin(\pi t/5)}{\pi t/5}\right) e^{-j\frac{\pi}{4}} \\ \text{C. } &\sqrt{2} \left(\frac{\sin(\pi t/5)}{\pi t/5}\right) e^{j\frac{\pi}{4}} \quad \text{D. } \sqrt{2} \left(\frac{\sin(\pi t/5)}{\pi t/5}\right) e^{j\frac{\pi}{4}} \end{aligned}$$

Answer ||| C

Solution ||| Correct option is (C).

$$\begin{aligned} x(t) &= -\sqrt{2} \left(\frac{\sin(\frac{\pi t}{5})}{\frac{\pi t}{5}}\right) \sin\left[\pi t - \frac{\pi}{4}\right] \\ &= -\sqrt{2} \left(\frac{\sin(\frac{\pi t}{5})}{\left(\frac{\pi t}{5}\right)}\right) \left[\cos \frac{\pi}{4} \sin \pi t - \sin \frac{\pi}{4} \cos \pi t\right] \\ &= \left(\frac{\sin(\frac{\pi t}{5})}{\left(\frac{\pi t}{5}\right)}\right) \cos \pi t - \left(\frac{\sin(\frac{\pi t}{5})}{\left(\frac{\pi t}{5}\right)}\right) \sin \pi t \end{aligned}$$

Let  $X_c$  be complex envelope of above signal. So, we have

$$\begin{aligned} X_c &= \frac{\sin \frac{\pi t}{5}}{\left(\frac{\pi t}{5}\right)} + j \frac{\sin \frac{\pi t}{5}}{\frac{\pi t}{5}} \\ &= \frac{\sin \frac{\pi t}{5}}{\frac{\pi t}{5}} [1 + j] = \sqrt{2} \frac{\sin\left(\frac{\pi t}{5}\right)}{\left(\frac{\pi t}{5}\right)} e^{j\frac{\pi}{4}} \end{aligned}$$

52. A random binary wave  $y(t)$  is given by

$$y(t) = \sum_{n=-\infty}^{\infty} X_n p(t - nT - \phi)$$

Where  $p(t) = u(t) - u(t - T)$ ,  $u(t)$  is the unit function and  $\phi$  is an independent random variable with uniform distribution in  $[0, T]$ . The sequence  $\{X_n\}$  consists of independent and identically distributed binary valued random variables with  $P\{X_n = +1\} = P\{X_n = -1\} = 0.5$  for each  $n$ .

The value of autocorrelation

$$R_{yy}\left(\frac{3T}{4}\right) = E\left[y(t)y\left(t - \frac{3T}{4}\right)\right]$$

equals\_\_\_\_\_.

A. 0.24 to 0.26 B. 1 to 2.5 C. 0.001 to 0.003 D. 2

Answer ||| A

Solution |||

$$y(t) = \sum_{n=-f}^x X_n P(t - nT - \phi)$$


$$R_{yy}(z) = \left[1 - \frac{|z|}{T}\right]$$

Derivation of above autocorrelation function can be found in any book dealing with random process.

[B.P. Lathi, Simon, Haykin, Schaum series]

$$R_{yy}\left(\frac{3T}{4}\right) = \left[1 - \frac{3\pi/4}{\pi}\right] = \frac{1}{4} = 0.25$$

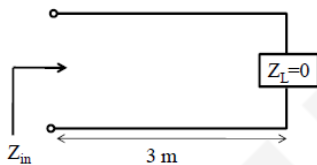53. Consider the 3 m long lossless air-filled transmission line shown in the figure. It has a characteristic impedance of  $120\pi\Omega$ , is terminated by a short circuit, and is excited with a frequency of 37.5 MHz. What is the nature of the input impedance ( $Z_{in}$ )?



- A. Open
- B. Short
- C. Inductive
- D. Capacitive

Answer ||| D

Solution ||| Correct option is (D).

Given

$L = 3m$  (lossless)

$Z_0 = 120\pi\Omega$ ,  $Z_L = 0\Omega$

For lossless line, we have

$$Z_{in} = Z_0 \left( \frac{Z_L + jZ_0 \tan \beta L}{Z_0 + jZ_L \tan \beta L} \right)$$

Now,  $\lambda = ?$

$f = 37.5 \text{ MHz}$

$C = f\lambda$

$$\text{So, } \lambda = \frac{3 \times 10^8}{37.5 \times 10^6} = 8$$

$$\beta L = \frac{2\pi}{\lambda}(L) = \frac{2\pi}{8}(3) = \frac{3\pi}{4}$$

Put  $Z_L = 0$  in equation (1),


$$Z_{in} = jZ_0 \tan \beta L$$

$$Z_{in} = j(120\pi) \tan \frac{3\pi}{4}$$

or  $Z_{in} < 0$  ( $\tan 3\pi/4 = \text{negative quantity}$ )

Hence, input impedance is capacitive in nature.

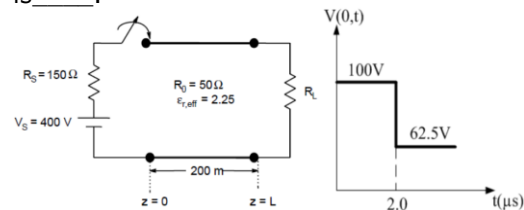54. A 200 m long transmission line having parameters shown in the figure is terminated into a load  $R_L$ . The line is connected to a 400 V source having source resistance  $R_S$  through a switch, which is closed at  $t = 0$ . The transient response of the circuit at the input of the line ( $z = 0$ ) is also drawn in the figure. The value of  $R_L$  (in  $\Omega$ ) is\_\_\_\_\_.




A. 25 B. 30 C. 45 D. 50

Answer ||| B

Solution ||| Correct answer is 30.

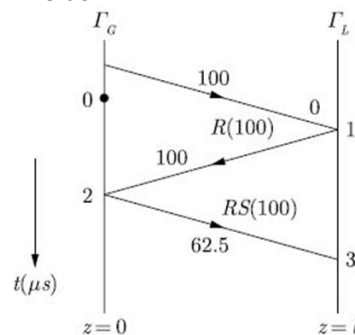We form the bounce diagram for the given transmission line as





Here,  $\Gamma_G$  and  $\Gamma_L$  are the reflection coefficients at generator and load end, defined as

$$\Gamma_L = \frac{R_L - 50}{R_L + 50} \dots\dots\dots(1)$$

$$\text{and } \Gamma_G = \frac{1}{2} \dots\dots\dots(2)$$

Again, we have

$$V(t = 2\mu s, Z = 0) = 62.5$$

So, we can write

$$62.5 = V(t = 0, z = 0) + V(t = 1, z = 0) + V(t = 2, z = 0)$$

$$62.5 = 100 + \Gamma_L(100) + \Gamma_G\Gamma_L(100)$$

Substituting equation (2), we get

$$\Gamma_L = \frac{-1}{4}$$

Hence, substituting the above result in equation (1), we obtain

$$R_L = 30 \Omega$$

55. A coaxial capacitor of inner radius 1 mm and outer radius 5 mm has a capacitance per unit length of 172 pF/m. If the ratio of outer radius to inner radius is doubled, the capacitance per unit length (in pF/m) is \_\_\_\_.

A. 120.22 B. 220 C. 150 D. 142

Answer ||| A

Solution ||| Correct answer is 120.22

Capacitance of coaxial capacitor is defined as

$$C = \frac{2\pi\epsilon l}{\ln\left(\frac{b}{a}\right)}$$

$$\text{So, } \frac{C_1}{C_2} = \frac{\ln\left(\frac{b_2}{b_1}\right)}{\ln\left(\frac{b_1}{b_1}\right)}$$

$$\frac{172 \text{ pF/m}}{C^2} = \frac{\ln\left(\frac{10}{1}\right)}{\ln(5)}$$

$$C_2 = 120.22 \text{ pF/m}$$

\*\*\*