

Analog Circuits (Formula Notes/Short Notes)

- Energy gap $E_{G/\text{Si}} = 1.21 - 3.6 \times 10^{-4} \cdot T \text{ ev}$; $E_{G/\text{Ge}} = 0.785 - 2.23 \times 10^{-4} \cdot T \text{ ev}$ } Energy gap depending on temperature
 - $E_F = E_C - KT \ln\left(\frac{N_C}{N_D}\right) = E_v + KT \ln\left(\frac{N_p}{N_A}\right)$
 - No. of electrons $n = N_c e^{-(E_c - E_f)/RT}$ (KT in ev)
 - No. of holes $p = N_v e^{-(E_f - E_v)/RT}$
 - Mass action law $n_p = n_i^2 = N_c N_v e^{-EG/KT}$
 - Drift velocity $v_d = \mu E$ (for si $v_d \leq 10^7 \text{ cm/sec}$)
 - Hall voltage $v_H = \frac{B \cdot I}{w_e}$. Hall coefficient $R_H = 1/\rho$. $\rho \rightarrow \text{charge density} = qN_0 = ne \dots$
 - Conductivity $\sigma = \rho \mu$; $\mu = \sigma R_H$.
 - Max value of electric field @ junction $E_0 = -\frac{q}{\epsilon_{\text{Si}}} N_d \cdot n_{n0} = -\frac{q}{\epsilon_{\text{Si}}} N_A \cdot n_{p0}$.
 - Charge storage @ junction $Q_+ = -Q_- = qA x_{n0} N_D = qA x_{p0} N_A$
 - Diffusion current densities $J_p = -q D_p \frac{dp}{dx}$; $J_n = -q D_n \frac{dn}{dx}$
 - Drift current densities $= q(p \mu_p + n \mu_n)E$
 - μ_p, μ_n decrease with increasing doping concentration .
 - $\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = KT/q \approx 25 \text{ mv} @ 300 \text{ K}$
 - Carrier concentration in N-type silicon $n_{n0} = N_D$; $p_{n0} = n_i^2 / N_D$
 - Carrier concentration in P-type silicon $p_{p0} = N_A$; $n_{p0} = n_i^2 / N_A$
 - Junction built in voltage $V_0 = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$
 - Width of Depletion region $W_{\text{dep}} = x_p + x_n = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) (V_0 + V_R)}$
* $\left(\frac{2\epsilon_f t}{q} = 12.93m \text{ for si}\right)$
 - $\frac{x_n}{x_p} = \frac{N_A}{N_D}$
 - Charge stored in depletion region $q_j = \frac{q \cdot N_A \cdot N_D}{N_A + N_D} \cdot A \cdot W_{\text{dep}}$
 - Depletion capacitance $C_j = \frac{\epsilon_s A}{W_{\text{dep}}}$; $C_{j0} = \frac{\epsilon_s A}{W_{\text{dep}}/V_R = 0}$
- $$C_j = C_{j0} / \left(1 + \frac{V_R}{V_0}\right)^m$$
- $$C_j = 2C_{j0} \text{ (for forward Bias)}$$
- Forward current $I = I_p + I_n$; $I_p = Aq n_i^2 \frac{D_p}{L_p N_D} (e^{V/V_T} - 1)$
 $I_n = Aq n_i^2 \frac{D_n}{L_n N_A} (e^{V/V_T} - 1)$
 - Saturation Current $I_s = Aq n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$
 - Minority carrier life time $\tau_p = L_p^2 / D_p$; $\tau_n = L_n^2 / D_n$

- Minority carrier charge storage $Q_p = \tau_p I_p$, $Q_n = \tau_p I_n$
 $Q = Q_p + Q_n = \tau_T I$ τ_T = mean transit time
- Diffusion capacitance $C_d = \left(\frac{\tau_T}{\eta V_T}\right) I = \tau \cdot g \Rightarrow C_d \propto I$.
 $\tau \rightarrow$ carrier life time, g = conductance $= I / \eta V_T$
- $I_{02} = 2^{(T_2 - T_1)/10} I_{01}$
- Junction Barrier Voltage $V_j = V_B = V_r$ (open condition)
 $= V_r - V$ (forward Bias)
 $= V_r + V$ (Reverse Bias)
- Probability of filled states above 'E' $f(E) = \frac{1}{1+e^{(E-E_f)/kT}}$
- Drift velocity of e^- $v_d \leq 10^7$ cm/sec
- Poisson equation $\frac{d^2V}{dx^2} = \frac{-\rho_v}{\epsilon} = \frac{-nq}{\epsilon} \Rightarrow \frac{dv}{dx} = E = \frac{-nqx}{\epsilon}$

Transistor :-

- $I_E = I_{DE} + I_{nE}$
- $I_C = I_{Co} - \alpha I_E \rightarrow$ Active region
- $I_C = -\alpha I_E + I_{Co} (1 - e^{V_C/V_T})$

Common Emitter :-

- $I_C = (1 + \beta) I_{Co} + \beta I_B \quad \beta = \frac{\alpha}{1-\alpha}$
- $I_{CEO} = \frac{I_{Co}}{1-\alpha} \rightarrow$ Collector current when base open
- $I_{CBO} \rightarrow$ Collector current when $I_E = 0 \quad I_{CBO} > I_{Co}$.
- $V_{BE,sat}$ or $V_{BC,sat} \rightarrow -2.5$ mv / 0C ; $V_{CE,sat} \rightarrow \frac{V_{BE,sat}}{10} = -0.25$ mv / 0C
- Large signal Current gain $\beta = \frac{I_C - I_{CBO}}{I_B + I_{CBO}}$
- D.C current gain $\beta_{dc} = \frac{I_C}{I_B} = h_{FE}$
- $(\beta_{dc} = h_{FE}) \approx \beta$ when $I_B > I_{CBO}$
- Small signal current gain $\beta' = \left. \frac{\partial I_C}{\partial I_R} \right|_{V_{CE}} = h_{fe} = \frac{h_{FE}}{1 - (I_{CBO} + I_B) \frac{\partial h_{FE}}{\partial I_C}}$
- Over drive factor $= \frac{\beta_{active}}{\beta_{forced \rightarrow under\ saturation}} \quad \because I_{C\ sat} = \beta_{forced} I_{B\ sat}$

Conversion formula :-

CC \leftrightarrow CE

- $h_{ic} = h_{ie}$; $h_{rc} = 1$; $h_{fc} = -(1 + h_{fe})$; $h_{oc} = h_{oe}$

CB \leftrightarrow CE

- $h_{ib} = \frac{h_{ie}}{1+h_{fe}}$; $h_{ib} = \frac{h_{ie} h_{oe}}{1+h_{fe}} - h_{re}$; $h_{fb} = \frac{-h_{fe}}{1+h_{fe}}$; $h_{ob} = \frac{h_{oe}}{1+h_{fe}}$

CE parameters in terms of CB can be obtained by interchanging B & E .

Specifications of An amplifier :-

$$\bullet \quad A_I = \frac{-h_f}{1+h_0 Z_L} \quad Z_i = h_i + h_r A_I Z_L \quad A_{VS} = \frac{A_v Z_i}{Z_i + R_s} = \frac{A_I Z_L}{Z_i + R_s} = \frac{A_I Z_L}{R_s}$$

$$A_V = \frac{A_I Z_L}{Z_i} \quad Y_0 = h_o - \frac{h_f h_r}{h_i + R_s} \quad A_{IS} = \frac{A_v R_s}{Z_i + R_s} = \frac{A_{VS} R_s}{Z_L}$$

Choice of Transistor Configuration :-

- For intermediate stages CC can't be used as $A_V < 1$
- CE can be used as intermediate stage
- CC can be used as o/p stage as it has low o/p impedance
- CC/CB can be used as i/p stage because of i/p considerations.

Stability & Biasing :- (Should be as min as possible)

$$\bullet \quad \text{For } S = \left. \frac{\Delta I_C}{\Delta I_{CO}} \right|_{V_{B0}, \beta} \quad S' = \left. \frac{\Delta I_C}{\Delta V_{BE}} \right|_{I_{CO}, \beta} \quad S'' = \left. \frac{\Delta I_C}{\Delta \beta} \right|_{V_{BE}, I_{CO}}$$

$$\Delta I_C = S \cdot \Delta I_{CO} + S' \Delta V_{BE} + S'' \Delta \beta$$

$$\bullet \quad \text{For fixed bias } S = \frac{1+\beta}{1-\beta \frac{\Delta I_B}{\Delta I_C}} = 1 + \beta$$

$$\bullet \quad \text{Collector to Base bias } S = \frac{1+\beta}{1+\beta \frac{R_C}{R_C+R_B}} \quad 0 < s < 1 + \beta = \frac{1+\beta}{1+\beta \left(\frac{R_C+R_E}{R_C+R_E+R_B} \right)}$$

$$\bullet \quad \text{Self bias } S = \frac{1+\beta}{1+\beta \frac{R_E}{R_E+R_{th}}} \approx 1 + \frac{R_{th}}{R_E} \quad \beta R_E > 10 R_2$$

$$\bullet \quad R_1 = \frac{V_{cc} R_{th}}{V_{th}} ; \quad R_2 = \frac{V_{cc} R_{th}}{V_{cc} - V_{th}}$$

$$\bullet \quad \text{For thermal stability } [V_{cc} - 2I_C (R_C + R_E)] [0.07 I_{CO} \cdot S] < 1/\theta ; \quad V_{CE} < \frac{V_{cc}}{2}$$

Hybrid -pi(π)- Model :-


$$g_m = |I_C| / V_T$$

$$r_{b'e} = h_{fe} / g_m$$


$$r_{b'b} = h_{ie} - r_{b'e}$$

$$r_{b'c} = r_{b'e} / h_{re}$$
 
$$g_{ce} = h_{oe} - (1 + h_{fe}) g_{b'c}$$



 - 3 Configurations are used on BJT, CE, CB & CC



COMPARISON		
	BE	BC
SATURATION	f/b	f/b
ACTIVE	f/b	r/b
CUT OFF	r/b	r/b

AMPLIFIER COMPARISON			
	CB	CE	CF
R_i	LOW	MED	HIGH
A_I	A_I	β	$\beta + 1$
A_V	High	High	<1
R_o	High	High	low

For CE :-

- $f_\beta = \frac{g_{b'e}}{2\pi(C_e + C_c)} = \frac{g_m}{h_{fe}2\pi(C_e + C_c)}$

- $f_T = h_{fe} f_\beta ; f_H = \frac{1}{2\pi r_{b'e} C} = \frac{g_{b'e}}{2\pi C}$ $C = C_e + C_c (1 + g_m R_L)$
 f_T = S.C current gain Bandwidth product
 f_H = Upper cutoff frequency

For CC :-

- $f_H = \frac{1+g_m R_L}{2\pi C_L R_L} \approx \frac{g_m}{2\pi C_L} = \frac{f_T C_e}{C_L} = \frac{g_m + g_{b'e}}{2\pi(C_L + C_e)}$

For CB:-

- $f_\alpha = \frac{1+h_{fe}}{2\pi r_{b'e}(C_C + C_e)} = (1 + h_{fe}) f_\beta = (1 + \beta) f_\beta$


- $f_T = \frac{\beta}{1+\beta} f_\alpha$ $f_\alpha > f_T > f_\beta$

Ebress moll model :-

$$I_C = -\alpha_N I_E + I_{Co} (1 - e^{V/V_T})$$

$$I_E = -\alpha_I I_C + I_{Eo} (1 - e^{V/V_T})$$

$$\alpha_I I_{Co} = \alpha_N I_{Eo}$$

 

Multistage Amplifiers :-


- $f_{H^*} = f_H \sqrt{2^{1/n} - 1} ; f_{L^*} = \frac{f_L}{\sqrt{2^{1/n}-1}}$

- Rise time $t_r = \frac{0.35}{f_H} = \frac{0.35}{B.W}$

- $t_r^* = 1.1 \sqrt{t_{r1}^2 + t_{r2}^2 + \dots}$

- $f_{L^*} = 1.1 \sqrt{f_{L1}^2 + f_{L2}^2 + \dots}$

 - $\frac{1}{f_H^*} = 1.1 \sqrt{\frac{1}{f_{H1}^2} + \frac{1}{f_{H2}^2} + \dots}$



Differential Amplifier :-

- $Z_i = h_{ie} + (1 + h_{fe}) 2R_e = 2 h_{fe} R_e \approx 2\beta R_e$

- $g_m = \frac{\alpha_0 |I_{EE}|}{4V_T} = \frac{I_C}{4V_T} = g_m$ of BJT/4 $\alpha_0 \rightarrow$ DC value of α


- $CMRR = \frac{h_{fe} R_e}{R_s + h_{ie}} ; R_e \uparrow \rightarrow Z_i \uparrow, A_d \uparrow \& CMRR \uparrow$

Darlington Pair :-


- $A_I = (1 + \beta_1)(1 + \beta_2)$; $A_v \approx 1$ (< 1)
- $Z_i = \frac{(1+h_{fe})^2 R_{e2}}{1+h_{fe} h_{oc} R_{e2}} \Omega$ [if Q_1 & Q_2 have same type] $= A_I R_{e2}$
- $R_o = \frac{R_s}{(1+h_{fe})^2} + \frac{2 h_{ie}}{1+h_{fe}}$
- $g_m = (1 + \beta_2) g_{m1}$

Tuned Amplifiers : (Parallel Resonant ckt used) :

- $f_0 = \frac{1}{2\pi\sqrt{LC}}$ \rightarrow 'Q' factor of resonant ckt which is very high
- $B.W = f_0 / Q$
- $f_L = f_0 - \frac{\Delta BW}{2}$
- $f_H = f_0 + \frac{\Delta BW}{2}$
- For double tuned amplifier 2 tank circuits with same f_0 used. $f_0 = \sqrt{f_L f_H}$.

 FIELD EFFECT TRANSISTOR, FET is Unipolar Device

 
- S=Source, G=Gate, D=Drain
- GS Junction in Reverse Bias Always
- V_{gs} Controls Gate Width
- VI CHARACTERSTICS



- Shockley Equation

$$\text{➤ } I_d = I_{dss} \left(1 - \frac{V_{gs}}{V_p} \right)^2, \quad g_m = g_{m0} \left(1 - \frac{V_{gs}}{V_p} \right)$$

 MOSFET (Metal Oxide Semiconductor FET, IGFET)



- Depletion Type MOSFET can work width $V_{gs} > 0$ and $V_{gs} < 0$
- Enhancement MOSFET operates with, $V_{gs} > V_t$, $V_t = \text{Threshold Voltage}$

- NMOSFET formed in p-substrate
- If $V_{GS} \geq V_t$ channel will be induced & i_D (Drain \rightarrow source)
- $V_t \rightarrow +ve$ for NMOS
- $i_D \propto (V_{GS} - V_t)$ for small V_{DS}
- $V_{DS} \uparrow \rightarrow$ channel width @ drain reduces .

$V_{DS} = V_{GS} - V_t$ channel width $\approx 0 \rightarrow$ pinch off further increase no effect

- For every $V_{GS} > V_t$ there will be $V_{DS,sat}$
- $i_D = K'_n [(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2] \left(\frac{W}{L} \right)$ \rightarrow triode region ($V_{DS} < V_{GS} - V_t$)

$$K'_n = \mu_n C_{ox}$$

- $i_D = \frac{1}{2} K'_n \left(\frac{W}{L} \right) [V_{DS}^2] \rightarrow$ saturation
- $r_{DS} = \frac{1}{K'_n \left(\frac{W}{L} \right) (V_{GS} - V_t)}$ \rightarrow Drain to source resistance in triode region

PMOS :-

- Device operates in similar manner except V_{GS} , V_{DS} , V_t are -ve
- i_D enters @ source terminal & leaves through Drain .

$V_{GS} \leq V_t \rightarrow$ induced channel $V_{DS} \geq V_{GS} - V_t \rightarrow$ Continuous channel

$$i_D = K'_p \left(\frac{W}{L} \right) [(V_{GS} - V_t)^2 - \frac{1}{2} V_{DS}^2] \quad K'_p = \mu_p C_{ox}$$

$V_{DS} \leq V_{GS} - V_t \rightarrow$ Pinched off channel .

- NMOS Devices can be made smaller & thus operate faster . Require low power supply .
- Saturation region \rightarrow Amplifier
- For switching operation Cutoff & triode regions are used

- **NMOS** **PMOS**

$V_{GS} \geq V_t$ $V_{GS} \leq V_t$ \rightarrow induced channel

$V_{GS} - V_{DS} > V_t$ $V_{GS} - V_{DS} < V_t$ \rightarrow Continuous channel(Triode region)

$V_{DS} \geq V_{GS} - V_t$ $V_{DS} \leq V_{GS} - V_t$ \rightarrow Pinchoff (Saturation)

Depletion Type MOSFET :- [channel is physically implanted , i_0 flows with $V_{GS} = 0$]

- For n-channel $V_{GS} \rightarrow +ve \rightarrow$ enhances channel .
 $\rightarrow -ve \rightarrow$ depletes channel
- $i_D - V_{DS}$ characteristics are same except that V_t is -ve for n-channel
- Value of Drain current obtained in saturation when $V_{GS} = 0 \Rightarrow I_{DSS}$.

$$\therefore I_{DSS} = \frac{1}{2} K'_n \left(\frac{W}{L} \right) V_t^2 .$$

MOSFET as Amplifier :-

- For saturation $V_D > V_{GS} - V_t$
- To reduce non linear distortion $v_{gs} << 2(V_{GS} - V_t)$
- $i_d = K'_n \left(\frac{W}{L} \right) (V_{GS} - V_t) v_{gs} \Rightarrow g_m = K'_n \left(\frac{W}{L} \right) (V_{GS} - V_t)$
- $\frac{v_d}{v_{gs}} = - g_m R_D$
- Unity gain frequency $f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$

JFET :-

- $V_{GS} \leq V_p \Rightarrow i_D = 0 \rightarrow$ Cut off
- $V_p \leq V_{GS} \leq 0, V_{DS} \leq V_{GS} - V_p$
 $i_D = I_{DSS} \left[2 \left(1 - \frac{V_{GS}}{V_p} \right) \left(\frac{V_{DS}}{-V_p} \right) - \left(\frac{V_{DS}}{V_p} \right)^2 \right] \right\} \rightarrow$ Triode
- $V_p \leq V_{GS} \leq 0, V_{DS} \geq V_{GS} - V_p$

$$\left. \begin{aligned} i_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2 \Rightarrow V_{GS} = V_p \left(1 - \sqrt{\frac{i_D}{I_{DSS}}} \right) \\ g_m &= \frac{2i_{DSS}}{|V_p|} \left(1 - \frac{V_{GS}}{V_p} \right) = \frac{2i_{DSS}}{|V_p|} \sqrt{\frac{i_D}{I_{DSS}}} \end{aligned} \right\} \rightarrow$$

Saturation

Zener Regulators :-

- For satisfactory operation $\frac{V_i - V_z}{R_s} \geq I_{Z_{min}} + I_{L_{max}}$
- $R_{S_{max}} = \frac{V_{s_{min}} - V_{z_0} - I_{Z_{min}} r_z}{I_{Z_{min}} + I_{L_{max}}}$
- Load regulation = $- (r_z \parallel R_s)$
- Line Regulation = $\frac{r_z}{R_s + r_z}$.
- For finding min R_L take $V_{s_{min}}$ & V_{z_k}, I_{z_k} (knee values (min)) calculate according to that .

Operational Amplifier:- (VCVS)

- Fabricated with VLSI by using epitaxial method
- High i/p impedance , Low o/p impedance , High gain , Bandwidth , slew rate .
- FET is having high i/p impedance compared to op-amp .
- Gain Bandwidth product is constant .
- Closed loop voltage gain $A_{CL} = \frac{A_{OL}}{1 \pm \beta A_{OL}}$ $\beta \rightarrow$ feed back factor
- $\Rightarrow V_0 = \frac{-1}{RC} \int V_i dt \rightarrow$ LPF acts as integrator ;
- $\Rightarrow V_0 = \frac{-R}{L} \int V_i dt ; \quad V_0 = \frac{-L}{R} \frac{dv_i}{dt}$ (HPF)
- For Op-amp integrator $V_0 = \frac{-1}{\tau} \int V_i dt$; Differentiator $V_0 = - \tau \frac{dv_i}{dt}$
- Slew rate SR = $\frac{\Delta V_0}{\Delta t} = \frac{\Delta V_0}{\Delta t} \cdot \frac{\Delta V_i}{\Delta t} = A \cdot \frac{\Delta V_i}{\Delta t}$
- Max operating frequency $f_{max} = \frac{\text{slew rate}}{2\pi \cdot \Delta V_0} = \frac{\text{slew rate}}{2\pi \times \Delta V_i \times A}$

- In voltage follower Voltage series feedback
- In non inverting mode voltage series feedback
- In inverting mode voltage shunt feed back
- $V_0 = -\eta V_T \ln \left(\frac{V_s}{RI_0} \right)$
- $V_0 = -V_{BE}$

$$= -\eta V_T \ln \left(\frac{V_s}{RI_{C0}} \right)$$

- Error in differential % error = $\frac{1}{CMRR} \left(\frac{V_c}{V_d} \right) \times 100 \%$

Power Amplifiers :-

- Fundamental power delivered to load $P_1 = \left(\frac{B_1}{\sqrt{2}} \right)^2 R_L = \frac{B_1^2}{2} R_L$
- Total Harmonic power delivered to load $P_T = \left[\frac{B_1^2}{2} + \frac{B_2^2}{2} + \dots \right] R_L$
 $= P_1 \left[1 + \left(\frac{B_2}{B_1} \right)^2 + \left(\frac{B_3}{B_1} \right)^2 + \dots \right]$
 $= [1 + D^2] P_1$

Where $D = \sqrt{D_1^2 + D_2^2 + \dots + D_n^2}$

$$D_n = \frac{B_n}{B_1}$$

D = total harmonic Distortion .

Class A operation :-

- o/p I_C flows for entire 360°
- ‘Q’ point located @ centre of DC load line i.e., $V_{ce} = V_{cc} / 2$; $\eta = 25 \%$
- Min Distortion , min noise interference , eliminates thermal run way
- Lowest power conversion efficiency & introduce power drain
- $P_T = I_C V_{CE} - i_c V_{ce}$ if $i_c = 0$, it will consume more power
- P_T is dissipated in single transistors only (single ended)

Class B:-

- I_C flows for 180° ; ‘Q’ located @ cutoff ; $\eta = 78.5\%$; eliminates power drain
- Higher Distortion , more noise interference , introduce cross over distortion
- Double ended . i.e ., 2 transistors . $I_C = 0$ [transistors are connected in that way] $P_T = i_c V_{ce}$
- $P_T = i_c V_{ce} = 0.4 P_0$ $P_T \rightarrow$ power dissipated by 2 transistors .

Class AB operation :-

- I_C flows for more than 180° & less than 360°
- 'Q' located in active region but near to cutoff ; $\eta = 60\%$
- Distortion & Noise interference less compared to class 'B' but more in compared to class 'A'
- Eliminates cross over Distortion

Class 'C' operation :-

- I_C flows for $< 180^\circ$; 'Q' located just below cutoff ; $\eta = 87.5\%$
- Very rich in Distortion ; noise interference is high .


Oscillators :-

- For RC-phase shift oscillator $f = \frac{1}{2\pi RC\sqrt{6+4K}}$ $h_{fe} \geq 4k + 23 + \frac{29}{k}$ where $k = R_c/R$

$$f = \frac{1}{2\pi RC\sqrt{6}} \quad \mu > 29$$

- For op-amp RC oscillator $f = \frac{1}{2\pi RC\sqrt{6}} \quad |A_f| \geq 29 \Rightarrow R_f \geq 29 R_1$

Wein Bridge Oscillator :-

 

$$f = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}},$$

$$\text{if } R_1 = R_2 = R, C_1 = C_2 = C, f = \frac{1}{2\pi R C}; A = \frac{1}{\beta} = 3$$

Hartley Oscillator :-

$$f = \frac{1}{2\pi\sqrt{(L_1+L_2)C}}$$


$$|h_{fe}| \geq \frac{L_2}{L_1}$$

$$|\mu| \geq \frac{L_2}{L_1}$$

$$|A| \geq \frac{L_2}{L_1}$$

↓

$$\frac{R_f}{R_1}$$

 


Colpits Oscillator :-

$$f = \frac{1}{2\pi\sqrt{L\frac{C_1 C_2}{C_1 + C_2}}} \quad |h_{fe}| \geq \frac{C_1}{C_2}$$

$$|\mu| \geq \frac{C_1}{C_2}$$

$$|A| \geq \frac{C_1}{C_2}$$


Phase shift oscillator:-

 

FET MODEL

$$f = \frac{1}{2\pi\sqrt{6RC}}, A = 29,$$

Minimum RC sections 3

 

BJT MODEL

$$f = \frac{1}{2\pi RC \sqrt{6 + \left(\frac{4R_C}{R}\right)}}, A = 29,$$


Minimum RC sections 3

Comparisons:

BJT	FET
Current controlled	Voltage controlled
High gain	Med gain
Bipolar	Unipolar
Temp sensitive	Little effect of T
High GBWP	Low GBWP

MOSFET	JFET
High $R_i = 10^{10}$	-10^8
$R_0 = 50 k\Omega$	$\geq 1m\Omega$
Depletion Enhancement Mode	Depletion Mode
Delicate	Rugged

Rectifiers:

 

Comparisons:

	HW	FW CT	FW BR
V_{DC}	$\frac{V_m}{\pi}$	$\frac{2V_m}{\pi}$	$\frac{2V_m}{\pi}$
V_{rms}	$\frac{V_m}{2}$	$\frac{V_m}{\sqrt{2}}$	$\frac{V_m}{\sqrt{2}}$
γ Ripple factor	1.21	0.482	0.482
η Rectification efficiency	40.6%	81%	81%
PIV Peak Inverse Voltage	V_m	$2V_m$	V_m