

ESE (Mains) 2019

Electronic Devices & Circuits
Imp. Questions with Solutions



1. A. Derive the condition for minimum conductivity in case of a semiconductor material. Find expression for minimum conductivity & give relation between intrinsic conductivity & minimum conductivity.

B. Find minimum conductivity in case of a semiconductor which has electron mobility = 1000 cm² / V-sec, hole mobility = 600 cm² / V-sec and intrinsic conductivity is 10⁻⁶/Ω - cm.

Ans.

A. Conductivity of a semiconductor is given by,

$$\sigma = nq\mu_n + pq\mu_p \quad \dots\dots\dots(1)$$

$$\& n = \frac{ni^2}{p} \quad \dots\dots\dots(\text{mass action law})$$

Putting this value in equation (1)

$$\therefore \sigma = \frac{ni^2}{p} q \mu_n + pq \mu_p$$

For minimum conductivity

$$\frac{d\sigma}{dp} = 0$$

$$\therefore \frac{d\sigma}{dp} = -\frac{ni^2}{p^2} q \mu_n + q \mu_p = 0$$

$$\therefore q \mu_p = \frac{ni^2}{p^2} q \mu_n$$

$$\therefore p = ni \sqrt{\frac{\mu_n}{\mu_p}} \quad \dots\dots\dots(ii)$$

From mass action law

$$n = \frac{ni^2}{p}$$

$$n = \frac{ni^2}{ni \sqrt{\frac{\mu_n}{\mu_p}}}$$

$$\therefore n = ni \sqrt{\frac{\mu_p}{\mu_n}} \quad \dots\dots\dots(iii)$$

∴ The condition for minimum conductivity is

$$p = ni \sqrt{\frac{\mu_n}{\mu_p}} \text{ and } n = ni \sqrt{\frac{\mu_p}{\mu_n}}$$

Substituting these values in equation (i)

$$\therefore \sigma_{\min} = ni \sqrt{\frac{\mu_p}{\mu_n}} \cdot q \cdot \mu_n + ni \sqrt{\frac{\mu_n}{\mu_p}} \cdot q \cdot \mu_p$$

$$\therefore \sigma_{\min} = 2niq \sqrt{\mu_n \mu_p} + niq \sqrt{\mu_n \mu_p}$$

$$\sigma_{\min} = niq \sqrt{\mu_n \mu_p}$$

This is the expression for minimum conductivity

$$\therefore \frac{\sigma_{\min}}{\sigma_i} = \frac{2niq \sqrt{\mu_n \mu_p}}{niq q \mu_n + niq q \mu_p}$$

$$\therefore \frac{\sigma_{\min}}{\sigma_i} = \frac{2\sqrt{\mu_n \mu_p}}{\mu_n + \mu_p}$$

$$\therefore \sigma_{\min} = \frac{2\sigma_i \sqrt{\mu_n \mu_p}}{\mu_n + \mu_p} \quad \dots\dots\dots(iv)$$

B. Given μ_n = 1000 cm²/ v - sec, μ_p = 600 cm² / v - sec & ni = 10⁻⁶ / Ω - cm

From equation (iv)

$$\sigma_{\min} = \frac{2 \times 10^{-6} \times \sqrt{1000 \times 600}}{1000 + 600}$$

$$\therefore \sigma_{\min} = 9.68 \times 10^{-7} / \Omega - \text{cm}$$

We can observe it is less than intrinsic conductivity.

2. An abrupt Ge junction diode has N_A = 10¹⁶ atoms /cm³ and N_D = 10¹⁴ atoms / cm³ at room temperature is forward biased with a 0.15 volt. Plot the carrier concentration and hole and electron current densities as a function of distance. Assume junction area as 2 mm², diffusion length of electrons and holes as 0.04 cm and 0.05 cm respectively.

(Assume D_n = 100 cm² / sec and D_p = 50 cm² / sec)

Ans.

N_A = 10¹⁶ atoms / cm³ and N_D = 10¹⁴ atoms / cm³

$$n_n = N_D \& p_n = \frac{ni^2}{n_n}$$

$$\therefore p_n = \frac{6.25 \times 10^{26}}{10^{14}}$$

$$\therefore p_n = 6.25 \times 10^{12} \text{ atoms/cm}^3$$

$$\text{now } p_p = N_A \text{ \& } n_p = \frac{n_i^2}{p_p}$$

$$\therefore n_p = \frac{6.25 \times 10^{26}}{10^{16}}$$

$$\therefore n_p = 6.25 \times 10^{16} \text{ atoms/cm}^3$$

Now we know that,

$$P_n(0) = P_{no} (e^{v/v_T} - 1) = 6.25 \times 10^{12} \times (e^{0.15/0.0259} - 1)$$

$$P_n(0) = 2.04 \times 10^{15}$$

$$\text{\& } n_p(0) = n_{po} (e^{v/v_T} - 1) = 6.26 \times 10^{10} (e^{0.15/0.0259} - 1)$$

$$\therefore n_p(0) = 2.04 \times 10^{13}$$

Now $L_n = 0.04 \text{ cm}$ and $L_p = 0.05 \text{ cm}$

$$\therefore n_p(x) = n_p(0) e^{-x/L_n}$$

$$\therefore n_p(x) = 2.04 \times 10^{13} e^{-x/0.04}$$

$$\text{\& } P_n(x) = P_n(0) e^{-x/L_p}$$

$$\therefore P_n(x) = 2.04 \times 10^{15} e^{-x/0.05}$$

Hole diffusion current $I_p(0) = -qD_p \frac{dP}{dx}$

$$= \frac{AqD_p P_{no} (e^{v/v_T} - 1)}{L_p}$$

$$= \frac{0.02 \times 1.6 \times 10^{-19} \times 50 \times 2.04 \times 10^{15}}{0.05}$$

$$\therefore \text{Hole diffusion current } I_p(0) = 6.53 \text{ mA}$$

$$\text{And } I_p(x) = I_p(0) e^{-x/L_p}$$

Similarly

Electron diffusion current

$$I_n(0) = qD_n \frac{dn}{dx}$$



$$= \frac{AqD_n n_{po} (e^{v/v_T} - 1)}{L_n}$$

$$= \frac{0.02 \times 1.6 \times 10^{-19} \times 100 \times 2.04 \times 10^{13}}{0.04}$$

$$\therefore \text{Electron diffusion current } I_n(0)$$

$$= 0.163 \text{ mA}$$

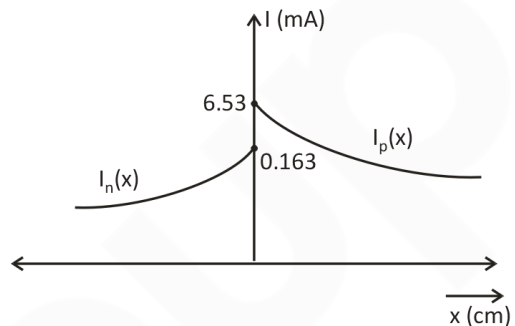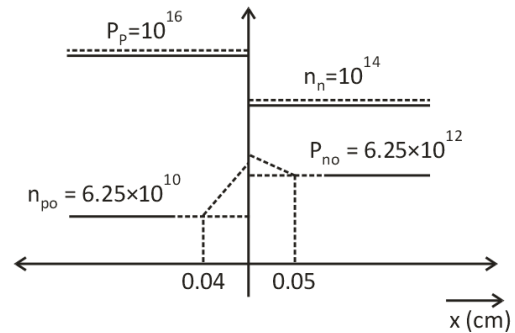
$$\text{And } I_n(x) = I_n(0) e^{-x/L_n}$$



3. For the circuit shown transistor θ_1 & θ_2 both operate in active region with $V_{BE1} = V_{BE2} = 0.7 \text{ V}$, $\beta_1 = 75$ & $\beta_2 = 50$ then

a) Find the currents I_{B1} , I_{C1} , I_{E1} , I_{B2} , I_{C2} , I_1 , I_2

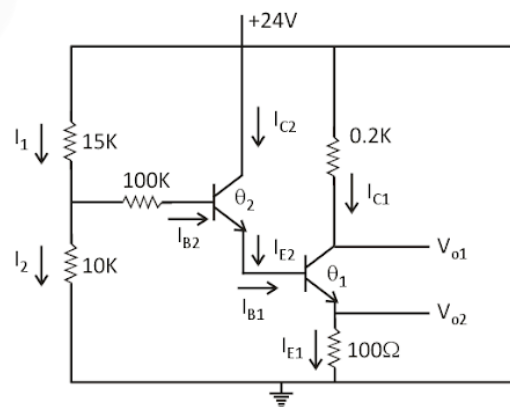b) Find output voltages V_{o1} and V_{o2}



Applying Thevenin's theorem we get

$$V_{th} = \frac{V_{CC}}{R_1 + R_2} \times R_2$$

$$= \frac{24}{15 + 10} \times 10$$


$$\therefore v_{th} = 9.6 \text{ V}$$

$$\text{\& } R_{th} = R_1 \parallel R_2$$

$$= 15 \parallel 10$$

$$R_{th} = 6 \text{ k}\Omega$$

\therefore Equivalent circuit will be

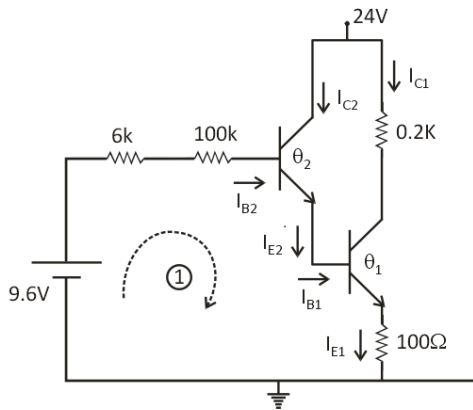

Applying KVL in loop (1)

$$- 9.6 + (106) I_{B2} + 0.7 + 0.7 + 0.1 I_{E1} = 0 \quad (i)$$

Now $I_{E2} = I_{B1}$

$$\therefore (1 + B_2) I_{B2} = I_{B1}$$

$$\& I_{E1} = (1+B_1) I_{B1} = (1+B_1) (1+B_2) I_{B2}$$

$$I_{E1} = 76 \times 51 \times I_{B2}$$

$$\therefore I_{E2} = 3876 I_{B2}$$

\therefore Equation (I) become,

$$- 9.6 + 106 I_{B2} + 0.7 + 0.7 + 0.1 \times 3876 I_{B2} = 0$$

$$\therefore 493.6 I_{B2} = 8.2$$

$$\therefore I_{B2} = 0.01661 \text{ mA}$$

$$\therefore I_{B2} = 16.61 \mu\text{A}$$

$$\therefore I_{C2} = B_2 I_{B2}$$

$$= 50 \times 0.01661$$

$$\therefore I_{C2} = 0.83 \text{ mA}$$

$$\& I_{E2} = I_{B2} + I_{C2}$$

$$= 0.01661 + 0.83$$

$$I_{E2} = 0.8472 \text{ mA}$$

Now $I_{E2} = I_{B1}$

$$\therefore I_{B1} = 0.8472 \text{ mA}$$

$$\therefore I_{C1} = B_1 I_{B1}$$

$$= 75 \times 0.8472$$

$$\therefore I_{C1} = 63.54 \text{ mA}$$

$$\& I_{E1} = I_{C1} + I_{B1}$$

$$= 63.54 + 0.8472$$

$$I_{E1} = 64.38 \text{ mA}$$

Now $V_{O1} = V_{CC} - I_{C1} \times 0.2$

$$= 24 - 63.54 \times 0.2$$


$$\therefore V_{O1} = 11.292 \text{ V}$$

And $V_{O2} = I_{E1} \times 0.1$

$$= 64.38 \times 0.1$$

$$\therefore V_{O2} = 6.438 \text{ V}$$

Now again redrawing the given circuit.

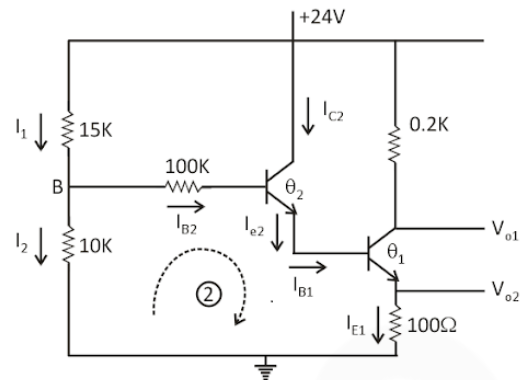

Applying KVL in loop (2)

$$\therefore -10 I_2 + 100 I_{B2} + 0.7 + 0.7 + 0.1 I_{E1} = 0$$

$$\therefore 10 I_2 = 100 \times 0.01661 + 0.7 + 0.7 + 0.1 \times 64.38$$

$$\therefore 10 I_2 = 9.497$$

$$\therefore I_2 = 0.9497 \text{ mA}$$

Now applying KCL at node B

$$\therefore I_1 = I_2 + I_{B2}$$

$$= 0.9497 + 0.01661$$

$$\therefore I_1 = 0.9663 \text{ mA}$$

4. A step-graded germanium diode has a resistivity of $2.5 \Omega\text{-cm}$ on the p side and $1.5 \Omega\text{-cm}$ on the n side. Calculate the height of the potential barrier.

For germanium $\mu_p = 1800 \text{ cm}^2/\text{V-s}$ and $\mu_n = 3800 \text{ cm}^2/\text{V-s}$ and $n_i = 2.5 \times 10^{13}/\text{cm}^2$ at 300°K . Prove formula used.

Sol.

Given, step-graded germanium diode has resistivity $\rho_p = 2.5 \Omega\text{-cm}$

Resistivity of n-side $\rho_n = 1.5 \Omega\text{-cm}$

Mobility of hole = $1800 \text{ cm}^2/\text{V-s}$,

Mobility of electron = $3800 \text{ cm}^2/\text{V-s}$

Intrinsic concentration $n_i = 2.5 \times 10^{13}/\text{cm}^2$

Acceptor concentration $N_A = ?$

$$\sigma_p = p q \mu_p \approx N_A q \mu_p \dots\dots\dots(\text{for p-type})$$

$$\frac{1}{\rho_p} = N_A q \mu_p \Rightarrow N_A = \frac{1}{\rho_p q \mu_p}$$

$$= \frac{1}{2.5 \times 1.6 \times 10^{-19} \times 1800}$$

$$N_A = 1.388 \times 10^{15} \text{ atoms/cm}^3$$

Donor concentration $N_D = ?$

$$\sigma = n q \mu_n \approx N_D q \mu_n (\text{for n-type})$$

$$\frac{1}{\rho_n} = N_D q \mu_n \Rightarrow N_D = \frac{1}{\rho_n q \mu_n}$$

$$= \frac{1}{1.5 \times 1.6 \times 10^{-19} \times 3800}$$


$N_D = 1.096 \times 10^{15} \text{ atoms/cm}^3$

Height of potential barrier

$$V_0 = \frac{KT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

$$\Rightarrow V_0 = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

Formula proof

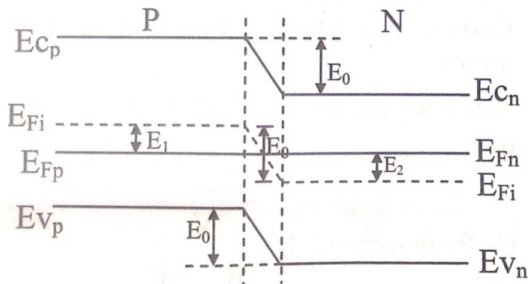

$$E_1 = E_{F_{Pi}} - E_{F_p} = KT \ln \left(\frac{N_A}{n_i} \right)$$

$$E_2 = E_{F_n} - E_{F_{ni}} = KT \ln \left(\frac{N_D}{n_i} \right)$$

$$\Rightarrow E_0 (\text{eV}) = E_1 + E_2 = E_{C_p} - E_{C_n} = E_{V_p} - E_{V_n}$$

$$\Rightarrow E_0 (\text{eV}) = E_1 + E_2 = KT \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

$$V_0 (\text{V}) = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

$E_{Fi} \rightarrow$ Fermi level in intrinsic


$E_{Fp} \rightarrow$ Fermi level in P-type semiconductor

$E_{Fn} \rightarrow$ Fermi level in n-type semiconductor


$$\therefore V_0 = 0.026 \ln \left(\frac{1.388 \times 10^{15} \times 1.096 \times 10^{15}}{(2.5 \times 10^{13})^2} \right)$$

$$= 0.2027 \text{ V}$$

5. For the circuits in fig. $\mu_n C_{OX} = 2.5 \mu\text{p}$
 $C_{OX} = 20 \mu\text{A/V}^2$, $|V_t| = 1\text{V}$, $\lambda = 0$, $\gamma = 0$, $L = 5 \mu\text{m}$, and $W = 15 \mu\text{m}$, unless otherwise specified. Find the labelled currents and voltages.

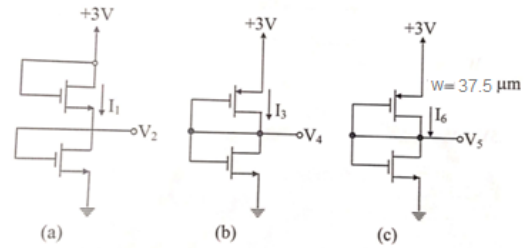

Sol.
(a)

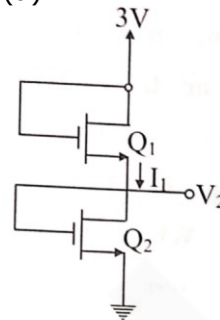

(a)

Q_2, Q_1 operating in saturation $i_{D1} = i_{D2}$


Also $V_{GS1} = V_{GS2}$

$$\therefore 3\text{V} = V_{GS1} + V_{GS2} \Rightarrow V_{GS1} = V_{GS2} = 1.5\text{V},$$

$$V_2 = 1.5\text{V}$$

$$I_1 = \frac{1}{2} \times 20 \times \frac{15}{5} (1.5 - 1)^2 = 7.5 \mu\text{A}$$

(b)

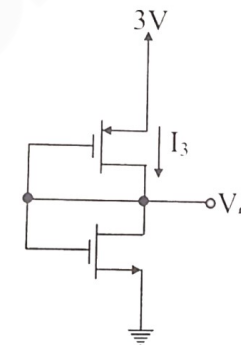

(b)

Both transistors have $V_D = V_G$ and therefore they are operating in saturation $i_{D1} = i_{D2}$

$$\frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_4 - 1)^2 = \frac{1}{2} \mu_p C_{OX} \frac{W}{L} (3 - V_4 - 1)^2$$


$$\therefore 2.5 (V_4 - 1)^2 = (2 - V_4)^2$$

$$1.58 (V_4 - 1)^2 = \pm (2 - V_4) \Rightarrow V_4 = 1.39$$

$$V_4 \approx 1.4\text{V}$$

$$I_3 = \frac{1}{2} \times 20 \times \frac{15}{5} (1.39 - 1)^2 = 4.6 \mu\text{A}$$

(c)

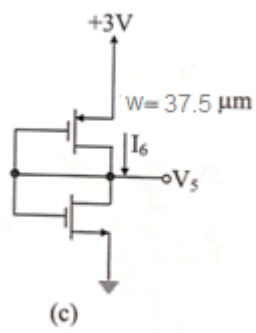

$$\frac{W_1}{L_1} = \frac{37.5}{5} = 7.5$$

$$\frac{W_2}{L_2} = \frac{15}{5} = 3$$

$$\frac{W_1}{L_1} = 2.5 \times \frac{W_2}{L_2}$$

$$\text{Now } \mu_n C_{OX} \frac{W_2}{L_2} = \mu_p C_{OX} \frac{W_1}{L_1}$$

$$\text{So } i_{D1} = i_{D2}$$

$$\Rightarrow V_{GS1} = V_{GS2} = \frac{3}{2} = 1.5V = V_5$$

$$I_6 = \frac{1}{2} \times 20 \times \frac{15}{5} (1.5 - 1)^2 = 7.5 \mu A$$

India's #1 Online Preparations App for GATE, ESE, State Engg. Exams, PSU's & JE Exams

- › Latest Job and Exam Notifications
- › Get Queries Resolved by Experts & Gradians
- › Practice 5000+ Topic wise Questions & earn Coins
- › All India Test Series with Latest Pattern
- › Exam Oriented Online Classroom Platform

