

ESE (Mains) 2019

Electronic Measurement & Instrumentation

Important Questions with Solutions



1. A resistor has voltage drop of 110.2V and current of 5.5A. the uncertainties in the measurement of voltage and current are $\pm 0.5V$ and ± 0.01 respectively calculate the uncertainty in power calculation.

Ans. Power (P) = voltage x current = V x I
 = 110.2 x 5.5
 = 606.1 w

Uncertainty in power =

$$\sqrt{\left(\frac{\partial P}{\partial V}\right)^2 w_v^2 + \left(\frac{\partial P}{\partial I}\right)^2 w_i^2} \quad (i)$$

Where w_v and w_i are uncertainties in calculation of voltage and current respectively.

$$\frac{\partial P}{\partial V} = \frac{\partial}{\partial V} VI = I = 5.5 \quad (ii)$$

$$\frac{\partial P}{\partial I} = \frac{\partial}{\partial I} VI = V = 110.2 \quad (iii)$$

By i, ii, iii

Uncertainty in power =

$$\sqrt{[5.5]^2 \times 0.5 + [110.2]^2 \times 0.01}$$


= ± 2.962 w

Uncertainty in power =

$$\pm \frac{2.962}{606.1} \times 100 = \pm 0.4888\%$$

2. A PMMC voltage has a reading of 9V when it is measuring a voltage source with an internal resistance of finite value on its scale of 10V. When scale of this is changed to 20v full scale then reading of 13 is obtained. Given sensitivity of voltmeter to be 50 k Ω /V. Find value of the voltage source and its internal resistance R.

Ans.

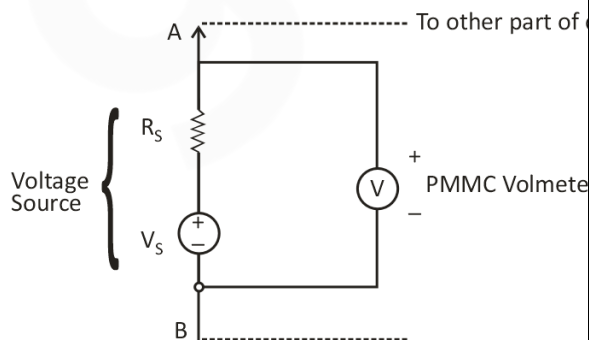

V_v = voltage across voltmeter =

$$V_s \frac{R_s}{R_s + R_v} \quad \dots\dots(i)$$

V_s = voltage of source

R_s and R_v are resistance of source & voltmeter respectively.

Case i

$$V_v = 9V, \quad V_s = ? \quad R_s = ?$$

$$R_v = \text{sensitivity} \times \text{range} = 50 \text{ k} \Omega / \text{V} \times 10 \text{ v}$$

$$= 500 \text{ k} / \Omega$$

by (1)

$$\therefore 9 = V_s R_v$$

$$\boxed{R_s + 500}$$

$$9 (R_s + 500) = V_s R_v$$

$$V_s \cdot (500) = 9 (R_s + 500) \quad \dots\dots(ii)$$

Case ii

$$V_v = 13V \quad V_s = ?$$

$$R_s = ?$$

$$R_v = 50 \text{ k} \Omega / \text{V} \times 20 \text{ v}$$

$$R_v = 1000 \text{ k} \Omega$$

by (1)

$$13 = \frac{V_s R_v}{(R_s + 1000)}$$

$$V_s \times (1000) = 1.5 (R_s + 1000)$$

.....(iii)

by (ii) & (iii)

$$\frac{9(R_s + 500)}{500} = \frac{13(R_s + 1000)}{1000}$$

$$18 R_s + 9000 = 13 R_s + 13000$$

$$\text{So } 5R_s = 4000$$


$$R_s = 800$$

3. Given a meter of range 0 – 1mA, having internal resistance of 5 Ω . How do you extend the range of it to 10 mA?

Ans. To extend the range of ammeter a shunt resistance is applied to ammeter to bypass excess current through this shunt resistor.

Only rated current flows through ammeter. But now the dial of ammeter has to be recalibrated by multiplying the values with multiplication factor m. by following above steps the range of ammeter is extended.

Numerical :

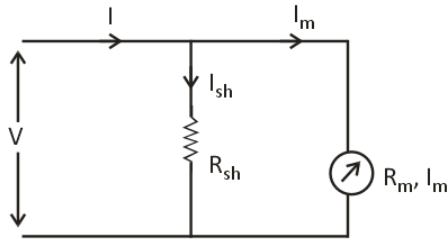

R_m = internal meter resistance
 R_{sh} = external shunt resistor to bypass excess current

I_m = meter current

I_{sh} = current in shunt arm

I = rated current of extended range meter

$\therefore V = I_m R_m = I_{sh} R_{sh}$ [KVL]

$I_m R_m = [I - I_m] R_{sh}$ ($\therefore I = I_m + I_{sh}$ KCL)

$$R_{sh} = \frac{R_m}{(m-1)} \quad \text{where } \left(m = \frac{I}{I_m} \right)$$

m = multiplication factor

$I = 10\text{mA}$, $I_m = 1 \text{ mA}$, $R_m = 5\Omega$,

$$m = \frac{I}{I_m} = 10$$

$$\therefore R_{sh} = \frac{5}{10-1}$$

$$R_{sh} = \frac{5}{9} = 0.556\Omega$$


So, by connecting shunt resistance of 0.556Ω and multiplying dial value by $m = 10$ the range of ammeter will be extended from 1 mA to 10 mA .

4. A) explain the following terms with respect to measurement system:-

- i) accuracy
- ii) precision
- iii) resolution

- iv) sensitivity
- v) linearity

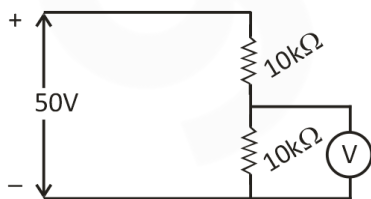B) A voltmeter is connected across $10\text{k}\Omega$ resistor as shown in figure



The voltmeter shows 24.5V , but it must have shown 25V . Why is this happening? Explain

Ans. i) Accuracy: The closeness with which instrument value or reading approaches the true value or quantity

being measured. It means conformity to truth.


ii) Precision: It is measure of reproducibility of the measurements precision is a measure of degree of agreement within a group of measurements.

iii) Resolution: The smallest increment in the quantity being measured that can be measured with certainty by an instrument.

iv) Sensitivity: sensitivity of an instrument is ratio of magnitude of output signal / response to the magnitude of input signal / quantity being measured.

v) linearity: linearity is simply measure of maximum deviation of calibration points from the straight line.

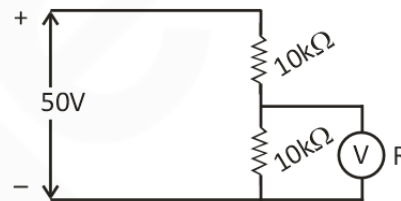B) The reduction in measured value of voltmeter is due to loading effect to voltmeter as voltmeter has some finite input resistance



Had the internal resistance of voltmeter infinite then no loading effect will occur and value shown by voltmeter will be true value itself

Let R_v be internal resistance of voltmeter So, R_v is parallel to $10\text{k}\Omega$ resistance and R_{eq} is equivalent Resistance

$$R_{eq} = R_v || 10\text{k}\Omega = \frac{10R_v}{10 + R_v}$$

\therefore voltage shown by voltmeter =

$$50 \times \frac{R_{eq}}{R_{eq} + 10\text{k}} \quad (\text{KVL})$$

$$24.5 = \frac{50R_{eq}}{R_{eq} + 10}$$

$$24.5 R_{eq} + 245 = 50 R_{eq}$$

$$R_{eq} = \frac{245}{25.5} = 9.60\text{k}\Omega$$

$$R_{eq} = 9.60\text{k}\Omega$$

$$R_{eq} = \frac{10R_v}{10 + R_v} = 9.60$$

$$10R_v = 96 + 9.6 R_v$$

$$0.4 R_v = 96$$

$$R_v = \frac{96}{0.4} = 240k\Omega$$

Therefore $R_v = 240k\Omega$ and this


resistance of voltmeter causes the net voltage to reduce and is called loading effect

5. Define gauge factor for strain gauge and derive the expression for the same. Also explain the significance of piezo-resistivity in the expression.

Ans. If a metal is stretched or compressed, its resistance changes on account of fact that both the length and diameter / area of conductor changes. Also there is change in value of resistivity when strained.

Gauge factor derivation:

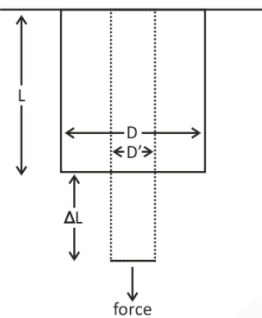Consider a wire having initial length L and diameter D when stress or force is applied its length increases by ΔL and diameter decreases to D'



$$\therefore \text{Resistance } R = \rho \frac{L}{A}$$

ρ = resistivity

L = length of wire

$$A = \text{area of wire} = \frac{\pi D^2}{4} \quad (i)$$

D = diameter of wire

$$R = \rho \frac{L}{A}$$

$$\ln R = \ln \rho + \ln(L) - \ln(A) \quad [\text{taking natural log both sides}]$$

differentiate the above equation with respect to stress (σ)

$$\frac{1}{R} \frac{dR}{d\sigma} = \frac{1}{\rho} \frac{d\rho}{d\sigma} + \frac{1}{L} \frac{dL}{d\sigma} - \frac{1}{A} \frac{dA}{d\sigma} \quad (ii)$$

$$\therefore A = \frac{\pi D^2}{4}$$

$$\frac{dA}{d\sigma} = \frac{\pi(2D)}{4} \frac{dD}{d\sigma} = \frac{\pi D}{2} \frac{dD}{d\sigma}$$

$$\therefore \frac{1}{A} \frac{dA}{d\sigma} = \frac{4^2}{\pi D^2} \times \frac{\pi D}{2} \frac{dD}{d\sigma} = \frac{2}{D} \frac{dD}{d\sigma}$$

$$\boxed{\frac{1}{A} \frac{dA}{d\sigma} = \frac{2}{D} \frac{dD}{d\sigma}} \quad \dots\dots(iii)$$

by (ii) & (iii)

$$\frac{1}{R} \frac{\partial R}{\partial \sigma} = \frac{1}{\rho} \frac{d\rho}{d\sigma} + \frac{1}{L} \frac{dL}{d\sigma} - \frac{2}{D} \frac{dD}{d\sigma}$$

Rearranging above equation for small variation:-

$$\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} - 2 \frac{dD}{D}$$

$$\frac{\Delta R}{R} = \frac{\Delta \rho}{\rho} + \frac{\Delta L}{L} - 2 \frac{\Delta D}{D}$$

$$\frac{\Delta R/R}{\Delta L/L} = \left\{ 1 - 2 \frac{\Delta D/D}{\Delta L/L} + \frac{\Delta \rho/\rho}{\Delta L/L} \right\}$$

$$\text{Gauge factor} = \frac{\Delta R/R}{\Delta L/L} = \left\{ 1 - \frac{2 \Delta D/D}{\Delta L/L} + \frac{\Delta \rho/\rho}{\Delta L/L} \right\} \quad \dots\dots$$

$$\therefore \left[\frac{-\Delta D}{\Delta L} \right] = \text{poissons ratio} = \mathcal{G}$$

$$\therefore \text{Gauge factor} = \frac{\Delta R/R}{\Delta L/L} = \left\{ 1 + 2\mathcal{G} + \frac{\Delta \rho/\rho}{\Delta L/L} \right\}$$

→ for resistor made of metal resistivity is not changed so gauge factor depends on GF = (1+2G) dimensions

→ For resistor made of semiconductors so gauge factor depends mainly on

$\left(\frac{\Delta \rho/\rho}{\Delta L/L} \right)$. As resistivity changes sharply.

India's #1 Online Preparations App for GATE, ESE, State Engg. Exams, PSU's & JE Exams

- › Latest Job and Exam Notifications
- › Get Queries Resolved by Experts & Gradians
- › Practice 5000+ Topic wise Questions & earn Coins
- › All India Test Series with Latest Pattern
- › Exam Oriented Online Classroom Platform

