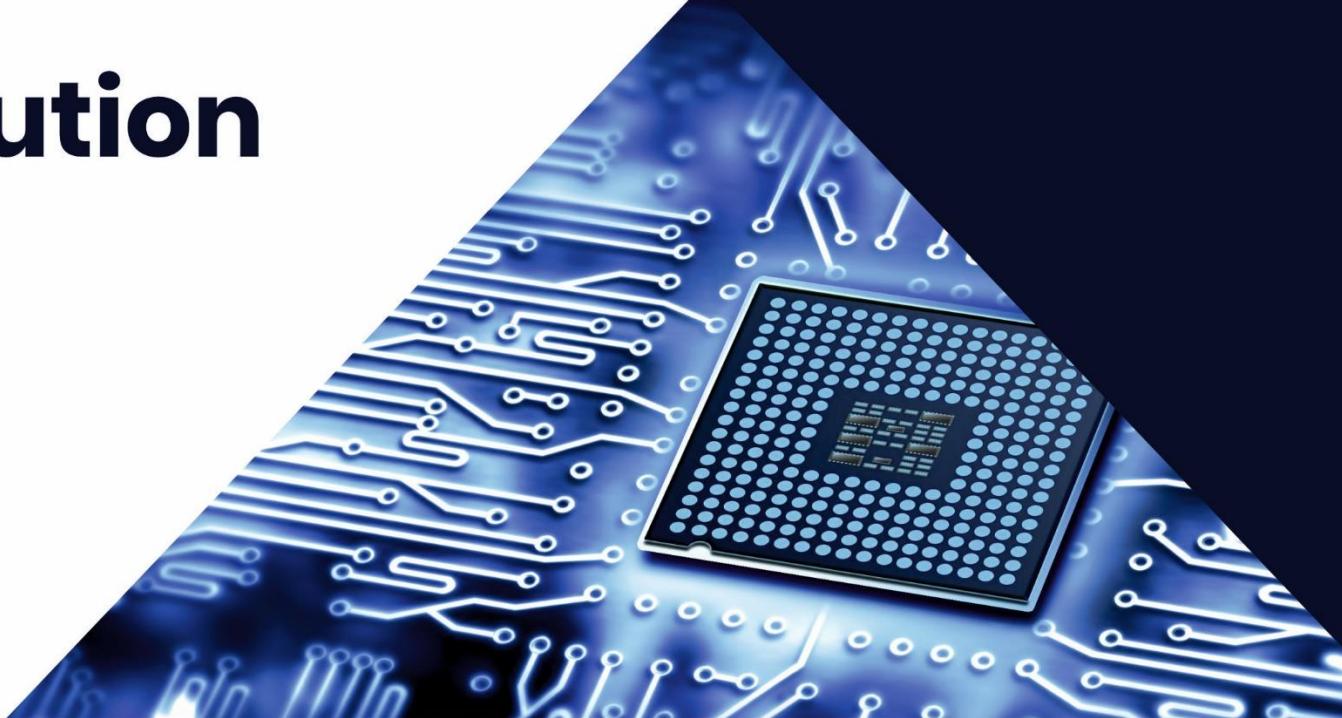


# **GATE 2020**

**Electronics &  
Communication  
Engineering**

**Solution**



**GENERAL APTITUDE**

1.

**ANS. C**

**SOL.** The untimely loss of life is a cause of serious global concern as thousands of people get killed **in** accidents every year while many other die **of** diseases like cardiovascular

2.

**ANS. D**

**SOL.** He was not only accused of theft **but also** of conspiracy.

3.

**Ans. D**

**SOL.** Explicit: Implicit:: Express: **Repress**

4.


**ANS. C**

**SOL.** The French-speaking couple were upset at the English announcements being longer than the French ones.

5.

**Ans. A**

**Sol.** Let  $x_2 > x_1$

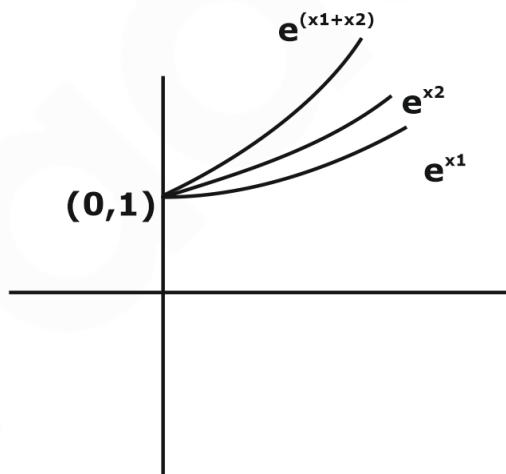

Check

$$\text{Let } x_2 = 3$$

$$x_1 = 2$$

$$e^{x_1+x_2} = e^5$$

$$e^{x_1} = e^2$$

$$e^{x_2} = e^3$$

Then  $e^5 > e^2 + e^3$ . Which is true

**Vision 2021 Batch-3****A Course for ESE & GATE Electronics Aspirants****START FREE TRIAL**

6.

**ANS. B****SOL.** East Asian crisis → subprime lending crisis → banking crisis → global financial crisis.

7.

**ANS. D****Sol.** 60 units of min hand = 5 units of hour hand.

$$\therefore 15 \text{ units of min hand} = \frac{5 \times 15}{50} \text{ units of hour hand}$$


$$= 1.25 \text{ units of hour hand}$$

$$60 \text{ units} = 360^\circ$$

$$1.25 \text{ units} = 6 \times 1.25^\circ$$

$$= 7.5^\circ.$$

8.

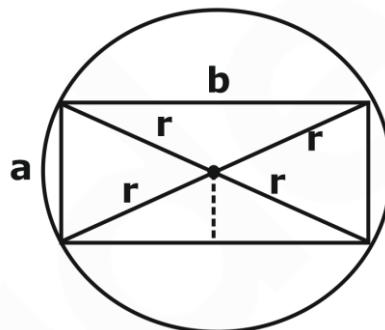**ANS. B****Sol.**

$$r^2 = \frac{a^2}{4} + \frac{b^2}{4}$$

$$\therefore \frac{b^2}{4} = r^2 - \frac{a^2}{4}$$

$$b = \pm \sqrt{4r^2 - a^2}$$

$$b^2 = 4r^2 - a^2$$

$$\text{Area } A = ab$$

$$= \pm a \sqrt{4r^2 - a^2}$$

$$A^2 = a^2 (4r^2 - a^2)$$

$$\frac{dA^2}{da} 4r^2 \times 2a - 4a^3 = 0$$

$$4a (2r^2 - a^2) = 0$$

$$\Rightarrow a^2 = 2r^2$$

$$\therefore b^2 = 4r^2 - 2r^2$$

**Vision 2021 Batch-3**

A Course for ESE &amp; GATE Electronics Aspirants

**START FREE TRIAL**

$$= 2r^2.$$

$$\therefore \text{area of rectangle} = (r\sqrt{2})^2$$

$$= 2r^2.$$

$$\text{area of circle} = \pi r^2.$$

$$\therefore \text{Required area} = (\pi - 2)r^2$$

9.

**Ans. B**

**Sol.**  $Ax^2 - bx + c = 0$

$$2\beta = \frac{b}{a} \Rightarrow \beta = \frac{b}{2a} \quad \dots \dots \dots (1)$$

$$\beta^2 = \frac{c}{a} \quad \dots \dots \dots (ii)$$

$$(i) \times (ii) \text{ given } \beta^3 = \frac{bc}{2a^2}$$

10.

**Sol.** No of students enrolled in P =  $3 + 5 + 5 + 6 + 4 = 23$

No of students enrolled in Q =  $4 + 7 + 8 + 7 + 5 = 31$

$$\therefore \text{ratio} = \frac{23}{(31-23)15} = \frac{23}{8} = 2.875$$

**Vision 2021** Batch-3

A Course for ESE & GATE Electronics Aspirants

[START FREE TRIAL](#)

## TECHNICAL

11.

**ANS. (6.25 -6.25)****Sol.**Given, characteristic impedance  $Z_0 = 50 \Omega$ Load impedance  $Z_L = 400$ And input impedance  $Z_{in} = (Z_0)^2 / Z_L$ 


$$\begin{aligned} &= 50^2 / 400 \\ &= 6.25 \Omega \end{aligned}$$

12.

**ANS. ( 48-48)****Sol.** Old Parameters –

$$V_1 = 40i_1 + 60i_2 \quad \dots(i)$$

$$V_2 = 60i_1 + 120i_2 \quad \dots(ii)$$

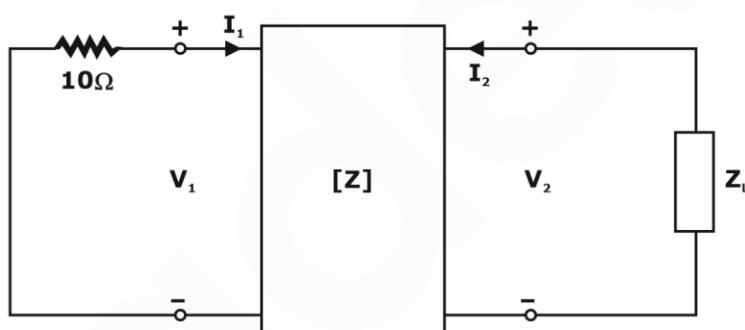
Z<sub>th</sub> by testing method

KVL in mesh (i)

$$10i_1 + V_1 = 0$$

$$V_1 = -10i_1$$

$$\text{And } i_2 = 1A$$

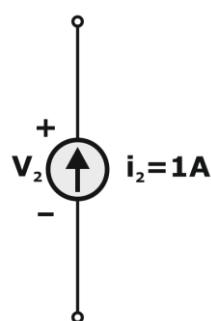

From eq. (i)

$$V_1 = 40i_1 + 60 \times 1 \quad \dots(iv)$$

**Vision 2021 Batch-3**

A Course for ESE &amp; GATE Electronics Aspirants

START FREE TRIAL

$$-10i_1 = 40i_1 + 60$$

$$i_1 = -6/5$$

$$V_2 = 60 \times \left( -\frac{6}{5} \right) + 120 \times 1$$

$$= -72 + 120$$

$$= 48 \text{ V}$$

∴ to deliver max. power to load  $Z_L$

$$Z_L = R_{th}$$

$$\therefore Z_L = \frac{V_2}{I_2} = \frac{48}{1}$$

$$= 48 \Omega$$

13.


**Ans. B**

**Sol.**  $U_{max}$  occurs at the edges of the depletion region in the device..

14.

**ANS.-B**

**Sol.**

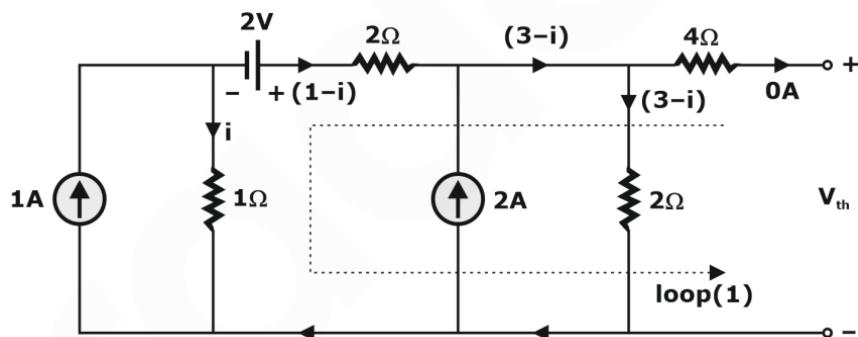

KVL in Loop (i)

$$(i \times 1) - 2(3 - i) - 2(1 - i) + 2 = 0$$

$$i - 6 + 2i - 2 + 2i + 2 = 0$$

$$5i = 6$$

$$i = 1.2 \text{ A}$$

$$\therefore V_{th} = 2 \times (3 - i)$$

$$= 2 \times (3 - 1.2)$$

$$= 3.6 \text{ volts}$$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

15.

**ANS. A**

$$\begin{aligned}
 \text{Sol. } E_{F_i} &= \frac{E_C + E_V}{2} - \frac{kT}{2} \ln \frac{N_C}{N_V} \\
 &= \frac{E_g}{2} - \frac{kT}{2} \ln \frac{N_C}{2N_C} (\because N_V = 2N_C) \\
 E_{F_i} &= \frac{E_g}{2} - \frac{kT}{2} \ln \left( \frac{1}{2} \right) \\
 E_{F_i} &= \frac{E_g}{2} + 9.01 \text{ meV}
 \end{aligned}$$

16.

**Ans. ( 6 - 6 )**

$$\text{Sol. Given } Y = \int_{-\infty}^{\infty} w(t)s(t)dt, \text{ where } \phi(t) = \begin{cases} 1 & 5 \leq t \leq 7 \\ 0 & \text{otherwise} \end{cases}$$

$$S_w(f) = 3 \text{ W/Hz}$$

$$E(Y) = \int_{-\infty}^{\infty} E(w(t))\phi(t)dt = 0$$

$$\begin{aligned}
 E[Y^2] &= S_w(f) \quad \text{energy } \varphi(t) \\
 &= 6
 \end{aligned}$$

$$\text{Var}[Y] = 6 - 0 = 6$$

17.

**ANS. (0.25 -0.25)**

**Sol.** There can be 4 outcomes.

$$\{HH\}, \{HT\}, \{TH\}, \{TT\}.$$

∴ Let 1 is denoted by head

∴ Let 0 is denoted by Tail.

$$\therefore M = \{1 1 0 0\}$$

$$N = \{1 0 1 0\}$$

$$X = \min(M, N) = 1 0 0 0.$$

$$P(X) = \frac{1}{4} \frac{1}{4} \frac{1}{4} \frac{1}{4} / 4$$

$$\text{Now, } X = 1$$

When {H H} comes up

$$\therefore P(X = 1) = P[\{H H\}]$$

$$= \frac{1}{4}$$

Now X = 0 when {H T}, {T H} or {T T} come up

When

$$\therefore P(X = 0) = \frac{1}{4}, \quad \therefore E(x) = \frac{1}{4} \times 1 = 0.25$$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants


**START FREE TRIAL**

18.

**ANS.C**

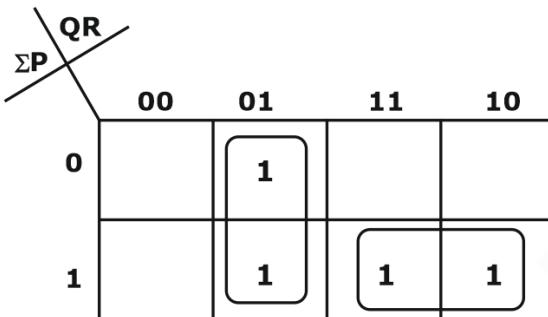**Sol.**

$$\begin{aligned} F &= \bar{P}\bar{Q}R + P\bar{Q}R + PQ \\ &= \bar{P}\bar{Q}R + P\bar{Q}R + PQR + PQR \\ &= \Sigma m(1, 5, 6, 7) \end{aligned}$$



		00	01	11	10
		0	1		
		1	1	1	1

19.

**ANS-D**

**Sol.**

$$\text{error probability} = a$$

$$\text{correct probability} = 1 - a$$

'N' Bits So

$$\text{Correct probability} = (1 - a)(1 - a) \dots 'N' \text{ times} = (1 - a)^N$$

$$\text{Erroneous probability} = 1 - \text{correct probability} = [1 - (1 - a)^N].$$

20.

**ANS. (160 -160)**

**Sol.** Closed loop characteristic equations

$$1 + G(s) H(s) = 0$$

$$1 + \frac{K(s+11)}{s(s+2)(s+8)} = 0$$

$$s^3 + 10s^2 + 16s + Ks + 11K = 0$$

$$s^3 + 10s^2 + (16 + K)s + 11K = 0$$

$$\begin{array}{c|cc}
s^3 & 1 & 16+K \\
s^2 & 10 & 11K \\
s^1 & \frac{10(16+K)-11K}{10} & 0 \\
\hline
s^0 & 11K & 0
\end{array}$$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

For marginal stable system

$$\frac{10(16 + K) - 11K}{10} = 0$$


$$160 + 10K - 11K = 0$$

$$K = 160$$

21.

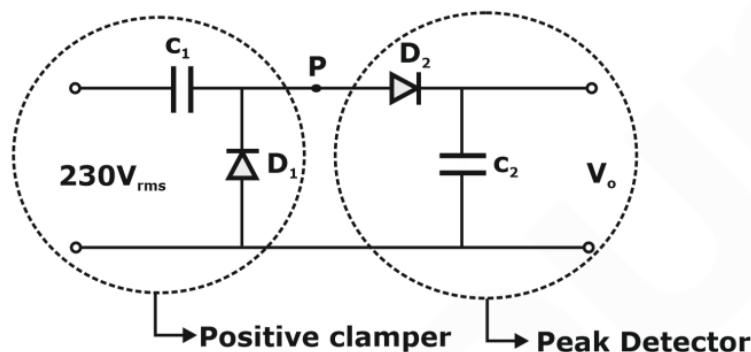**ANS. (644 -657)**

**Sol.** The circuit shown is a voltage doubler. So  $V_o = 2V_m$



So the peak value at 'P' is  $2V_m$ , Then the voltage across  $C_2$  which is  $2V_m$ .

$$\therefore V_o = 2V_m \text{ where } V_m = 230\sqrt{2} = 325.27V$$

$$V_o = 650.5V$$

22.

**Ans. C**

**Sol.**  $Y(n) = \max_{-\infty \leq K \leq n} [X(K)]$

$$Y(n) = \max[\delta(K)] = 1 \quad -\infty \leq K \leq n$$

$Y(n)$  is 1 for all  $n$ .

23.

**Ans. D**

**Sol.**  $Y(n) = \sum_{K=0}^3 (-1)^K X(n-K)$

$$Y(n) = X(n) - X(n-1) + X(n-2) - X(n-3)$$

$$Y(z) = 1 - z^{-1} + z^{-2} - z^{-3}$$

$$y(z) = \frac{z^3 - z^2 + z^1 - 1}{z^3}$$

3 poles at  $z = 0$  and number of zeros is 4

So the option (D) is correct

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

24.

**Ans. C****Sol.**

25.

**Ans. D****Sol.**  $D^2 - 6D + 9 = 0$ 

$$\Rightarrow (D - 3)^2 = 0$$

 $D = 3, 3 \rightarrow \text{equal roots}$ 

$$\therefore y = (c_1 + c_2)e^{3x}.$$

26.

**ANS. 2.80 -2.85****Sol.** Given

$$V_s = 200 \cos 5t$$

$$i(t) = 10 \cos\left(5t - \frac{\pi}{4}\right)$$

By KVL

$$V_s(t) = i(t) Z$$

$$\text{And } z = R + j\omega L = R + jX_L$$

$$|Z| = \sqrt{R^2 + X_L^2} = \frac{V_m}{i_m} = \frac{200}{10}$$

$$\therefore |Z| = 20$$

$$\text{Or simply } \sqrt{R^2 + X_L^2} = 20 \quad \dots(i)$$

Given,

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left(\frac{X_L}{R}\right)$$

$$= 45^\circ$$

$$\therefore \frac{X_L}{R} = \tan(45^\circ) = 1$$

$$\therefore X_L = R \quad \dots(ii)$$

From equation (i) and (ii)

$$\sqrt{R^2 + X_L^2} = 20$$

$$\sqrt{R^2 + R^2} = 20$$

$$R\sqrt{2} = 20$$

$$R = 14.14 \Omega$$

$$\text{Or } \omega L = 14.14$$

$$\text{Given } \omega = 5 \text{ rad/sec}$$


$$\therefore L = 2.828 \text{ H}$$

**Vision 2021 Batch-3****A Course for ESE & GATE Electronics Aspirants****START FREE TRIAL**

27.

**ANS. (6 -6)**

**Sol.** Applying virtual ground

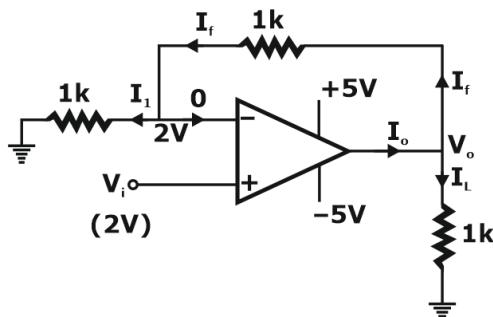

$$I_1 = I_f$$

$$\frac{2-0}{1K} = \frac{V_o - 2V}{1K}$$

$$2mA = \frac{V_o - 2V}{1K}$$

$$V_o = 4V$$

$$\therefore I_C = \frac{V_o - 0}{1K} = \frac{4-0}{1K} = 4mA$$

$$\therefore I_o = I_L + I_f = 4 mA + 2 mA (\because I_f = I_1 = 2mA)$$

$$= 6mA$$

28.

**Sol.** 3.050 -3.080

$$(13A)_{16} = (?)_{10}$$

$$= 1 \times (16)^2 + 3 \times (16)^1 + 10 \times (16)^0 \quad \{A = 10\}$$

$$= 256 + 48 + 10$$

$$= 314$$

$$(13A)_{16} = (314)_{10}$$

Output voltage = Resolution  $\times$  Decimal equivalent

$$= \frac{10}{2^{10}} \times 314 = \frac{10}{2^{10}} \times 314 = \frac{10}{1024} \times 314 = 3.065$$

29.

**ANS.** 14 - 14

**Sol.**



**Vision 2021** Batch-3

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

16K

$16 \times 2^{10} \times 8$  Bit

$2^4 \times 2^{10} \times 8$  bits

[8 data line for 8085 microprocessor]

$2^{14} \times 8$  Bits

$n = 14$

So, required address line = 14

30.

**Ans. C**

**Sol.** Given number of closed loop poles 2 in contour and number of closed loop 3 zero in contour.

$P = 2$  and  $Z = 3$ . So effective number of encirclements to the origin is once in clockwise direction.

31.

**ANS. (0.5-0.5)**

**Sol.** There are only two symbols

$$X = -2$$

$$X = 2$$

Maximum entropy occurs for equal probability

$$H(X)_{\max} = \log_2^2 = 1$$

$$P(X = 2) = \frac{1}{2}$$

$$P(X = -2) = \frac{1}{2}$$

32.

**ANS. B**

**Sol.**  $Z = jX$

$$R = 0 \text{ (constant)}$$

Hence, its mapping to the smith chart will represent a circle which has centre

$$\left( \frac{R}{R+1}, 0 \right) \equiv (0, 0)$$

33.

**ANS. C**

$$\text{Sol. } \frac{\partial f}{\partial x} = e^{(1-x \cos y)} (-\cos y) + ze^{(-\frac{1}{1+y^2})}$$

$$\left( \frac{\partial f}{\partial x} \right)_{(1,0,e)} = e^0 (-1) + ee^{-1}$$

$$= -1 + 1 = 0$$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

34.

**ANS. A**

$$\text{Sol. } V_N = V_i \frac{1k}{2k} + V_o \frac{1k}{2k}$$

$$V_N = \frac{V_i + V_o}{2}$$

$$V_N > 0 \Rightarrow V_o = +V_{\text{sat}}$$

$$\text{Where } V_N = \frac{V_i + V_o}{2}$$

$$\text{If } V_o = +V_{\text{sat}} \Rightarrow V_N = \frac{1+5}{2} = 3V \text{ if } V_i = 1V \text{ peak}$$

$$V_N = \frac{-1+5}{2} = 2V \text{ if } V_i = -1V \text{ peak}$$

$$\text{If } V_o = -V_{\text{sat}} \Rightarrow V_N = \frac{1-5}{2} = -2 \text{ if } V_i = +1V \text{ peak}$$

$$\Rightarrow V_N = \frac{-1-5}{2} = -3 \text{ if } V_i = -1V \text{ peak}$$

So the output is either  $+V_{\text{sat}}$  or  $-V_{\text{sat}}$  as  $V_N$  is not crossing '0'.

35.

**Ans. C**


**Option c is correct**

36.

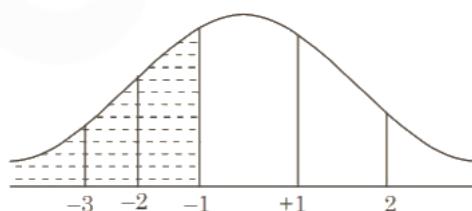**Ans. (3 -3)**


**Sol.** as ML detector is used, the decision boundary between two adjacent signal points will be their arithmetic mean.  $\therefore$

for  $s_1 = -3$ , the probability of error ( $P_1$ ):



$$P_1 = 1 - (\text{shaded area})$$

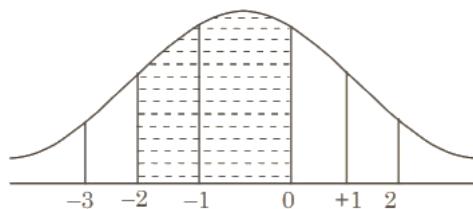for  $s_2$  : The probability of error ( $P_2$ )




**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

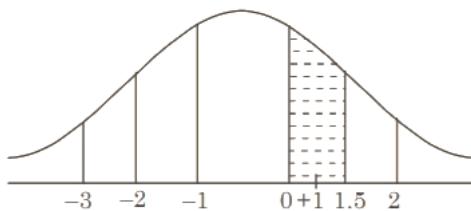**START FREE TRIAL**


$$P_2 = 1 - (\text{shaded area})$$

for  $s_3$ : the probability of error  $P_3$ .



$$P_3 = 1 - (\text{shaded area})$$

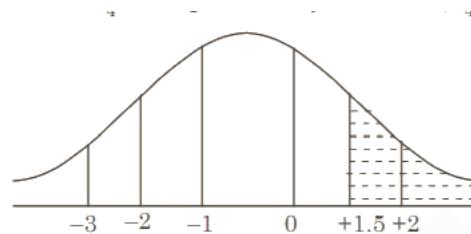for  $s_4$ : The probability of error ( $P_4$ )



$$P_4 = 1 - (\text{shaded area}) \text{ By concluding above graph}$$

$P_3$  i.e. probability of error when  $s_3$  is transmitted is larger among the four.

$$\therefore I = 3$$

37.

**ANS. D**


$$\text{Sol. } s^3 + 3s^2 + 2s + K(s + 3) = 0$$

$$1 + \frac{K(s+3)}{s(s^2 + 3s + 2)} = 0$$

$$1 + \frac{K(s+3)}{s(s+1)(s+2)} = 0$$

Compare it with  $1 + G(s)H(s) = 0$
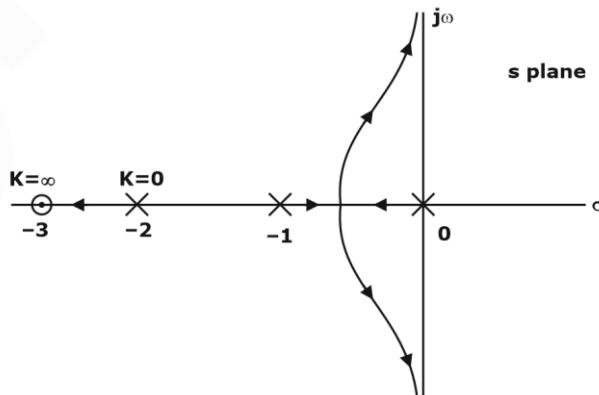
$$G(s)H(s) = \frac{K(s+3)}{s(s+1)(s+2)}$$



Breakaway point is in between  $(0, -1)$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

38.

**ANS. C**

**Sol.**  $x(t) = m(t) \cos(2\pi f_c t)$

$$m'(t) = 4 \cos(1000 \pi t)$$

$$f_c = 1 \text{ MHz}$$

$$Z(t) = m(t) \cos(2\pi f_c t) \cos[2\pi(f_c + 40)t]$$

$$= \frac{m(t)}{2} \cos[2\pi 2f_c + 40] + \cos(\pi \times 40)t$$

$$= \cos(1080\pi t) + \cos(920\pi t)$$

$$= f_{m1} = 540 \text{ Hz}, f_{m2} = 460 \text{ Hz}$$

$$\text{So } y(t) = \cos 920\pi t$$

39.

**Ans. B**

**Sol.** From the figure,  $E_C - E_V = 1 \text{ eV} = 0.5 \text{ eV} + q\varphi_B + 0.2 \text{ eV}$

$$\Rightarrow q\varphi_B = 0.3 \text{ eV}$$

$$\Rightarrow \varphi_B = 0.3 \text{ V, where } q\varphi_B = E_i - E_{FS}$$

The magnitude of depletion charge density

$$\rho_S = \sqrt{2\epsilon_S N_A \psi_S} \quad \dots(1)$$

$$\text{where, } \psi_S = 2\varphi_B = 2 \times 0.3 \text{ V} = 0.6 \text{ V} \quad \dots(2)$$

Voltage across capacitor,

$$V_{TH} = V_{FB} + \frac{\sqrt{2\epsilon_S N_A \psi_S}}{C_{ox}} + \psi_S \quad \dots(3)$$

$$\text{where, } V_{FB} = \varphi_{ms} = \varphi_m - \varphi_s$$

$$= 3.87 - 4.8$$

$$V_{FB} = \varphi_{ms} = -0.93 \text{ V} \quad \dots(4)$$

From (1), (2), (3) & (4),

$$\rho_S = 1.7 \times 10^{-8} \text{ C/cm}^2$$

40.

**ANS. (-2 - -2)**

**Sol.** Magnitude will become constant for all pass system

$$H(z) = \frac{z-a}{z+b}$$

$$b = \frac{1}{\alpha^*}$$

$$\alpha = \frac{1}{0.5}$$

$$a = 2$$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

41.

**Ans. D**

**Sol.**  $X(t) = \cos(200\varphi t)$

$$t = \frac{n}{400} \quad n = 0, 1, \dots, 7$$

$$x(n) = \cos\left(200\pi \times \frac{n}{400}\right) = \cos\left(\frac{\pi}{2} \cdot n\right)$$

$$x[0] = 1$$

$$x[1] = 0$$

$$x[2] = -1$$

$$x[3] = 0$$

$$x[4] = 1$$

$$x[5] = 0$$

$$x[6] = -1$$

$$x[7] = 0$$

$$x[0] = \{1, 0, -1, 0, 1, 0, -1, 0\}$$

$$X(K) = \sum_{n=0}^7 x[n] e^{-j\frac{\pi}{4}K \cdot n}$$

$$X(3) = \sum_{n=0}^7 x[n] e^{-j\frac{\pi}{4}7 \cdot n}$$

$$\left(\frac{1}{\sqrt{2}} - j\frac{1}{2}\right)^7 \neq 0$$

$$e^{-j\frac{7\pi}{4}} = \cos \frac{7 \times 180}{4} - j \frac{\sin 7 \times 180}{4} = \frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}}$$

42.

**Ans. A**


**Sol.** If output of sequence is 1, then it is transversed. So,

S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	S <sub>4</sub>
0	1	0	1	0

43.

Ans. A

Sol.

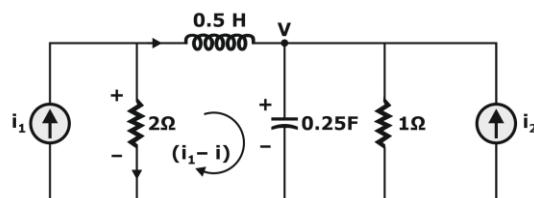

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

KVL in Loop

$$-0.5 \frac{di}{dt} - V + (i_1 - i)2 = 0$$

$$\frac{di}{dt} = -2V + (-4i) + 4i_1 \dots (i)$$

KCL at node V

$$-i + C \frac{dV}{dt} + \frac{V}{1} - i_2 = 0$$

$$-i + 0.25 \frac{dV}{dt} + V - i_2 = 0$$

$$0.25 \frac{dV}{dt} = -V + i + i_2$$

$$\frac{dV}{dt} = -4V + 4i + 4i_2 \dots (ii)$$

write eqn. (i) and (ii) in matrix form

$$\frac{d}{dt} \begin{bmatrix} V \\ i \end{bmatrix} = \begin{bmatrix} -4 & 4 \\ -2 & -4 \end{bmatrix} \begin{bmatrix} V \\ i \end{bmatrix} + \begin{bmatrix} 0 & 4 \\ 4 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

option (A) is correct.

44.

**Ans. C**

**Sol.**

$$\left. \begin{array}{l} X_1 + 2X_2 = b_1 \\ 2X_1 + 4X_2 = b_2 \end{array} \right\} 2b_1 = b_2$$

$$3X_1 + 7X_2 = b_3 \dots (i)$$

$$3X_1 + 9X_2 = b_4 \dots (ii)$$

In eqn. (i) we can write as

$$3X_1 + 6X_2 + X_2 = b_3$$

$$3b_1 + X_2 = b_3$$

$$X_2 = b_3 - 3b_1$$

and in eqn. (ii)

$$3X_1 + 6X_2 + 3X_2 = b_4$$

$$3b_1 + 3[b_3 - 3b_1] = b_4$$

$$-6b_1 + 3b_3 - b_4 = 0$$

$$6b_1 - 3b_3 + b_4 = 0$$

option (B) is correct

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

45.

**Ans. C**

**Sol.** During sampling, MOSFET must be as ON switch.

$$\begin{aligned} \Rightarrow V_{GS} &> V_{TH} \\ \Rightarrow (V_G - V_S) &> V_{TH} \\ \Rightarrow V_G &> V_S + V_{TH} \\ \Rightarrow V_G &> 10 + 3V \quad \because V_S = V_{I, \max} = 10V \\ \Rightarrow V_G &> 13V \quad \dots(1) \end{aligned}$$

During hold, MOSFET must be as OFF switch.

$$\begin{aligned} \Rightarrow V_{GS} &< V_{TH} \\ \Rightarrow (V_G - V_S) &< V_{TH} \\ \Rightarrow V_G &< (V_S + V_{TH}) \\ \Rightarrow V_G &< -7V \\ \therefore V_S &= V_{I, \min} = -10V \end{aligned}$$

46.

**Ans. D**

**Sol.**  $\frac{dy}{y-1} = x dx$


$$\int \frac{dy}{y-1} = \int x dx$$

Such that  $y \neq 1$ .

47.

Ans- (58.50 – 58.80)

Sol.

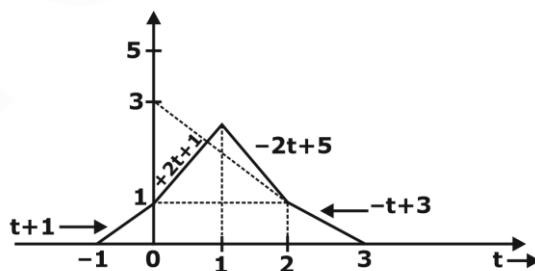

$$E = \frac{1}{2\pi} \int_{-\infty}^{\infty} |X(\omega)|^2 d\omega = \int_{-\infty}^{\infty} x^2(t) dt$$

$$\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega = 2\pi \int_{-\infty}^{\infty} x^2(t) dt$$

**Vision 2021 Batch-3**  
A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**


$$\int_{-\infty}^{\infty} x^2(t) dt = \int_{-1}^0 (t+1)^2 dt + \int_0^1 (2t+1)^2 dt + \int_1^2 (-2t+5)^2 dt + \int_2^3 (-t+3)^2 dt \\ = 9.33$$

$$\int_{-\infty}^{\infty} |X(\omega)|^2 = 2\pi \times 9.33 = 2 \times 3.14 \times 9.33 = 58.5924$$

48.

**Ans. D**

**Sol.**

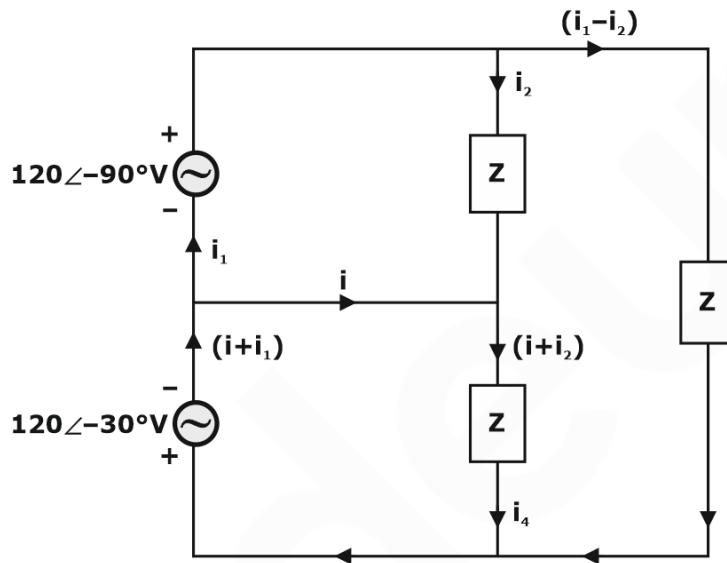

$$i_2 = \frac{120 \angle -90^\circ}{Z} = \frac{120 \angle -90^\circ}{(80 - 35j)}$$

$$= 1.3742 \angle -66.37^\circ$$

And

$$+ 120 \angle -30^\circ + Z i_4 = 0$$

$$i_4 = \frac{-(120 \angle -30^\circ)}{Z}$$

$$= \frac{120 \angle 150}{Z}$$

$$= \frac{120 \angle 150}{(80 - 35j)}$$

$$= 1.3742 \angle 173.62^\circ$$

$$i_4 = i + i_2$$

$$\therefore i = i_4 - i_2$$

$$= (1.3742 \angle 173.62) - 1.3742 \angle -66.37^\circ$$

$$= 2.38 \angle 143.625^\circ$$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

49.

**Ans. (1 - 1)**

**Sol.** Given,

$$\vec{H}(x, y, z, t) = (a_x + 2a_y + b + a_z) \cdot \cos(\omega t + 3x - y - z) A / m$$

For a uniform wave,

$$\vec{k} \cdot \vec{H}_0 = 0, \vec{k} \cdot \vec{E}_0 = 0, \vec{E}_0 \cdot \vec{H}_0 = 0$$

i.e.,  $\vec{E}$ ,  $\vec{H}$  and  $\vec{k}$  are mutually perpendicular to each other.

( $\vec{k}$  is the vector along the direction of wave propagation)

Comparing the given expression of  $\vec{H}$  with the standard expression.

$$\vec{k} = 3a_x - a_y - a_z$$

$$\text{And, } \vec{H}_0 = (a_x + 2a_y + ba_z)$$

$$\text{Then, } \vec{k} \cdot \vec{H}_0 = 3 - 2 - b = 0$$

$$\Rightarrow b = 1$$

50.

**Ans. – (2- 2)**

**Sol.**  $S_{PM}(t) = \cos[1000\pi t + K_p m(t)]$

$$S_{FM}(t) = \cos\left[1000\pi t + K_f \int_{\infty}^t m(\tau) d\tau\right]$$

Maximum instantaneous frequency in FM.


$$f_i = \frac{1}{2\pi} \left[ \frac{d}{dt} \theta_i(t) \right]$$

$$f_i = \frac{1}{2\pi} [1000\pi t + K_f m(t)] \quad \dots (i)$$

And maximum instantaneous frequency in PM

$$f_i = \frac{1}{2\pi} \left[ 1000\pi + \frac{d}{dt} k_p m(t) \right]$$

$$\frac{d}{dt} m(t)$$

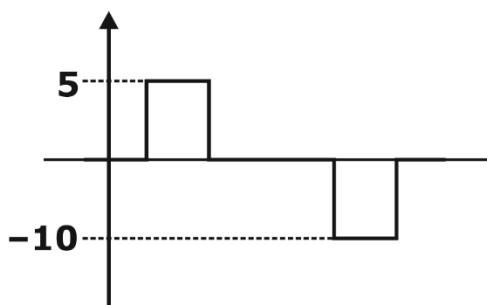

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

$$f_i = \frac{1}{2\pi} [1000\pi + K_p \times 5] \quad \dots \text{(ii)}$$

Given maximum instantaneous frequency is same

$$\frac{1}{2\pi} [1000\pi + K_f m(t)] = \frac{1000\pi}{2\pi} + \frac{5K_p}{2\pi}$$

$$K_f \times 10 = 5 K_p$$

$$\frac{K_p}{K_f} = 2$$

51.


**Ans. (0.8 to 0.8)**

**Sol.**  $S_{12} = \dot{S}_{21} = \frac{2n}{n^2 + 1} = \frac{4}{4+1} = 0.8$

52.

**Ans. B**

**Sol.**

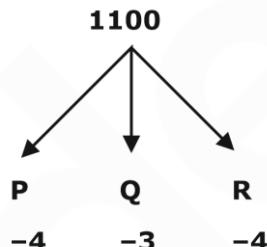

$$P + Q + R = -11$$

53.

**Ans. B**

**Sol.** Fill factor,  $FF = \frac{P_o}{V_{OC} I_{SC}}$  ... (1)

$$\text{Efficiency, } \eta = \frac{P_o}{P_{in}}$$

$$\text{where } P_{in} = 100 \frac{\text{mW}}{\text{cm}^2} \times \text{Area}$$

$$= 100 \frac{\text{mW}}{\text{cm}^2} \times 1 \text{ cm}^2$$

$$= 100 \text{ mW.}$$

$$0.15 = \frac{P_o}{100 \text{ mW}}$$

$$\therefore P_o = 15 \text{ mW} \dots (2)$$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

$$(1) \Rightarrow 0.8 = \frac{15\text{mW}}{0.7 \times I_{SC}}$$

$$I_{SC} = 0.027\text{A}$$


Optical generation rate,

$$\begin{aligned} G_{avg} &= \frac{I_{SC}}{q \times \text{Area} \times \text{thickness}} \\ &= \frac{0.027}{1.6 \times 10^{-19} \times 1 \times 200 \times 10^{-4}} \\ &= 0.837 \times 10^{19} / \text{cm}^3/\text{S} \end{aligned}$$

54.

**Ans. D**

**Sol. B**

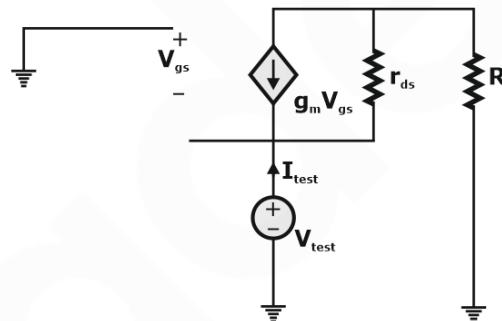

$$V_{test} = -V_{gs}$$

$$= r_{ds} (I_{test} - g_m V_{test}) + I_{test} R$$

$$V_{test}(1 + g_m r_{ds}) = I_{test}(r_{ds} + R)$$

$$\frac{V_{test}}{I_{test}} = R_{eq} = \frac{r_{ds} + R}{1 + g_m r_{ds}}$$

55.

**ANS. A**

$$\text{Sol. } A_V = \frac{-[R_C || R_L]}{r_e}$$

$$r_e = \frac{26\text{mV}}{I_E}$$

DC analysis of the circuit gives,

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

$$I_E = \frac{10 - 0.7}{20k} = 0.465 \text{ mA}$$

$$\therefore r_e = 55.9 \Omega$$

$$\therefore A_V = \frac{-(10k || 10k)}{55.9} = -89.4$$


56.

**ANS.B**

57.

Ans. 2.25 (2.25 – 2.25)

**Sol.** From the figure

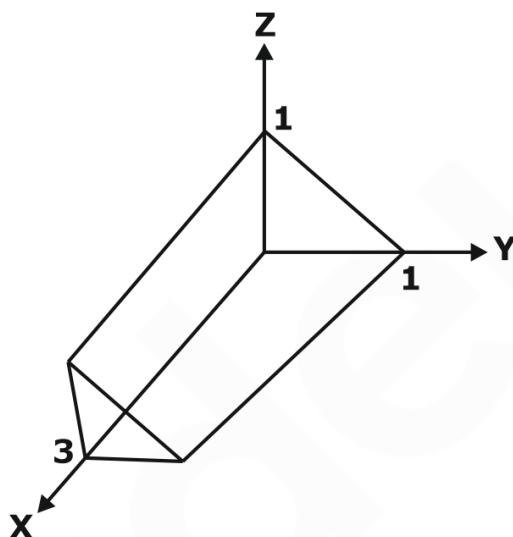

$$X = 0 \text{ to } 3.$$

$$Y = 0 \text{ to } 1$$

$$Z = 0 \text{ to } 1 - Y$$

$$= \int_0^3 \int_0^1 \int_0^{1-Y} X \, dZ \, dY \, dX$$

$$= \int_0^3 \int_0^1 X(Z) \, dY \, dX$$

$$= \int_0^3 \int_0^1 X(1-Y) \, dY \, dX$$

$$= \int_0^3 X \left( Y - \frac{Y^2}{2} \right) \Big|_0^1 \, dX$$

$$= \int_0^3 X \frac{1}{2} \, dX$$

$$= \frac{X^2}{4} \Big|_0^3 = \frac{9}{4} = 2.25$$

**Vision 2021** Batch-3


A Course for ESE & GATE Electronics Aspirants

[START FREE TRIAL](#)

58.

ANS. (4 - 4)

Sol.

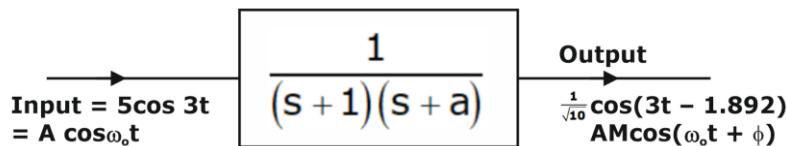

Where  $M = |G(j\omega)|_{\omega=\omega_0}$

$$G(j\omega) = \frac{1}{(1+j\omega)+(a+j\omega)}$$

$$|G(j\omega)| = \frac{1}{\sqrt{(\omega^2 + 1)(\omega^2 + a^2)}}$$

$$M = |G(j\omega)|_{\omega=3} = \frac{1}{\sqrt{(10)(a^2 + 9)}}$$

$$AM = \frac{1}{\sqrt{10}} = \frac{5}{\sqrt{10}\sqrt{a^2 + 9}}$$

$$a^2 + 9 = 25$$

$$a^2 = 16$$

$$a = 4$$

$$\therefore a > 0$$

59.

**Ans. A**

insufficient data

60.

**Ans. 76.92 (76 -78)**


**Sol.** Total maximum propagation delay =  $(T_{pd} + T_{setup})_{max} = 8\text{ns} + 5\text{ns} = 13\text{ns}$

$$\text{frequency of operation} = \left( \frac{1000}{13} \right) \text{MHz} = 76.92 \text{ MHz}$$

61.

**Ans. 800 (800 -800)**

**Sol.**

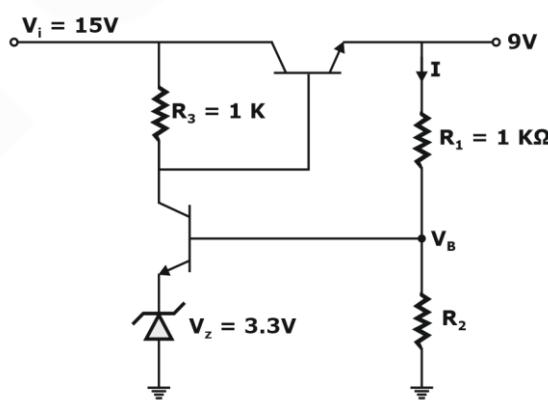

$$\text{Voltage } V_B = V_z + V_{BE}$$

$$= 3.3 + 0.7$$

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

$$V_B = 4V \dots(i)$$

$$\therefore I = \frac{9 - 4}{1K}$$

$$I = 5 \text{ mA}$$

Since base current is negligible,

$$V_B = 9 \times \frac{R_2}{R_1 + R_2}$$


$$4 = \frac{9R_2}{1K + R_2} \Rightarrow R_2 = 800\Omega$$

62.

**ANS. B**

**Sol.** The circuit shows an LPF.

Applying virtual ground,

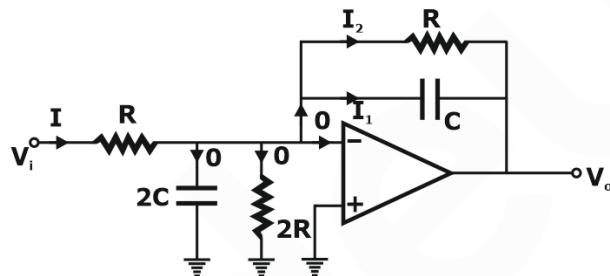

$$I = I_1 + I_2$$

$$\frac{V_i - 0}{R} = \frac{0 - V_o}{R} + \frac{0 - V_o}{1/CS}$$

$$= -V_o \left[ \frac{1}{R} + CS \right]$$

$$\frac{V_o}{V_i} = \left[ \frac{1}{1 + RCS} \right]$$

$$\therefore \omega = \frac{1}{RC}$$

$$\Rightarrow f = \frac{1}{2\pi RC} = \frac{1}{2\pi(2 \times 10^3)(1 \times 10^{-6})} = 79.58 \text{ Hz}$$

63.

**Ans. B\***

**Sol.** insufficient data

Ans.

Sol. We know that

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

$$C_d \propto \frac{1}{\sqrt{V_0 + V_R}}$$


$$\frac{1}{(C_d)^2} = K(V_0 + V_R)$$

$$\frac{1}{(50 \times 10^{-12})^2} = K[V_0 + V_R]$$

Reverse bias voltage given  $V_R = 0.2V$

$V_0$  = applied voltage.
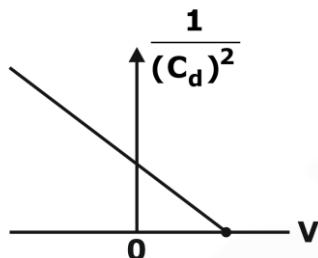
$$K = \frac{1}{2500 (V_0 + V_R)} \times 10^{24}$$



value of  $V_0$  is not given so

slope will not to be calculated

64.

**ANS. (0.3 – 0.3)**

**Sol.** Given (0.3 to 0.3)

$$f_x(x) = \begin{cases} 1/12 & -2 \leq x \leq 10 \\ 0 & \text{otherwise} \end{cases}$$


$$\text{As } y = 2x - 6$$

$$\text{So, } f_y(y) = \begin{cases} 1/24 & -10 \leq y \leq 14 \\ 0 & \text{otherwise} \end{cases}$$

If  $x \geq 5$  then  $y \geq 4$

$$\text{So, } P(y \leq 7/x \geq 5) = P(Y \leq 7/y \geq 4)$$
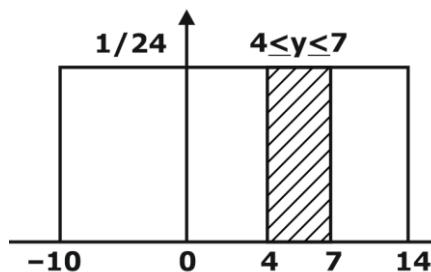
$$= \frac{P(4 \leq y \leq 7)}{P(4 \leq y \leq 14)} = \frac{3}{10} = 0.3$$



**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**

**65.**

**ANS. (30 -30)**

**Sol.** OLTF =  $\frac{K(s+1)}{(s+3)} \times \frac{1}{s(s+1)}$

$$\text{OLTF} = \frac{K}{s(s+3)}$$

It is type '1' system

Steady state error for unit ramp input

$$e_{ss} = \frac{1}{K_V}$$

Where

$$K_p = \lim_{s \rightarrow \infty} s \times \frac{K}{s(s+3)} = \frac{K}{3}$$

$$e_{ss} = \frac{1}{K/3} = \frac{3}{K}$$

According to question,  $e_{ss} = 0.1$

$$0.1 = \frac{3}{K} \Rightarrow K = 30$$

\*\*\*\*\*

**Vision 2021 Batch-3**

A Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**



# OUR TOP GRADIANS IN GATE 2020



Ghanendra Singh

AIR-6

ECE



Himanshu Kumar

AIR-9

EE



Nikhil Kumar

AIR-9

EE



Raja Majhi

AIR-30

ECE



Samanwaya Deep  
Chakraborty

AIR-41

ECE



Abhishek

AIR-45

ECE

Classroom 

Vision 2021-Course for ESE & GATE (Batch-3)

Electronics & Communication Engineering



800+hrs  
Live Class



7000+  
Practise  
Question



Test Series

# Vision 2021

A Course for ESE & GATE Electronics Aspirants  
Batch-3

## Why take this course?

- › **650+ Hours** of Live Classes for ESE & GATE Technical Syllabus
- › **150+ Hours** of Live Classes for ESE Prelims Paper 1 Syllabus
- › **750+ Quizzes & Conventional Assignments** for Practice
- › Subject & Full-Length **Mock Tests** for GATE & ESE



MN Ramesh | Rakesh talreja | Chandan Jha | Vijay Bansal