

GATE 2020

Electrical Engineering

Solution



GENERAL APTITUDE

1.

Ans. C

Sol. This book, including all its chapters **is** interesting. The students as well as the instructor **are** in agreement about it.

2.

Ans. B

Sol. People were prohibited **from parking** their vehicles near the entrance of the main administrative building.

3.

Ans. C

Sol. Do: Undo : Trust : **Distrust**

4.

Ans. B

Sol. Stock market **plunged** at the news of the coup

5.

Ans C

Sol. Teams having member greater than one with Q as his always member

Case-1: 2 member in the team

$$Q \text{ --- } {}^3C_1 = \frac{3!}{2!1!} = 3$$

Case-2: 3 members in the team

$$Q \text{ --- } {}^3C_2 = \frac{3!}{2!1!} = 3$$

Case-3: 4 member in the team

$$Q \text{ --- } {}^3C_3 = \frac{3!}{3!1!} = 1$$

$$3 + 3 + 1 = 7$$

6.

Ans B

Sol. In 1993, the holding period of loans is 360 days & after each revision one quarter of days was reduced.

After 1st revision: Number of days left = 360 – 90 = 270

After 2nd revision: Number of days left = 270 – 90 = 180

After 3rd revision: Number of days left = 180 – 90 = 90

Hence, the holding period of loans in 2004 after the third revision was 90 days.

7.

Ans C

Sol.
$$\begin{matrix} Z & WV & RQP & KJIH \\ (-2) & (-3) & (-4) & \end{matrix}$$

8.

Ans. B

Sol.
$$\begin{array}{r} \text{X} \text{ X} \text{ 37} \\ \downarrow \downarrow \\ 9 \text{ 10} \end{array} = 9 \times 10 = 90$$

$$\begin{array}{r} \text{X} \text{ 37} \text{ X} \\ \downarrow \downarrow \\ 9 \text{ 10} \end{array} = 9 \times 10 = 90$$

$$\begin{array}{r} \text{37} \text{ X} \text{ X} \\ \downarrow \downarrow \\ 10 \text{ 10} \end{array} = 10 \times 10 = 100$$

$$= 90 + 90 + 100 = 280$$

X 3 7 X and X X 3 7 will repeat twice

$$= 280 - 1 = 279$$

9.

Ans. A

Sol. Let radius of circle = $r = AO = OB = OC$

$$\overline{AC} = \sqrt{r^2 + r^2} = \sqrt{2}r = \overline{CB}$$

$$\frac{\overline{AC} + \overline{CB}}{AB} = \frac{\sqrt{2}r + \sqrt{2}r}{2r}$$

$$= \frac{2\sqrt{2}r}{2r} = \sqrt{2}$$

10.

Ans C

Sol. Revenue of Q in 2015 is 20 % more than in 2014.

Q has earned a profit of 10% on expenditure in 2014.

Let the total revenue of Q in 2014 be x

Total revenue of Q in 2014 is

$$1.2x = 45$$

$$x = 37.5$$

Let expenditure of Q in 2014 be y ,

%profit on expenditure is given as

$$10 = \frac{\text{revenue} - \text{expenditure}}{\text{expenditure}} \times 100$$

$$0.1 = \frac{37.5 - y}{y}$$

$$0.1y = 37.5 - y$$

$$1.1y = 37.5$$

$$y = 34.09 \text{ or } 34.1$$

TECHNICAL

11.

Ans A

Sol. $ax^3 + bx^2 + cx + d$

Let $a = 1, b = 2, c = 2, d = 1$

$f(x) = x^3 + 2x^2 + 2x + 1$


if $x = 0$ is a solution

$f(0) = 0$ implies that $d = 0$

12.

Ans. A

Sol.

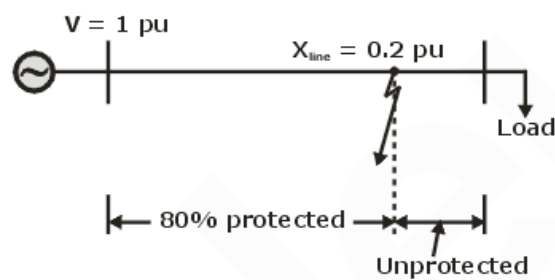


$$I_f = \frac{V}{0.8 \times \text{line}} = \frac{1}{0.8 \times 0.2} = \frac{1}{0.16} = 6.25$$

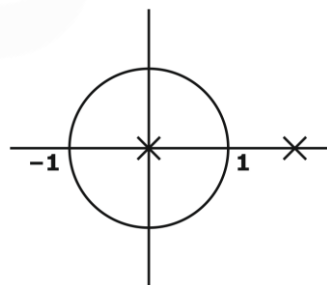13.

Ans B

Sol. $\oint_c \frac{(z^2 + 1)}{z(z - 2)} dz$



$$\begin{aligned} \oint_c \frac{(z + 1)}{z(z - 2)} &= 2\pi i (\text{Re}(z = 0)) \\ &= 2\pi i \left[\frac{0 + 1}{0 - 2} \right] \\ &= 2\pi i \left[-\frac{1}{2} \right] = -\pi i \end{aligned}$$

14.

Ans 2

Sol. $G(s) = \frac{k}{(s+a)(s-b)(s+c)}$

No. of open loop poles in right half of s plane

$P = 1$

Nyquist plot encircles the origin of $(1 + G(s))$ plane once in clockwise direction

$N = -1$

We know that

$N = P - Z$

$Z = P - N$

$= 1 - (-1) = 2$

No. of closed loop poles $Z = 2$

No. of closed loop poles lying in the right half of s plane = 2

15.

Ans 1.7 – 1.75


Sol. Reading of $A_2(I_2) = 1 \angle 10^\circ$ A

Reading of $A_3(I_3) = 1 \angle 70^\circ$ A

Apply KCL,

$\bar{I}_1 = \bar{I}_2 + \bar{I}_3$

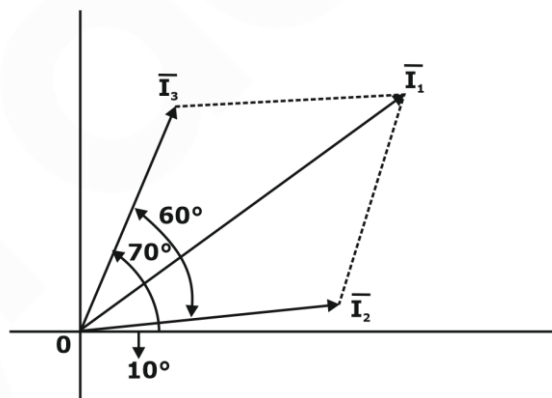$\bar{I}_1 = 1 \angle 10^\circ + 1 \angle 70^\circ$



Using parallelogram method.

$I_1 = \sqrt{I_2^2 + I_3^2 + 2I_2I_3 \cos 60^\circ}$

$= \sqrt{(1)^2 + (1)^2 + 2(1)(1) \cos 60^\circ} = \sqrt{3}$

$I_1 = 1.732$ A

16.

Ans 0.88 – 0.8863

Sol. $\frac{dy}{dx} + y = 2x$

This is linear first order differential equation.

Integrating factor = $e^{\int 1 dx} = e^x$

Solution is given as

$$ye^x = \int e^x 2x dx + c$$

$$ye^x = 2[xe^x - e^x] + c$$

$$y = 2(x-1) + ce^{-x}$$

At $x = 0, y = 1$

$$c = 3$$

$$y = 2(x-1) + 3e^{-x}$$

At $x = \ln 2$, then $y =$

$$y = 2(\ln 2 - 1) + 3e^{-\ln 2}$$

$$y = 2(\ln 2 - 1) + \frac{3}{2}$$

$$y = -0.6137 + 1.5 = 0.886$$

17.

Ans. D

Sol. Voltage gain of common source amplifier, $A_v = -g_m R_D$

$$= -520 \times 10^{-6} \times 4.7 \times 10^3 = -2.44$$


18.

Ans.

Sol. The voltage regulation for lagging loads ($R_a = 0$)

FIG

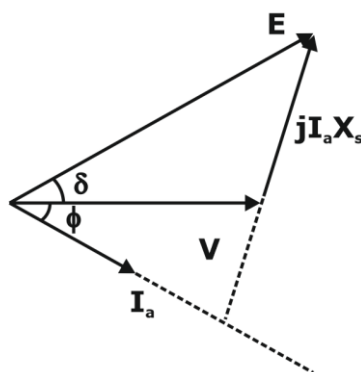
E is always greater than V, hence voltage regulation is always positive



The voltage regulation for leading loads ($R_a = 0$)

There is no generalisation like lagging loads, the voltage regulation depends upon two factors for a

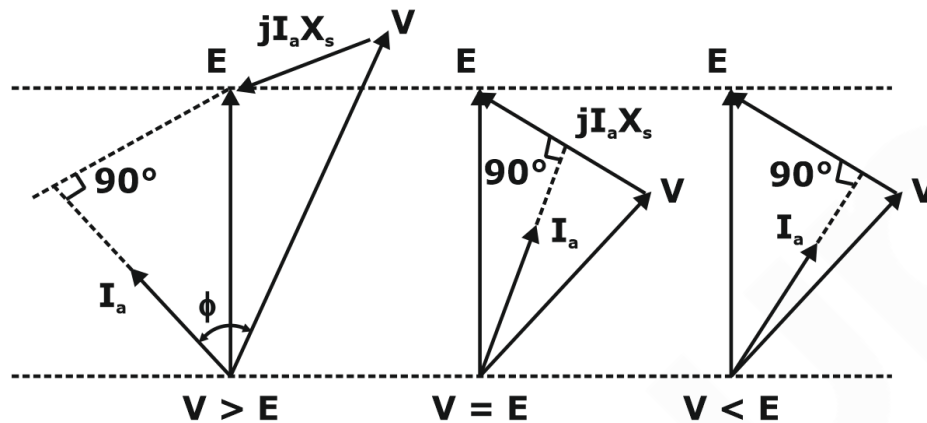- (i) Quantity of load (load magnitude)
- (ii) Quality of load (load power factor)



19.

Ans. D

Sol. $\frac{d^2 y(t)}{dt^2} + 4y(t) = 6r(t)$

$r(t)$ is Input

$y(t)$ is output

Taking Laplace transform both sides

$$s^2 y(s) + 4y(s) = 6 R(s)$$

$$(s^2 + 4) y(s) = 6R(s)$$

$$T(s) = \frac{Y(s)}{R(s)} = \frac{6}{(s^2 + 4)}$$

For calculation of poles,

$$s^2 + 4 = 0$$

$$s = \pm j2$$


Poles of this system are

$$+ 2j, -2j$$

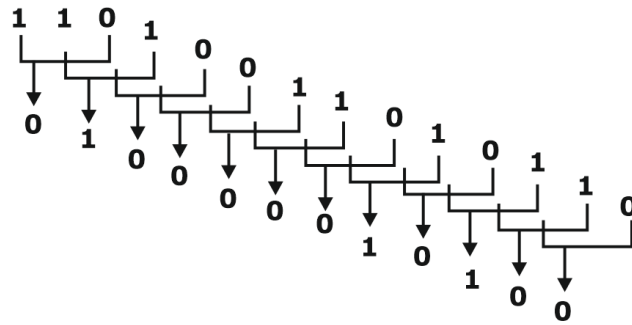20.

Ans. C

Sol. In case of overlapping sequence detector, to detect (1,0,1) in the input sequence (1,1,0,1,0,0,1,1,0,1,0,1,1,0) is



Hence, the output of the sequence detector is (0,1,0,0,0,0,0,1,0,1,0,0).

21.

Ans. C

Sol. 1. $\int_{-1}^1 \cos\left(\frac{n\pi x}{l}\right) \cos\left(\frac{m\pi x}{l}\right) dx = \begin{cases} 2l & \text{if } n = m = 0 \\ l & \text{if } n = m \neq 0 \\ 0 & \text{if } m \neq n \end{cases}$

2. $\int_0^l \cos\left(\frac{n\pi x}{l}\right) \cos\left(\frac{m\pi x}{l}\right) dx = \begin{cases} l & \text{if } n = m = 0 \\ l/2 & \text{if } n = m \neq 0 \\ 0 & \text{if } m \neq n \end{cases}$

3. $\int_{-1}^1 \sin\left(\frac{n\pi x}{l}\right) \sin\left(\frac{m\pi x}{l}\right) dx = \begin{cases} l & \text{if } m = n \\ 0 & \text{if } m \neq n \end{cases}$

4. $\int_0^l \sin\left(\frac{n\pi x}{l}\right) \cos\left(\frac{m\pi x}{l}\right) dx = \begin{cases} l/2 & \text{if } n = m \\ 0 & \text{if } n \neq m \end{cases}$

5. $\int_{-1}^1 \sin\left(\frac{n\pi x}{l}\right) \cos\left(\frac{m\pi x}{l}\right) dx = 0$

A. $\frac{1}{\pi} \sin m\theta \cos n\theta = 0$

Put $l = \pi$ in rule 4

$$\int_0^\pi \sin\left(\frac{n\pi x}{\pi}\right) \sin\left(\frac{m\pi}{\pi}\right) dx$$

Given that, $m \neq n$

$$\frac{1}{\pi} \int_0^\pi \sin x \sin mx dx = 0$$

(C). $\frac{1}{2\pi} \int_{-\pi}^\pi \sin p\theta \cos \theta d\theta = 0$

Put $l = \pi$ in rule 5

$$\int_{-\pi}^{\pi} \sin\left(\frac{n\pi x}{\pi}\right) \cos\left(\frac{m\pi x}{\pi}\right) dx$$

Given that $m \neq 0$

$$\int_{-\pi}^{\pi} \sin nx \cos mx \, dx = 0$$

$$(D). \lim_{\alpha \rightarrow \infty} \frac{1}{2\alpha} \int_{-\alpha}^{\alpha} \sin p\theta \, d\theta = 0$$

When, $\alpha \rightarrow \infty$,

$$\frac{1}{2\alpha} \int_{-\alpha}^{\alpha} \sin p\theta \sin \theta \, d\theta = \frac{1}{\infty} (\text{finite}) = 0$$

22.

Ans. C

$$\text{Sol. } x[n] = \left(\frac{1}{2}\right)^{(n-k)} \cdot u(n-k)$$

$$|z| > \frac{1}{2}$$

$$\frac{1}{1 - \frac{1}{2}z^{-1}} \xrightarrow{\text{Z.T.}} \left(\frac{1}{2}\right)^n \cdot u[n]$$

$$|z| > \frac{1}{2}$$

23.

Ans A

Sol.

24.

Ans 162.41 – 162.59

Sol. $P_i = P_h + P_e$

$$\left. \begin{aligned} P_h &= KhfB_m^{1.6} = K_1 f \\ P_e &= Kcf^2 B_m^2 = K_2 f^2 \end{aligned} \right\} \text{Keeping } \frac{V}{f} = \text{constant}$$

$$K_1 \cdot 50 + K_2 \cdot (50)^2 = 450$$

$$K_1 + K_2 \cdot (50) = \frac{450}{50} = 9$$

at 160V₁, 40 Hz

$$K_1 \cdot 40 + K_2 \cdot (40)^2 = 370$$

$$K_1 + K_2 \cdot (4) = \frac{370}{40} = 8$$

$$\begin{array}{r} K_1 + K_2 \cdot 50 = 9 \\ K_1 + K_2 \cdot 40 = 8 \\ \hline \end{array}$$

$$K_2 \cdot 10 = 1 \Rightarrow K_2 = \frac{1}{10}$$

$$K_1 = 9 - \frac{1}{10} \times 50 = 4$$

$\therefore 100V, 25 \text{ Hz}$

$$P_e = p_h = K_c$$

$$= K_1 \cdot (25) + K_2 \cdot (25)^2$$

$$= 4 \times 25 + \frac{1}{10} \times (25)^2$$

$$= 100 + 62.5 = 162.5 \text{ watt}$$

25.

Ans 19.90 – 20.20

Sol. We know that output waveform can be expressed in Fourier series form

From the given wave form,

$$V_{on}(t) = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin\left(\frac{n\pi}{2}\right) \sin n\omega t$$

$$n - 26 = 2d$$

$$d = \frac{\pi}{2} - 6$$

for eliminating 3rd harmonics

$$\frac{4V_s}{3\pi} \sin\left(\frac{3\pi}{2}\right) \sin 3d = 0$$

$$\sin 3d = 0$$

$$3d = \pi \Rightarrow d = \frac{\pi}{3}$$


$$\left| \frac{V_{05}}{V_{01}} \right| = \left| \frac{\frac{4V_s}{5\pi} \sin\left(\frac{5\pi}{2}\right) \sin 5d}{\frac{4V_s}{\pi} \sin\left(\frac{\pi}{2}\right) \sin d} \right|$$

$$= \frac{1}{5} \times 100\% = 20\%$$


26.

Ans. B

Sol. Given signal flow graph is

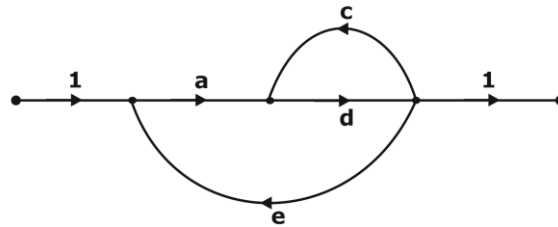

It can be reduced as

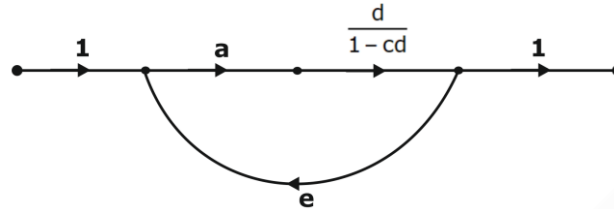

It is matching with option (2)


So, given signal flow graph and option (2) are equivalent.

27.

Ans. D

Sol. In a single-phase full bridge diode rectifier, since load is a series combination of finite resistance (R) and a very high Inductance (L). Load current is constant (I_o)

Source current is square wave form.

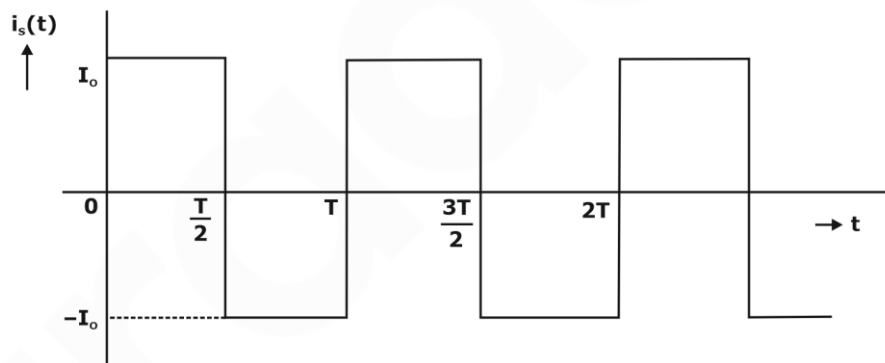

Fourier series representation of source current

$$i_s(f) = \sum_{n=1,3,5}^{\infty} \frac{4I_o}{n\pi} \sin n\omega t, \quad \left| \begin{array}{l} \text{where} \\ \omega = \frac{2\pi}{T} \end{array} \right.$$

Two most dominant frequency

Components are $f, 3f$ [fundamental and third harmonics]


50 Hz, 150 Hz.

28.

Ans 0

Sol. So. The schematic shown is a MOS capacitor

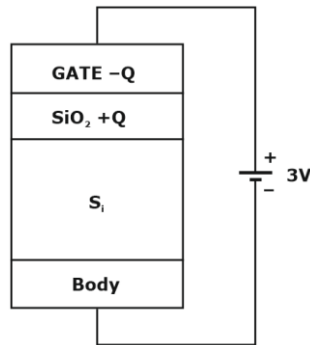When + 3V is applied, change inside the SiO₂ layer is + Q. Since it is MOS capacitor, the change in the GATE is Q.



29.

Ans. A

Sol. For generator buses, the solution of economic load dispatch is a processor to the load flow analysis.

30.

Ans. C

Sol. Given that:

x_R = rms value of $x(t)$

x_A = average value of $x(t)$

also, as $x(t) = x(t - T)$, i.e., $x(t)$ is a periodic waveform with period T

therefore, the rms value of x_R is given as

$$x_R = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

And the average value of x_A is given as

$$x_A = \frac{\int_0^T x(t) dt}{T}$$

Now, therefore $y(t)$ is also periodic signal with period " T ",

Now, rms value is

$$y_R = \sqrt{\frac{1}{T} \int_0^T y^2(t) dt} = \sqrt{\frac{1}{T} \int_0^T k^2 x^2(t) dt}$$

$$y_R = \sqrt{k^2 \frac{1}{T} \int_0^T x^2(t) dt} = k \sqrt{\frac{1}{T} \int_0^T x^2(t) dt} = k x_R$$

Now, average value is

$$y_A = \frac{\int_0^T y(t) dt}{T} = \frac{\int_0^T k y(t) dt}{T} = k \frac{\int_0^T y(t) dt}{T} = k x_A$$

31.

Ans 3

Sol. Voltage across parasitic inductance,

$$V_L = L_{\text{par}} \frac{di}{dt}$$

The value of $\frac{di}{dt}$ is highest at point 3. Hence voltage across parasitic inductance is highest at point 3.

3.

So, IGBT experiences the highest current stress at point 3.

32.

Ans A

Sol. Load Impedance

$$Z = 10 \angle -60^\circ = 10 \cos 60 - j 10 \sin 60^\circ.$$

$$= (5 - j 8.66) \Omega$$

Load is capacitive.

Maximum load power = 2 kW = 2000 watts.

Power consumed by load $P = I^2 R$

$$2000 = I^2 \times R$$


$$I = 20 \text{ aptitude}$$

Output R.M.S. Voltage

$$V = IZ = 20 \times 10 = 200 \text{ volt.}$$

Maximum R.M.S output voltage = 200 volt.

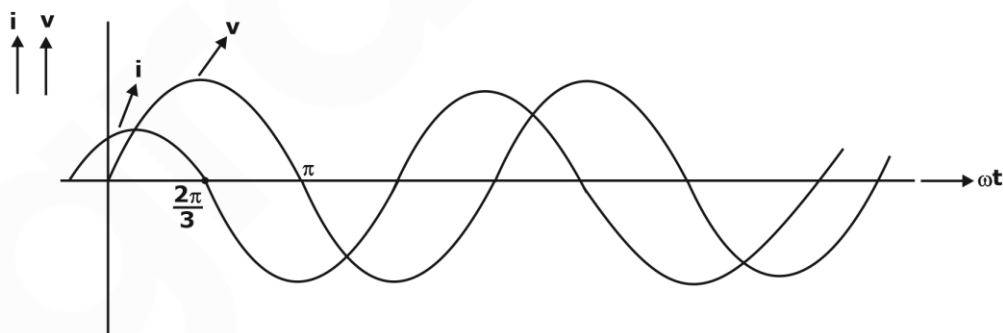Since load is capacitive, current would lead the voltage.



Minimum range of variation in L is (0 to 120°)

Note:- After 120°, current would change direction.

33.

Ans 4.10 – 4.40

Sol. Given data,

$$f = 50 \text{ Hz}$$

$$P = 4$$

$$\text{No. load slip} = s_1 = 1\% = 0.01$$

$$\text{Full load slip} = s_2 = 5\% = 0.05$$

$$\text{Let, No load speed} = N_1$$

$$\text{Full load speed} = N_2$$

$$\therefore N_s = \frac{120f}{P} = \frac{120 \times 50}{4} = 1500 \text{ rpm}$$

$$N_1 = N_s(1 - s_1) = 1500(1 - 0.01) = 1485 \text{ rpm}$$

$$N_2 = N_s(1 - s_2) = 1500(1 - 0.05) = 1425 \text{ rpm}$$


$$\text{Speed Regulation} = \frac{N_1 - N_2}{N_2} \times 100$$

$$= \frac{1485 - 1425}{1425} \times 100 = 4.21\%$$

34.

Ans 13.80 – 14.20

Sol.

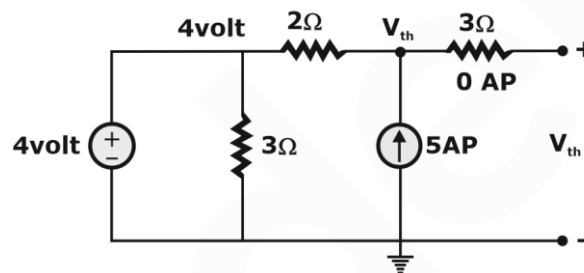

Apply KCL at node A

$$\frac{V_{th} - 4}{2} = 5$$


$$V_{th} - 4 = 10$$

$$V_{th} = 14 \text{ V}$$

35.

Ans 125 – 135

Sol.

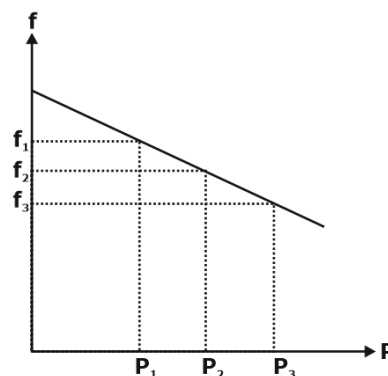

$$f_1 = 50 \text{ Hz}, f_2 = 49.75 \text{ Hz}, f_3 = 49.25 \text{ Hz}.$$

$$P_1 = 100 \text{ MW}, P_2 = 110 \text{ MW}, P_3 = ?$$

$$\frac{f_1 - f_2}{P_2 - P_1} = \frac{f_2 - f_3}{P_3 - P_2} \quad (\text{Same droop})$$

$$\frac{0.25}{10} = \frac{0.5}{P_3 - 110}$$

$$\Rightarrow P_3 = 110 + 20$$

$$P_3 = 130 \text{ MW}$$

36.

Ans A

$$\text{Sol. } H(s) = \frac{s^2 + 100}{s - p}$$

$$\text{D.C. gain} = 5$$

$$\text{D.C. gain} = H(s)|_{s=0}$$

$$= \left. \frac{s^2 + 100}{s - p} \right|_{s=0} = 5$$

$$\frac{100}{-p} = 5 \Rightarrow p = -20$$

$$H(s) = \frac{s^2 + 100}{(s + 20)}$$

For frequency domain $s = j\omega$

$$H(j\omega) = \frac{100 + (j\omega)^2}{20 + (j\omega)} = \frac{100 - \omega^2}{(20 + j\omega)}$$

$$\text{Gain} = |H(j\omega)| = \left| \frac{100 - \omega^2}{20 + j\omega} \right|$$

$$= \frac{100 - \omega^2}{\sqrt{400 + \omega^2}}$$

Frequency at unity gain

$$\frac{100 - \omega^2}{\sqrt{400 + \omega^2}} = 1$$

$$(100 - \omega^2)^2 = (400 + \omega^2)$$

Solving this equation

$$\omega = 8.84 \text{ rad/sec and } 11.08 \text{ rad/sec}.$$

Smallest positive frequency = 8.84 rad/sec.

37.

Ans -3.05 - -2.95

Sol. $f = y a_x - x a_y$

$$\int_C f \cdot d\ell = \int_C (y a_x - x a_y) \cdot (dx a_x + dy a_y)$$

$$= \int_C (y dx - x dy)$$

But $y = x^2$

$$dy = 2x dx$$

$$\int_C f \cdot d\ell = \int_C x^2 dx - x(2x dx)$$

$$= \int_C x^2 dx - 2x^2 dx = -\int_C x^2 dx$$


$$= -\int_{-1}^2 x^2 dx = -\left[\frac{x^3}{3}\right]_{-1}^2$$

$$= -\left[\frac{8}{3} - \left(-\frac{1}{3}\right)\right] = -3$$

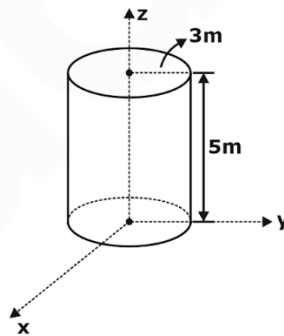38.

Ans. B

Sol. $\vec{D} = (15 \hat{a}_r + 2r \hat{a}_\phi - 3rz \hat{a}_z) \text{ C/m}^2$



$$Q_{\text{enclosed}} = \int \vec{D} \cdot d\vec{s} = \int (\nabla \cdot \vec{D}) dv$$

$$\nabla \cdot \vec{D} = \frac{1}{r} \frac{\partial}{\partial r} r D_r + \frac{1}{r} \frac{\partial}{\partial \phi} D_\phi + \frac{\partial D_z}{\partial z}$$

$$= \frac{1}{r} \frac{\partial}{\partial r} (15r) + \frac{1}{r} \frac{\partial}{\partial \phi} (2r) + \frac{\partial}{\partial z} (-3rz)$$

$$= \frac{15}{r} + (-3r) = \frac{15}{r} - 3r$$

$$Q_{\text{enclosed}} = \int_V \left(\frac{15}{r} - 3r \right) r dr d\phi dz$$

$$= \int_0^5 \int_0^{2\pi} \int_0^3 (15 - 3r^2) dr d\phi dz$$

$$= \int_0^5 \int_0^{2\pi} \left[15r - \frac{3r^3}{3} \right]_0^3 d\phi dz$$

$$= \int_0^5 \int_0^{2\pi} (45 - 27) d\phi dz$$

$$= 18 \times 5 \times 2\pi = 180\pi \text{ C}$$

39.

Ans. C

Sol. $\epsilon_x = 2.25$

$$\vec{E} = 2\pi\hat{a}_\pi + \frac{3}{\pi}\hat{a}_\phi + 6\hat{a}_z$$

Gauss Law,

$$\nabla \cdot \vec{E} = \frac{\rho_v}{\epsilon_0\epsilon_\pi}$$

$$\Rightarrow \frac{\rho_v}{\epsilon_0\epsilon_\pi} = \frac{1}{\pi} \frac{\partial}{\partial \pi} (\pi E_\pi) + \frac{1}{\pi} \frac{\partial E_\phi}{\partial \phi} + \frac{\partial E_z}{\partial z} = \frac{1}{\pi} \frac{\partial}{\partial \pi} (2\pi^2) + \frac{1}{\pi} \frac{\partial}{\partial \phi} \left(\frac{3}{\pi} \right) + \frac{\partial}{\partial z} (b)$$

$$= \frac{1}{\pi} \times 4\pi = 4$$

$$\rho_v = \epsilon_0(2.25 \times 4) = (9.00)\epsilon_0 = 9\epsilon_0$$

40.

Ans. B

Sol. By Schwarz inequality,

$$y(t) = \int_{-\infty}^{\infty} x(\tau)h(t-\tau) d\tau$$

$$z(t) = \int_{-\infty}^{\infty} |x(\tau)| |h(t-\tau)| d\tau$$

Hence $z(t) \geq y(t)$ for all value of t .

41.

Ans 210

Sol. $M \leftarrow 2001H$

$A \leftarrow 21H$

$M \leftarrow 2002H$

$[A] \leftarrow [A] + [M]$

$[A] \leftarrow 21H + B1H$

$M \leftarrow 2003H$

Display

21H + B-1H

$$(21)_{16} = (33)_{10}$$

$$(B - 1)_{16} = (177)_{10}$$

$$= (210)_{10}$$

So, it display 210.

42.

Ans

Sol. (4.70 - 4.80)

$$I = I_0 e^{\frac{V_D}{\eta V_T}}$$

$$V_T = 29 \pm 2 \text{ mV}$$

$$\ln\left(\frac{I}{I_0}\right) = \frac{V_D}{\eta V_T}$$

$$\ln I - \ln I_0 = \frac{V_D}{\eta V_T}$$

Differentiating partially with respect to V_T

$$\frac{\partial I}{I} = 0 + \frac{V_D}{\eta} \left(\frac{-1}{V_T^2} \right) \times \partial V_T$$

$$\frac{\partial I}{I} = \frac{-IV_0}{V_T^2}$$

$$\eta = 1$$

Resultant uncertainty

$$w_{\text{res}} = w_I \sqrt{\left(\frac{\partial I}{\partial V_T} \right)^2} \times w_V^2 = \pm \frac{\partial I}{\partial V_T} \times w_V$$

$$w_{\text{res}} = w_I = \pm \frac{IV_0}{V_T^2} w_V$$

$$W_I = \pm \frac{IV_0}{V_T^2} w_V \pm \frac{I \times 0.02}{(0.029)^2} \times 0.02$$


$$= \pm 0.0475I$$

$$\frac{W_I}{I} = \pm 0.0475 \times 100 = \pm 7.75\%$$

43.

Ans. B

Sol.

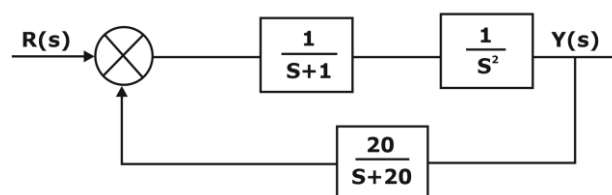

Closed loop characteristic equation

$$1 + G(s) H(s) = 0$$

$$1 + \frac{1}{(s+1)} \frac{1}{s^2} \frac{20}{(s+20)} = 0$$

$$s^2 (s+1)(s+20) + 20 = 0$$

$$s^4 + 21s^3 + 20s^2 + 20 = 0$$


It is 4th order system (degree = 4) It is unstable system because coefficient of s is zero.

It is 4th order unstable system.

44.

Ans 4.51 – 5.10

Sol.

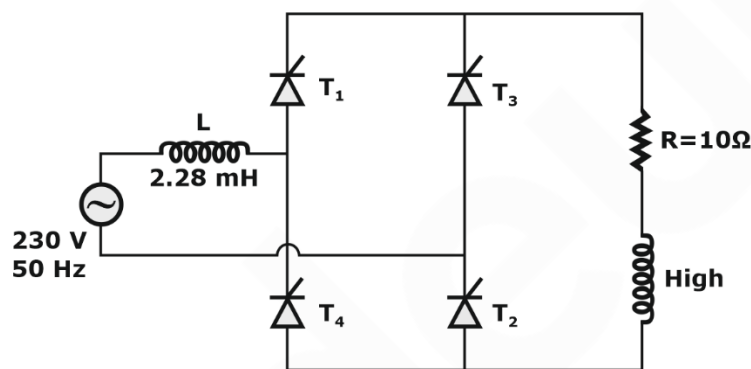

$$V_0 = \frac{1}{\pi} \int_{\alpha+\mu}^{(\pi+\alpha)} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} [\cos \alpha + \cos(\alpha + \mu)]$$

$$I_0 = \frac{V_0}{R} = \frac{V_m}{\pi R} [\cos \alpha + \cos(\alpha + \mu)] \quad \dots(i)$$

from α to $(\alpha + \mu)$

$$L_s \frac{di}{dt} = V_m \sin \omega t$$

$$\int_{-I_0}^{I_0} di = \frac{V_m}{\omega L_s} [-\cos \omega t]_{\alpha}^{(\alpha+\mu)}$$

$$2I_0 = \frac{V_m}{\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$I_0 = \frac{V_m}{2\omega L_s} [\cos \alpha - \cos(\alpha + \mu)] \quad \dots(ii)$$

from eqn. (i) & eqn. (ii)

$$\frac{V_m}{\pi R} [\cos \alpha + \cos(\alpha + \mu)] = \frac{V_m}{2\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$\frac{V_m}{\pi R} [\cos \alpha + \cos(\alpha + \mu)] = \frac{V_m}{2\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$\frac{2\omega L_s}{\pi R} [\cos \alpha + \cos(\alpha + \mu)] = [\cos \alpha - \cos(\alpha + \mu)]$$

$$\cos \alpha \left[1 - \frac{2\omega L_s}{\pi R} \right] = \cos(\alpha + \mu) \left[1 + \frac{2\omega L_s}{\pi R} \right]$$

$$\cos(\alpha + \mu) = \frac{\cos \alpha \left[1 - \frac{2\omega L_s}{\pi R} \right]}{\left(1 + \frac{2\omega L_s}{\pi R} \right)}$$

$$\cos(45^\circ + \mu) = \frac{1}{\sqrt{2}} \left(\frac{1 - 0.0456}{1 + 0.0456} \right)$$

$$= \frac{1}{\sqrt{2}} \left(\frac{0.9544}{1.0456} \right)$$

$$\cos(45^\circ + \mu) = 0.6454$$


$$45^\circ + \mu = 49.804$$

$$\mu = 4.804^\circ$$

45.

Ans. D

Sol.

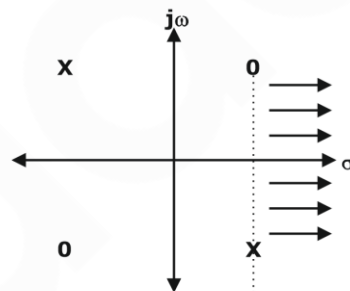

Unstable because ROC does not include unity circle.


All pass : poles and zeroes are in image.

→ poles are not real conjugate.

46.

Ans 1.01 – 1.03

Sol.

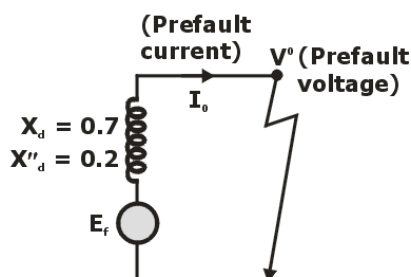

$$I^0 = \frac{E_f - V^0}{j0.7} = \frac{(1 + j0.7) - 1}{j0.7} = 1 \text{ pu.}$$

$$\text{Now, } E_f'' = V^0 + I^0(j \times d'') = 1 + j0.2$$

$$E_f'' = 1.02 \text{ p.u.}$$

47.


Ans A

Sol.

Let current I_i

$$V_1 = V_i t_i \text{ and } V_2 = V_j t_j$$
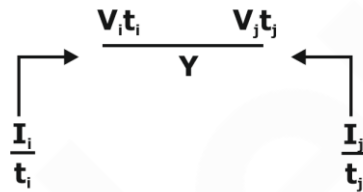
$$I_1 = \frac{I_i}{t_i} \text{ \& } I_2 = \frac{I_j}{t_j}$$



$$\frac{I_i}{t_i} = (V_i t_i - V_j t_j) Y \Rightarrow I_i = V_i t_i^2 \cdot Y V_j t_j \cdot Y \cdot t_j$$

Similarly

$$\frac{I_j}{t_j} = (V_j t_j - V_i t_i) Y$$

$$I_j = -V_i t_i t_j Y + V_j t_j^2 \cdot Y$$

$$\therefore [Y] = \begin{bmatrix} Y t_i^2 & -Y t_i t_j \\ -Y t_i t_j & Y t_j^2 \end{bmatrix}$$

48.

Ans A

Sol.

For a conservative field,

$$\oint \vec{f} \cdot d\vec{\ell} = 0$$

$$\text{or } \nabla \times \vec{f} = 0$$

$$\begin{vmatrix} \hat{a}_x & \hat{a}_y & \hat{a}_z \\ \frac{d}{dx} & \frac{d}{dy} & \frac{d}{dz} \\ (5y - K_1 z) & (3z + K_2 x) & (K_3 y - 4x) \end{vmatrix}$$

$$= \hat{a}_x(K_3 - 3) - \hat{a}_y(-4 + K_1) + \hat{a}_z(K_2 - 5)$$


$$= 0$$

$$\Rightarrow K_3 = 3, K_1 = 4, K_2 = 5$$

49.

Ans A

Sol.

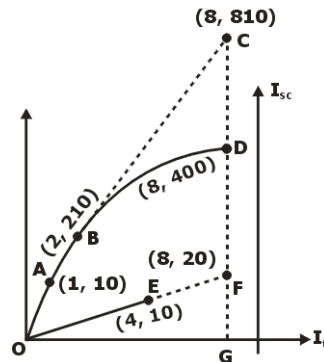

$$\& Z_s(\text{Sat}) = \frac{I_{OC}}{I_{SC}}$$

- Extend Seg OAB to Point C.

Coordinates of C(8, 810)

- Extend OE to F

Coordinates of F(8, 20)

$$\text{Now, } Z_s(\text{unsat}) = \frac{GC}{GF} = \frac{810}{20}$$

$$Z_s(\text{sat}) = \frac{GD}{GF} = \frac{400}{20}$$

$$\frac{Z_s(\text{unsat})}{Z_s(\text{sat})} = \frac{810}{400} = 2.025$$

50.

Ans B

Sol.

51.

Ans 4.95 – 5.05

Sol.

$$f = 10 \text{ KHz}$$

$$T = \frac{1}{f} = \frac{1}{10 \times 10^3} = 100 \mu \text{ sec.}$$

$$D = 0.6$$

$$T_{ON} = DT = 0.6 \times 100 = 6 \mu\text{sec}$$

$$T_{OFF} = (1 - D) T = 40 \mu\text{sec}.$$

Consider 1st cycle:

During T_{ON}

$$V_L = V_S = 50 \text{ volt}$$

$$V_L = L \frac{di}{dt}$$

$$\int_{I_{min}}^{I_{max}} di = \frac{V_L}{L} \int dt$$

$$= \int_0^{I_{max}} di = \frac{50}{10 \times 10^{-3}} \int_0^{T_{ON}} dt$$

$$I_{max} = 5 \times 10^3 \times T_{ON}$$

$$= 5 \times 10^3 \times 60 \times 10^{-6}$$

$$= 300 \times 10^{-3} = 300 \text{ mA}$$


During T_{off} ($V_L = -50 \text{ volt}$)

$$\int_{I_{max}}^{I_{min}} di = \frac{-50}{10 \times 10^{-3}} \int_{T_{ON}}^T dt$$

$$(I_{min} - 300) = -5 \times 10^3 \times 0.4 \times 10 \times 10^{-6}$$

$$= -200 \text{ mA}$$

$$I_{min} = 100 \text{ mA}$$

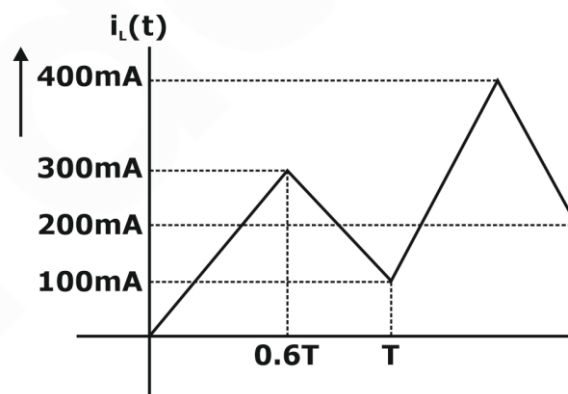

Current in Inductor after 1st cycle = 100 mA

Current in Inductor after 10th cycle = $100 \times 10 = 1000 \text{ mA} = 1 \text{ A}$

$$\text{Energy stored in Inductor} = \frac{1}{2} LI^2$$

$$= \frac{1}{2} \times 10\text{mH} \times (1)^2$$

$$= 5 \text{ mJ}$$

52.

Ans A

Sol. $y = 3x^2 + 3x + 1$

$$\frac{dy}{dx} = 6x + 3 = 0$$

$$x = \frac{-1}{2}$$

$$\frac{d^2y}{dx^2} = 6(+ve) \text{ so it is minimum}$$

Minimum value of y at $x = -1/2$

$$y = 3\left[\frac{-1}{2}\right]^2 + 3\left[\frac{-1}{2}\right] + 1$$

$$= \frac{3}{4} - \frac{3}{2} + 1 = \frac{3 - 6 + 4}{4} = \frac{1}{4}$$

$$y_{\min} = \frac{1}{4}$$

for maximum value, calculate y at boundary

$$y|_{x=0} = 3(0)^2 + 3(0) + 1 = 1$$

$$y|_{x=-2} = 3[-2]^2 + 3[-2] + 1$$


$$= 12 - 6 + 1$$

$$y_{\max} = 7$$

53.

Ans 123 - 127

Sol.

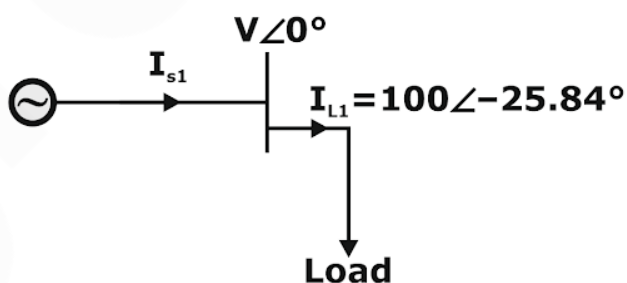


$$f_1 = 0.9, \cos \phi_1 = 0.9$$

$$\phi_1 = 25.84^\circ$$

$$|I_{L1}| = 100A$$

$$I_{L1} = 100 \angle -25.84^\circ$$

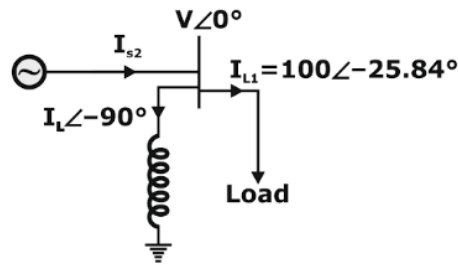

(i) $I_{S1} = I_{L1} = 100 \angle -25.84^\circ$

(ii) $I_{S2} = I_{L1} + I_L \angle -90^\circ$

$= 100 \angle -25.84 + I_L \angle -90^\circ$

$Q_{sh \text{ reactor}} = Q_{load}$

$V I_L = V I_{L1} \sin 25.84$

$I_L = 100 \sin 25.84$

$= 43.58 \text{ A}$

then, $I_{s2} = 100 \angle -25.84 + 43.58 \angle -90^\circ$

$= 100 \cos 25.84 + 43.58 \cos 90^\circ + 100 \sin (-25.84) + I 43.58 \sin (-90^\circ)$


$= 90.00147 - 87.165$

$\approx 125.3 \angle -44^\circ$

54.

Ans. 1.11 – 1.13

Sol.

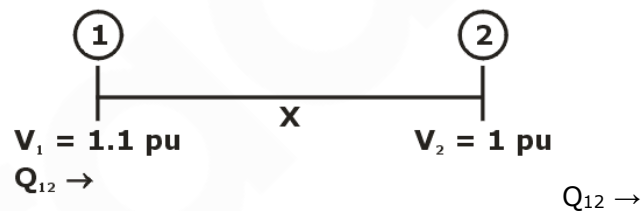

$$Q_{12} = \frac{|V_1|^2}{X} - \frac{|V_1||V_2|}{X} \cos \delta$$

For a highly stable system, δ is very small, $\cos \delta \approx 1$

$$Q_{12} = \frac{|V_1|^2}{X} - \frac{|V_1||V_2|}{X}$$

$$Q_{12} = \frac{|V_1|}{X} (|V_1| - |V_2|) \dots (1)$$

Let, for $Q_{12} \rightarrow 102 Q_{12}$ (20% increase)

$V_1 \rightarrow V'_1$

Then,

$$\frac{1.2 Q_{12}}{Q_{12}} = \frac{|V'_1| (|V'_1| - |V'_2|)}{|V_1| (|V_1| - |V_2|)} \times \frac{X}{X}$$

$$1.2 = \frac{|V'_1| (|V'_1| - 1)}{1.1(1.1 - 1)}$$

$$|V'_1|^2 - |V'_1| - 0.132 = 0$$

$$|V'_1| = 1.118, (-0.118 \text{ not possible})$$

$$\approx 1.12 \text{ (Rounded off to two decimal places)}$$

55.

Ans. A

$$\text{Sol. } T(s) = \frac{K}{(\tau s + 1)}$$

$$r(t) = 5u(t)$$

$$R(s) = \frac{5}{s}$$


$$C(s) = T(s) \cdot R(s) = \frac{K}{(\tau s + 1)} \times \frac{5}{s}$$

$$C(\infty) = \lim_{s \rightarrow 0} sC(s) = \lim_{s \rightarrow 0} s \frac{5K}{s(\tau s + 1)} = 5K$$

According to question

$$C(\infty) = 10$$

$$5K = 10 \Rightarrow K = 2$$

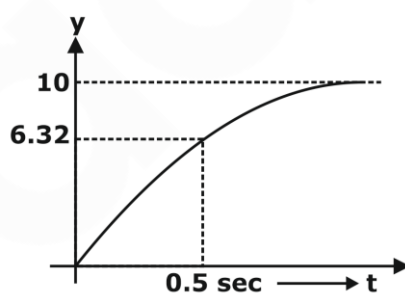

Time constant

$$\tau = 0.5$$


$$T(s) = \frac{K}{(\tau s + 1)}$$

$$= \frac{2}{(0.5s + 1)}$$

56.

Ans 138.10 – 139.20

Sol. Given data,

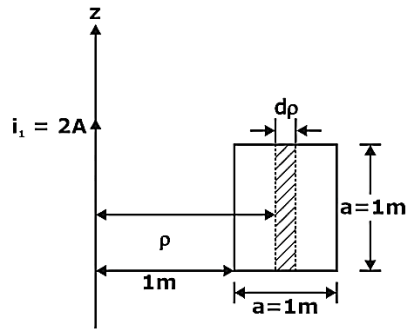

$$M = \frac{\phi}{i_1}$$

where, ϕ is the flux linked with square loop due to current in the wire.

Let, magnetic field intensity due to long wire be,

$$\vec{H} = \frac{I}{2\pi\rho} \hat{a}_\phi$$

$$\vec{B} = \frac{\mu I}{2\pi\rho} \hat{a}_\phi$$

Now flux linked with the elemental strip,

$$d\phi = \vec{B} \cdot d\vec{s}$$

$$= \frac{\mu I}{2\pi\rho} (1 \cdot d\rho)$$

$$\phi = \frac{\mu I}{2\pi} \int_1^2 \frac{d\rho}{\rho}$$

$$= \frac{\mu I}{2\pi} \ln 2$$

Now,

$$M = \frac{\phi}{i_1} = \left(\frac{\mu I}{2\pi} \ln 2 \right) \times \frac{1}{I}$$

$$= \frac{4\pi \times 10^{-7}}{2\pi} \times 0.693$$

$$= 1.386 \times 10^{-7} \text{ H}$$

$$= 138.6 \times 10^{-9} \text{ H} = 138.6 \text{ nH}$$

57.

Ans B

Sol. $I_D = I_S \left[e^{V_D/nVT} - 1 \right]$ in the diode current equality for forward bias and reverse bias.

$$I_1 = I_3 \left[e^{-0.03/\frac{15}{3} \times 26\text{mV}} - 1 \right]$$

$$2 \div 1 \Rightarrow 1.5 \left[e^{-0.03/0.03} - 1 \right] = \left[e^{V_D/0.03} - 1 \right]$$

$$\Rightarrow V_D = -0.0887V \approx -0.09V$$

58.

Ans B

Sol. For maximum power transfer, R_1 should be as small as possible & R_2 should be as large as possible.

\therefore Option D is correct.

59.

Ans. A

Sol.

$$y(z) - az^{-1} y(z) = b_0 x(z) - b_1 z^{-1} x(z)$$

$$\frac{y(z)}{x(z)} = \frac{b_0 - b_1 z^{-1}}{1 - az^{-1}}$$

So, system must be causal.

60.

Ans 54 – 56

Sol.

we know that voltage across capacitor

$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)]e^{-t/\tau}$$

In case (i)

$$0 = 10 + [-V_1 - 10] e^{-0.4t/\tau}$$

$$0 = 10 + [10 + V_1] e^{-0.4}$$

$$10 + V_1 = 10e^{0.4} \dots (i)$$

In case (ii)

$$0 = 10 + [-V_2 - 10]e^{-0.2}$$

$$10 + V_2 = 10e^{0.2} \dots (ii)$$

$$(10 + V_1) = 10e^{0.4}$$

$$10 + V_1 = 10 \times 1.491$$

$$10 + V_1 = 14.91$$

$$V_1 = 4.91 \text{ volt} \quad (10 + V_2) = 10e^{0.2}$$

$$= 10 \times 1.221$$

$$10 + V_2 = 12.21$$

$$V_2 = 2.21 \text{ volt}$$

% change in Initial capacitor voltage


$$= \frac{4.91 - 2.21}{4.91} \times 100$$

$$= 0.5498 \times 100 = 54.98 \% \approx 55\%$$

61.

Ans 0.08

Sol.

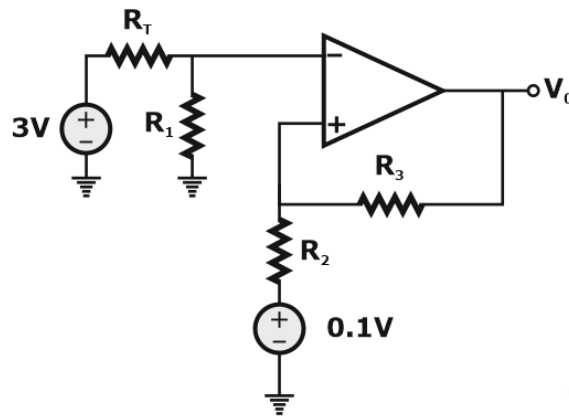

Given

$$R_T = 2(1 + 2T) \text{ k } \Omega$$

Case-i $\alpha = -4\%$

$$R_T = 2 \left(1 - \frac{4 \times 150}{100} \right) = -10 \text{ k}\Omega$$

$$V_0 = 3 \times \frac{1 \text{ k}\Omega}{R_1 + R_T}$$

$$V_0 = 3 \times \frac{R_1}{R_1 + R_T} \left(1 + \frac{R_3}{R_2} \right) - 0.1 \times \frac{R_3}{R_2}$$

$$V_0 = -1.2$$

Case-ii $R_T = 2(1 + 2T)$

$\alpha = -3.75\%$

$$R_T = -9.25$$

$$V_0 = 3 \times \frac{1}{1 - 9.25} [3] - 0.2$$

$$V_0 = -1.290$$

Case-iii $\alpha = 4.25$

$$R_T = 2(1 + 2T)$$

$$R_T = 10.75$$

$$V_0 = -1.12$$


$$V_0 = -1.2 \pm 0.08$$

$$\text{Error} = 0.08.$$


62.

Ans A

Sol.

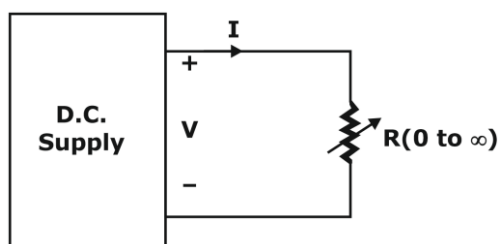

V – I Characteristic of D.C. supply

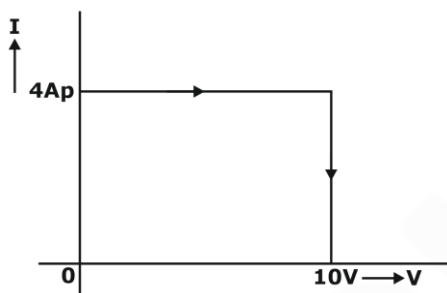

$$R = \frac{V}{I} = \frac{10}{4} = 2.5\Omega$$

If $R > 2.5\Omega$, $I < 4\text{ A}$

If $R < 2.5\Omega$, $V < 10\text{ volt}$

Load Resistance for maximum power transferred

$$R_L = 2.5\Omega$$

Corresponding load voltage

$$V_o = IR = 4 \times 2.5 = 10\text{ Volt}$$

Corresponding load current


$$I_o = 4\text{ A}$$

$$R_L = 2.5\Omega, I_o = 4\text{ A}, V_o = 10\text{ volt.}$$

63.

Ans 45.90 – 46.10

Sol.

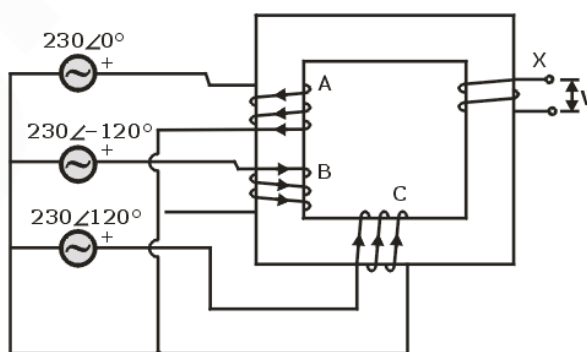

$$V = \frac{2}{20}(130 \angle 0^\circ) - \frac{2}{20}(230 \angle -120^\circ) - \frac{2}{20}(230 \angle 120^\circ) = 46 \angle 0^\circ$$

64.

Ans D

Sol. Closed loop characteristic equation

$$1 + G(s) H(s) = 0$$

$$1 + \frac{5^2 + 5 + 1}{5^3 + 25^2 + 25 + k} \times 1 = 0$$

$$5^3 + 35^2 + 35 + K + 1 = 0$$

Routh array

$$\begin{array}{c|cc} 5^3 & 1 & 3 \\ 5^2 & 3 & k+1 \\ 5 & \frac{8-k}{3} & 0 \\ 5^0 & k+1 & 0 \end{array}$$

For poles on $j\omega$,


$$\frac{8-k}{3} = 0 \Rightarrow K = 8$$

Value of $K = 8$

65.

Ans B

Sol. Given—

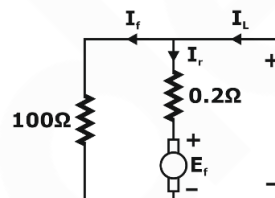

$$I_f = \frac{250}{100} = 2.54$$

at No load:—

$$E_1 = 250 - 0.2 \times 5 - 2 = 247 \text{ V.}$$

at loaded condition:

$$I_L = 50 \text{ A}$$

$$\therefore I_a = 50 - 2.5 = 47.5 \text{ A}$$

$$\therefore E_2 = 250 - 47.5 \times 8.2 - 2 = 238.5$$

$$\therefore E = \frac{P\phi N}{60A} \propto \phi N$$

$$\therefore \frac{E_1}{E_2} = \frac{\phi_1 \cdot N_1}{\phi_2 \cdot N_2}$$

$$\Rightarrow \frac{E_2}{E_1} = \frac{\phi_2 \cdot N_2}{\phi_1 \cdot N_1}$$

$$\Rightarrow \frac{238.5}{247} = \frac{0.95\phi_1 \cdot N_2}{\phi_1 \cdot 1200}$$

$$N_2 = 1219.688 \approx 1220 \text{ rpm}$$



OUR TOP GRADIANS IN GATE 2020



Ghanendra Singh

AIR-6

ECE



Himanshu Kumar

AIR-9

EE



Nikhil Kumar

AIR-9

EE



Raja Majhi

AIR-30

ECE



**Samanwaya Deep
Chakraborty**

AIR-41

ECE



Abhishek

AIR-45

ECE

Classroom

Vision 2021-Course for ESE & GATE (Batch-3)

Electrical Engineering



800+hrs
Live Class



7000+
Practise
Question



Test Series

Vision 2021

A Course for ESE & GATE Electrical Aspirants
Batch-3

Why take this course?

- › **650+ Hours** of Live Classes for ESE & GATE Technical Syllabus
- › **150+ Hours** of Live Classes for ESE Prelims Paper 1 Syllabus
- › **750+ Quizzes** & Conventional Assignments for Practice
- › Subject & Full-Length **Mock Tests** for GATE & ESE



Ashutosh Saxena | Vijay Bansal | MN Ramesh | Rakesh Talreja