


ESE Mains Achiever's Study Plan

Electronics & Communication Engineering

Networks Part-1



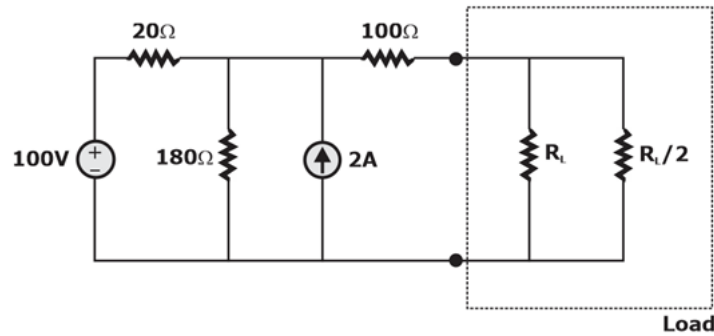
1. Define and prove maximum power transfer theorem also find power dissipated by load resistor R_L in maximum power transfer case.



Sol. Maximum power transfer theorem states that maximum power is transferred from source to load if load impedance is equal to the source impedance (or impedance seen across load terminal)

Prove of MPT:

Consider a circuit as shown below:

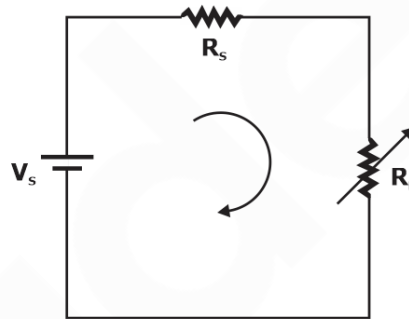

Consider a voltage source V_s having impedance R_s and having load impedance R_L .

$$\text{Current (I) in circuit} = \frac{V_s}{R_s + R_L}$$

Power dissipated in load resistance

$$(R_L) = I^2 R_L$$

$$P = I^2 R_L$$

For finding maximum power find

$$\frac{dP}{dR_L} = 0$$

$$\text{So, } \frac{dP}{dR_L} = \frac{d}{dR_L} I^2 R_L = \frac{d}{dR_L} \frac{V_s^2}{(R_s + R_L)^2} R_L$$

$$= V_s^2 \left[\frac{d}{dR_L} \frac{R_L}{(R_s + R_L)^2} \right]$$

Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

$$= V_s^2 \left[\frac{(R_s + R_L)^2 \times 1 - R_L (2(R_s + R_L))}{(R_s + R_L)^2} \right]$$

$$= V_s^2 \frac{(R_s + R_L) [(R_s + R_L) - 2R_L]}{(R_s + R_L)^2} = 0$$

So, $(R_L = R_s)$


Which is condition of maximum power transfer theorem.

Solution of numerical:

Net load resistance:

$$R'_L = R_L \parallel \frac{R_L}{2} = \frac{1}{3}R_L$$

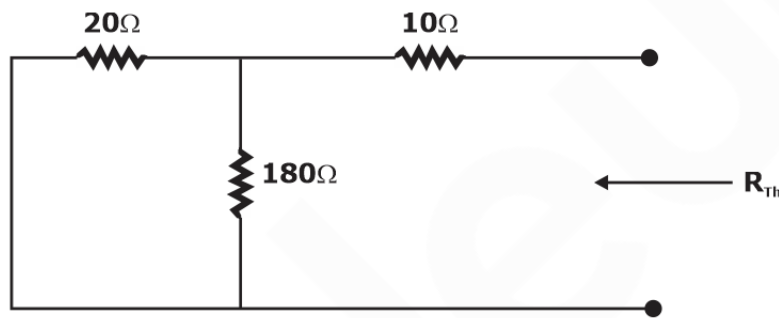Thevenin's resistance across load resistance:




Replace the independent sources with internal impedance.

$$R_{Th} = (20 \parallel 180) + 10 \Omega$$

$$R_{Th} = 18 + 10 = 28 \Omega$$

Open circuit voltage across R_L

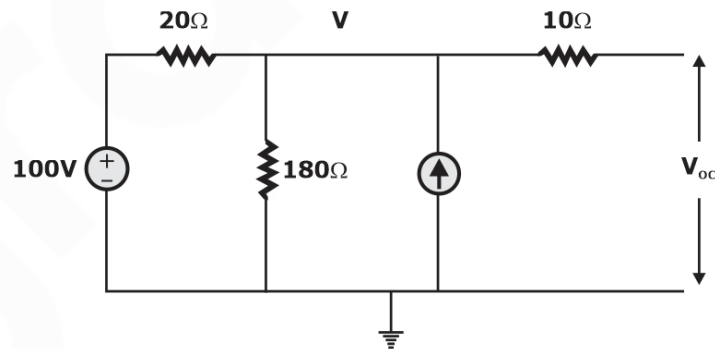

By nodal analysis

$$\frac{V - 100}{20} + \frac{V - 0}{180} = 2$$

$$V \left(\frac{1}{20} + \frac{1}{180} \right) = 2 + \frac{100}{20} = 7$$

$$V = 18 \times 7 = 126 \text{ V}$$

Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants


START FREE TRIAL

$V = V_{OC}$ (as current in $10\ \Omega$ resistor is zero)

By MPT, $R_{Th} = \text{load resistance } R'_L = \frac{1}{3} R_L$

$R_L = 3 \times R_{Th} = 28 \times 3 = 84\ \Omega$

So, equivalent circuit will be :

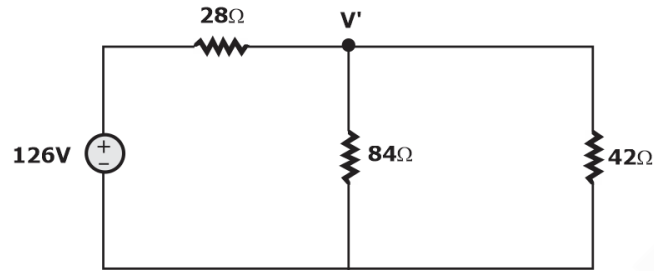

By nodal analysis:

$$\frac{V' - 126}{28} + \frac{V' - 0}{84} + \frac{V' - 0}{42} = 0$$

$$V' \left(\frac{1}{28} + \frac{1}{84} + \frac{1}{42} \right) = \frac{126}{28}$$


$$= 63\ \text{V}$$

Power dissipated in

$$R_L = \frac{(V')^2}{R_L} = \frac{63^2}{84} = 47.25\ \text{watt}$$


The power dissipated in load resistor of R_L is 47.25 W

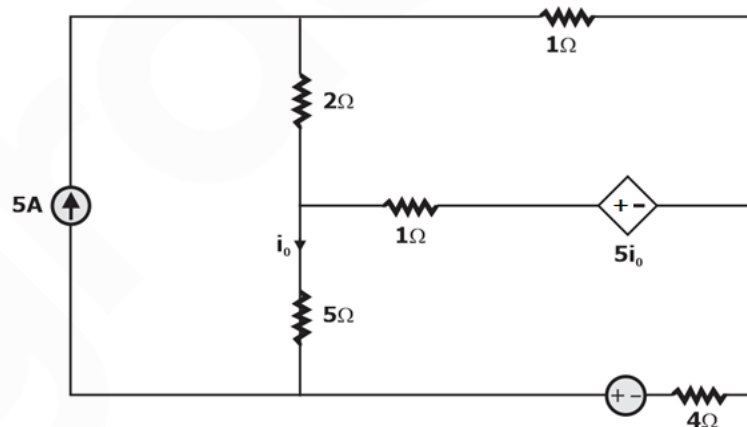2. State superposition theorem. Find i_0 in the circuit using superposition theorem.



Sol. superposition theorem states that in a circuit having more than one independent sources the response in any branch can be calculated by algebraic sum of individual responses of each source and replacing all other source with their internal impedance. Consider 5A current source:

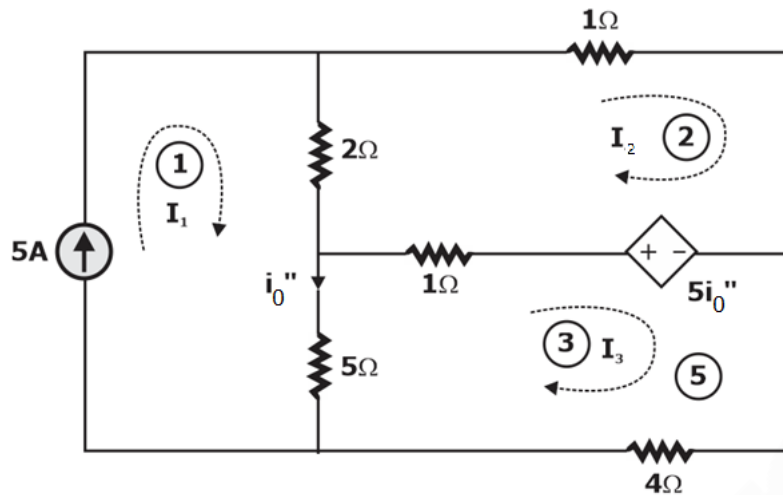Vision 2021 **Batch-3**
 A Course for ESE & GATE Electronics Aspirants
 START FREE TRIAL



Applying loop equations:

In loop (1):

$$I_1 = 5A \dots\dots\dots(i)$$

In loop (2)

$$-2I_1 + 4I_2 - I_3 - 5i_0' = 0 \dots\dots\dots(ii)$$

$$\therefore i_0' = I_1 - I_3 \dots\dots\dots(iii)$$

By (ii) & (iii)

$$-2I_1 + 4I_2 - I_3 - 5(I_1 - I_3) = 0$$

$$-7I_1 + 4I_2 - 6I_3 = 0 \dots\dots\dots(iv)$$

In loop (3)

$$-5I_1 - I_2 + 10I_3 + 5i_0' = 0$$

$$-I_2 + 5I_3 = 0$$

By (i), (iv) & (v)

$$I_1 = 5A$$

$$I_2 = 12.5A$$

$$I_3 = 2.5A$$

$$i_0' = I_1 - I_3 = 2.5A \dots\dots\dots(vi)$$


Vision 2021

Batch-3

START FREE TRIAL

A Course for ESE & GATE Electronics Aspirants

Considering voltage source of 20 V:

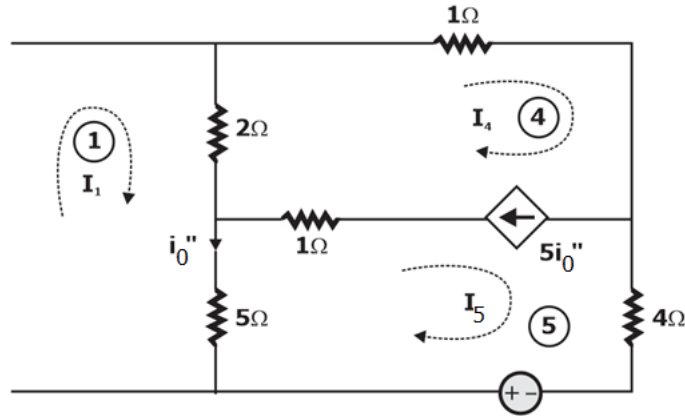

In loop 4

$$4I_4 - I_5 - 5i''_0 = 0 \dots\dots\dots(vii)$$

$$4I_4 - I_5 - 5(-I_5) = 0 (\because I''_0 = -I_5)$$

$$4I_4 + I_5 = 0 \dots\dots\dots(viii)$$

In loop 5:

$$-I_4 + 10I_5 + 5i''_0 - 20 = 0$$

$$-I_4 + 5I_5 = 20 \dots\dots(ix)$$

By (viii) & (ix)

$$I_4 = \frac{-10}{3} \text{ A}$$


$$I_5 = \frac{10}{3} \text{ A}$$

$$i''_0 = -I_5 = \frac{-10}{3} = -3.33 \text{ A}$$

$$\therefore \text{response } i_0 = i'_0 + i''_0 = 2.5 - 3.33$$

$$= -\frac{5}{6} = -0.833 \text{ A}$$

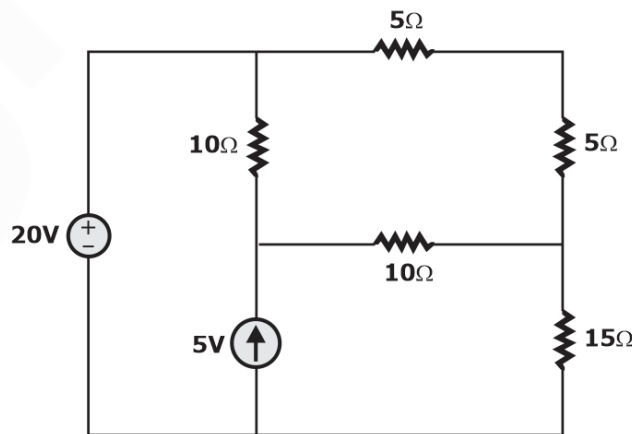3. Determine current in various branches of circuit shown below using mesh analysis




Sol. In the above given circuit taking currents as

Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

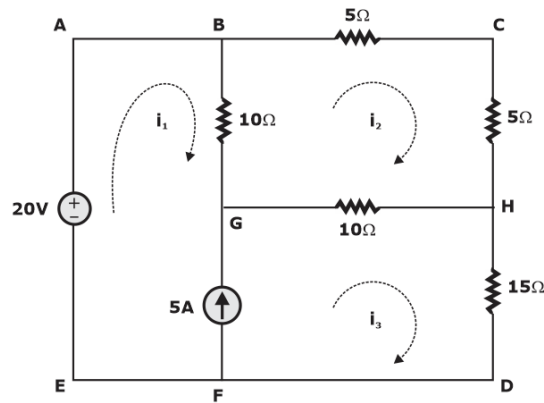

∴ Current source exists in loop so super mesh exists

Applying loop equation in ABGHDFE

$$- 20 + 10 (i_1 - i_2) + 10 (i_3 - i_2) + 15 i_3 = 0$$

$$10i_1 - 20i_2 + 25i_3 = 20 \dots\dots\dots (i)$$

Applying loop equation in GBCH

$$10 (i_2 - i_1) + (5 + 5)i_2 + 10 (i_2 - i_3) = 0$$

$$- 10i_1 + 30i_2 - 10i_3 = 0 \dots\dots\dots (ii)$$

Loop equation can't be applied EABGF & GHDF as it is super mesh

By KCL at node G :

$$i_3 - i_1 = 5$$

$$- i_1 + i_3 = 5 \dots\dots\dots (iii)$$

Writing equation in matrix form:

$$\begin{bmatrix} 10 & -20 & 25 \\ -10 & 30 & -10 \\ -1 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 5 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 10 & -20 & 25 \\ -10 & 30 & -10 \\ -1 & 0 & 1 \end{bmatrix} \text{Det}(\Delta) = 1050$$

$$i_1 = \frac{\Delta_1}{\Delta}$$

$$\Delta_1 = \begin{bmatrix} 20 & -20 & 25 \\ 0 & 30 & -10 \\ 5 & 0 & 1 \end{bmatrix} \Rightarrow \text{Det}|\Delta_1| = -2150$$

$$\Delta_2 = \begin{bmatrix} 10 & 20 & 25 \\ -10 & 0 & -10 \\ -1 & 5 & 1 \end{bmatrix} \Rightarrow \text{Det}|\Delta_2| = -350$$

$$\Delta_3 = \begin{bmatrix} 10 & 20 & 20 \\ -10 & 30 & 0 \\ -1 & 0 & 5 \end{bmatrix} \Rightarrow \text{Det}|\Delta_3| = 3100$$

Current in different branches are

Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants


START FREE TRIAL

$$i_1 = \frac{\Delta_1}{\Delta} = -2.047A$$

$$i_2 = \frac{\Delta_2}{\Delta} = -0.33A$$

$$i_3 = \frac{\Delta_3}{\Delta} = 2.95A$$

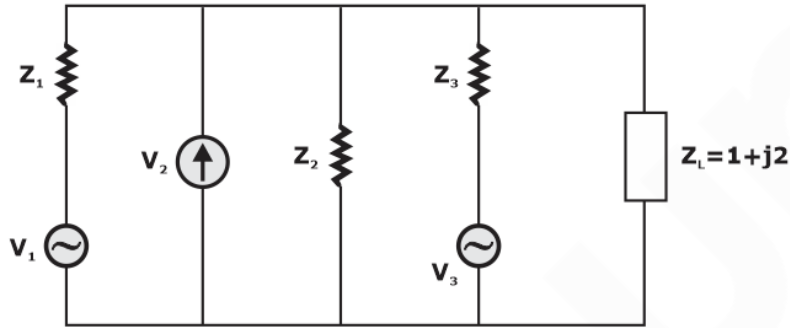4. Explain Millman's theorem. In the circuit given below, find the net response using Millman's theorem i.e. find current through Z_L .




$$V_1 = 5\angle 0^\circ, Z_1 = 1.5 \angle 0^\circ \Omega$$

$$I_2 = 2\angle 0^\circ, Z_2 = 5 \Omega$$

$$V_3 = 10\angle 45^\circ, Z_3 = 10 \Omega$$

Sol. Millman's Theorem:

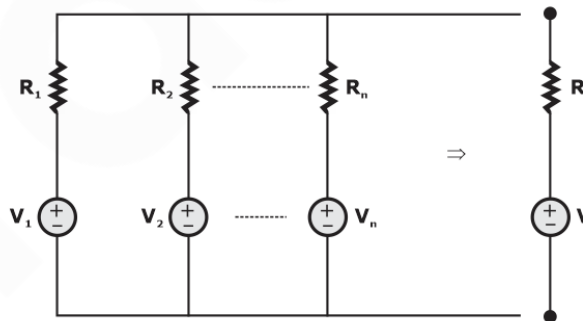Millman's theorem states that in any network having independent voltage source having internal resistances and connected parallel, the entire combination above can be replaced by single voltage source V in series with resistance R where



$$V = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

$$R = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}\right)}$$


Rearranging the circuit given in question by source transformation

Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

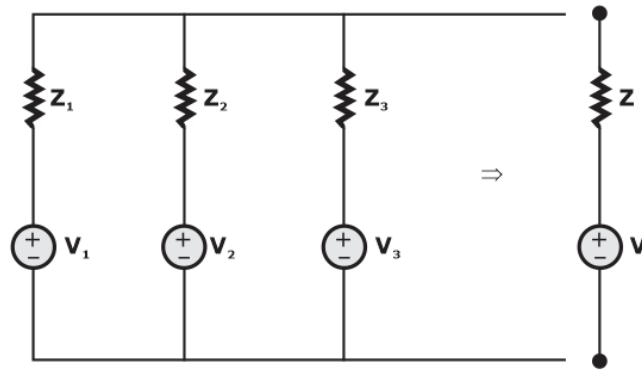

$$V_2 = I_2 Z_2 = 2 \times 5 = 10 \angle 0^\circ \text{ V}$$

$$V = \frac{V_1 G_1 + V_2 G_2 + V_3 G_3}{G_1 + G_2 + G_3} = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

$$V = \frac{\frac{5}{1.5} + \frac{10}{5} + \frac{10 \angle 45^\circ}{10}}{\left(\frac{1}{1.5} + \frac{1}{5} + \frac{1}{10}\right)}$$


$$= \frac{6.04 + j0.707}{0.967}$$

$$= 6.246 + j0.73$$

$$Z = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\left(\frac{1}{1.5} + \frac{1}{5} + \frac{1}{10}\right)}$$

$$= \frac{30}{29} = 1.03 \Omega$$

So net reduced circuit

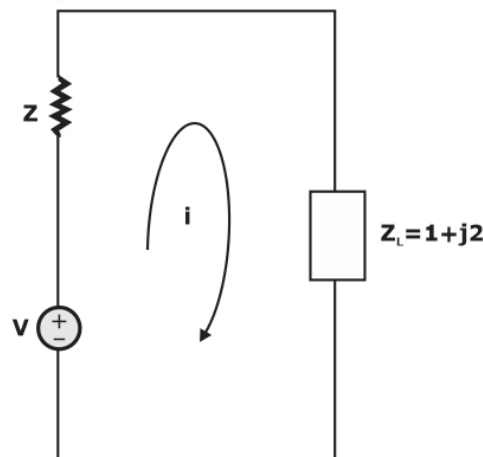

Vision 2021 **Batch-3**
 A Course for ESE & GATE Electronics Aspirants
 START FREE TRIAL


$$i = \frac{V}{z + z_L} = \frac{6.246 + j0.73}{(1.03 + 1 + j2)}$$

$$i = 2.215 \angle -35.92^\circ \text{A}$$


The current through load

$$Z_L = 2.215 \angle -37.92^\circ \text{A}$$

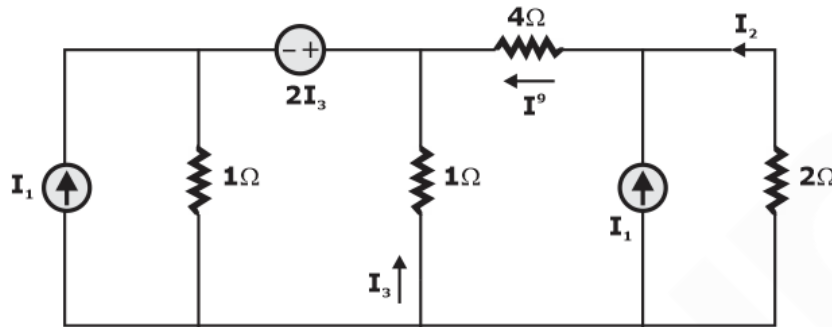5. For the network shown below determine ratio of current I_1/I_2 .



Sol.

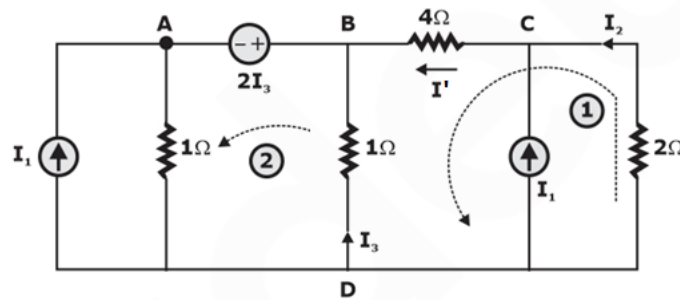

Applying KCL at node C,

$$I_1 + I_2 = I' \dots\dots\dots (i)$$

KVL in node 1:

$$2I_2 + 4I' - I_3 = 0$$

$$2I_2 + 4(I_1 + I_2) - I_3 = 0$$

$$4I_1 + 6I_2 - I_3 = 0 \dots\dots\dots (ii)$$

KVL in node 2:

$$-1 (I_1 + I' + I_3) - 2I_3 - I_3 = 0$$

$$I_1 + I_3 + I_1 + I_2 + 2I_3 + I_3 = 0$$

$$2I_1 + I_2 + 4I_3 = 0 \dots\dots\dots (iii)$$

Equation (ii) $\times 4$ and adding to (iii)

$$4I_1 + 6I_2 - 4I_3 + 2I_1 + I_2 + 4I_3 = 0$$

$$6I_1 + 7I_2 = 0$$

$$\frac{I_1}{I_2} = \frac{-7}{6} \text{ is the required ratio:}$$

Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants

START FREE TRIAL



OUR TOP GRADIANS IN GATE 2020



Ghanendra Singh

AIR-6

ECE



Himanshu Kumar

AIR-9

EE



Nikhil Kumar

AIR-9

EE



Raja Majhi

AIR-30

ECE



**Samanwaya Deep
Chakraborty**

AIR-41

ECE



Abhishek

AIR-45

ECE

Classroom 

Vision 2021-Course for ESE & GATE (Batch-3)

Electronics & Communication Engineering



800+hrs
Live Class



7000+
Practise
Question



Test Series

Vision 2021

A Course for ESE & GATE Electronics Aspirants
Batch-3

Why take this course?

- › **650+ Hours** of Live Classes for ESE & GATE Technical Syllabus
- › **150+ Hours** of Live Classes for ESE Prelims Paper 1 Syllabus
- › **750+ Quizzes** & Conventional Assignments for Practice
- › Subject & Full-Length **Mock Tests** for GATE & ESE



MN Ramesh | Rakesh Talreja | Chandan Jha | Vijay Bansal