


# ESE Mains Achiever's Study Plan

Electronics & Communication Engineering

Networks Part-3



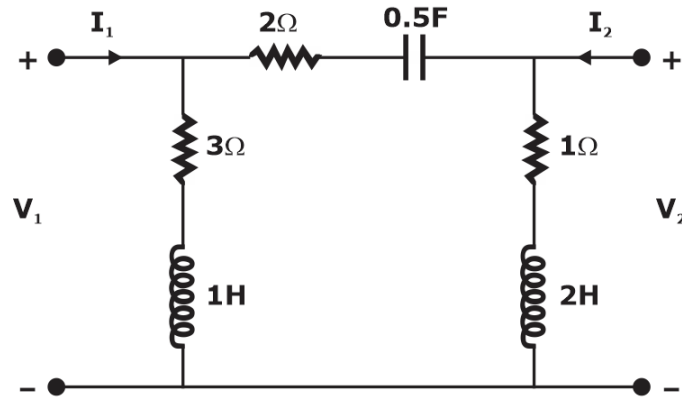1. Find the Y parameter of the circuit shown below:




Sol. The Y parameter or short circuit parameter

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

To calculate  $Y_{11}$  and  $Y_{21}$ ,  $V_2 = 0$  or short circuit

So, the circuit will be

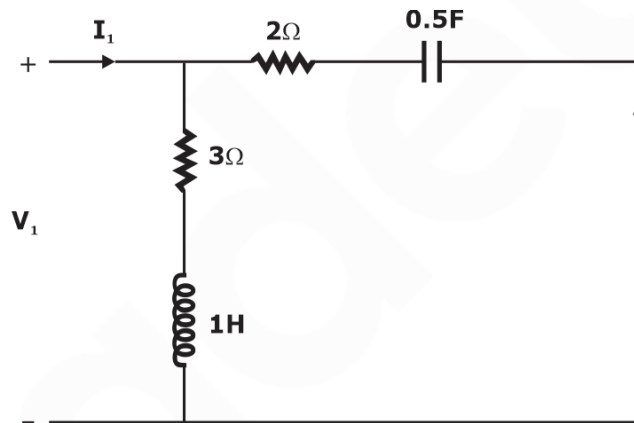

$1\Omega$  and  $2H$  inductors can be removed as they are redundant.

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$\text{So, } V_1 = I_1 [3 + s] \parallel \left( \frac{2s + 2}{s} \right)$$

$$V_1 = I_1 [3 + s] \parallel \left( \frac{2s + 2}{s} \right) = I_1 \frac{(3 + s) \times \left( \frac{2s + 2}{s} \right)}{(3 + s) + \left( \frac{2s + 2}{s} \right)} = I_1 \left[ \frac{2(s + 3)(s + 1)}{s(s + 3) + 2(s + 1)} \right]$$

$$V_1 = I_1 \left[ \frac{2(s^2 + 4s + 3)}{s^2 + 3s + 2s + 2} \right] \dots\dots(i)$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{s^2 + 5s + 2}{2(s^2 + 4s + 2)} \dots(A)$$

# Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

From circuit of figure - 1

$$I_2 = -I_1 \left[ \frac{3+s}{3+s+2+\frac{2}{s}} \right] \quad (\text{by current division rule})$$


$$I_2 = -I_1 \left[ \frac{s(s+3)}{s^2+5s+2} \right] \dots\dots(ii)$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{-I_1 s(s+3)}{I_1 \times \frac{2(s^2+4s+3)}{s^2+5s+2}}$$

$$Y_{21} = \frac{-s(s+3)}{2(s^2+4s+3)}$$

$$Y_{21} = -\frac{s}{2(s+1)} \quad \dots\dots(B)$$

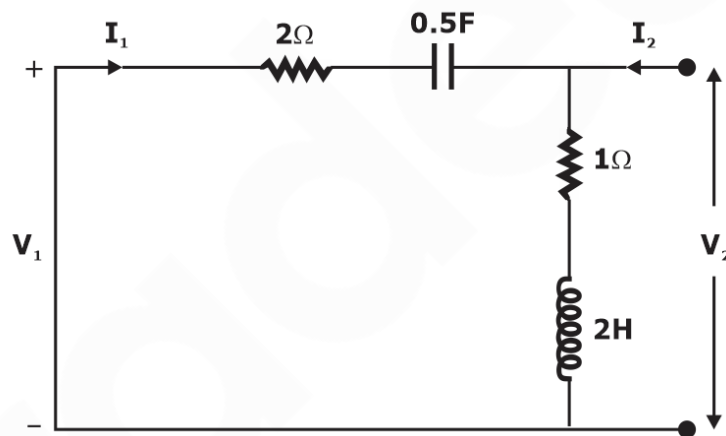For  $Y_{12}$  and  $Y_{22}$  we have  $V_1 = 0$  or short circuited.



For  $Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$  , for  $Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$

$$V_2 = I_2 \left[ (1+2s) \parallel \left( \frac{2s+2}{s} \right) \right] = I_2 \left[ \frac{(1+2s) \times \left( \frac{2s+2}{s} \right)}{(1+2s) + \left( \frac{2s+2}{s} \right)} \right] = I_2 \left[ \frac{2(1+2s)(s+1)}{2s^2+s+2s+2} \right]$$

$$V_2 = I_2 \left[ \frac{2(1+2s)(s+1)}{2s^2+3s+2} \right] \dots\dots(iii)$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \left[ \frac{2s^2+3s+2}{4s^2+6s+2} \right] \dots\dots(C)$$

# Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

$$I_1 = -I_2 \frac{(1+2s)}{1+2s+2+\frac{2}{s}} = -I_2 \frac{(2s+1)s}{2s^2+3s+2}$$

$$I_1 = -I_2 \frac{s(2s+1)}{(2s^2+3s+2)} \dots\dots\dots(iv)$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = \frac{-\frac{s(2s+1)}{(2s^2+3s+2)}}{\frac{2(2s+1)(s+1)}{(2s^2+3s+2)}} = -\frac{s}{2(s+1)}$$


$$Y_{12} = -\frac{s}{2(s+1)}$$

So the Y parameter matrix will be

$$[Y] = \begin{bmatrix} \frac{s^2+5s+2}{2(s^2+4s+2)} & -\frac{s}{2(s+1)} \\ -\frac{s}{2(s+1)} & \frac{2s^2+3s+2}{4s^2+6s+2} \end{bmatrix}$$

$Y_{12} = Y_{21}$  therefore network is symmetrical

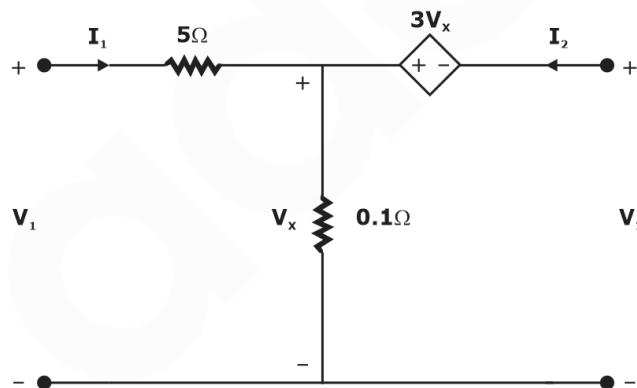2. Determine h-parameter of the network shown below:



Sol. Applying KVL in loops

$$-V_1 + 5I_1 + V_x = 0 \dots(i)$$

$$-V_2 - 3V_x + V_x = 0$$

$$\text{or } -V_2 = 2V_x \dots(ii)$$

$$V_x = \frac{(I_1 + I_2)}{0.1} = 10(I_1 + I_2) \dots\dots\dots(iii)$$

By (i) and (iii)

$$-V_1 + 5I_1 + 10 I_1 + 10I_2 = 0$$

$$15I_1 + 10I_2 = V_1 \dots\dots\dots(iv)$$

# Vision 2021

Batch-3

A Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

By (ii) and (iii)

$$-V_2 = 2 \times 10 (I_1 + I_2)$$

$$20I_1 + 20I_2 = -V_2 \dots\dots(v)$$

$$I_2 = \frac{-V_2 - 20I_1}{20} \dots\dots(vi)$$

The h parameter is given as

$$V_1 = h_{11}I_1 + h_{12}V_2 \dots\dots(A)$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \dots\dots(B)$$

By (iv) and (vi)

$$V_1 = 15I_1 + 10 \times \frac{(-V_2 - 20I_1)}{20} = 15I_1 - 0.5V_2 - 10I_1$$

$$V_1 = 5I_1 - 0.5V_2 \dots\dots(C)$$

Rewriting equation (vi)

$$I_2 = \frac{-20I_1 - V_2}{20}$$

$$I_2 = -I_1 - 0.05V_2 \dots\dots(D)$$

Comparing A, B, C and D

$$h_{11} = 5, h_{12} = -0.5, h_{21} = -1, h_{22} = -0.05$$

$\therefore h_{21} \neq -h_{12}$  so the above h parameter is not reciprocal.

\*\*\*\*\*



# OUR TOP GRADIANS IN GATE 2020



**Ghanendra Singh**

**AIR-6**

ECE



**Himanshu Kumar**

**AIR-9**

EE



**Nikhil Kumar**

**AIR-9**

EE



**Raja Majhi**

**AIR-30**

ECE



**Samanwya Deep  
Chakraborty**

**AIR-41**

ECE



**Abhishek**

**AIR-45**

ECE

**Classroom** 

**Vision 2021-Course for ESE & GATE (Batch-3)**

**Electronics & Communication Engineering**



**800+hrs**  
Live Class



**7000+**  
Practise  
Question



Test Series

# Vision 2021

A Course for ESE & GATE Electronics Aspirants  
Batch-3

## Why take this course?

- › **650+ Hours** of Live Classes for ESE & GATE Technical Syllabus
- › **150+ Hours** of Live Classes for ESE Prelims Paper 1 Syllabus
- › **750+ Quizzes** & Conventional Assignments for Practice
- › Subject & Full-Length **Mock Tests** for GATE & ESE



MN Ramesh | Rakesh Talreja | Chandan Jha | Vijay Bansal