




**The Most Comprehensive
Preparation App For All Exams**

POWER ELECTRONICS (FORMULA NOTES)


Important Fourier series representations :

1)

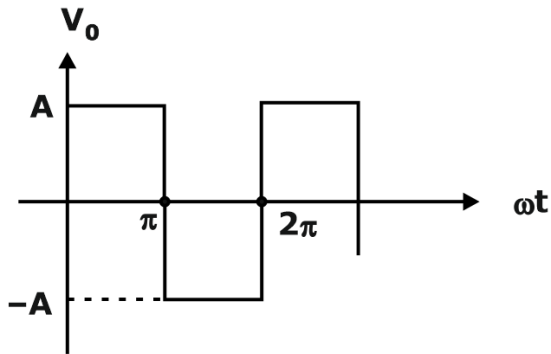


$$V_o = \sum_{n=1,3,5} \frac{4A}{n\pi} \sin n\omega t$$

2)

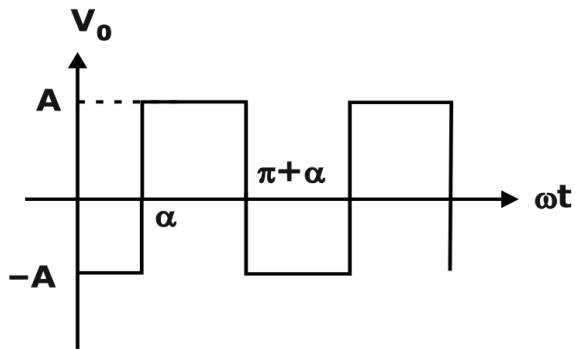


$$V_o = \sum_{n=1,3,5} \frac{4A}{n\pi} \sin(n\omega t - n\alpha)$$

3)

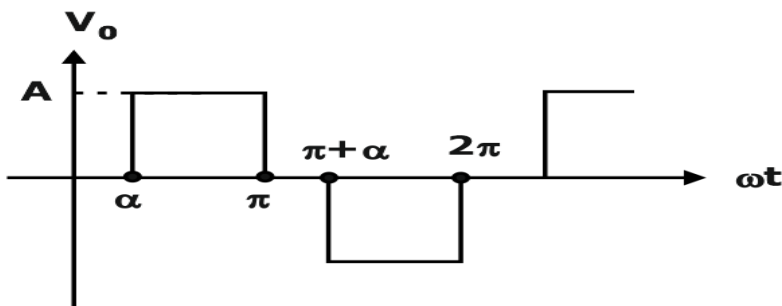

$$V_o = \sum_{n=1,3,5} \frac{4A}{n\pi} \cos\left(\frac{n\alpha}{2}\right) \sin\left(n\omega t - \frac{n\alpha}{2}\right)$$

4)

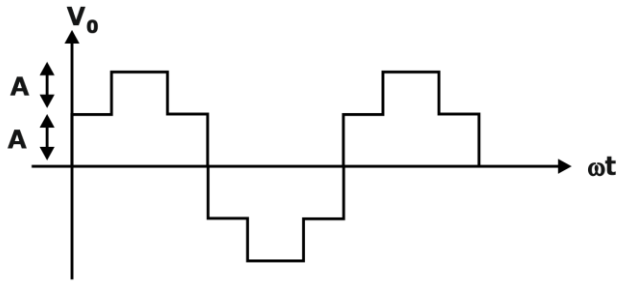

$$V_0 = \sum_{n=1,5,7} \frac{6A}{n\pi} \sin n\omega t$$

Each pulse width of 60° Duration


5) For output of half wave uncontrolled rectifier Fourier series expression is

$$V_0 = \frac{A}{\pi} + \frac{A}{2} \sin \omega t + \sum_{n=2,4,6} \frac{2A}{\pi(1-n^2)} \cos n\omega t \quad \text{Where } A = \text{Amplitude of signal}$$

6) For output of Full wave uncontrolled rectifier Fourier series expression is

$$V_0 = \frac{2A}{\pi} + (\text{fundamental} = 0) + 2 \sum_{n=2,4,6} \frac{2A}{\pi(1-n^2)} \cos n\omega t$$

7)

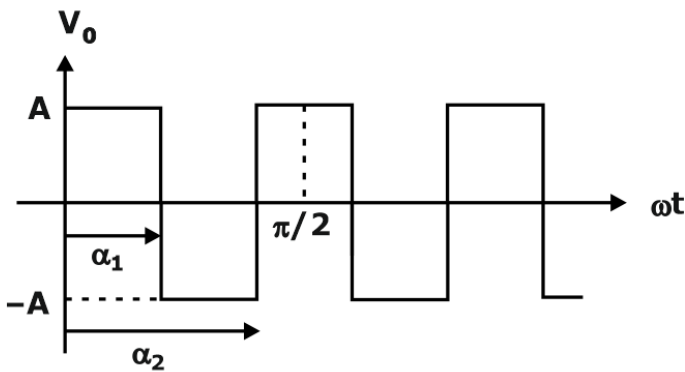


$$V_0 = \frac{4A}{n\pi} (1 - 2 \cos n\alpha_1 + 2 \cos n\alpha_2)$$

| Diode | BJT/MOSFET/IGBT | SCR and GTO | Triac |
|--|---|---|---|
| <ul style="list-style-type: none"> Uncontrolled device Unipolar and unidirectional | <ul style="list-style-type: none"> Fully controlled Unipolar and unidirectional (Without body diodes) | <ul style="list-style-type: none"> SCR-Semi controlled GTO- Fully controlled Both are Bipolar and unidirectional | <ul style="list-style-type: none"> Semi controlled device Bipolar and Bidirectional |


- Conduction losses in BJT is less than MOSFET.
- Switching time in MOSFET is less than BJT.
- Majority carrier devices: MOSFET and Schottky diode are having Positive Temperature Coefficient property.
- Minority carrier devices: SCR, BJT, GTO, IGBT, Power diode and having Negative Temperature Coefficient property.

Static V-I characteristics of SCR

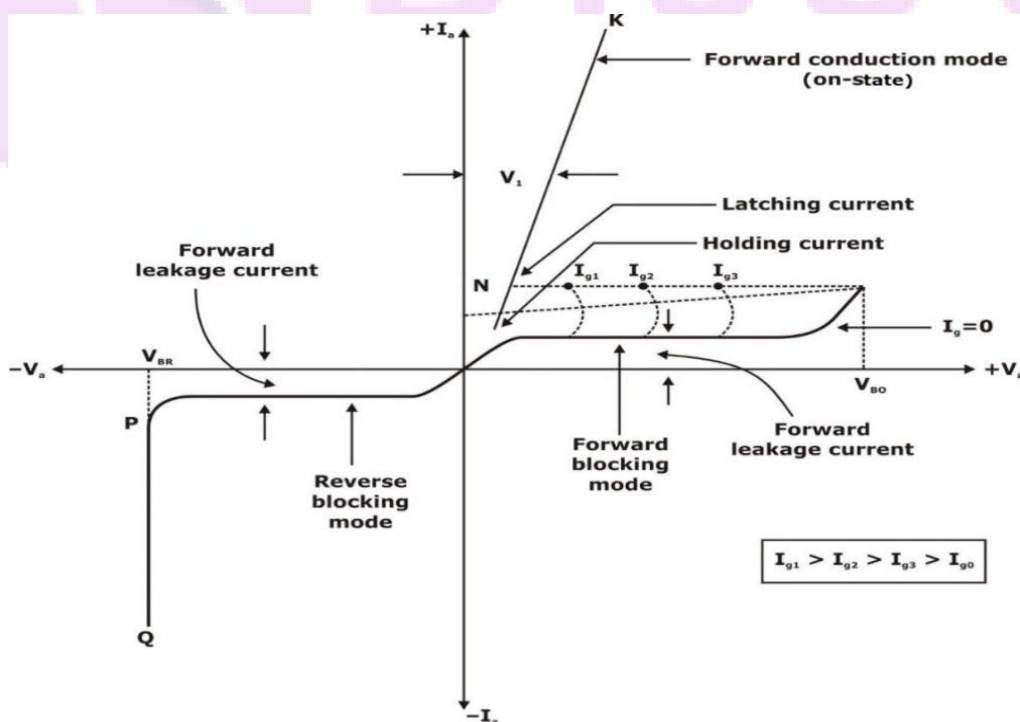

- Latching Current: Minimum current required for conduction even after the gate pulse is removed.
- Holding Current: Minimum Current below which SCR is turned off
- Usually Latching current is 1.5 to 3 times of Holding current

Heat Sink Model:

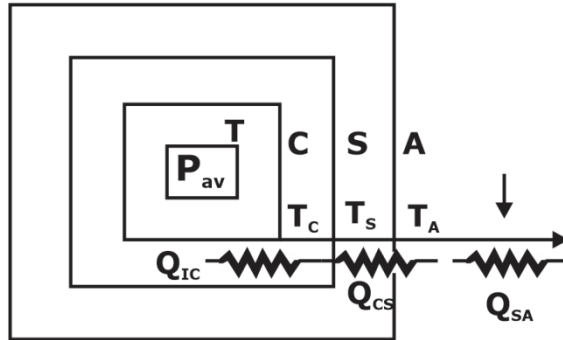

$$P_{\text{avg}} = \frac{T_J - T_C}{Q_{JC}} = \frac{T_C - T_S}{Q_{CS}} = \frac{T_S - T_A}{Q_{SA}}$$

$$\text{Rating of thyristor} \propto \sqrt{P_{\text{avg}}}$$

Charge stored in depletion region:

Let Q_R be the charge stored in depletion region of power diode.

$$Q_R = \frac{1}{2} I_{\text{RM}} t_{\text{rr}}$$

$$I_{\text{RM}} = \frac{2Q_R}{t_{\text{rr}}} = t_a \frac{di}{dt}$$

$$\text{If } t_a \approx t_{\text{rr}}, t_{\text{rr}} = \sqrt{\frac{2Q_R}{di/dt}}$$

$$I_{\text{RM}} = t_{\text{rr}} \frac{di}{dt} = \sqrt{2Q_R} \left(\frac{di}{dt} \right)$$

$$t_{\text{rr}} \propto \sqrt{Q_R}$$

$$Q_R \propto I_f$$

$$t_{\text{rr}} \propto \sqrt{I_f}$$

$$I_{\text{RM}} \propto \sqrt{I_f}$$

Relation Between α and β :

$$\alpha = \frac{I_C}{I_E} \quad \beta = \frac{I_C}{I_B}$$

$$\frac{I_E}{I_C} = 1 + \frac{I_B}{I_C}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 + \alpha}$$

Design of Snubber circuit:

For Inductor (L):

$$\left(\frac{di}{dt}\right)_{\max} = \frac{V_s}{L}$$

$$L = \frac{V_s}{(di/dt)_{\max}}$$

For resistor (R_s):

$$\left(\frac{dv_a}{dt}\right)_{\max} = R_s \left(\frac{di}{dt}\right)_{\max}$$

$$\text{or } R_s = \frac{L}{V_s} \left(\frac{dv_a}{dt}\right)_{\max}$$

For Capacitor (C_s):

$$C_s = \left(\frac{2\xi}{R_s}\right)^2 L \quad \text{where } 0.5 < \xi < 1$$

Design of Snubber circuit:

$$\text{String efficiency} = \frac{\text{Actual voltage/current rating of string.}}{n \times \text{individual voltage/current rating of SCR}}$$

Where n is the number of SCR in string.

Derating factor, DRF = 1 - string efficiency.

Parallel Operation of Thyristors:

When current required by the load is more than the rated current of a single thyristor, SCR's are connected in parallel in a string

Series Operation of Thyristors:

Consider n thyristor connected in series, Let SCR₁ has minimum leakage current I_{bmn} . SCR with lower leakage current blocks more voltage.

Remaining (n-1) SCRs have the same leakage current I_{bmx}

$$I_{bmx} > I_{bmn}$$

$$R_s = \frac{nV_{bm} - V_s}{(n-1)\Delta I_b}$$

Here V_{bm} is the maximum permissible blocking voltage as SCR₁.

R_s is the static equalizing resistance

$$\text{Similarly Static equalizing capacitance } C = \frac{(n-1)\Delta Q_T}{nV_{bm} - V_s}$$

ΔQ_T = difference in recovery charge

Ratings of Thyristors:

1) $I_{T_{rms}}$ Rating: The actual Thyristor rms in a converter must always be less than thyristor RMS ratings.

$$[(I_T)_{rms} \text{ value in a converter}] < (I_T)_{rms} \text{ rating.}$$

2) ($I_{T_{avg}}$) Rating: (average on-state current ratings)

$$(I_{Tavg}) \text{ rating} = \frac{(I_T)_{rms} \text{ Rating}}{\text{Form Factor of thyristor current waveform}}$$

Average rating of a thyristor depends on:

- Conduction angle of thyristor increases which decrease the form factor and then increase the average thyristor rating.
- Type of load: Smoothness of thyristor current waveform increase the FF decreases and therefore $(I_{Tavg})_{Rating}$ increases.
- Type of converter: because FF of thyristor waveform depends on average value of converter.

11.3. I²t Rating of thyristor: specified to select a proper fuse for overcurrent protection.

I²t current Rating of thyristor > I²t current Rating of Fuse.

11.4. Surge current rating of thyristor:

General values

$$(I_T)_{rms} = 35A$$

$$(I_s)_{rms} = 2000A \text{ for one cycle and } 3000A \text{ for } 2MW$$

N-cycle surge current rating: (I_m): It is the surge current that the SCR can withstand for n-cycles.

$$(I_{sn})^2 \left(\frac{nT}{2} \right) = I^2t \text{ rating of thy}$$

from the equation, we can find the value of 'I_{sn}'

One-cycle surge current rating (I_s): It is the surge current that the SCR can withstand

for a cycle. $I_{s1}^2 = (I_{sn})^2$ $I_{s1} = \sqrt{n} I_{sn}$

Sub-cycle surge current rating: It is the surge current that the SCR can withstand for

1/nth period of a cycle. $(I_{s/n})^2 = (I_{sn})^2$ $\frac{I_s}{n} = \sqrt{n} I_{s1}$

RECTIFIERS

➤ For n-pulse converter:

Source current has $nk \pm 1$ Harmonics $k=1,2,3,\dots$

Output voltage has nk Harmonics.

Single Phase Half Wave controlled rectifier:

R-load:

Average output voltage $V_{o,avg} = \frac{V_m}{2\pi} (1 + \cos \alpha)$

RMS output voltage $V_{o,rms} = \sqrt{\frac{V_m^2}{4\pi} \left((\pi - \alpha) + \frac{\sin 2\alpha}{2} \right)}$

RL-Load:

$$\text{Average output voltage } V_{o,avg} = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$\text{RMS output voltage } V_{o,avg} = \frac{V_m}{2\sqrt{\pi}} \left(\sqrt{(\beta - \alpha) + \frac{1}{2}(\sin 2\alpha - \sin 2\beta)} \right)$$

$$\text{Circuit Turnoff time: } t_c = \frac{2\pi - \beta}{\omega}$$

For a constant output current refer below table:

| | 1- ϕ Full conv. | 3 ϕ Full conv. | 1 ϕ Semi conv. | 3 ϕ semi conv |
|--|--------------------------------|---------------------------------------|---|--|
| Output voltage | $\frac{2V_m}{\pi} \cos \alpha$ | $\frac{3V_{m,line}}{\pi} \cos \alpha$ | $\frac{V_m}{\pi} (1 + \cos \alpha)$ | $\frac{3V_{m,line}}{2\pi} (1 + \cos \alpha)$ |
| Fundamental source current RMS(I_{s1}) | $\frac{2\sqrt{2}}{\pi} I_0$ | $\frac{\sqrt{6}}{\pi} I_0$ | $\frac{2\sqrt{2}}{\pi} I_0 \cos\left(\frac{\alpha}{2}\right)$ | $\frac{\sqrt{6}}{\pi} I_0 \cos\left(\frac{\alpha}{2}\right)$ |
| Source current RMS(I_s) | I_0 | $\sqrt{\frac{2}{3}} I_0$ | $I_0 \sqrt{\frac{\pi - \alpha}{\pi}}$ | $\alpha \leq 60^\circ \rightarrow I_0 \sqrt{\frac{2}{3}}$ $\alpha > 60^\circ \rightarrow I_0 \sqrt{\frac{\pi - \alpha}{\pi}}$ |
| Displacement power factor(DPF) | $\cos \alpha$ | $\cos \alpha$ | $\cos\left(\frac{\alpha}{2}\right)$ | $\cos\left(\frac{\alpha}{2}\right)$ |

➤ Distortion factor(DF) = $\frac{I_{s1}}{I_s}$

➤ Input power Factor= DF*DPF

➤ Total Harmonic distortion = $\sqrt{\left(\frac{1}{DF}\right)^2 - 1}$

For R-Load refer below table:

| | 3 ϕ Half wave rectifier | 3 ϕ full wave rectifier |
|---------------|---|--|
| Continuous | $\alpha < 30^\circ$ $\frac{3V_{m,line}}{2\pi} \cos \alpha$ <p>Hint: Integrate from $30 + \alpha$ to $150 + \alpha$ and Time period $T=120^\circ$ and function take in phase, You will get above formula Like this</p> $\frac{1}{\left(\frac{2\pi}{3}\right)} \int_{30+\alpha}^{150+\alpha} V_{m,phase} \sin \omega t \, d\omega t$ | $\alpha < 60^\circ$ $\frac{3V_{m,line}}{\pi} \cos \alpha$ <p>Hint: Integrate from $60 + \alpha$ to $120 + \alpha$ and Time period $T=60^\circ$ and function take in line, You will get above formula</p> |
| Discontinuous | $\alpha \geq 30^\circ$ $V_0 = \frac{3V_{m,phase}}{2\pi} \left(1 + \cos\left(\alpha + \frac{\pi}{6}\right)\right)$ <p>Hint: Integrate from $30 + \alpha$ to 180° and Time period $T=120^\circ$ and function take in phase, You will get above formula</p> | $\alpha \geq 60^\circ$ $V_0 = \frac{3V_{m,line}}{\pi} \left(1 + \cos\left(\alpha + \frac{\pi}{3}\right)\right)$ <p>Hint: Integrate from $60 + \alpha$ to 180° and Time period $T=60^\circ$ and function take in line, You will get above formula</p> |

Effect of Source Inductance:

- **1 ϕ Half wave:**

$$V_0 = \frac{V_m}{2\pi} (1 + \cos \alpha) - fL_s I_0$$

$$I_0 = \frac{V_m}{\omega L_s} (\cos \alpha - \cos(\alpha + \mu))$$

- **1 ϕ Full wave:**

$$V_0 = \frac{2V_m}{\pi} \cos \alpha - 4fL_s I_0$$

$$I_0 = \frac{V_m}{2\omega L_s} (\cos \alpha - \cos(\alpha + \mu))$$

$$\text{Regulation} = \frac{\cos \alpha - \cos(\alpha + \mu)}{2 \cos \alpha}$$

Displacement power factor: $\cos\left(\alpha + \frac{\mu}{2}\right)$


➤ 3 ϕ Full Wave:

$$V_0 = \frac{3V_{m,line}}{\pi} \cos \alpha - 6fL_s I_0$$

$$I_0 = \frac{V_{m,line}}{2\omega L_s} (\cos \alpha - \cos(\alpha + \mu))$$

Single Phase Full converter:


Source current waveform:

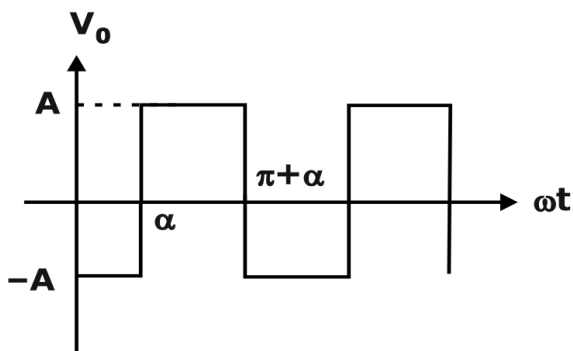

Fundamental source current is $i_{s1} = \frac{2\sqrt{2}}{\pi} I_0$

Single phase half controlled or Semi converter:

Source current waveform:

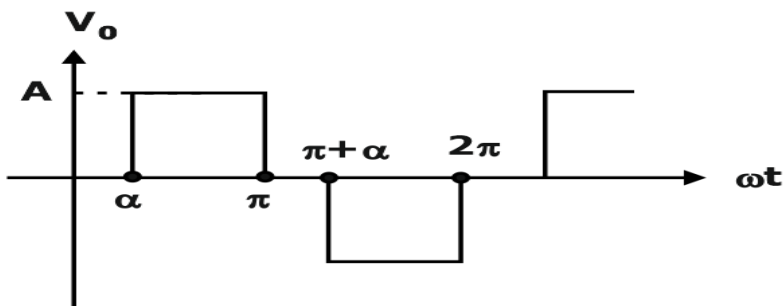

➤ In this there are two configurations:

Symmetrical configuration: On one leg one thyristor and one diode

Unsymmetrical configuration: on one leg two thyristors or two diodes

γ = represents conduction in below table

D- Diode, T-Thyristor, α -Firing angle

| Symmetrical configuration | Unsymmetrical configuration | Full converter with Freewheeling diode |
|---------------------------|-----------------------------|--|
| $\gamma_T = \pi$ | $\gamma_T = \pi - \alpha$ | $\gamma_T = \pi - \alpha$ |
| $\gamma_D = \pi$ | $\gamma_D = \pi + \alpha$ | $\gamma_D = 2\alpha$ |

3-Phase:

Phase Voltage reference:

$$V_{an} = V \angle 0$$

$$V_{bn} = V \angle -120$$

$$V_{cn} = V \angle +120$$

Line Voltage reference

$$V_{AB} = V \angle 0$$

$$V_{BC} = V \angle -120$$

$$V_{CA} = V \angle +120$$

3 Phase half wave controlled Rectifiers:

- Take phase voltage reference in the integration function for the below mentioned limits for calculations
- For R-Load $\alpha < 30^\circ$
 - $\alpha < 30^\circ$: Continuous conduction: $30 + \alpha$ to $150 + \alpha$
 - $\alpha \geq 30^\circ$: Discontinuous conduction: $30 + \alpha$ to 180°
- For current stiff load:
 - Without Freewheeling diode: $30 + \alpha$ to $150 + \alpha$
 - With Freewheeling diode: $\alpha < 30^\circ$: $30 + \alpha$ to $150 + \alpha$
 - $\alpha \geq 30^\circ$: $30 + \alpha$ to 180°
- ✓ Mentioned limits are useful while calculating output voltage average or RMS values for those particular conditions. Use phase as reference while doing calculations of average and RMS

3 Phase Full wave controlled Rectifiers:

- Take Line voltage reference in the integration function for the below mentioned limits for calculations
- Limits are $60 + \alpha$ to $120 + \alpha$ for calculating output voltage average or RMS values
- Circuit Turnoff time:

$$\alpha \leq 60^\circ, t_c = \frac{240^\circ - \alpha}{\omega}$$



$$\alpha > 60^\circ, t_c = \frac{180^\circ - \alpha}{\omega}$$

3 Phase Semi converter:

- $\alpha < 60^\circ$ it is 6 Pulse converter
- $\alpha \geq 60^\circ$ it is 3 Pulse converter
- Freewheeling Action Duration:
 - $\alpha < 60^\circ$, Duration = zero (No freewheeling action)
 - $\alpha \geq 60^\circ$, Duration = $3\left(\alpha - \frac{\pi}{3}\right)$
- Limits for calculating output voltage average or RMS values (Line voltages are reference)
 - $\alpha < 60^\circ$: $60^\circ + \alpha$ to $120^\circ \rightarrow V_{AB}$ reference
 - $\quad \quad \quad$: 120° to $180^\circ + \alpha \rightarrow V_{AC}$ reference
 - $\alpha \geq 60^\circ$: $60^\circ + \alpha$ to $240^\circ \rightarrow V_{AC}$ reference

Commutation Techniques

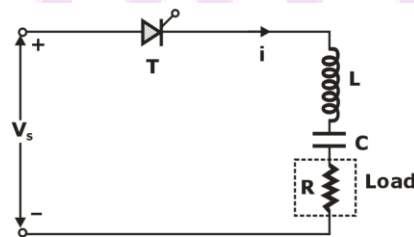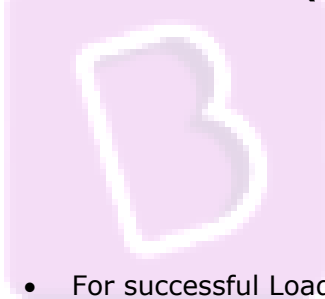1) Class A Commutation (Load Commutation/self-commutation)




- For successful Load commutation, circuit must be under damped
- For under damped $I = I_p e^{-\alpha t} \sin \omega_r t$

$$I_p = \frac{V_s}{\omega_r L}, \alpha = \text{Damping factor} = \frac{R}{2L}, \omega_r^2 = \omega_0^2 - \alpha^2$$

$$\omega_r \text{ is ringing frequency, } \omega_0 = \text{Natural frequency} = \frac{1}{\sqrt{LC}}$$

- Conduction time of thyristor, $t_c = \frac{\pi}{\omega_r}$

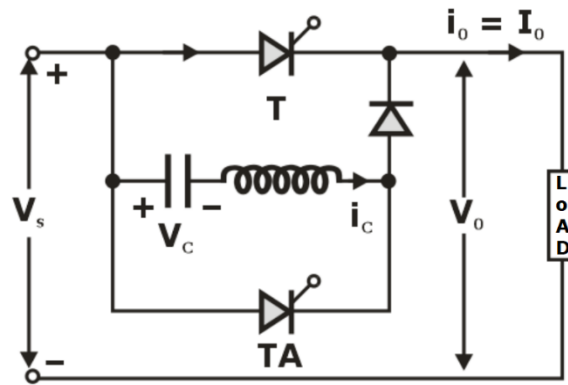2) Class B Commutation/Current Commutation/Resonant pulse commutation:



- Voltage across capacitor $V_c = V_s \cos \omega_0 t$
- Circuit turn-off time for the main thyristor (T_1); $t_c = C \frac{V_{ab}}{I_0}$

$$V_{ab} = V_s \cos \omega_0 (t_3 - t_2)$$

Where t_3 = time when the main thyristor is turned off

t_2 = time when auxiliary thyristor is turned off

$$\omega_0 (t_3 - t_2) = \sin^{-1} \left(\frac{I_0}{I_p} \right)$$


- Main thyristor peak current = I_0
- Auxiliary Thyristor peak current = $V_s \sqrt{\frac{C}{L}}$
- Conduction time of auxiliary thyristor = $\pi \sqrt{LC}$
- Conduction time of main thyristor = $\pi \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_0}{I_p} \right)$

Minimum Conduction time of main thyristor = $\pi \sqrt{LC}$

Maximum Conduction time of main thyristor = $\frac{3}{2} \pi \sqrt{LC}$

- Time for which capacitor current exists = $\frac{C}{I_0} (V_{ab} + V_s)$

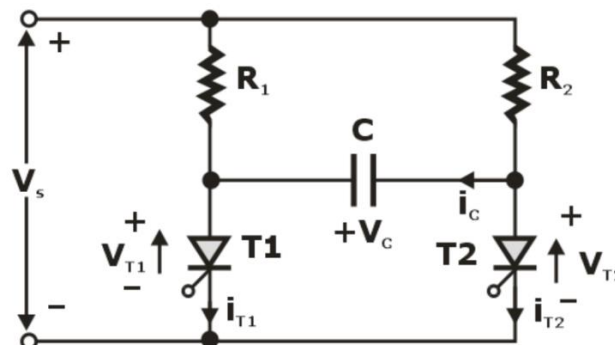Class C Commutation (Impulse/Complementary commutation):



When T_1 is turned on at $t=0$

- The charging current $I_s = \frac{V_s}{R_2} \cdot e^{-t/R_2 C}$

- Voltage across capacitor

$$V_c(t) = V_s(1 - e^{-t/R_2 C})$$

When T_1 is to be turned-off, T_2 is turned-on at T_1

- The charging current $I_c(t) = -\frac{2V_s}{R_1} \cdot e^{-t/R_1 C}$

- The Voltage across capacitor

$$V_c(t) = V_s[2e^{-t/R_1 C} - 1]$$

- Maximum current though thyristor T_1

$$I_{T_1(max)} = V_s \left[\frac{1}{R_1} + \frac{2}{R_2} \right]$$

- Maximum current though thyristor T_2 ,

$$I_{T_2(max)} = V_s \left[\frac{2}{R_1} + \frac{1}{R_2} \right]$$


Circuit turn-off time t_{c_1} for thyristor T_1

$$t_{c_1} = R_1 C \ln(2)$$

Circuit turn-off time t_{c_2} for thyristor T_2

$$t_{c_2} = R_2 C \ln(2)$$

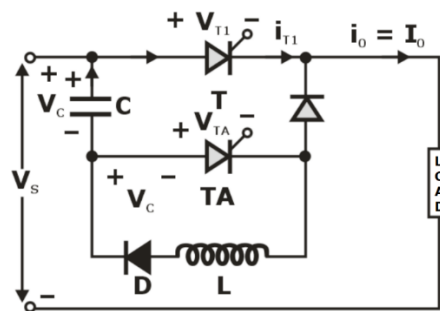Class D Commutation (Voltage commutation):



- Maximum thyristor current Peak = $I_0 + V_s \sqrt{\frac{C}{L}}$
- Auxiliary Thyristor peak current = I_0
- Capacitor peak current = $V_s \sqrt{\frac{C}{L}}$

- Circuit turn-off time for main thyristor T_1 is $t_c = C \frac{V_s}{I_0}$


For R-load it $t_c = RC \ln 2$

- Circuit turn-off time for main thyristor (TA)

$$t_{c1} = \frac{\pi}{2\omega_0}$$

DC-DC Converters

Buck Converter:

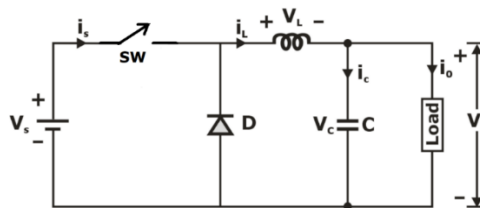

In Buck regulator, the average output voltage V_0 is less than the input voltage V_s .

$$\Delta I = \frac{(V_s - V_0) T_{ON}}{L}$$

$$\Delta I = \frac{V_0 T_{OFF}}{L}$$

$$V_0 = V_s \frac{T_{ON}}{T} = V_s \alpha$$

Where $\Delta I = I_2 - I_1$ is the peak to peak current ripple of the inductor L.

The peak to peak ripple current is $\Delta I = \frac{V_s \alpha (1 - \alpha)}{fL}$

The peak to ripple voltage of the capacitor is $\Delta V_c = \frac{V_s \alpha (1 - \alpha)}{8LCf^2}$

Condition for continuous inductor current and capacitor voltage:


If I_L is average inductor current, the inductor ripple current $\Delta I = 2I_L$, which gives the

critical value of the inductor L_c as $L_c = L = \frac{(1 - \alpha)R}{2f}$

If V_c is the average capacitor voltage, the capacitor ripple voltage $\Delta V_c = 2V_0$, which gives

the critical value of capacitor C_c as $C_c = C = \frac{1 - \alpha}{16Lf^2}$

Boost Converter:

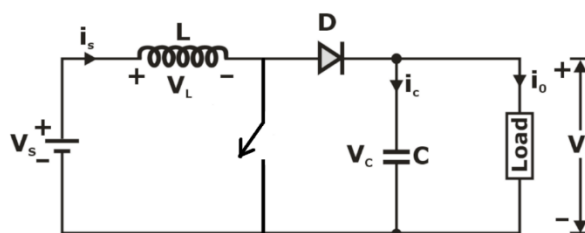

$$\Delta I = \frac{V_S T_{ON}}{L} = \frac{(V_0 - V_S) T_{OFF}}{L}$$

where $\Delta I = I_2 - I_1$ is peak to peak ripple current of the inductor L.

The average output voltage,

$$V_0 = V_S \frac{T}{T_{OFF}} = \left(\frac{1}{1 - \alpha} \right) V_S$$

The peak to peak current ripple is, $\Delta I = \frac{V_S \alpha}{fL}$

The peak to peak ripple voltage of capacitor, $\Delta V_C = \frac{I_0 \alpha}{fC}$

Condition of continuous inductor current and capacitor voltage:


If V_C is the average capacitor voltage, the capacitor ripple voltage $\Delta V_C = 2V_0$, which gives

the critical value of the capacitor C_C as $C_C = \frac{\alpha}{2fR}$

If I_L is average inductor current, the inductor ripple current $\Delta I = 2I_L$, which gives the

critical value of the inductor L_C as $L_C = L = \frac{\alpha(1 - \alpha)^2 R}{2f}$

Buck Boost Converter:

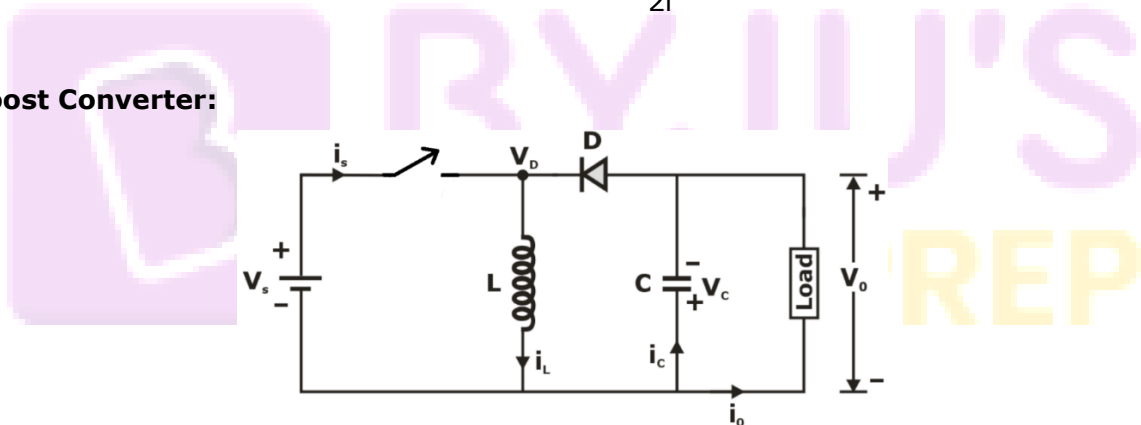

$$\Delta I = \frac{V_S T_{ON}}{L} = \frac{-V_0 T_{OFF}}{L}$$

where $\Delta I = I_2 - I_1$ is the peak to peak ripple current of inductor L.

The average output voltage is, $V_0 = -\frac{V_S \alpha}{1 - \alpha}$

The peak to peak current ripple is, $\Delta I = \frac{V_S \alpha}{fL}$

peak to peak ripple voltage of the capacitor is, $\Delta V_C = \frac{I_0 \alpha}{fC}$

Condition of continuous inductor current and capacitor voltage:

If V_C is the average capacitor voltage, the capacitor ripple voltage, $\Delta V_C = 2V_0$, which gives


the critical value of the capacitor C_C as $C_C = \frac{\alpha}{2fR}$.

If I_L is average inductor current, the inductor ripple current $\Delta I = 2I_L$, which gives the

critical value of the inductor L_c as $L_c = L = \frac{(1-\alpha)^2 R}{2f}$

| Expression for V_0 | BUCK | BOOST | BUCK BOOST |
|----------------------|----------------------------------|--|--|
| In CCM | $V_0 = \alpha V_s$ | $V_0 = \frac{V_s}{1-\alpha}$ | $V_0 = -\frac{\alpha V_s}{1-\alpha}$ |
| In DCM | $V_0 = \frac{\alpha}{\beta} V_s$ | $V_0 = \frac{\beta V_s}{\beta-\alpha}$ | $V_0 = -\frac{\alpha V_s}{\beta-\alpha}$ |

Steady State analysis of Type A Chopper:

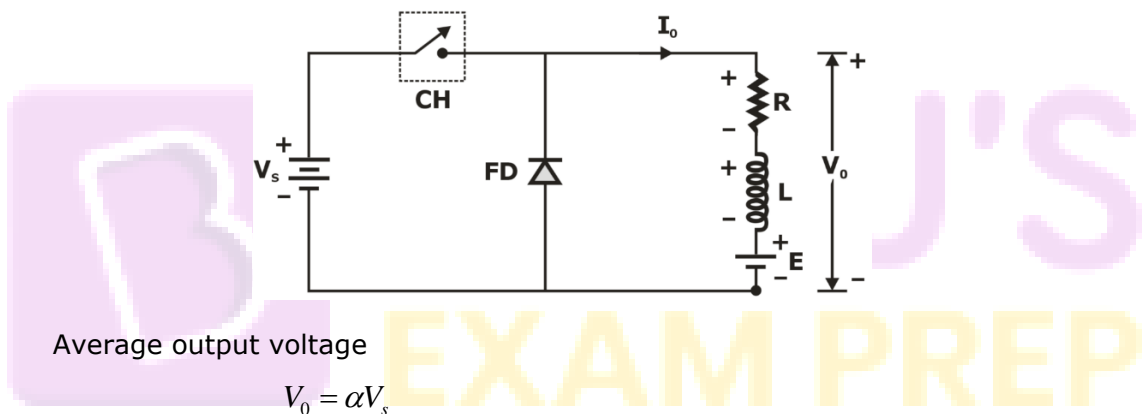

$$V_{or} = \sqrt{\alpha} V_s \text{ (Rms value of output voltage)}$$

$$I_{max} = \frac{V_s}{R} \left[\frac{1 - e^{-T_{on}/T_a}}{1 - e^{-T/T_a}} \right] - \frac{E}{R}$$

$$I_{min} = \frac{V_s}{R} \left[\frac{e^{T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right] - \frac{E}{R}$$


Where, $T_a =$ load time constant

$$T_a = \frac{L}{R}$$

Current ripple,

$$(\Delta I) = I_{max} - I_{min}$$
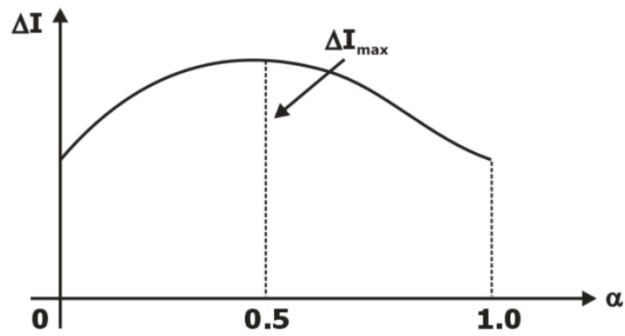
$$\Delta I = \frac{V_s}{R} \left[\frac{(1 - e^{-T_{on}/T_a})(1 - e^{-T_{off}/T_a})}{(1 - e^{-T/T_a})} \right]$$



$$T_{on} = \alpha T$$

$$T_{off} = (1 - \alpha) T$$

Per unit ripple (or) Ripple is a function of duty cycle ' α '. Ripple is minimum at $\alpha = 0$, increases maximum at $\alpha = 0.5$ and decrease at $\alpha = 1.0$. For $\alpha = 0.5$, ripple would be maximum.

$$(\Delta I)_{max} = \frac{V_s}{R} \left(\frac{(1 - e^{-0.5x})(1 - e^{-0.5x})}{1 - e^{-x}} \right) \quad \left(\text{Let, } \frac{T}{T_a} = x \right)$$

$$(\Delta I)_{max} = \frac{V_s}{R} \tanh\left(\frac{R}{4fL}\right)$$

Inverters

Series Inverters: In a series inverter, the commutating elements L and C are connected in series with the load resistance R. The load resistance R can also be in parallel with C. The value of L and C are such that those form an underdamped circuit i.e.

$$R^2 < \frac{4L}{C}$$

$f = \left[\frac{1}{2 \left(\frac{T}{2} + T_{off} \right)} \right]$ is the frequency of output voltage.

Where, $\frac{T}{2}$ is the time period of oscillations.

T_{off} is the time gap between turn-off one thyristor and turn-on of the second thyristor.

$$\frac{T}{2} = \frac{\pi}{\sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2} \right)}}$$

The period of oscillation

Bridge Inverter: Bridge circuits are commonly used in DC-AC conversion. Moreover, an output transformer is not essential in a bridge circuit.

1 ϕ Half Bridge Inverter - The output voltage volt $V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin n\omega t$

1 ϕ Full Bridge Inverter- The output voltage

$$V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t$$

Where, n = order of harmonic

$\omega=2\pi f$, is frequency of the output voltage in red/sec

Key points:

- The load impedance (Z_n) is

$$Z_n = \left[R^2 + \left(n\omega L - \frac{1}{n\omega C} \right)^2 \right]^{1/2}$$

- Phase angle, $\phi_n = \tan^{-1} \frac{\left[n\omega L - \frac{1}{n\omega C} \right]}{R}$

3 phase Full Bridge VSI:

| | 180 ⁰ Conduction | 120 ⁰ Conduction |
|-------------------------------|-----------------------------|--|
| Line Voltage RMS | $V_s \sqrt{\frac{2}{3}}$ | $V_s \frac{1}{\sqrt{2}}$ |
| Phase voltage RMS | $V_s \frac{\sqrt{2}}{3}$ | $V_s \frac{1}{\sqrt{6}}$ |
| Fundamental line voltage RMS | $V_s \frac{\sqrt{6}}{\pi}$ | $V_s \frac{3}{\pi\sqrt{2}}$ |
| Fundamental phase voltage RMS | $V_s \frac{\sqrt{2}}{\pi}$ | $V_s \frac{1}{\pi} \sqrt{\frac{3}{2}}$ |

180⁰ Conduction:

1) Pole Voltages = $V_{A0} = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin n\omega t$

2) Line Voltages = $\sum_{n=1,3,5} \left(\frac{4V_s}{n\pi} \cos \left(n \frac{\pi}{6} \right) \right) \sin(n(\omega t + 30^\circ))$

When n=3, 9, 15 Line voltage= 0, So Line voltages are free from Triplet harmonics

3) Phase Voltage= $\sum_{n=6k \pm 1} \frac{2V_{dc}}{n\pi} \sin n\omega t$

$n = 6k \pm 1$ is due to stepped waveform

120° Conduction:

- 1) Pole and Phase Voltage are of same waveform
- 2) Triplet harmonics are absent in Phase and pole voltages
- 3) Line voltage contains $n = 6k \pm 1$ Harmonics

Pulse Width Modulation:

- Let N = number of pulses per half cycle

$$\text{Each pulse width} = \frac{2d}{N}$$

Then Output voltage Expression is

$$V_0 = \sum_{n=1,3,5} \left(N \frac{4V_s}{n\pi} \sin n\gamma \sin \frac{nd}{N} \right) \sin n\omega t$$

$$\text{Where } \gamma = \frac{\pi - 2d}{N+1} + \frac{d}{N}$$

- Number of pulses per half cycle $N = \frac{f_c}{2f}$

f = reference input frequency

f_c = Carrier input frequency

- Modulation Index $m_a = \frac{V_{Ref}}{V_{carrier}}$
- Relation between Pulse width and modulation index

$$\frac{2d}{N} = \frac{\pi}{N} (1 - m_a)$$

Amplitude Modulation Depth:

$$m_0 = \frac{\hat{V}_m}{\hat{V}_c}$$

Where V_m , V_c are the modulating and carrier signal voltage, respectively.

For sinusoidal PWM, the amplitude modulation depth must be less than 1.0

Output Voltages by Sinusoidal PWM:

- In single phase half bridge VSI

$$\text{Fundamental peak pole voltage} = V_{Ao1}^{\wedge} = m_a \frac{V_s}{2}$$

- In single phase Full bridge VSI

$$\text{Fundamental peak pole voltage} = V_{Ao1}^{\wedge} = m_a V_s$$

- In Three phase Full bridge VSI

$$\text{Peak Fundamental Phase voltage } \hat{V}_{an1} = m_a \frac{V_{DC}}{2}$$

The fundamental line-line rms voltage is given by

$$V_{LL0_1} = \frac{\sqrt{3}}{2\sqrt{2}} m_a V_{DC}$$

- If peak value of carrier input and zero crossing of reference sinusoidal coincidence then, Number of Pulses per half cycle will be $N = \frac{f_c}{2f}$
- If Zero Crossing of carrier input and reference sinusoidal coincidence then, Number of Pulses per half cycle will be $N = \frac{f_c}{2f} - 1$
- If N is the number of pulses per half cycle then the predominant harmonics in the output is $2N \pm 1$

