



Rajasthan RVUNL

Electrical Engineering

Power Electronics

100 Days Important Formula Notes



POWER ELECTRONICS (FORMULA NOTES)

Charge stored in depletion region:

Let Q_R be the charge stored in depletion region of power diode.

$$Q_R = \frac{1}{2} I_{RM} t_{rr}$$

$$I_{RM} = \frac{2Q_R}{t_{rr}} = t_a \frac{di}{dt} = \sqrt{2Q_R} \left(\frac{di}{dt} \right)$$

$$\text{If } t_a \approx t_{rr}, t_{rr} = \sqrt{\frac{2Q_R}{di/dt}}$$

$$I_{RR} = t_{rr} \cdot \frac{di}{dt} = \sqrt{2Q_R} \left(\frac{di}{dt} \right)$$

$$t_{rr} \propto \sqrt{Q_R}$$

$$Q_R \propto I_f$$

$$t_{rr} \propto \sqrt{I_f}$$

$$I_{RM} \propto \sqrt{I_f}$$

Relation Between α and β :

$$\alpha = \frac{I_C}{I_E} \quad \beta = \frac{I_C}{I_B}$$

$$\frac{I_E}{I_C} = 1 + \frac{I_B}{I_C}$$

$$\frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 + \alpha}$$

Design of Snubber circuit:

For Inductor (L):

$$\left(\frac{di}{dt}\right)_{\max} = \frac{V_s}{L}$$

$$L = \frac{V_s}{(di/dt)_{\max}}$$

For resistor (R_s):

$$\left(\frac{dv_a}{dt}\right)_{\max} = R_s \left(\frac{di}{dt}\right)_{\max}$$

$$\text{or } R_s = \frac{L}{V_s} \left(\frac{dv_a}{dt}\right)_{\max}$$

For Capacitor (C_s):

$$C_s = \left(\frac{2\xi}{R_s}\right)^2 L \quad \text{where } 0.5 < \xi < 1$$

Design of Snubber circuit:

$$\text{String efficiency} = \frac{\text{Actual voltage/current rating of string.}}{n \times \text{individual voltage/current rating of SCR}}$$

where n is the number of SCR in string.

Derating factor, DRF=1- string efficiency.

Series Operation of Thyristors:

Consider n thyristor connected in series as shown in figure. Let SCR1 has minimum leakage current I_{bmn}. SCR with lower leakage current blocks more voltage.

Remaining (n-1) SCRs have the same leakage current I_{bmx}

$$I_{bmx} > I_{bmn}$$

Here V_{bm} is the maximum permissible blocking voltage as SCR1.

$$I = I_1 + I_{bmn}$$

$$I_1 = I - I_{bmn}$$

$$I = I_2 + I_{bmx}$$

$$I_2 = I - I_{bmx}$$

Where, I = total string current

Voltage across SCR1 is V_{bm}= I₁R

Voltage across (n-1) SCRs =(n-1) I₂ R

For a string voltage (V_s), the voltage equation for the series circuit is

$$V_s = I_1 R + (n-1)I_2 R = V_{bm} + (n-1)R(I - I_{bmx})$$

$$= V_{bm} + (n-1)R(I_1 + I_{bmn} - I_{bmx})$$

$$= V_{bm} + (n-1)R[(I_1 - (I_{bmx} - I_{bmn}))]$$

Rajasthan RVUNL

A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

$$V_s = V_{bm} + (n-1)R_1 I_1 - (n-1)R \Delta I_b \quad [\because \Delta I_b = I_{bmx} - I_{bmn}]$$

$$AS, RI_1 = V_{bm}$$

$$V_s = V_{bm} + (n-1)V_{bm} - (n-1)R \Delta I_b$$

$$V_s = nV_{bm} - (n-1)R \Delta I_b$$

$$R_s = \frac{nV_{bm} - V_s}{(n-1) - \Delta I_b}$$

'R_s' is the static equalizing resistance.

Parallel Operation of Thyristors:

When current required by the load is more than the rated current of a single thyristor, SCR's are connected in parallel in a string.

Class A Commutation (Load Commutation)

$$I(t) = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t \quad \text{Conduction time of thyristor, } t_0 = \frac{\pi}{\omega_0} = \pi \sqrt{LC}$$

where, $\omega_0 =$ resonant frequency $\frac{1}{\sqrt{LC}}$

Class B Commutation:

- Resonant current $dI_c = -V_s \sqrt{\frac{C}{L}} \sin \omega_0 t$
- Peak resonant current $I_p = V_s \sqrt{\frac{C}{L}}$
- Voltage across capacitor $V_c = V_s \cos \omega_0 t$
- Circuit turn-off time for the main thyristor (T_1); $t_c = C \frac{V_{ab}}{I_0}$
- Reverse voltage across the main thyristor (T_1)

$$V_{sb} = V_s \cos \omega_0 (t_3 - t_2)$$

Where $t_3 =$ time when the main thyristor is turned off

$t_2 =$ time when auxiliary thyristor is turned off

$$\omega_0 (t_3 - t_2) = \sin^{-1} \left(\frac{I_0}{I_p} \right) \text{ and}$$

Class C Commutation:

When T_1 is turned on at $t=0$

- The charging current $I_s = \frac{V_s}{R_z} \cdot e^{-t/R_z C}$
- Voltage across capacitor

$$V_c(t) = V_s(1 - e^{-t/R_2 C})$$

When T₁ is to be turned-off, T₂ is turned-on at T₁

- The charging current $I_c(t) = -\frac{2V_s}{R_1} \cdot e^{-t/R_1 C}$

- The Voltage across capacitor

$$V_c(t) = V_s[2e^{-t/R_1 C} - 1]$$

- Maximum current through thyristor T₁

$$I_{T_1(max)} = V_s \left[\frac{1}{R_1} - \frac{2}{R_2} \right]$$

- Maximum current through thyristor T₂,

$$I_{T_2(max)} = V_s \left[\frac{2}{R_1} + \frac{1}{R_2} \right]$$

Circuit turn-off time t_{c1} for thyristor T₁

$$t_{c1} = R_1 C \ln(2)$$

Circuit turn-off time t_{c2} for thyristor T₂

$$t_{c2} = R_2 C \ln(2)$$

Class D Commutation:

- Capacitor current**

$$I_c = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t = I_p \sin \omega_0 t$$

- Circuit turn-off time for main thyristor (T₁)

$$t_c = C \frac{V_s}{I_0}$$

- Circuit turn-off time for main thyristor (TA)

$$t_{c1} = \frac{\pi}{2\omega_0}$$

Single Phase Half Wave Diode Rectifier:

With R Load:

- RMS value of output voltage**

$$V_{0 rms} = \frac{V_m}{2}$$

V_m = Maximum value of source voltage (V_s)

- Average value of output voltage,

$$V_{0 DC} = \frac{V_m}{\pi}$$

Rajasthan RVUNL

A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

- Average value of output voltage,
- Power delivered $P = I_{0\text{ rms}}^2 \cdot R$

$$I_0 \text{ rms} = \text{rms value of load current} = \frac{\text{Power delivered to load}}{\text{Input } V_A}$$

- Input power Factor = $\frac{V_{0\text{ rms}} \cdot I_{0\text{ rms}}}{V_s - I_{0\text{ rms}}} = 0.707$

With L load:

- **Output current** $I_0 = \frac{V_m}{\omega L} (1 - \cos \omega t)$
- Maximum value of current $I_0 = \frac{2X_m}{\omega L}$
- Average value of current $I_0 = \frac{I_{\text{max}}}{2}$
- RMS value of fundamental current

$$I_{1\text{ rms}} = \frac{I_0}{\sqrt{2}}$$

- Output voltage $V_0 = V_m \sin \omega t = V_s$
- Average value of current voltage $V_0 = 0$

With C Load:

- Output voltage $V_0 = V_m \sin \omega t = V_s = V_c$
- Diode voltage $V_D = V_m (\sin \omega t - 1)$
- Output current $I_0 = \omega c V_m \cos \omega t$
- Average value of diode voltage $V_D = V_m$
- RMS value of diode voltage

$$V_{\text{rms } D} = 1.225 V_m$$

Single-Phase Full wave Mid-point Diode Rectifier:

Average output voltage,

$$V_0 = \frac{1}{\pi} \int_0^\pi V_m \sin \omega t d(\omega t)$$

$$V_0 = \frac{2V_m}{\pi}$$

Average output current,

$$i_0 = \frac{V_0}{\pi}$$

Rms value of load voltage,

Rajasthan RVUNL

A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

$$V_{0(rms)} = \sqrt{\left[\frac{1}{2} \int_0^\pi V_m^2 \sin^2 \omega t \, d(\omega t) \right]}$$

$$V_{0(rms)} = \frac{V_m}{\sqrt{2}} = V_s$$

Rms value of load current,

$$I_{0(rms)} = \frac{V_s}{R}$$

Power delivered to load = $V_{0(rms)} I_{0(rms)}$

$$\therefore \text{Input power factor} = \frac{V_{0(rms)} I_{0(rms)}}{V_s I_{0(rms)}}$$

Single-Phase Full wave Diode Bridge Rectifier:

Average value of diode current,

$$I_D = \frac{1}{2\pi} \int_0^\pi I_m \sin \omega t \, d(\omega t) = \frac{I_m}{\pi}$$

Rms value of diode current,

$$I_{D(rms)} = \sqrt{\left[\frac{1}{2\pi} \int_0^\pi I_m^2 \sin^2 \omega t \, d(\omega t) \right]}$$

$$I_{D(rms)} = \frac{I_m}{2}$$

Single phase half wave-controlled rectifier with R Load

Average output voltage,

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

Average output current,

$$I_o = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

Rms value of output voltage,

$$V_{or} = \frac{V_m}{2\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

Commutation time or turn off time of the thyristor,

$$t_c = \frac{\pi}{\omega} \text{ sec}$$

Input power factor of the converter,

$$p.f. = \frac{V_{or} \cdot I_{or}}{V_s \cdot I_{or}} = \frac{1}{\sqrt{2\pi}} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

Rajasthan RVUNL

A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

Single phase half wave-controlled rectifier with RL load:

Average output voltage,

$$V_0 = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

Average output current,

$$I_0 = \frac{V_m}{2\pi R} (\cos \alpha - \cos \beta)$$

Rms value of output voltage.

$$V_{or} = \frac{V_m}{2\sqrt{\pi}} \left[(\beta - \alpha) - \frac{1}{2} (\sin 2\beta - \sin 2\alpha) \right]^{\frac{1}{2}}$$

Commutation time or turn off time for the thyristor,

$$t_c = \frac{2\pi - \beta}{\omega} \text{ sec}$$

Single phase half wave-controlled rectifier with RLE load:

The minimum value of firing angle at which thyristor can be triggered is

$$\theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right)$$

Average output current,

$$I_0 = \frac{1}{2\pi R} [V_m (\cos \alpha - \cos(\gamma + a)) - E\gamma]$$

Average output voltage,

$$V_0 = \frac{1}{2\pi} [V_m (\cos \alpha - \cos \beta) + E(2\pi + \alpha - \beta)]$$

Input power factor,

$$p.f. = \frac{(I_{or}^2 R + EI_0)}{V_s I_{or}}$$

Commutation time or turn off time of thyristor,

$$t_c = \frac{2\pi - \beta}{\omega} \text{ sec}$$

Three Phase Half Wave Diode Rectifier:

The peak inverse voltage (PIV) = $\sqrt{3} V_{mp}$ for each of the three diode D₁, D₂ and D₃. The average output voltage.

Rajasthan RVUNL

A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

$$\begin{aligned}
 V_0 &= \frac{1}{2\pi/3} \int_{\pi/6}^{5\pi/6} V_{mp} \sin \omega t \, d(\omega t) \\
 &= \frac{3\sqrt{3}}{2\pi} V_{mp} \\
 &= \frac{3\sqrt{6}}{2\pi} V_{ph} \quad (\because V_{mp} = \sqrt{2} V_{ph}) \\
 &= \frac{3}{2\pi} V_{ml} \quad (\because V_{ml} = \sqrt{3} V_{mp} = \sqrt{6} V_{ph})
 \end{aligned}$$

Rms value of output voltage,

$$V_{0(rms)} = \sqrt{\left[\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_{mp}^2 \sin^2 \omega t \, d(\omega t) \right]}$$

$$V_{0(rms)} = 0.84068 V_{mp}$$

Three-Phase Mid-point 6-Pulse Diode Rectifier:

Average output voltage,

$$V_0 = \frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} V_{mp} \sin \omega t \, d(\omega t)$$

$$V_0 = \frac{3V_{mp}}{\pi}$$

Rms value of output voltage,

$$V_{0(rms)} = \sqrt{\left[\frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} (V_{mp} \sin \omega t)^2 \, d(\omega t) \right]}$$

$$V_{0(rms)} = 0.9558 V_{mp}$$

THREE PHASE DIODE BRIDGE RECTIFIER

Average Value of load voltage,

$$V_0 = \frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} V_{ml} \sin \omega t \, (d\omega t)$$

$$V_0 = \frac{3V_{ml}}{\pi}$$

Rms value of output voltage,

$$V_{0(rms)} = \sqrt{\left[\frac{1}{\pi/3} \int_{\pi/3}^{2\pi/3} V_{ml}^2 \sin^2 \omega t \, d(\omega t) \right]}$$

$$V_{0(rms)} = 0.9558 V_{ml}$$

THREE PHASE HALF-WAVE-CONTROLLED RECTIFIER:

If V_{mp} is the peak value of phase voltage, the average value of the output voltage,

Rajasthan RVUNL

A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

$$V_o = \begin{cases} \frac{3\sqrt{3}}{2\pi} V_{mp} \cos \alpha & ; \text{for } 0 < \alpha < 30^\circ \\ \frac{3}{2\pi} V_{mp} (1 + \cos(\alpha + 30^\circ)) & ; \text{for } 30^\circ < \alpha < 150^\circ \end{cases}$$

If V_{ml} is the peak value of line voltage, average output voltage,

$$V_o = \frac{3V_{ml}}{\pi} \cos \alpha$$

If I_0 is the load current, average value of source current,

$$I_s = I_0 \sqrt{\frac{2}{3}}$$

Average value of thyristor current,

$$I_s = I_0 \sqrt{\frac{1}{3}}$$

EFFECT OF SOURCE INDUCTANCE IN SINGLE PHASE RECTIFIER

1. It reduces the average output voltage.
2. It limits the maximum firing angle,

$$\alpha_{\max} = 180^\circ - (\omega t_q + \mu_0)$$

where, ωt_q = device turn-off time (in degrees)

μ_0 = overlap angle at $\alpha = 0$

3. Displacement angle, $\theta_1 = -(\alpha + \mu/2)$
4. Fundamental displacement factor,

$$\text{Fundamental Displacement Factor} = \cos\left(\alpha + \frac{\mu}{2}\right)$$

5. Current distortion factor (g) increase because the waveform is smoother than without L_s waveform

$$\text{Total Harmonic Distortion} = \left(\frac{1}{g^2} - 1\right)^{1/2}$$

6. Power factor (F.F.) = current distortion factor x fundamental displacement factor

7. Average reduction voltage = $\frac{V_m}{2\pi} [\cos \alpha - \cos(\alpha + \mu)] = \frac{\omega L_s}{2\pi} I_0$

DC DRIVES

$$E_a = \frac{Z\phi NP}{60A} = Z\phi n \left(\frac{P}{A}\right) \quad \omega_m = 2\pi n$$

$$E_a = Z\phi \left(\frac{\omega_m}{2\pi}\right) \left(\frac{P}{A}\right) = \left(\frac{Z}{2\pi} \cdot \frac{P}{A}\right) \phi \omega_m \quad \Rightarrow \boxed{E_a = K_a \phi \omega_m}$$

Where, $K_a = \frac{Z}{2\pi} \left(\frac{P}{A} \right)$

$E_a I_a$ (Electrical power) = $T_e \omega_m$ (Mechanical power)

$$T_e = \frac{E_a I_a}{\omega_m} \Rightarrow T_e = K_a \phi I_a$$

Buck Converter:

In Buck regulator, the average output voltage V_0 is less than the input voltage V_s .

$$\Delta I = \frac{(V_s - V_0) T_{ON}}{L}$$

$$\Delta I = \frac{V_0 T_{OFF}}{L} \quad V_0 = V_s \frac{T_{ON}}{T} = V_s \alpha$$

Where $\Delta I = I_2 - I_1$ is the peak to peak current ripple of the inductor L.

The peak to peak ripple current is $\Delta I = \frac{V_s \alpha (1 - \alpha)}{fL}$

The peak to ripple voltage of the capacitor is $\Delta V_C = \frac{V_s \alpha (1 - \alpha)}{8LCf^2}$

Condition for continuous inductor current and capacitor voltage:

If I_L is average inductor current, the inductor ripple current $\Delta I = 2I_L$, which gives the critical

value of the inductor L_c as $L_c = L = \frac{(1 - \alpha)R}{2f}$

If V_C is the average capacitor voltage, the capacitor ripple voltage $\Delta V_C = 2V_0$, which gives

the critical value of capacitor C_c as $C_c = C = \frac{1 - \alpha}{16Lf^2}$

Boost Converter:

$$\Delta I = \frac{V_s T_{ON}}{L} = \frac{(V_0 - V_s) T_{OFF}}{L}$$

where $\Delta I = I_2 - I_1$ is peak to peak ripple current of the inductor L.

The average output voltage,

$$V_0 = V_s \frac{T}{T_{OFF}} = \left(\frac{1}{1 - \alpha} \right) V_s$$

The peak to peak current ripple is, $\Delta I = \frac{V_s \alpha}{fL}$

The peak to peak ripple voltage of capacitor, $\Delta V_C = \frac{I_0 \alpha}{fC}$

Condition of continuous inductor current and capacitor voltage:

Rajasthan RVUNL

A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

If V_c is the average capacitor voltage, the capacitor ripple voltage $\Delta V_c = 2V_0$, which gives the critical value of the capacitor C_c as $C_c = \frac{\alpha}{2fR}$

Buck Boost Converter:

$$\Delta I = \frac{V_s T_{ON}}{L} = \frac{-V_0 T_{OFF}}{L}$$

where $\Delta I = I_2 - I_1$ is the peak to peak ripple current of inductor L.

The average output voltage is, $V_0 = -\frac{V_s \alpha}{1 - \alpha}$

The peak to peak current ripple is, $\Delta I = \frac{V_s \alpha}{fL}$

peak to peak ripple voltage of the capacitor is, $\Delta V_c = \frac{I_0 \alpha}{fC}$

Condition of continuous inductor current and capacitor voltage:

If V_c is the average capacitor voltage, the capacitor ripple voltage, $\Delta V_c = 2V_0$, which gives the critical value of the capacitor C_c as $C_c = \frac{\alpha}{2fR}$.

Inverters

Series Inverters: In a series inverter, the commutating elements L and C are connected in series with the load resistance R. The load resistance R can also be in parallel with C. The value of L and C are such that those form an underdamped circuit i.e.

$$R^2 < \frac{4L}{C}$$

$$f = \left[\frac{1}{2 \left(\frac{T}{2} + T_{off} \right)} \right]$$

The frequency of output voltage.

Where, $\frac{T}{2}$ is the time period of oscillations.

T_{off} is the time gap between turn-off one thyristor and turn-on of the second thyristor.

$$\frac{T}{2} = \frac{\pi}{\sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2} \right)}}$$

The period of oscillation

Rajasthan RVUNL
A Technical Course for AEN & JEN (Electrical) START FREE TRIAL

Parallel Inverter: During the working of this inverter, capacitor C comes in parallel with the load

$$V_c = 2V_s \left[2 \exp\left(-\frac{n^2 r}{2RC}\right) - 1 \right]$$

Where, $n = \frac{N_2}{N_1}$ (turns ratio)

$$C = \frac{n^2 \cdot t_c}{4R \ln 2}$$

Commutating capacitance,

Where, t_c = Circuit turn-off time

Bridge Inverter: Bridge circuits are commonly used in DC-AC conversion. Moreover, an output transformer is not essential in a bridge circuit.

1φ Half Bridge Inverter - The output voltage volt $V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin n\omega t$

1φ Full Bridge Inverter- The output voltage

$$V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t$$

Where, n = order of harmonic

$\omega = 2\pi f$, is frequency of the output voltage in rad/sec

Key points:

- The load impedance (Z_n) at frequency

$$n_f, Z_n = \left[R^2 + \left(n\omega L - \frac{1}{n\omega C} \right)^2 \right]^{-1/2}$$

- Phase angle, (ϕ_n), $\phi_n = \tan^{-1} \frac{\left[n\omega L - \frac{1}{n\omega C} \right]}{R}$ rad

- Output current or load current at the instant of commutation $I_0 = I_o = \frac{V_0}{Z_n}$ or $\omega t = \pi$ rad

- Fundamental load power

$$(P_{01}) P_{01} = I_{01}^2 R = V_{01} \cdot I_{01} \cos \phi_1$$

Amplitude Modulation Depth:

$$m_0 = \frac{\hat{V}_m}{\hat{V}_c}$$

Where V_m, V_c are the modulating and carrier signal voltage, respectively.

For sinusoidal PWM, the amplitude modulation depth must be less than 1.0

Output Voltages:

Rajasthan RVUNL

A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

$$\hat{V}_{kg1} = m_a \frac{V_{DC}}{2}$$

$$V_{kg1} = \frac{1}{2\sqrt{2}} m_a V_{DC}$$

the fundamental line-line voltage is given by

$$V_{LL0_1} = \frac{\sqrt{3}}{2\sqrt{2}} m_a V_{DC}$$

Available output voltage:

Assuming that the DC voltage is created using a diode rectifier and capacitor dc link, the maximum available DC voltage is given by

$$V_{DC} = \sqrt{2} V_{LL_s}$$

where V_{LL_s} is the line-line supply voltage. The maximum output using sinusoidal PWM ($m_a=1$) is

$$V_{LL0_1} = \frac{\sqrt{3}}{2\sqrt{2}} \sqrt{2} V_{LL_s} = \frac{\sqrt{3}}{2} V_{LL_s}$$

Resistive Load:

$$I(t) = \frac{V_s}{R}$$

where, $V_s = DV$ voltage source

$R =$ Load resistance

R-C (Resistive-Capacitive Load):

$$I(t) = \frac{V_s}{R} e^{-t/RC}$$

$$V_c(t) = V_s(1 - e^{-t/\tau})$$

Where, $V_c(t) =$ Voltage across capacitor at time t

Where, $V_c(t) =$ Voltage across capacitor at time t

Initial rate of rise of capacitor voltage:

$$\left(\frac{dV_c}{dt}\right)_{t=0} = \frac{V_s}{RC} = \frac{V_s}{\tau} \text{ and time constant } \tau = \frac{V_s}{\left(\frac{dV_c}{dt}\right)_{t=0}}$$

R-L Load:

$$I(t) = \frac{V_s}{R} (1 - e^{-Rt/L})$$

$$V_L = V_s e^{-Rt/L}; V_L = \text{Voltage across inductor}$$

$$\text{Initial rate of rise of current } \left(\frac{dI}{dt}\right)_{t=0} = \frac{V_s}{L}$$

L-C Load:

Rajasthan RVUNL
A Technical Course for AEN & JEN (Electrical)

START FREE TRIAL

$$I(t) = I_p \sin \omega_0 t$$

Where, $I_p = V_s \sqrt{\frac{C}{L}}$ and

$$\omega_0 = \frac{1}{\sqrt{LC}} = \text{resonant frequency}$$

$$\Rightarrow I(t) = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t$$

Key Points

- Voltage across inductor, $V_L = V_s (\cos \omega_0 t)$
- Voltage across capacitor, $V_C = V_s (1 - \cos \omega_0 t)$

$$t_1 = \pi \sqrt{LC} = \frac{\pi}{\omega_0}$$

- Conduction time,

R-L-Load:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Damping factor, $\xi = \frac{R}{2L}$

Resonant frequency $\omega_0 = \frac{1}{\sqrt{LC}}$ rad/s

Ringing frequency,

(or damped resonant frequency)

$$\omega_d = \sqrt{\omega_0^2 - \xi^2}$$
