

# ESE 2021 (Paper-2)






Electronics &  
Telecommunication Engineering

**18th July**

**SET-C**

Questions & Answer Key

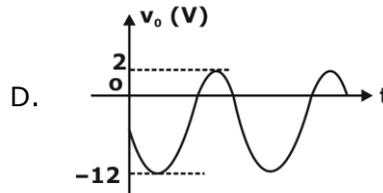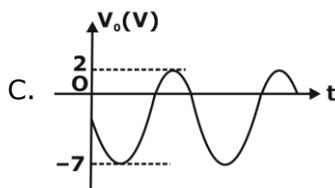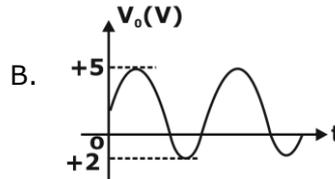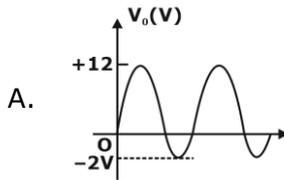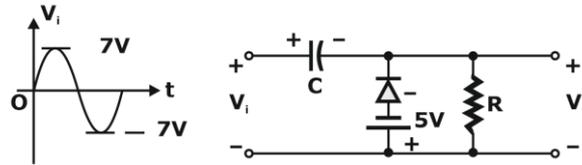1. A sinusoidal input is given to the network below. The output waveform is



Ans. A

2. For enhancement-type n-channel MOSFET with drain current  $I_D = 10\text{mA}$ ,  $V_{GS} = 8\text{V}$  and  $V_T = 2\text{V}$ , the device constant  $k$  is

- A.  $0.139\text{ mA/V}^2$
- B.  $0.278\text{ mA/V}^2$
- C.  $0.387\text{ mA/V}^2$
- D.  $0.556\text{ mA/V}^2$

Ans. B

3. Which one of the following statement is correct regarding shunt-series feedback amplifier topology?

- A. The currents are compared and the output voltages are sampled.
- B. The currents are compared and the output currents are sampled.
- C. The voltages are compared and the output currents are sampled.
- D. The voltages are compared and the output voltages are sampled.

Ans. B

4. A Hartley oscillator uses  $L_1 = 2\text{ mH}$  and  $L_2 = 1.5\text{ mH}$ . The range of capacitance so that the frequency of oscillation can be varied between  $1000\text{kHz}$  are

- A.  $C_{\text{max}} = 7.2\text{ pF}$  and  $C_{\text{min}} = 1.8\text{ pF}$
- B.  $C_{\text{max}} = 9.2\text{ pF}$  and  $C_{\text{min}} = 0.8\text{ pF}$
- C.  $C_{\text{max}} = 7.2\text{ pF}$  and  $C_{\text{min}} = 0.8\text{ pF}$
- D.  $C_{\text{max}} = 9.2\text{ pF}$  and  $C_{\text{min}} = 1.8\text{ pF}$

Ans. A

5. Which one of the following statements is correct regarding integrated circuit fabrication?
- A. IC offers increased reliability, improved performance, high speed and lower power consumption.
  - B. IC is a miniature, low cost electronic circuit fabricated on a multi crystal chip of silicon.
  - C. IC is a miniature, high cost electronic circuit fabricated on a multi crystal chip of silicon.
  - D. IC offers decreased reliability, improved performance, low speed and higher power consumption.

Ans. A


6. What is the value of capacitor of the wien bridge oscillator at resonant frequency of 10 kHz with resistance of 100 kΩ?
- A. 149 pF
  - B. 159 pF
  - C. 169 pF
  - D. 189 pF

Ans. B

7. A monolithic metal oxide semiconductor (MOS) non-polarized capacitor which is a parallel plate capacitor with SiO<sub>2</sub> as dielectric. A surface thin film of metal (aluminium) is the top plate. The bottom plate consists of the heavily doped n<sup>+</sup> region that is formed during emitter diffusion. What is the typical value of capacitance for an oxide thickness of 500 Å of this MOS capacitor?
- A. 0.1 pF/mil<sup>2</sup>
  - B. 0.2 pF/mil<sup>2</sup>
  - C. 0.3 pF/mil<sup>2</sup>
  - D. 0.4 pF/mil<sup>2</sup>

Ans. D

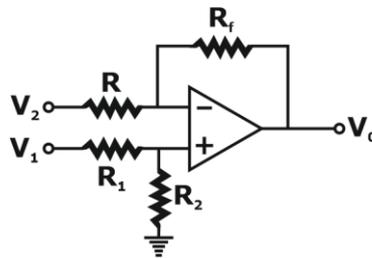8. For the given figure, the output voltage is



- A.  $v_0 = -\frac{R_f}{R} V_2 + \left(\frac{R+R_f}{R_1+R_2} V_1\right)$
- B.  $V_0 = -\frac{R}{R_f} V_2 + \left(\frac{R+R_f}{R_f}\right) \left(\frac{R+R_f}{R_1+R_2} V_1\right)$
- C.  $V_0 = -\frac{R_f}{R} V_2 + \left(\frac{R+R_f}{R_f}\right) \left(\frac{R_1+R_2}{R+R_f} V_1\right)$
- D.  $V_0 = -\frac{R_f}{R} V_2 + \left(\frac{R+R_f}{R}\right) \left(\frac{R_2}{R_1+R_2} V_1\right)$

Ans. D

# Vision 2023

Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

9. In a BJT switching circuit, supply voltage is  $V_{CC} = 9\text{ V}$ , biasing resistors are  $R_B = 15\text{ k}\Omega$ ,  $R_C = 6.8\text{ k}\Omega$  and the transistor has an  $h_{FE}$  value of 25. What is the minimum input voltage required to switch the transistor into saturation when  $V_{CE} = 0.2\text{ V}$ ?
- A. 1.48 V
  - B. 0.78 V
  - C. 5 V
  - D. 2.8 V

Ans. A

**Directions:** Each of the next six, (06) items consist of two statements, one labelled as 'Statement (I)' and the other labelled as 'Statement (II)'. You are to examine these two statement carefully and select the answer to these items using the codes given below:

**Codes:**

- A. Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I).
  - B. Both Statement (I) and Statement (II) are individually true, but Statement (II) is not the correct explanation of Statement (I).
  - C. Statement (I) is true, but Statement (II) is false.
  - D. Statement (I) is false, but Statement (II) is true.
10. Statement (I): Ge and Si are said to have negative temperature coefficient of resistivity. Statement (II): Ge and Si shown a reduction in resistance with increase in temperature.

**Codes:**

- A. Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I).
- B. Both Statement (I) and Statement (II) are individually true, but Statement (II) is not the correct explanation of Statement (I).
- C. Statement (I) is true, but Statement (II) is false.
- D. Statement (I) is false, but Statement (II) is true.

Ans. A

11. Statement (I): A linear network which contains two or more independent sources can be analyzed to obtain the various voltages and branch currents by allowing the sources to act one at a time, then superposing the results. Statement (II): Superposition cannot be directly applied to the computation of the power.

**Codes:**

- A. Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I).
- B. Both Statement (I) and Statement (II) are individually true, but Statement (II) is not the correct explanation of Statement (I).
- C. Statement (I) is true, but Statement (II) is false.
- D. Statement (I) is false, but Statement (II) is true.

Ans. B

12. Statement (I): Metals are extremely good conductors of electricity and heat, and are not transparent to visible light.

Statement (II): Ceramics are compounds between metallic and non-metallic elements.

**Codes:**

- A. Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I).
- B. Both Statement (I) and Statement (II) are individually true, but Statement (II) is not the correct explanation of Statement (I).
- C. Statement (I) is true, but Statement (II) is false.
- D. Statement (I) is false, but Statement (II) is true.

Ans. B

13. Statement (I): M-ary PSK can be used to transmit digital data over a non-linear bandpass channel, whereas M-ary QAM requires the use of a linear channel.

Statement (II): M-ary PSK and M-ary QAM are examples of non-linear modulation.

**Codes:**

- A. Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I).
- B. Both Statement (I) and Statement (II) are individually true, but Statement (II) is not the correct explanation of Statement (I).
- C. Statement (I) is true, but Statement (II) is false.
- D. Statement (I) is false, but Statement (II) is true.

Ans. C

14. Statement (I): Linear system may have multiple equilibrium states.

Statement (II): If a system is BIBO stable, it must also be zero-input or asymptotically stable.

**Codes:**

- A. Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I).
- B. Both Statement (I) and Statement (II) are individually true, but Statement (II) is not the correct explanation of Statement (I).
- C. Statement (I) is true, but Statement (II) is false.
- D. Statement (I) is false, but Statement (II) is true.

Ans. D

15. Statement (I): The total flux out of a closed surface is equal to the net charge enclosed within the surface.

Statement (II): An electric field is completely specified by intensity vector.

**Codes:**

- A. Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I).
- B. Both Statement (I) and Statement (II) are individually true, but Statement (II) is not the correct explanation of Statement (I).
- C. Statement (I) is true, but Statement (II) is false.
- D. Statement (I) is false, but Statement (II) is true.

Ans. B

16. A current of 5 A in primary coil of a circuit is reduced to zero at a uniform rate in  $10^{-3}$  seconds. If coefficient of mutual inductance is 2 H, then the induced emf in the secondary coil is

- A.  $10^{-4}$  V
- B.  $10^4$  V
- C.  $10^{-6}$  V
- D.  $10^6$  V

Ans. B

17. A wire of resistor  $10 \Omega$  is drawn out so that its length is increased to twice its original length.

Then the new resistance is

- A.  $20 \Omega$
- B.  $5 \Omega$
- C.  $30 \Omega$
- D.  $40 \Omega$

Ans. D

18. What is the magnitude of emf induced in a 200 turn coil with cross-sectional area of  $0.16 \text{ m}^2$ , if the magnetic field through the coil changes from  $0.10 \text{ Wh/m}^2$  to  $0.50 \text{ Wh/m}^2$  at a uniform rate over a period of 0.02 seconds?

- A.  $-520 \text{ V}$
- B.  $-640 \text{ V}$
- C.  $-725 \text{ V}$
- D.  $-815 \text{ V}$

Ans. B

19. In an AC circuit, the voltage source  $V$  is the follows :  $V = 100 \sin (100t)$  volt. The rms value of voltage is

- A.  $35.35 \text{ V}$
- B.  $40.35 \text{ V}$
- C.  $80.7 \text{ V}$
- D.  $70.7 \text{ V}$

Ans. D

20. Which one of the following statements is not correct regarding the characteristics of ideal transformer?

- A. There is no leakage flux.
- B. There are no losses in electric circuit or in magnetic circuit.
- C. The resistance of both the windings is infinite.
- D. The permeability of the core is infinite and zero reluctance.


Ans. C

21. Which one of the following is not the indication of a fully-charged cell?

- A. Intensity
- B. Gassing
- C. Voltage
- D. Specific gravity of the electrolyte

Ans. A

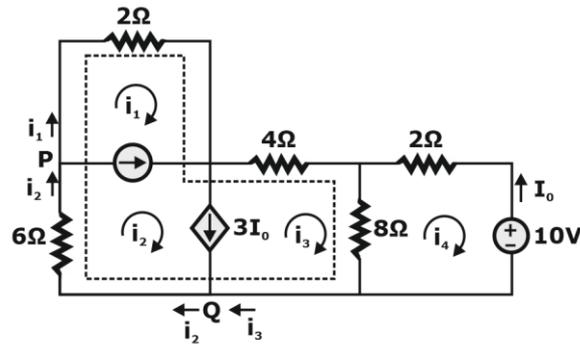
22. For the given circuit, the currents  $i_1$  and  $i_3$  are



- A.  $i_1 = 2.5 \text{ A}$  and  $i_3 = 3.93 \text{ A}$
- B.  $i_1 = 7.5 \text{ A}$  and  $i_3 = 2.5 \text{ A}$
- C.  $i_1 = 3.93 \text{ A}$  and  $i_3 = 2.14 \text{ A}$
- D.  $i_1 = 7.5 \text{ A}$  and  $i_3 = 3.93 \text{ A}$

Ans. D

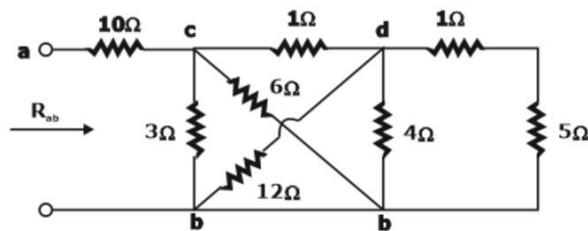23. What is the equivalent resistance  $R_{ab}$  in the given circuit?



- A.  $34.08 \Omega$
- B.  $11.20 \Omega$
- C.  $42.16 \Omega$
- D.  $17.82 \Omega$

Ans. B

24. Consider the following statements for inductors:

1. An inductor acts like a short circuit to DC.
2. The current through an inductor cannot change instantaneously.
3. The current through an inductor can change instantaneously.
4. An inductor acts like an open circuit to DC

Which of the above statements is/are correct?

- A. 1 only
- B. 1 and 2 only
- C. 2 only
- D. 3 and 4 only

Ans. B

25. What is the phase angle between

$$i_1 = -4 \sin (377t + 25^\circ) \text{ and}$$

$$i_2 = 5 \cos (377t - 40^\circ)?$$

- A.  $155^\circ$ , ( $i_1$  leads  $i_2$ )
- B.  $145^\circ$ , ( $i_2$  leads  $i_1$ )
- C.  $135^\circ$ , ( $i_1$  leads  $i_2$ )
- D.  $125^\circ$ , ( $i_2$  leads  $i_1$ )

Ans. A

26. Which one of the following laws states that the line integral of the tangential component of H around a closed path is the same as the net current  $I_{enc}$  enclosed by the path?

- A. Biot-Savart's law
- B. Lenz's law
- C. Gauss's law
- D. Ampere's circuit law

Ans. D

27. Consider the following statements regarding an ideal transformer:

1. Coils have very large reactances.
  2. Coupling coefficient is equal to unity.
  3. Primary and secondary coils are not
- Which of the above statements is/are correct?

- A. 2 only
- B. 1 and 2 only
- C. 2 and 3 only
- D. 1 only

Ans. B

28. The total efficiency of an injection laser with a GaAs active region is 18%. The voltage applied to the device is 2.5 V and the bandgap energy for GaAs is 1.43 eV. The external power efficiency of the device is

- A. 5%
- B. 10%
- C. 15%
- D. 20%

Ans. B

29. The slope of the output characteristics of a transistor in CE configuration is higher than that in CB configuration due to which one of the following effects?
- A. Zener effect
  - B. Early effect
  - C. Avalanche effect
  - D. Transistor effect

Ans. B

30. Which one of the following statements is correct regarding the comparison between Avalanche and Zener effect?
- A. Zener effect is caused by impact ionization.
  - B. Zener diodes have higher resistance.
  - C. Avalanche effect occurs at voltages usually above 7 V.
  - D. Avalanche diodes have lower resistance.

Ans. C

31. Current was measured during a test as if 30.4 A, flowing in a resistor of  $0.105 \Omega$ . It was discovered later that the ammeter reading was low by 1.2 percent and the marked resistance was high by 0.3 percent. What is the true power as percentage of the power that was originally calculated?
- A. 118.4%
  - B. 109.7%
  - C. 102.1%
  - D. 104.8%

Ans. C

32. The LVDT is used in an accelerometer to measure seismic mass displacements. The LVDT and signal conditioning outputs are  $0.31 \text{ mV/mm}$  with a  $\pm 20 \text{ mm}$  core displacement. The spring constant is  $240 \text{ N/m}$  and the core mass is  $0.05 \text{ kg}$ . The natural frequency and maximum measurable acceleration are respectively,
- A.  $69.3 \text{ rad/s}$  and  $69.3 \text{ m/s}^2$
  - B.  $69.3 \text{ rad/s}$  and  $96 \text{ m/s}^2$
  - C.  $15.59 \text{ rad/s}$  and  $96 \text{ m/s}^2$
  - D.  $15.59 \text{ rad/s}$  and  $31.18 \text{ m/s}^2$

Ans. B



38. Which one of the following does not come under the category of ceramic material?

- A.  $\text{Al}_2\text{O}_3$
- B.  $\text{SiO}_2$
- C.  $\text{Si}_2\text{N}_4$
- D.  $\text{SiC}$

Ans. C

39. Consider the following statements corrosion of ceramic material:

1. Ceramic materials are much better suited to withstand most of these environments for reasonable time periods than are metals.
  2. Corrosion of ceramic materials generally involves simple chemical dissolution, in contrast to the electrochemical processes found in metals.
  3. Ceramic materials are not frequently used because of their non-resistance to corrosion
- Which of the above statements is/are correct?

- A. 1 and 3 only
- B. 2 and 3 only
- C. 3 only
- D. 1 and 2 only

Ans. D

40. For a ferromagnetic material, which one of the following relationships is correct between magnetic flux density and magnetization

- A.  $B \cong 2\mu_0 M$
- B.  $B \cong \mu_0 M$
- C.  $B \cong \frac{\mu_0 M}{2}$
- D.  $B \cong \frac{\mu_0}{M}$

Ans. B

41. Which of the following statement is not correct regarding ferrites?

- A. Ferrites, with large magnetostrictive effects, are used in electromechanical transducers.
- B. Ferrites have very high resistivity.
- C. Hard magnetic ferrites are used for the manufacture of light weight permanent magnets.
- D. Soft magnetic materials can be used for making permanent magnets.

Ans. D

42. Which one of the following materials displays the behavior of antiferromagnetic?
- A. Manganese oxide
  - B. Iron
  - C. Nickel
  - D. Cobalt

Ans. A

43. Consider the following statement for superconductivity:
1. Superconducting magnets capable of generating high fields with low power consumption are currently being employed in scientific test and research equipment.
  2. One of the potential applications of superconducting materials is electrical power transmission through superconducting materials — power losses would be extremely low, and the equipment would operate at low voltage levels.
  3. Type II superconductors are preferred over type I for most practical applications by virtue of their higher critical temperatures and critical magnetic fields?

Which of the above statement is/are correct?

- A. 1 only
- B. 2 and 3 only
- C. 3 only
- D. 1, 2 and 3

Ans. D

44. Which one of the following statement is not correct regarding the features of ceramics?
- A. Ceramics are hard, strong and dense.
  - B. Ceramics are stronger in compression than in tension.
  - C. Ceramics have very poor dielectric properties.
  - D. Ceramics are weak in impact strength.

Ans. C

45. What is the packing efficiency of diamond?
- A. 0.17
  - B. 0.34
  - C. 0.24
  - D. 0.48

Ans. B

46. Which one of the following has all the poles of the function lie on the  $j\omega$  axis?
- A. L-C function
  - B. R-L function
  - C. R-C function
  - D. Y function

Ans. A

47. Which one of the following is an LC immittance function?

- A.  $Z(s) = \frac{Ks(s^2+4)}{(s^2+1)(s^2+3)}$
- B.  $Z(s) = \frac{s^5+4s^3+5s}{3s^4+6s^2}$
- C.  $Z(s) = \frac{K(s^2+1)(s^2+9)}{(s^2+2)(s^2+10)}$
- D.  $Z(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+4)}$


Ans. D

48. Which one of the following is not the property of positive real function?

- A. If  $F(s)$  is positive real, then  $\frac{1}{F(s)}$  is not a positive real.
- B. The sum of positive real functions is positive real.
- C. The poles and zeros of a positive real function cannot be in the right half of the  $S$  plane.
- D. Only simple poles with real positive residues can exist on the  $j\omega$  axis.

Ans. A

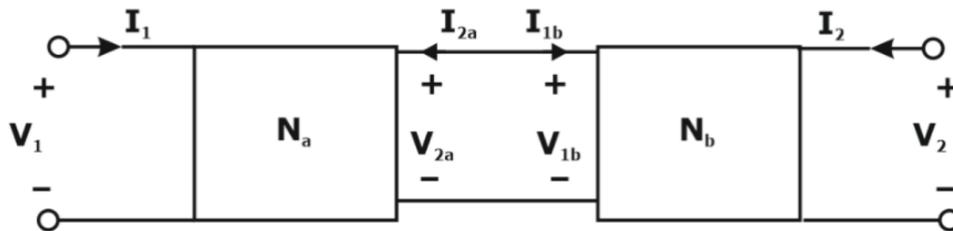49. Which one of the following is the transmission matrix equation for network  $N_a$  if two network  $N_a$  and  $N_b$  are cascaded as shown in the figure?



- A.  $\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} -V_{2a} \\ I_{2a} \end{bmatrix}$
- B.  $\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$
- C.  $\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & -D_a \end{bmatrix} \begin{bmatrix} -V_{2a} \\ I_{2a} \end{bmatrix}$
- D.  $\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ -C_a & -D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$

Ans. B

50. Which one of the following theorems becomes important if the circuit has sources operating at different frequencies?

- A. Norton theorem
- B. Thevenin theorem
- C. Superposition theorem
- D. Maximum power transfer theorem


Ans. C

**Vision 2023**

Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

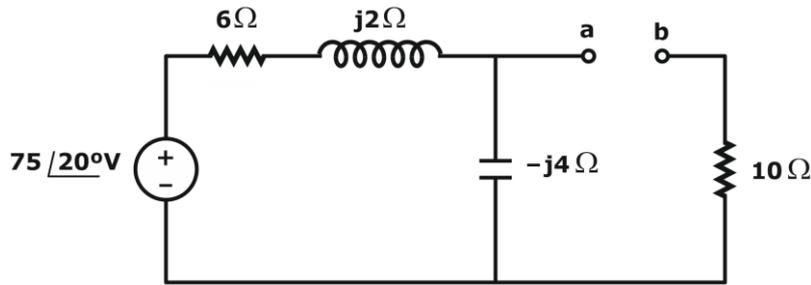51. What is the value of  $Z^{th}$  at terminal a – b of the given Thevenin circuit?



- A.  $Z_{th} = (8 \cdot 4 - j1 \cdot 2)\Omega$
- B.  $Z_{th} = (10 \cdot 3 - j2 \cdot 3)\Omega$
- C.  $Z_{th} = (11 \cdot 3 - j2 \cdot 9)\Omega$
- D.  $Z_{th} = (12 \cdot 4 - j3 \cdot 2)\Omega$

Ans. D

52. Consider the following statements for accuracy of the instrument:

1. The accuracy of the instrument may be specified in terms of limits of error.
2. The specification of a point accuracy given any information about the general accuracy of the instrument.
3. The best way to conceive the idea of accuracy is to specify it in terms of the true value of the quantity being measured.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 2 and 3 only

Ans. B

53. Consider the following statements for deflection and null type instruments:

1. Deflection type of instruments are more accurate than null type of instruments.
2. Deflection type of instruments can be highly sensitive as compared with the null type of instruments.
3. Null type of instruments are more suitable for measurements under dynamic conditions than deflection type of instruments.

Which of the above statements are **not** correct ?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 2 and 3 only

Ans. C

54. A digital timer with eight readout is stated to have accuracy of 0.005 percent of reading,  $\pm 1$  in the final digit. Readout is in s, ms and  $\mu\text{s}$ . Assuming that the instrument meets its specifications, the maximum likely errors when the reading is 05000000  $\mu\text{s}$  is
- A.  $\pm 251 \mu\text{s}$
  - B.  $\pm 260 \mu\text{s}$
  - C.  $\pm 261 \mu\text{s}$
  - D.  $\pm 250 \mu\text{s}$

Ans. D

55. Which one of the following is essentially a permanent magnet moving coil instrument designed to be sensitive to extremely low current levels?
- A. Multimeter
  - B. Galvanometer
  - C. Electrodynamic Wattmeter
  - D. Electrodynamic Voltmeter

Ans. B

56. A strain gauge is bonded to a beam 0.1 m long and has a cross-sectional area 4  $\text{cm}^2$ . Young's modulus for steel is 207  $\text{GN/m}^2$ . The strain gauge has an unstrained resistance of 240  $\Omega$  and a gauge factor of 2.2. When a load is applied, the resistance of gauge changes by 0.013  $\Omega$ . The change in length of the steel beam is
- A.  $1.23 \times 10^{-6} \text{ m}$
  - B.  $2.45 \times 10^{-6} \text{ m}$
  - C.  $4.92 \times 10^{-6} \text{ m}$
  - D.  $9.84 \times 10^{-6} \text{ m}$

Ans. B

57. A digital frequency meter has a time base derived from a 1 MHz clock generator frequency-divided by decade counters. What is the measured frequency when a 1.512 kHz sine wave is applied and the time base uses six decade counters?
- A. 1.512 kHz
  - B. 15.12 kHz
  - C. 1.412 kHz
  - D. 14.12 kHz

Ans. A

58. Which of the following instruments have large scales for easy reading?
- A. Vacuum-tube voltmeter (VTVM) and a FET-input multimeter
  - B. Vacuum-tube voltmeter (VTVM) and an analog electronic ammeter
  - C. FET-input multimeter and an analog electronic ammeter
  - D. FET-input multimeter and an analog electronic voltmeter

Ans. A

59. If a resistor is known to have a resistance of  $500\Omega$  with a possible error of  $\pm 50\Omega$ , the  $\pm 50\Omega$  is
- A. Relative error
  - B. Absolute error
  - C. Gross error
  - D. Systematic error

Ans. B


60. Consider the following statements for dynamic characteristics of a measurement system:
1. Fidelity is defined as the degree to which a measurement system indicates changes in the measured quantity without any dynamic error.
  2. Dynamic error is the difference between the true value of the quantity changing with time and the value indicated by the measurement system if no static error is assumed.
  3. Measuring lag is the retardation in the response of a measurement system to changes in the measured quantity.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 2 and 3 only

Ans. C

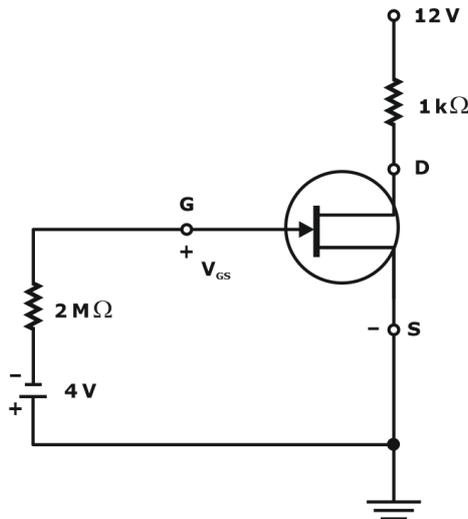61. The circuit given below is the fixed biasing of the n-channel JFET. The pinch-off voltage and the maximum drain-to-source current is  $-8\text{ V}$  and  $10\text{ mA}$  respectively. What are the values of  $V_{GSQ}$  and  $I_{DQ}$ , respectively?



- A.  $+ 4\text{V}$  and  $25\text{ mA}$
- B.  $+ 4\text{V}$  and  $2.5\text{ mA}$
- C.  $- 4\text{V}$  and  $25\text{ mA}$
- D.  $- 4\text{V}$  and  $2.5\text{ mA}$

Ans. D

**Vision 2023**  
Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

62. Consider the following statements regarding JFET:

1. The relationship between the drain current and gate-to-source voltage of a JFET is a nonlinear.
2. The minimum current for JFET occurs at pinch-off voltage defined by  $V_{GS} = V_P$ .
3. A current controlled device is one in which a current defines the operating conditions of the device.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 2 and 3 only

Ans. C

63. What is the maximum closed-loop voltage gain that can be used when the input signal varies by 0.2 V in 10  $\mu$ s with slew rate of op-amp  $SR = 2$  V/ $\mu$ s?

- A. 40
- B. 50
- C. 80
- D. 100

Ans. D

64. Consider the following statements regarding 555 timer:

1. It operates on  $-5$  V to  $+18$  V supply voltage in both free running and one-shot modes.
2. It has a high current output and it can source or sink 500 mA.
3. The output can drive TTL and has a temperature stability of 80 parts per million (ppm) per degree celsius change in temperature of equivalently 0.008%/ $^{\circ}$ C

Which of the above statements are **not** correct ?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 2 and 3 only

Ans. C

65. Consider the following statements for negative feedback:

1. It has more linear operation.
2. It has improved frequency response
3. It has better stabilized voltage gain
4. It has higher output impedance.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 2 and 3 only
- C. 1, 2 and 3 only
- D. 2, 3 and 4 only

Ans. C

66. The simplified form of the function

$$F(A, B, C, D) = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$$

- A.  $\bar{A} \bar{C} \bar{D} + \bar{A} \bar{B} C + AB \bar{C} + A \bar{C} D + BD$
- B.  $\bar{A} \bar{C} \bar{D} + \bar{A} BC + AB \bar{C} + ACD + BD$
- C.  $\bar{A} \bar{C} D + \bar{A} BC + AB \bar{C} + ACD + BD$
- D.  $\bar{A} \bar{C} D + \bar{A} BC + \bar{A} B \bar{C} + ACD$

Ans. C

67. Consider the following statements regarding the Moore and Mealy models:

1. In the Mealy circuit, the final output depends only on the present state of memory elements.
2. In the Moore circuit, output can change in between the clock edges if the external inputs change.
3. The implementation of a logic function in Mealy circuit needs more number of states than Moore circuit.

Which of the above statements are not correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 2 and 3 only

Ans. C

68. In a Johnson's counter, all the negative triggered J-K flip-flops are used. Initially all the flip-flops are in reset condition and the outputs are  $Q_3 Q_2 Q_1 Q_0 = 0000$ . What are the outputs of the flip-flops after the fifth negative going pulse?

- A.  $Q_3 Q_2 Q_1 Q_0 = 0101$
- B.  $Q_3 Q_2 Q_1 Q_0 = 1000$
- C.  $Q_3 Q_2 Q_1 Q_0 = 0010$
- D.  $Q_3 Q_2 Q_1 Q_0 = 1110$

Ans. \*

## OUR STAR FACULTY



**Abhinav Negi**

9+ Years of Experience  
M.Tech. IIT Delhi  
Produced 50+ Students  
under AIR 100 in GATE



**Ankit Sharma**

11+ Years of Experience  
AIR-128, ESE-2011  
Mentored 20,000+ Students



**Md. Ansari**

8+ Years of Experience M.E,  
IISc Bangalore



**Dheeraj Sardana**

10+ Years of Experience  
Mentored 15000+ Students  
Produced AIR 4 & 30+ Rankers  
under AIR 100 in GATE



**Chandra Shekhar**

13+ Years of Experience  
B.Tech, IIT Delhi



**Ashutosh Saxena**

10+ Years of Experience  
M.Tech, IIT BHU  
Sr. Faculty for ESE & GATE



**Ankit Joshi**

15+ Years of Experience  
Produced AIR 1 in  
GATE 2 times  
Produced 50+ Students  
under AIR 100 in GATE



**Sanjay Rathi**

18+ Years of Experience  
ESE AIR 16 & AIR 21  
Produced many top rankers  
under AIR 100



**Rakesh Talreja**

10+ Years of Experience  
M.Tech, IISc Bangalore (AIR-9)



**Chandan Jha**

9+ Years of Experience  
M.Tech, NIT Hamirpur

**BARC 2021**



Boostup Course for EE | EC | ME

**Course Starts from 20th July**



**Enrolment Started!**



**120+**  
of Live Classes



**10+**  
Subject-wise Formula Notes



**60+**  
Quizzes



**7+**  
Mock Tests

### Includes

- > Complete Practice of BARC
- > Formula Revision Notes Pdfs
- > Daily Tests & Weekly Tests for Practice
- > Full-Length Mock Tests

For More Information: **9650052904**

[www.gradeup.co](http://www.gradeup.co)

**Vision 2023**

Course for ESE & GATE Electronics Aspirants

**START FREE TRIAL**


69. Consider the following statements regarding PROM/EPROM:
1. The erasable programmable ROM using ultraviolet erasing is known as EPROM.
  2. The ROM that makes use of the electrical voltage for erasing is known as electrically alterable ROM.
  3. A PROM can be programmed many times after fabrication.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 2 and 3 only

Ans. A

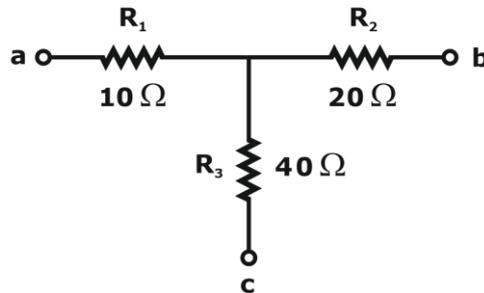
70. What are the values of  $R_a$ ,  $R_b$  and  $R_c$  respectively, after transforming the Wye network shown in the figure to a delta network?



- A.  $140 \Omega$ ,  $70 \Omega$ ,  $45 \Omega$
- B.  $70 \Omega$ ,  $140 \Omega$ ,  $35 \Omega$
- C.  $140 \Omega$ ,  $70 \Omega$ ,  $35 \Omega$
- D.  $40 \Omega$ ,  $70 \Omega$ ,  $25 \Omega$

Ans. B & C

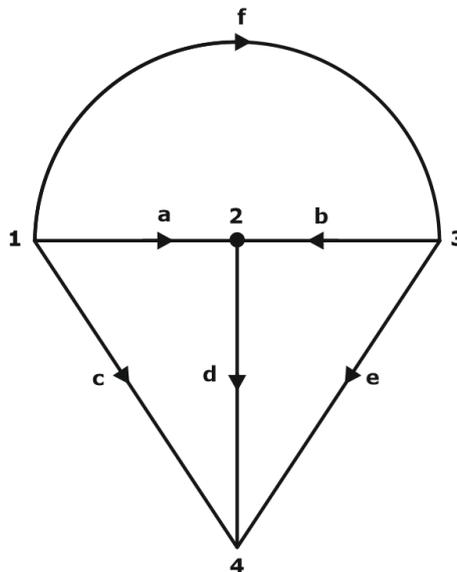71. The number of links in the graph shown in the figure is



- A. 3
- B. 4
- C. 2
- D. 5

Ans. A

72. Which one of the following contains lesser number of nodes than the original graph?
- A. Proper subgraph
  - B. Improper subgraph
  - C. Planar graph
  - D. Non-planar graph

Ans. A


73. Consider the following statements regarding duality:
1. The dual networks are obtained for both AC and DC circuits and they are based on Kirchhoff's laws.
  2. Dual circuits are not obtained in planar networks.
  3. Two networks are said to be dual networks if mesh equations of one network have the same form as the nodal equations of the other.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 2 and 3 only
- D. 1, 2 and 3

Ans. D

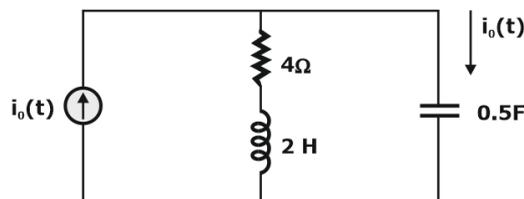74. The current gain  $\frac{I_o(\omega)}{I_i(\omega)}$  for the given circuit is




- A.  $\frac{s(s+2)}{s^2+2s+1}$ , where  $s = j\omega$
- B.  $\frac{s(s+1)}{s^2+s+1}$ , where  $s = j\omega$
- C.  $\frac{s(s+2)}{s^2+2s+2}$ , where  $s = j\omega$
- D.  $\frac{s(s+2)}{s^2+s+2}$ , where  $s = j\omega$

Ans. A

**Vision 2023**  
Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

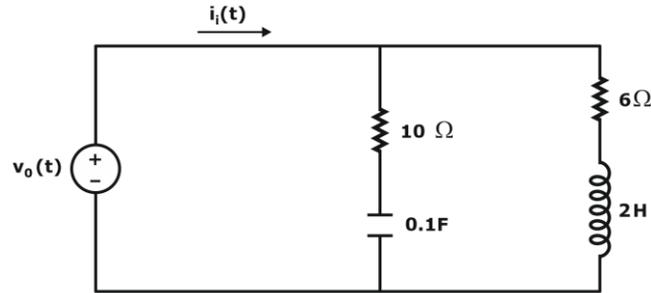75. The poles and zeros of the given circuit are



- A. poles:  $- 0.683$  and  $- 7.317$   
Zeros:  $- 1$  and  $- 3$
- B. poles:  $- 0.483$  and  $- 5.317$   
Zeros:  $- 3$  and  $- 4$
- C. poles:  $- 0.383$  and  $- 4.317$   
Zeros:  $- 2$  and  $- 3$
- D. poles:  $- 0.583$  and  $- 6.317$   
Zeros:  $- 1$  and  $- 4$

Ans. A

76. Which one of the following traffics can adjust, over wide ranges, to changes in delay and throughput across an internet and still meet the needs of its applications?

- A. Elastic traffic
- B. Inelastic traffic
- C. Internet traffic
- D. Service traffic

Ans. A

77. A data message of 10 ms duration having 4800 bits crosses 9 nodes (10 hops) to reach its destination. The data rate and total delay for circuit switched connection (assuming node delays as 1 ms) are respectively,

- A. 240 kbps, 20 ms
- B. 240 kbps, 21 ms
- C. 120 kbps, 21 ms
- D. 480 kbps, 20 ms

Ans. D

78. Consider the following statements regarding the OSI model:

1. Application layer provides the control structure for communication between applications; establishes, manages and terminates connections between cooperating applications.
2. Data link layer provides for the reliable transfer of information across the physical link.
3. Transport layer provides end-to-end error recovery and flow control of data.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 3 and 3 only

Ans. D





88. Express the Boolean function  $F = A + \bar{B}C$  as a sum of minterms?

- A.  $ABC + \bar{A}\bar{B}C$
- B.  $A\bar{B}C + \bar{A}BC + A\bar{B}\bar{C}$
- C.  $ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}C$
- D.  $AB\bar{C} + A\bar{B}C + \bar{A}\bar{B}\bar{C}$

Ans. C

89. Consider the following statements regarding n-channel JFET:


- 1. The maximum drain current  $I_{DSS}$  occurs when gate-to-source voltage  $V_{GS} = 0\text{ V}$  and drain-to-source voltage  $V_{DS} \geq |V_P|$ . ( $V_P$  is pinch-off voltage).
- 2. For gate-to-source voltage  $V_{GS}$  less than the pinch-off level, the drain current is 0 A.
- 3. For all levels of  $V_{GS}$  between 0 V and the pinch-off level, the current  $I_D$  will range between  $I_{DSS}$  and 0 A, respectively.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 3
- D. 2 and 3 only

Ans. B

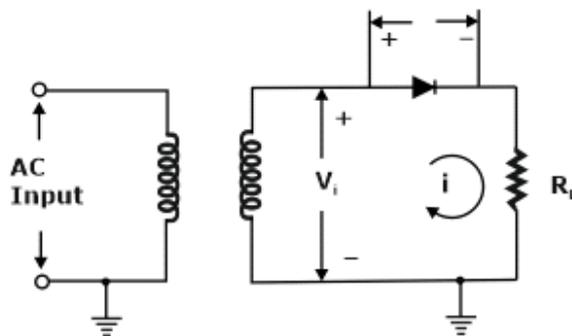90. The circuit given below is a half wave rectifier. The internal resistance of a diode  $R_f$  is  $20\ \Omega$  and load resistance  $R_L$  is  $1\text{ k}\Omega$ . The input AC source with rms voltage is 110 V. What is the DC voltage across the diode?



- A. - 28.54 V
- B. - 38.54 V
- C. - 48.54 V
- D. - 58.54 V

Ans. C



95. Consider the following statements regarding the Read Only Memory (ROM):
1. The stored data is lost if the power is removed.
  2. It consists of an address decoder with  $n$  input lines and a programmable OR array with  $n$  output lines.
  3. The minterms are ORed through the programmable switches which can be made ON or OFF to select a particular minterm. The programmable switches can be implemented by either bipolar, CMOS, nMOS or pMOS technologies.
  4. Mask-programmed ROMs are used in the applications where the system requires data to be stored and to be changed during the operation.

Which of the above statements are **not** correct ?

- A. 1 and 2 only
- B. 1, 3 and 4 only
- C. 1, 2 and 4 only
- D. 2, 3 and 4 only

Ans. C

96. if each core in a 16-core processor has a yield of 90% and nothing else on the chip fails, what is the yield of the chip?

- A.  $(0.9)^8$
- B.  $(0.9)^{16}$
- C.  $(0.1)^8$
- D.  $(0.1)^{16}$

Ans. B

97. What is the simplified value of  $y(n)$ ,

$$y(n) = \sum_{n=-5}^5 \sin(2n)\delta(n+7) ?$$

- A.  $\sin 10$
- B.  $-\sin 10$
- C. 1
- D. 0

Ans. D

98. The energy of the signal  $x(n) = (-0.4)^n u(n)$  is

- A.  $1/16$
- B.  $1/36$
- C.  $5/3$
- D.  $25/4$

Ans. \*

99. Consider the following statements for a system given by

$$y(n) = x(n) \sum_{k=-\infty}^{\infty} \delta(n - 3k)$$

1. The system is linear.
2. The system is non-linear.
3. The system is causal.
4. The system is non-causal.

Which of the above statements is/are correct?

- A. 1 only
- B. 2 only
- C. 2 and 4 only
- D. 1 and 3 only

Ans. D

100. Which one of the following is the zero-input response of the system

$$y[n] - 3y[n - 1] - 4y[n - 2] = 0$$

described by the homogeneous second-order difference equation if  $y[-2] = 0$  and  $y[-1] = 5$ ?

- A.  $y_{zi}(n) = (-1)^{n+1} + (-4)^{n+2}, n \geq 0$
- B.  $y_{zi}(n) = (1)^{n+1} + (4)^{n+2}, n \geq 0$
- C.  $y_{zi}(n) = (-1)^{n+1} + (4)^{n+2}, n \geq 0$
- D.  $y_{zi}(n) = (1)^{n+1} + (-4)^{n+2}, n \geq 0$

Ans. C

101. Consider the following statements regarding Epitaxial Growth:

1. Thin layers are grown on a substrate wafer, this technique is known as epitaxial growth. deposition is also called
2. Physical vapour deposition is also called vapour phase epitaxy.
3. OMCVD is a technique to grow epitaxial layers from metalorganic compounds.
4. High throughput and slow deposition rate are disadvantages of the CVD technique

Which of the above statements are correct.

- A. 2 and 3 only
- B. 1 and 3 only
- C. 1, 2 and 3 only
- D. 1, 3 and 4 only

Ans. D

10+ Gradians Under AIR 10



Sahi Prep Hai Toh Life Set Hai



Hurry up! Enrolment Started for Limited Seats

Enrol Now

Vision GATE 2022 (English)

Course for GATE Exclusive CE | ME | EE | EC | CS

550+ Hrs. of Live Classes

4000+ Practice Questions

30+ Mock Tests

100+ Chapter-wise Study Note

VISION 2022 (Hindi)

Course for ESE, GATE & PSUs CE | ME | EE | EC | CS

850+ Hrs. of Live Classes

8000+ Practice Questions

100+ Mock Tests

100+ Chapter-wise Study Note

VISION 2023 (Hindi/Eng.)

Course for ESE & GATE 2023 CE | ME | EE | EC

950+ Hrs. of Live Classes

8000+ Practice Questions

200+ Mock Tests

120+ Chapter-wise Study Note

To get unlimited access to your preferred courses subscribe to Gradeup Super For More Information: 9650052904

Vision 2023

Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

102. FIR filter having anti-symmetrical impulse response with even filter order can be used to design
- A. low-pass, high-pass, band-pass and band-stop
  - B. low-pass and band-pass only
  - C. high-pass and band-stop only
  - D. differentiator and Hilbert transformer.

Ans. D

103. An HR filter having numerator order M and denominator order N is to be realized using direct form II structure. How much total number of multiplication, additions and memory locations are required respectively?
- A. M+N, M+N and M+N
  - B. M+N, M+N, and maximum of {M+N}
  - C. M+N+1, M+N+1 and M+N
  - D. M+N+1, M+N maximum of { M+M}

Ans. D

104. In 8051, the accumulator register contains 80H and B register contains 8FH. The content of the accumulator and status of the carry flag after the addition operation are respectively.
- A. 0FH, 1
  - B. 10FH,0
  - C. FFH, 1
  - D. 10FH, 1

Ans. A

105. Which one of the following operations is not commutative?
- A. Scaling and reversal of a signal  $x[n]$
  - B. Scaling and folding of a signal  $x[n]$
  - C. Folding and time reversal of a signal  $x[n]$
  - D. Folding and time delaying of a signal  $x[n]$

Ans. D

106. Which one of the following systems provides a mechanism for translating program-generated addresses into correct main memory locations?
- A. Virtual memory system
  - B. Main memory system
  - C. Physical addresses system
  - D. Memory' space system

Ans. A

107. Consider the following statements regarding memory:
1. Integrated circuit RAM chips are available in both static and dynamic modes.
  2. The dynamic RAM stores the binary information in the form of electric charges that are applied to capacitors.
  3. The static RAM is easier to use and has shorter read and write cycles.
  4. RAM and ROM chips are available in a variety of sizes.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1, 3 and 4 only
- C. 2, 3 and 4 only
- D. 1, 2, 3 and 4

Ans. D

108. Which one of the following messaging systems attempts to avoid double copy operations by using virtual-memory management techniques?

- A. Math message system
- B. Duplex message system
- C. Packet message system
- D. Data message system

Ans. B

109. Which one of the following storage devices used is when the operating system abstracts from the physical properties of its storage deviant to define a logical storage unit?

- A. Volatile storage devices
- B. Non-volatile devices
- C. Flash storages
- D. Cache storage device

Ans. B

110. Which one of the following is not correct when we define either a class that does not implement either a mathematical entity like a matrix or a complex number of a low level type such as a linked list?

- A. Don't use global data (use members)
- B. Don't use local functions
- C. Don't use public data members
- D. Don't use inline functions, except as a significant optimization

Ans. \*

111. Which one of the following is also called as pseudo instructions that are not directly translated into machine language instructions?
- A. Macro expansions
  - B. Assembly directives
  - C. Micro expansions
  - D. Labels

Ans. B

112. The components of  $\vec{P} = 2\hat{a}_x - \hat{a}_z$  along  $\vec{Q} = 2\hat{a}_x - \hat{a}_y + 2\hat{a}_z$  is
- A.  $0.745\hat{a}_x + 0.298\hat{a}_y - 0.596\hat{a}_z$
  - B.  $4\hat{a}_x - 2\hat{a}_y + 4\hat{a}_z$
  - C.  $0.2222\hat{a}_x - 0.1111\hat{a}_y + 0.2222\hat{a}_z$
  - D.  $0.4444\hat{a}_x - 0.2222\hat{a}_y + 0.4444\hat{a}_z$

Ans. D

113. Consider the following equations with time factor  $e^{j\omega t}$ :

1.  $\oint \vec{D}_s \cdot d\vec{S} = \int \rho_{vs} dv$
2.  $\oint \vec{E}_s \cdot d\vec{\ell} = -j\omega \oint \vec{B}_s$
3.  $\oint \vec{B}_s \cdot d\vec{S} = 0$
4.  $\oint \vec{H}_s \cdot d\vec{S} = 0 \int (\vec{J}_s + j\omega \vec{D}_s) \cdot d\vec{\ell}$

Which of the above Time-Harmonic Maxwell's equations are correct?

- A. 1 and 2 only
  - B. 1 and 3 only
  - C. 1, 2 and 3 only
  - D. 3 and 4 only
- Ans. C
114. If  $\vec{A} = \rho \cos \phi \hat{a}_\rho + \sin \phi \hat{a}_\phi$ , then the surface integration of curl of  $\vec{A}$  (for  $30^\circ \leq \phi \leq 60^\circ$  and  $2 \leq \rho \leq 5$ ) is
- A. 6.750
  - B. 4.941
  - C. 0.732
  - D. 1.765

Ans. B

115. Which one of the following is not the basic rule for boundary conditions at the surface between two different materials?
- A. The tangential components of electric field intensity are continuous across the boundary.
  - B. The normal components of electric flux density are discontinuous at the boundary by an amount equal to the surface-charge density on the boundary.
  - C. The tangential components of magnetic field intensity are discontinuous at the boundary by an amount equal to the surface-current density on the boundary.
  - D. The normal components of electric field intensity are continuous across the boundary.

Ans. D

116. A uniform plane wave propagating in a medium has

$$\vec{E} = 2e^{-\alpha z} \sin(10^8 t - \beta z) \hat{a}_y \text{ V/m,}$$

If the medium is characterized by  $\epsilon_r = 1$ ,  $\mu_r = 20$  and  $\sigma = 3 \text{ S/m}$ . The values of  $\alpha$  and  $\beta$  are respectively,

- A. 30.70 Np/m, 30.70 rad/m
- B. 61.40 Np/m, 61.40 rad/m
- C. 122.80 Np/m, 122.80 rad/m
- D. 15.35 Np/m, 15.35 rad/m

Ans. B

117. A distortionless transmission line has the following parameters:

Characteristic impedance  $z_0 = 60\Omega$  wave velocity =  $0.6c$ , where  $c$  is the speed of light in a vacuum,  $\alpha = 20 \text{ mNp/m}$ . The values of transmission line parameters  $R$ ,  $L$ ,  $G$  and  $C$  at 100 MHz are respectively,

- A. 1.2  $\Omega/\text{m}$ , 333 nH/m, 333  $\mu\text{S/m}$ , 92.59 pF/m
- B. 1.2  $\Omega/\text{m}$ , 11 H/m, 333  $\mu\text{S/m}$ , 92.59 F/m
- C. 2.4  $\Omega/\text{m}$ , 333 nH/m, 333  $\mu\text{S/m}$ , 92.59 F/m
- D. 2.4  $\Omega/\text{m}$ , 111 H/m, 333 S/m, 92.59 pF/m

Ans. A

118. Consider the following statements regarding the Smith's chart:

1. Smith's chart is a graphical indication of the impedance of a transmission line and of the corresponding reflection coefficient as one moves along the line.
2.  $\lambda$  distance on the line corresponds to a  $720^\circ$  movement on the Smith's chart.
3. The admittance chart can be obtained by shifting each and every point on the impedance chart by  $90^\circ$ .
4. Counter-clockwise movement on the chart corresponds to moving towards the generator.

Which of the above statements are correct?

- A. 1 and 2 only
- B. 1 and 3 only
- C. 1, 2 and 4 only
- D. 2, 3 and 4 only

Ans. A

119. Consider the following statements regarding the load matching and impedance measurements:

1. A mismatched load can be properly matched to a line by inserting prior to the load a transmission line  $\lambda/4$  long
2. For matching of  $120 \Omega$  load to a  $75 \Omega$  line, the quarter-wave transformer must have a characteristic impedance of  $190 \Omega$
3. The main disadvantage of signal-stub matching is that it is a narrow-band or frequency-sensitive device.

Which of the above statements are not correct?

- A. 1 and 2 only
- B. 2 and 3 only
- C. 1 and 3 only
- D. 1, 2 and 3

Ans. A

120. 20. Which of the following antennas are used directly as radiators aboard satellites to illuminate comparatively large areas of the Earth and they are widely used as primary feeds for reflector-type antennas both in transmitting and receiving modes?

- A. Dipole antennas
- B. End fire-array antennas
- C. Microstrip antennas
- D. Horn antennas

Ans. D

121. Which one of the following is correct for the given system?

$$y[n] = x[n] - x[n - 1]$$

- A. Time invariant and causal
- B. Time variant and non-causal
- C. Time variant and causal
- D. Time invariant and non-causal

Ans. A

122. Two vectors  $V_1$  and  $V_2$  are orthogonal if their dot product is

- A. 1
- B. 0
- C. infinity
- D. 0.5

Ans. B

123. A discrete-time LTI system with rational system function  $H(z)$  is causal if and only if

- A. the ROC is the exterior of a circle outside the outermost pole.
- B. the ROC is the interior of a circle outside the outermost pole.
- C. the ROC is the exterior of a circle outside the innermost pole.
- D. the ROC is the interior of a circle outside the innermost pole.

Ans. A

124. A feedback system has an open-loop transfer function of

$$G(s)H(s) = \frac{K(1-s)}{s(s^2+5s+9)}$$

By using the Routh criterion, the maximum value of  $K$  for the closed-loop system to be stable is

- A. 2.5
- B. 5
- C. 7.5
- D. 9

Ans. C

125. The steady-state error of type 1 system with input  $r(t) = t^2/2, t \geq 0$ , is

- A. 0
- B. 1/2
- C. 1
- D.  $\infty$

Ans. D

126. Which one of the following statements is correct regarding constant  $N$  circles?

- A. The locus of constant, closed-loop magnitude frequency response for unity feedback systems.
- B. The locus of constant, closed-loop phase frequency response for unity feedback systems.
- C. A subsystem inserted into the forward or feedback path for the purpose of improving the transient response or steady-state error.
- D. A system that monitors its output and corrects for disturbances. It is characterized by feedback paths from the output.

Ans. B

127. Which one of the following digital modulation schemes has the bit error rate as  $\frac{1}{2} \operatorname{erfc} \left( \sqrt{\frac{E_b}{N_0}} \right)$  ?
- A. Coherent binary PSK
  - B. Coherent binary FSK
  - C. DPSK
  - D. Noncoherent binary FSK

Ans. A

128. Which one of the following conditions is justifying a second order approximation?
- A. Closed-loop zeros near the closed-loop second order pole pair are nearly cancelled by the close proximity of higher order closed loop poles.
  - B. Closed-loop zeros cancelled by the close proximity of higher-order closed-loop poles are far removed from the closed-loop second order pole pair.
  - C. Closed-loop zeros near the closed-loop second-order pole pair are not cancelled by the close proximity of higher order closed loop poles.
  - D. Closed-loop zeros cancelled by the close proximity of higher-order closed-loop poles are far removed from the closed-loop second-order zero pair.

Ans. A

129. Consider the following statements regarding the disadvantages of a passive Wad network over an active PD controller:
1. No additional power supplies are required.
  2. Noise due to differentiation is reduced.
  3. Additional pole does not reduce the number of branches of the root locus that cross the imaginary axis into the right half-plane.
  4. Addition of the single zero of the PD controller tends to reduce the number of branches of the root locus that cross into the right half-plane.
- Which of the above statements is/are correct?

- A. 1 only
- B. 2 only
- C. 3 and 4 only
- D. 1, 2 and 4 only

Ans. C

130. Which one the following characteristics is correct regarding RISC processor?
- A. Relatively very large addressing modes
  - B. Multi-cycle instruction execution
  - C. All operations are not done within the registers of the CUP
  - D. Relatively few instructions

Ans. D

**Vision 2023**

Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

131. Which one of the following instruction in a stack computer consists of an operation code only with no address field?
- A. PUSH X
  - B. POP X
  - C. ADD
  - D. LOAD A

Ans. C

132. Which one of the following statements is correct regarding arithmetic and logical operations?
- A. When two 3-bit unsigned numbers are multiplied, the results is an 8-bit product that must be stored in three memory words.
  - B. When two 16-bit unsigned numbers are multiplied, the result is a 32-bit product that must be stored in two memory words.
  - C. Operations that are implemented in a computer with one machine instruction are said to be implemented by software.
  - D. Operations implemented by set of instructions that constituted a program are said to be implemented by hardware.

Ans. B

133. Which one of the following techniques the simplicity of the direct mapping technique in terms of determining the target set?
- A. Set-associative-mapping technique
  - B. Set-associative-direct mapping technique
  - C. Direct mapping set technique
  - D. Indirect mapping set technique

Ans. A

134. Which one of the following memories is primarily used to store machine microcode, desktop bootstrap loaders, and video game cartridges ?
- A. Mask-programmed ROM
  - B. Static-RAM
  - C. Dynamic-RAM
  - D. Non-Programmed ROM

Ans. D

135. In which one of the following situations is the CPU often idle ?
- A. The speeds of the mechanical LO devices are intrinsically slower than those of electronic devices.
  - B. The speeds of the electromechanical I/O devices are intrinsically faster than those of electronic devices.

C. The speeds of the electrical I/O devices are intrinsically slower than those of electronic devices.

D. The speeds of the electrical I/O devices are intrinsically faster than those of electronic devices.

Ans. A

136. A white noise of magnitude  $0.001 \mu \text{ W/Hz}$  is applied to an RC low-pass filter of  $R = 1 \text{ k}\Omega$  and  $C = 0.1 \mu\text{F}$ . The output noise power of the RC low-pass filter is

A.  $0.5 \mu\text{W}$

B.  $1.5 \mu\text{W}$

C.  $2.5 \mu\text{W}$

D.  $3.5 \mu\text{W}$

Ans. B

137. The two random variables X and Y are uncorrelated if and only if their covariance is

A. 0

B. 1

C. -1

D. infinity

Ans. A

138. the antenna current of an AM transmitter is 8A when only the carrier signal is transmitted. What is the antenna current when the carrier signal is modulated by sinusoidal signal  $V(t) = 1.4 \sin(2\pi \times 500t)$  with modulation index 0.8?

A. 3.2 A

B. 7.2 A

C. 9.2 A

D. 11.2 A

Ans. C

139. A 10 Mhz carrier signal is frequency modulated by along-modulation signal. The maximum frequency deviation is 75 kHz. If the frequency of the modulating signal is 300 kHz, then the modulation index and the approximate transmission bandwidth of the FM signal are respectively,

A. 0.28, 750 kHz

B. 0.25, 600 kHz

C. 0.75, 750 kHz

D. 0.75, 450 kHz

Ans. B

140. Consider the following statements for baseband transmission model:

1. Channel signal-to-noise ratio is defined as the ratio of the average power of the modulated signal to the average power of noise in the message bandwidth both measured at the receiver input.
2. Channel signal-to-noise ratio is defined as the ratio of the average power of the modulated signal to the average power of noise in the message bandwidth both measured at the receiver output.
3. Figure of merit =  $\frac{(SNR)_o}{(SNR)_c}$ , where o stands for output and c stands for channel.
4. Figure of merit =  $\frac{(SNR)_c}{(SNR)_o}$ , where o stands for output and c stands for channel.

Which of the above statements are correct?

- A. 1 and 3 only
- B. 2 and 3 only
- C. 1 and 4 only
- D. 2 and 4 only

Ans. A

141. What is the entropy of a communication system that consists of six messages with probabilities  $1/8, 1/8, 1/8, 1/8, 1/4$  respectively?

- A. 1 bit/message
- B. 2.5 bit/message
- C. 3 bit/message
- D. 4.5 bit/message

Ans. B

142. Discrete samples of an analog signal are uniformly quantized to PCM. If the maximum value of analog sample is to be represented with 0.1% accuracy, then the minimum number of binary digits required per sample is

- |       |       |
|-------|-------|
| A. 4  | B. 8  |
| C. 10 | D. 12 |

Ans. C

143. Six analog information signals, each band-limited to 4 kHz, are required to be time-division multiplexed and transmitted by a TDM system. The minimum transmission bandwidth and the signalling rate of the PAM/TDM channel are respectively,

- A. 24 kHz and 48 kbps
- B. 24 kHz and 8 kbps
- C. 48 kHz and 48 kbps
- D. 48 kHz and 16 kbps

Ans. A

144. A 2000 bps binary information data signal is required to be transmitted in half-duplex mode using BFSK digital modulation technique. If the separation between two carrier frequencies is 4000 Hz, then the minimum bandwidth of the BFSK signal is
- A. 4 kHz
  - B. 6 kHz
  - C. 8 kHz
  - D. 12 kHz

Ans. C

145. If voice activity interference reduction factor is 2.5, antenna sectorization gain factor is 2.5 and interference increase factor is 1.6, then the performance improvement factor in CDMA digital cellular system is
- A. 1.2
  - B. 2.5
  - C. 3.1
  - D. 3.9

Ans. D

146. The temperature at a particular place varies between 14°C and 34°C. For the purpose of transmitting the temperature record of that place using PCM, the record is sampled at an appropriate sampling rate and the samples are quantized. If the error in representation of the samples due to quantization is not to exceed  $\pm 1\%$  of the dynamic range, what is the minimum number of quantization levels that can be used?
- A. 100
  - B. 50
  - C. 30
  - D. 15

Ans. B

147. A multimode step index fiber with a core diameter of 80  $\mu\text{m}$  and a relative index difference of 1.5% is operating at a wavelength of 0.85  $\mu\text{m}$ . If the core refractive index is 1.18, then the normalized frequency for the fiber is
- A. 37.9
  - B. 75.8
  - C. 151.6
  - D. 303.2

Ans. B

148. The even and odd components of the signal  $x(t) = e^{-2t} \cos t$  are respectively,
- A.  $\cos 2t \cos t$  and  $-\sin 2t \cos t$
  - B.  $\sinh 2t \cos t$  and  $-\cosh 2t \cos t$
  - C.  $\cos 2t \cos t$  and  $-\sin 2t \cos t$
  - D.  $\cosh 2t \cos t$  and  $-\sinh 2t \cos t$

Ans. D

149. What is the convolution integral  $c(t)$  for a system with input  $x(t)$  and impulse response  $h(t)$ , where  $x(t) = u(t - 1) - u(t - 3)$  and  $h(t) = u(t) - u(t - 2)$ ?

- A.  $c(t) = \begin{cases} 0, & t < 1 \\ t - 1, & 1 \leq t < 3 \\ 5 - t, & 3 \leq t < 5 \\ 0, & t \geq 5 \end{cases}$
- B.  $c(t) = \begin{cases} 0, & t < 1 \\ t - \frac{1}{2}, & 1 \leq t < 2 \\ \frac{3}{2} - t, & 2 \leq t < 5 \\ 0, & t \geq 5 \end{cases}$
- C.  $c(t) = \begin{cases} 0, & t < 1 \\ 5 - t, & 1 \leq t < 4 \\ 0, & t \geq 4 \end{cases}$
- D.  $c(t) = \begin{cases} 2, & t \leq t \leq 2 \\ 1, & 3 \leq t \leq 5 \\ 0, & \text{otherwise} \end{cases}$

Ans. A

150. The power and energy of the unit step sequence are respectively,
- A. 1/2 and 0
  - B. 1/2 and infinity
  - C. 2 and 0
  - D. 2 and infinity

Ans. B

\*\*\*\*

## OUR STAR FACULTY



**Abhinav Negi**

9+ Years of Experience  
M.Tech. IIT Delhi  
Produced 50+ Students  
under AIR 100 in GATE



**Ankit Sharma**

11+ Years of Experience  
AIR-128, ESE-2011  
Mentored 20,000+ Students



**Md. Ansari**

8+ Years of Experience M.E,  
IISc Bangalore



**Dheeraj Sardana**

10+ Years of Experience  
Mentored 15000+ Students  
Produced AIR 4 & 30+ Rankers  
under AIR 100 in GATE



**Chandra Shekhar**

13+ Years of Experience  
B.Tech, IIT Delhi



**Ashutosh Saxena**

10+ Years of Experience  
M.Tech, IIT BHU  
Sr. Faculty for ESE & GATE



**Ankit Joshi**

15+ Years of Experience  
Produced AIR 1 in  
GATE 2 times  
Produced 50+ Students  
under AIR 100 in GATE



**Sanjay Rathi**

18+ Years of Experience  
ESE AIR 16 & AIR 21  
Produced many top rankers  
under AIR 100



**Rakesh Talreja**

10+ Years of Experience  
M.Tech, IISc Bangalore (AIR-9)



**Chandan Jha**

9+ Years of Experience  
M.Tech, NIT Hamirpur

**BARC 2021**



Boostup Course for EE | EC | ME

Course Starts from 20th July



Enrolment Started!



**120+**  
of Live Classes



**10+**  
Subject-wise Formula Notes



**60+**  
Quizzes



**7+**  
Mock Tests

### Includes

- › Complete Practice of BARC
- › Formula Revision Notes Pdfs
- › Daily Tests & Weekly Tests for Practice
- › Full-Length Mock Tests

For More Information: **9650052904**

[www.gradeup.co](http://www.gradeup.co)

**Vision 2023**

Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

10+ Gradians Under AIR 10



Sahi Prep Hai Toh Life Set Hai



Hurry up! Enrolment Started for Limited Seats

Enrol Now

Vision GATE 2022 (English)

Course for GATE Exclusive CE | ME | EE | EC | CS

550+ Hrs. of Live Classes

4000+ Practice Questions

30+ Mock Tests

100+ Chapter-wise Study Note

VISION 2022 (Hindi)

Course for ESE, GATE & PSUs CE | ME | EE | EC | CS

850+ Hrs. of Live Classes

8000+ Practice Questions

100+ Mock Tests

100+ Chapter-wise Study Note

VISION 2023 (Hindi/Eng.)

Course for ESE & GATE 2023 CE | ME | EE | EC

950+ Hrs. of Live Classes

8000+ Practice Questions

200+ Mock Tests

120+ Chapter-wise Study Note

To get unlimited access to your preferred courses subscribe to Gradeup Super For More Information: 9650052904

Vision 2023

Course for ESE & GATE Electronics Aspirants

START FREE TRIAL

## Live Courses

-  Daily Study Plan
-  India's Best ESE, GATE & PSU Faculty
-  Best Study Material
-  Complete Doubt Resolution



## Online Mock Tests

-  Based on Latest Exam Pattern
-  Designed by Experts

