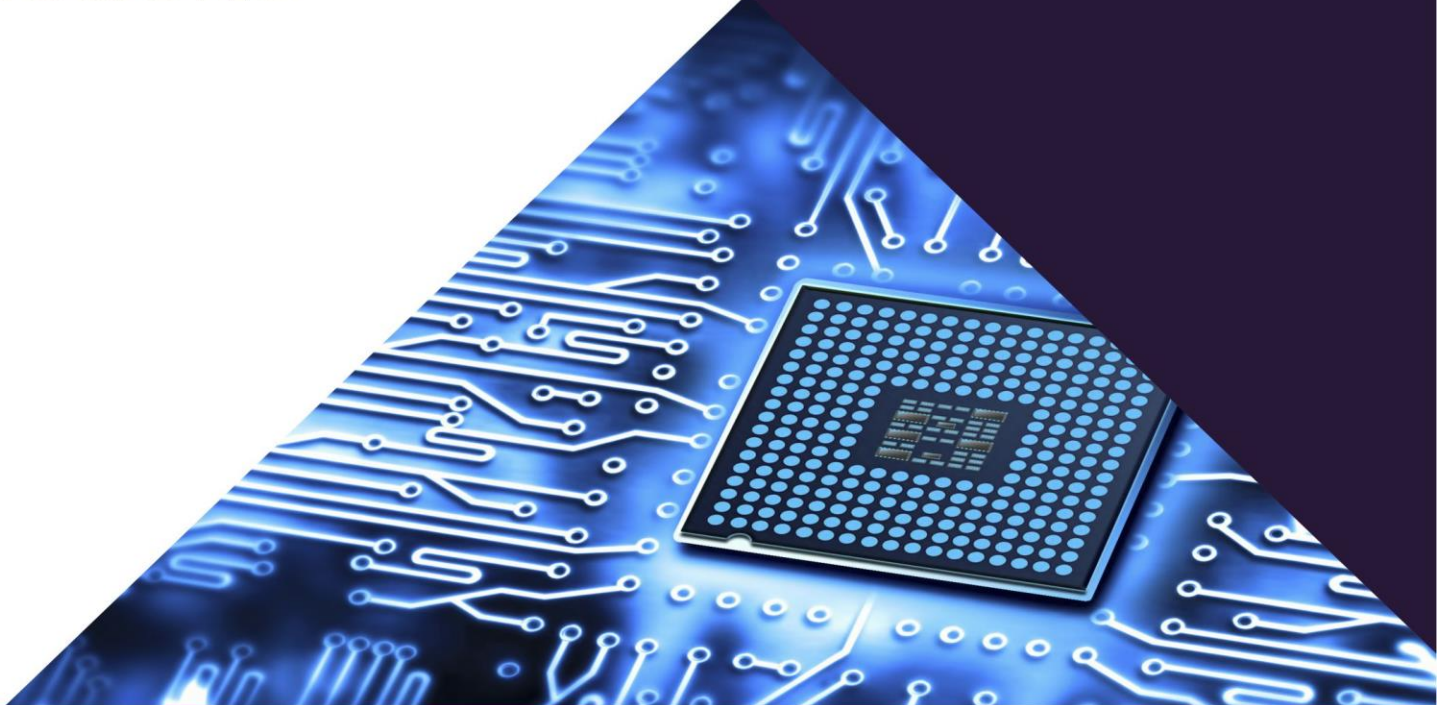


GATE 2019


Electronics
& Communication
Engineering

► Questions




SECTION: GENERAL APTITUDE

- The strategies that the company _____ to sell its products _____ house-to-house marketing.
 - uses, include
 - used, includes
 - uses, including
 - use, includes
- The boat arrived _____ dawn.
 - under
 - in
 - on
 - at
- Five different books (P, Q, S, R, T) are to be arranged on a shelf. The books R and S are to be arranged first and second, respectively from the right side of the shelf. The number of different orders in which P, Q and T may be arranged is _____.
 - 12
 - 120
 - 6
 - 2
- When he did not come home, she _____ him lying dead on the roadside somewhere.
 - concluded
 - looked
 - noticed
 - pictured
- It would take one machine 4 hours to complete a production order and another machine 2 hours to complete the same order. If both machines work simultaneously at their respective constant rates, the time taken to complete the same order is _____ hours.
 - 2/3
 - 3/4
 - 4/3
 - 7/3
- The bar graph in Panel (a) shows the proportion of male and female illiterates in 2001 and 2011. The proportions of males and females in 2001 and 2011 are given in Panel (b) and (c), respectively. The total population did not change during this period. The percentage increase in the total number of illiterates from 2001 to 2011 is _____.

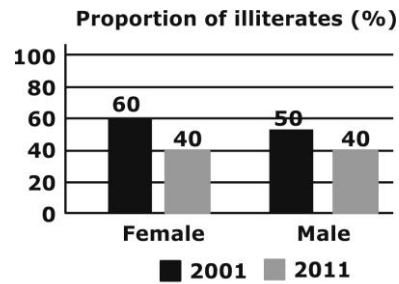

Panel (a)

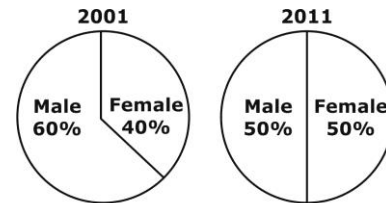

Panel (b)

Panel (c)

- 34.43
 - 35.43
 - 30.43
 - 33.43
- Four people are standing in a line facing you. They are Rahul, Mathew, Seema and Lohit. One is an engineer, one is a doctor, one a teacher and another a dancer. You are told that :
 - Mathew is not standing next to Seema
 - There are two people standing between Lohit and the engineer
 - Rahul is not a doctor
 - The teacher and the dancer are standing next to each other
 - Seema is turning to her right to speak to the doctor standing next to her
 Who among them is an engineer?
 - Seema
 - Rahul
 - Lohit
 - Mathew
 - "Indian history was written by British historians – extremely well documented and researched, but not always impartial. History had to serve its purpose: Everything was made subservient to the glory of the Union Jack. Latter-day Indian scholars presented a contrary picture."

From the text above, we can infer that :
Indian history written by British historians _____

- A. was not well documented and researched and was always biased
- B. was not well documented and researched and was sometimes biased
- C. was well documented and researched but was sometimes biased
- D. was well documented and not researched but was always biased

9. Two design consultants, P and Q started working from 8 AM for a client. The client budgeted a total of USD 3000 for the consultants. P stopped working when the hour hand moved by 210 degrees on the clock. Q stopped working when the hour hand moved by 240 degrees. P took two tea breaks of 15 minutes each during her shift, but took no lunch break. Q took only one lunch break for 20 minutes, but no tea breaks. The market rate for consultants is USD 200 per hour and breaks are not paid. After paying the consultants, the client shall have USD _____ remaining in the budget.
- A. 000.00 B. 166.67
 - C. 300.00 D. 433.33

10. Five people P, Q, R, S and T work in a bank. P and Q don't like each other but have to share an office till T gets a promotion and moves to the big office next to the garden. R, who is currently sharing an office with T wants to move to the adjacent office with S, the handsome new intern. Given the floor plan, what is the current location of Q, R and T? (O = Office, WR = Washroom)

A.

WR	O1 P,Q	O2	O3 R,T	O4 S
Manager	Entry		Teller	Teller
Garden				

B.

WR	O1 P,Q	O2	O3 R	O4 S
Manager T	Entry		Teller 1	Teller 2
Garden				

C.

WR	O1 P	O2 Q	O3 R	O4 S
Manager	Entry		Teller 1	Teller 2
Garden				

D.

WR	O1 P,Q	O2	O3 T	O4 R,S
Manager	Entry		Teller 1	Teller 2
Garden				

TECHNICAL


1. Which one of the following functions is analytic over the entire complex plane?

- A. $e^{1/z}$
- B. $\ln(z)$
- C. $\frac{1}{1-z}$
- D. $\cos(z)$


2. Which one of the following options describes correctly the equilibrium band diagram at $T = 300$ K of a Silicon pnn+p⁺⁺ configuration shown in the figure?

p	n	n ⁺	p ⁺⁺
---	---	----------------	-----------------


A.

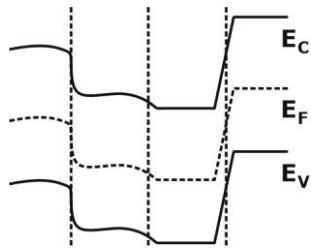


B.

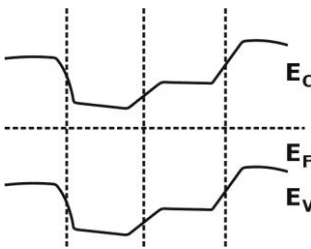


C.

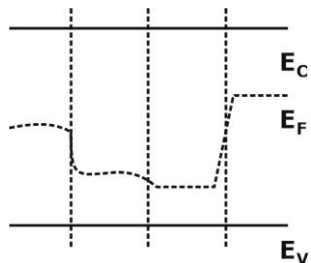


D.

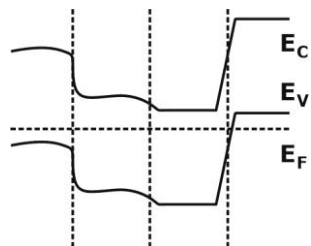

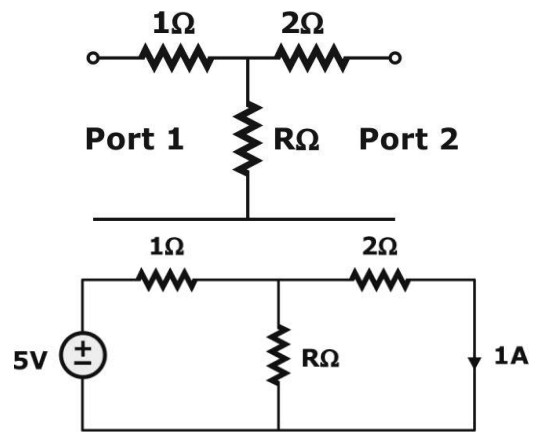3. Consider the two-port resistive network shown in the figure. When an excitation of 5 V is applied across Port 1, and Port 2 is shorted, the current through the short circuit at Port 2 is measured to be 1 A (see (a) in the figure).




(a)

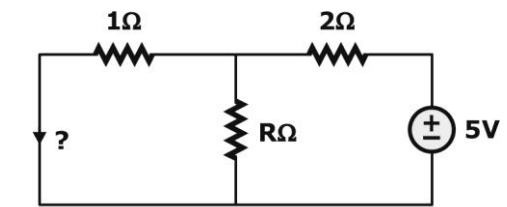

(b)

- A. 0.5 A
- B. 1 A
- C. 2 A
- D. 2.5 A

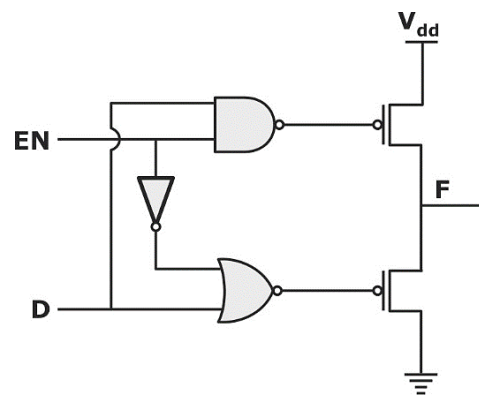4. In the circuit shown, what are the values of F for $E_N = 0$ and $E_N = 1$, respectively?



- A. Hi-Z and D
- B. Hi-Z and \bar{D}
- C. 0 and 1
- D. 0 and D

5. The number of distinct eigenvalues of the matrix

$$A = \begin{bmatrix} 2 & 2 & 3 & 3 \\ 0 & 1 & 1 & 1 \\ 0 & 0 & 3 & 3 \\ 0 & 0 & 0 & 2 \end{bmatrix}$$



is equal to _____.

6. The families of curves represented by the solution of the equation


$$\frac{dy}{dx} = -\left(\frac{x}{y}\right)^n$$

for $n = -1$ and $n = +1$, respectively, are

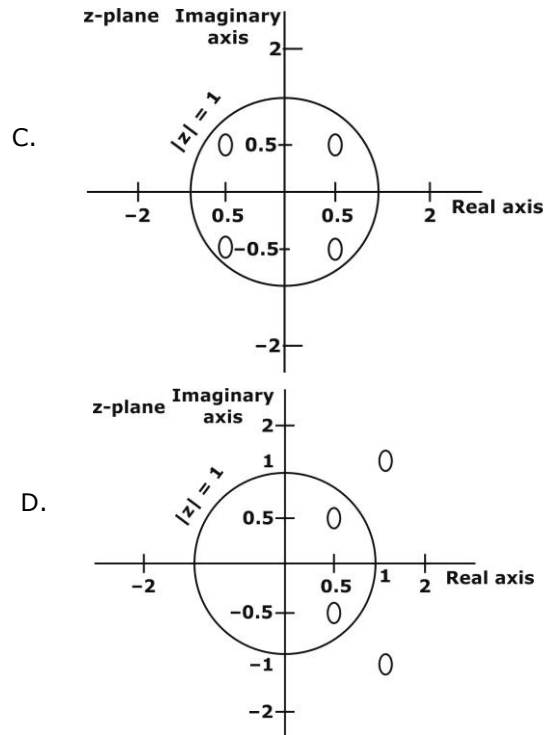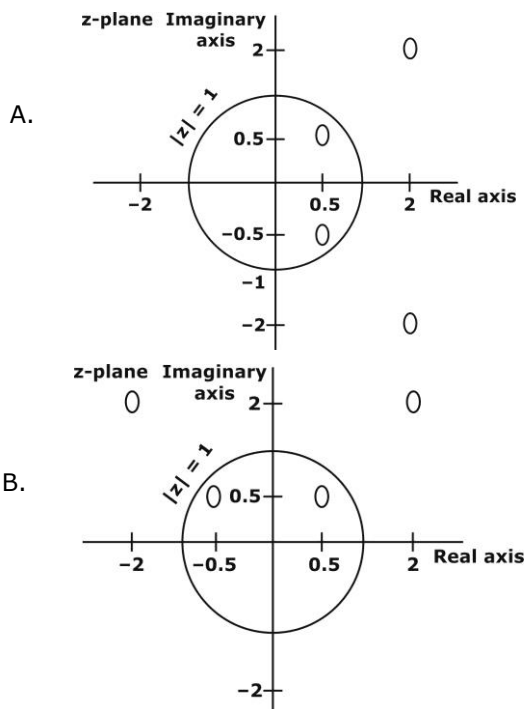
- A. Hyperbolas and Circles
 - B. Circles and Hyperbolas
 - C. Parabolas and Circles
 - D. Hyperbolas and Parabolas
7. Let $H(z)$ be the z-transform of a real-valued discrete-time signal $h[n]$. If $P(z) = H(z) H\left(\frac{1}{z}\right)$ has a zero at $z = \frac{1}{2} + \frac{1}{2}j$, and $P(z)$ has a total of four zeros, which one of the following plots represents all the zeros correctly?



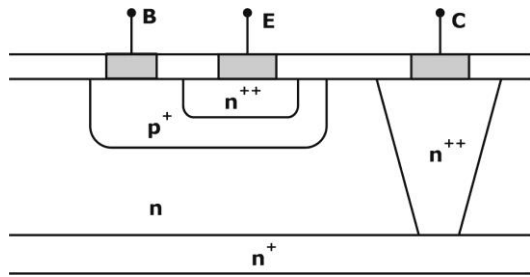
8. The value of the integral $\int_0^\pi \int_y^\pi \frac{\sin x}{x} dx dy$, is equal to _____.
9. Radiation resistance of a small dipole current element of length l at a frequency of 3 GHz is 3 ohms. If the length is changed by 1%, then the percentage change in the radiation resistance, rounded off to two decimal places, is _____%.
10. Let $Y(s)$ be the unit-step response of a causal system having a transfer function $G(s) = \frac{3-s}{(s+1)(s+3)}$ that is, $Y(s) = \frac{G(s)}{s}$. The forced response of the system is
- A. $u(t) - 2e^{-t}u(t) + e^{-3t}u(t)$
 - B. $u(t)$
 - C. $2u(t) - 2e^{-t}u(t) + e^{-3t}u(t)$
 - D. $2u(t)$
11. The correct circuit representation of the structure shown in the figure is




A.

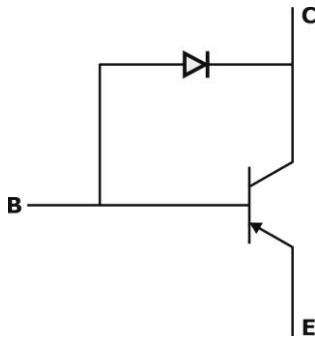


B.

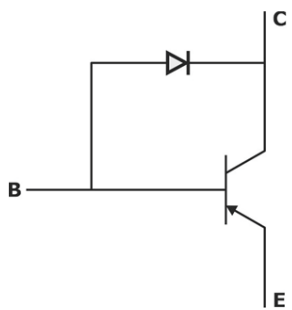


C.

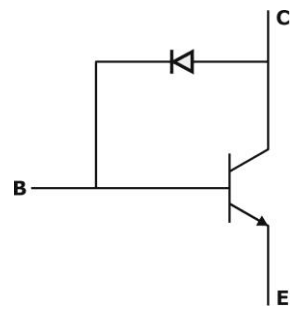

D.

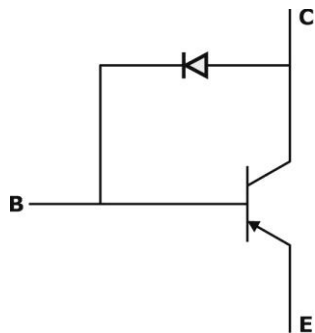


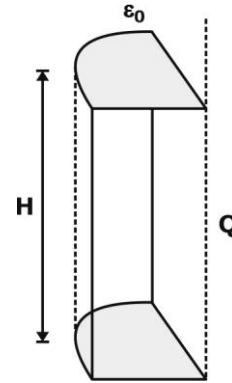12. What is the electric flux ($\int \vec{E} \cdot d\hat{a}$) through a quarter-cylinder of height H (as shown in the figure) due to an infinitely long line charge along the axis of the cylinder with a charge density of Q?




- A. $\frac{H \epsilon_0}{4Q}$ B. $\frac{HQ}{\epsilon_0}$
 C. $\frac{HQ}{4\epsilon_0}$ D. $\frac{4H}{Q\epsilon_0}$

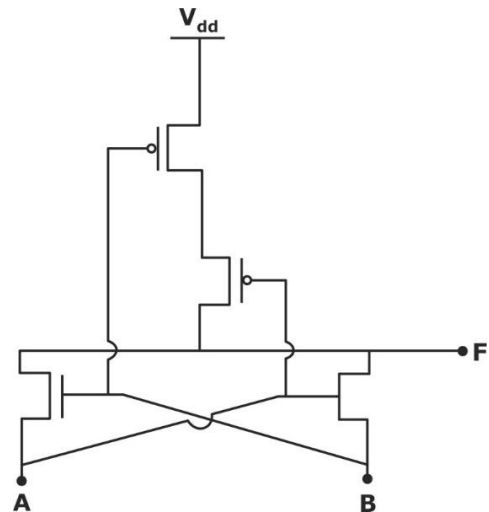13. In the circuit shown, A and B are the inputs and F is the output. What is the functionality of the circuit?



- A. XOR B. SRAM Cell
 C. Latch D. XNOR

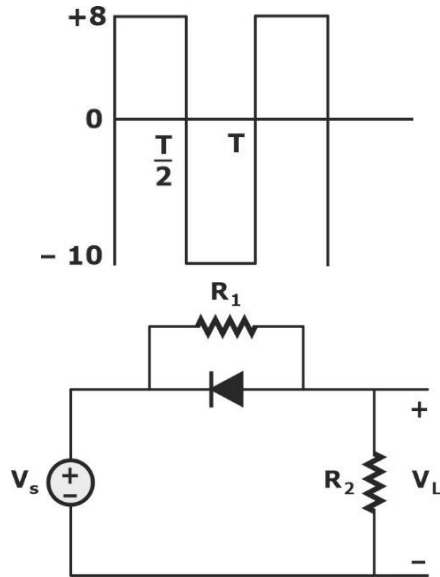14. In the circuit shown, V_s is a square wave of period T with maximum and minimum values of 8 V and -10 V, respectively. Assume that the diode is ideal and $R_1 = R_2 = 50 \Omega$. The average value of V_L is _____ volts (rounded off to 1 decimal place).




15. If X and Y are random variables such that $E[2X + Y] = 0$ and $E[X + 2Y] = 33$, then $E[X] + E[Y] =$ _____.
16. A standard CMOS inverter is designed with equal rise and fall times ($\beta_n = \beta_p$). If the width of the pMOS transistor in the inverter is increased, what would be the effect on the LOW noise margin (N_{ML}) and the HIGH noise margin N_{MH} ?
- A. N_{ML} increases and N_{MH} decreases.
 B. Both N_{ML} and N_{MH} increase.
 C. N_{ML} decreases and N_{MH} increase.
 D. No change in the noise margins.
17. In the table shown, List I and List II, respectively, contain terms appearing on the left-hand side and the right-hand side of Maxwell's equations (in their standard form). Match the left-hand side with the corresponding right-hand side.


List I		List II	
1	$\nabla \cdot \mathbf{D}$	P	0
2	$\nabla \times \mathbf{E}$	Q	ρ
3	$\nabla \cdot \mathbf{B}$	R	$-\frac{\partial \mathbf{B}}{\partial t}$
4	$\nabla \times \mathbf{H}$	S	$\mathbf{J} + \frac{\partial \mathbf{D}}{\partial t}$

- A. 1 - Q, 2 - R, 3 - P, 4 - S
 B. 1 - Q, 2 - S, 3 - P, 4 - R
 C. 1 - R, 2 - Q, 3 - S, 4 - P
 D. 1 - P, 2 - R, 3 - Q, 4 - S

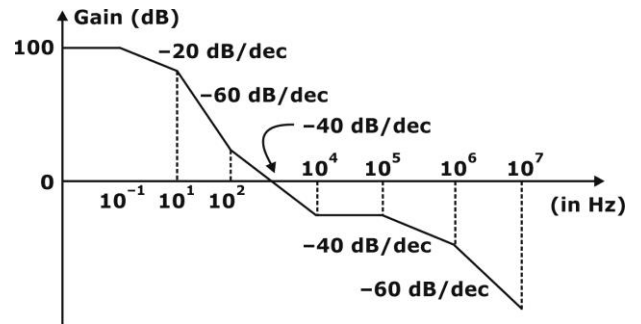
18. For an LTI system, the Bode plot for its gain is as illustrated in the figure shown. The number of system poles N_p and the number of system zeros N_z in the frequency range $1 \text{ Hz} \leq f \leq 10^7 \text{ Hz}$ is



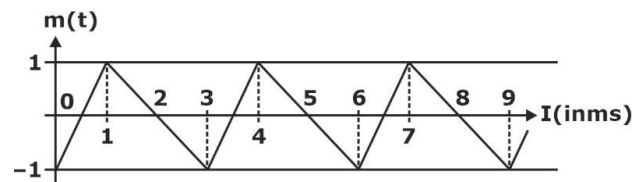- A. $N_p = 6, N_z = 3$
 B. $N_p = 5, N_z = 2$
 C. $N_p = 4, N_z = 2$
 D. $N_p = 7, N_z = 4$
19. The baseband signal $m(t)$ shown in the figure is phase-modulated to generate the PM signal $\phi(t) = \cos(2\pi f_c t + k m(t))$. The time t on the x-axis in the figure is in milliseconds. If the carrier frequency is $f_c = 50 \text{ kHz}$ and $k = 10\pi$, then the ratio of the minimum instantaneous frequency (in kHz) to the maximum instantaneous frequency (in kHz) is _____ (rounded off to 2 decimal places).



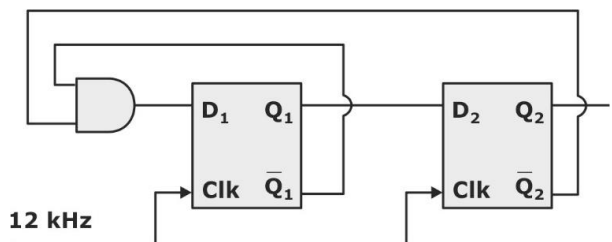20. In the circuit shown, the clock frequency, i.e., the frequency of the Clk signal, is 12 kHz. The frequency of the signal at Q_2 is _____ kHz.



21. A linear Hamming code is used to map 4-bit messages to 7-bit codewords. The encoder mapping is linear. If the message 0001 is mapped to the codeword 0000111, and the message 0011 is

mapped to the codeword 100110, then the message 0010 is mapped to

- A. 1111000 B. 0010011
- C. 1111111 D. 1100001

22. Let Z be an exponential random variable with mean 1. That is, the cumulative distribution function of Z is given by


$$F_Z(x) = \begin{cases} 1 - e^{-x} & \text{if } x \geq 0 \\ 0 & \text{if } x < 0 \end{cases}$$

Then $\Pr(Z > 2 | Z > 1)$, rounded off to two decimal places, is equal to _____.

23. Consider the signal $f(t) = 1 + 2\cos(\pi t) + 3\sin\left(\frac{2\pi}{3}t\right) + 4\cos\left(\frac{\pi}{2}t + \frac{\pi}{4}\right)$, where t is in seconds.

Its fundamental time period, in seconds, is _____.

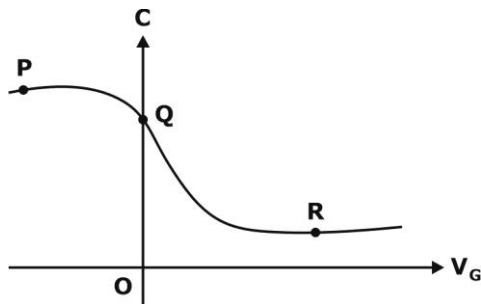24. The figure shows the high-frequency C-V curve of a MOS capacitor (at T = 300 K) with $\Phi_{ms} = 0$ V and no oxide charges. The flat-band, inversion, and accumulation conditions are represented, respectively, by the points




- A. Q, R, P B. Q, P, R
- C. R, P, Q D. P, Q, R

25. The value of the contour integral


$$\frac{1}{2\pi j} \oint \left(z + \frac{1}{z}\right)^2 dz$$

evaluated over the unit circle $|z| = 1$ is _____.

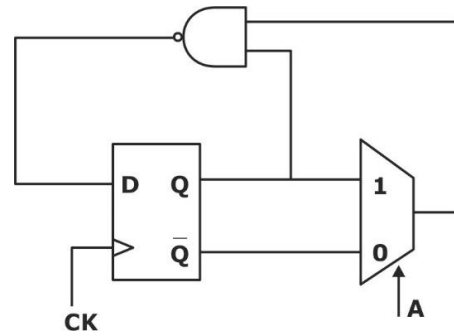
26. The state transition diagram for the circuit shown is




A.

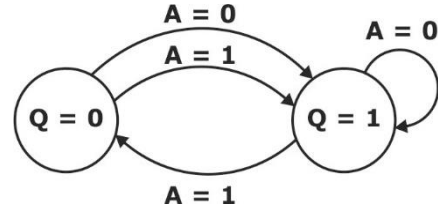


B.

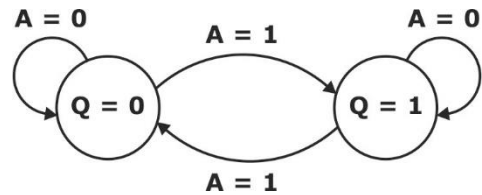


C.

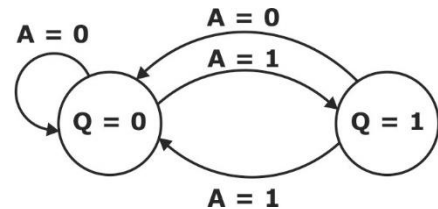

D.

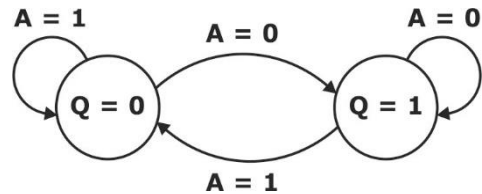


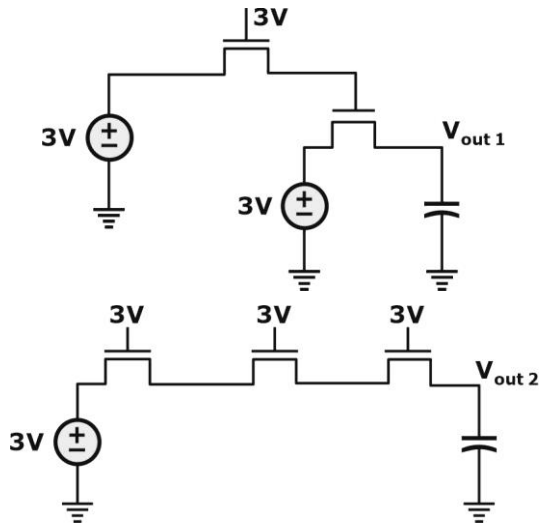27. In the circuits shown, the threshold voltage of each nMOS transistor is 0.6 V. Ignoring the effect of channel length modulation and body bias, the values of $V_{out 1}$ and $V_{out 2}$, respectively, in volts, are



- A. 2.4 and 2.4
- B. 1.8 and 1.2
- C. 1.8 and 2.4
- D. 2.4 and 1.2

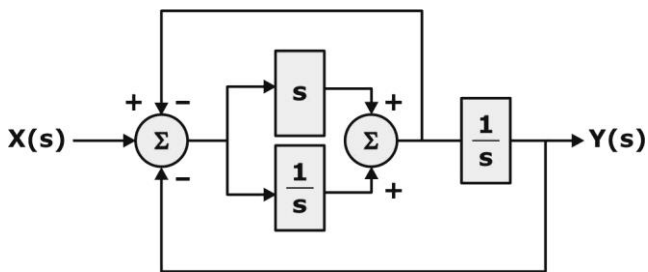28. The block diagram of a system is illustrated in the figure shown, where $X(s)$ is the input and $Y(s)$ is the output. The transfer function $H(s) = \frac{Y(s)}{X(s)}$ is




- A. $H(s) = \frac{s^2 + 1}{2s^2 + 1}$
- B. $H(s) = \frac{s^2 + 1}{s^3 + 2s^2 + s + 1}$
- C. $H(s) = \frac{s + 1}{s^2 + s + 1}$
- D. $H(s) = \frac{s^2 + 1}{s^3 + s^2 + s + 1}$

29. A random variable X takes -1 and $+1$ with probabilities 0.2 and 0.8 , respectively. It is transmitted across a channel which adds noise N , so that the random variable at the channel output is $Y = X + N$. The noise n is independent of X , and is uniformly distributed over the interval $[-2, 2]$. The receiver makes a decision

$$\hat{X} = \begin{cases} -1, & \text{if } Y \leq \theta \\ +1, & \text{if } Y > \theta \end{cases}$$

Where the threshold $\theta \in [-1, 1]$ is chosen so as to minimize the probability of error $\Pr[\hat{X} \neq X]$. The minimum probability of error, rounded off to 1 decimal place, is _____.

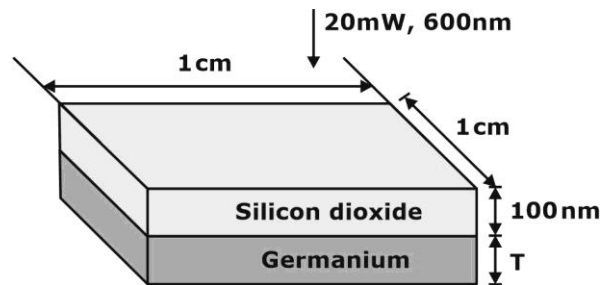30. A germanium sample of dimensions $1 \text{ cm} \times 1 \text{ cm}$ is illuminated with a 20 mW , 600 nm laser light source as shown in the figure. The illuminated sample surface has a 100 nm of loss-less Silicon dioxide layer that reflects one-fourth of the incident light. From the remaining light, one-third of the power is reflected from the Silicon dioxide-Germanium interface, one-third is absorbed in the Germanium layer, and one-third is transmitted through the other side of the sample. If the absorption coefficient of Germanium at 600 nm is $3 \times 10^4 \text{ cm}^{-1}$ and the bandgap is 0.66 eV , the thickness of the Germanium layer, rounded off to 3 decimal places, is _____ μm .




31. In the circuit shown, the threshold voltages of the pMOS ($|V_{tp}|$) and nMOS (V_{tn}) transistors are both equal to 1 V . All the transistors have the same output resistance r_{ds} of $6 \text{ M}\Omega$. The other parameters are listed below.

$$\mu_n C_{ox} = 60 \mu\text{A/V}^2; \left(\frac{W}{L}\right)_{n\text{MOS}} = 5$$

$$\mu_p C_{ox} = 30 \mu\text{A/V}^2; \left(\frac{W}{L}\right)_{p\text{MOS}} = 10$$

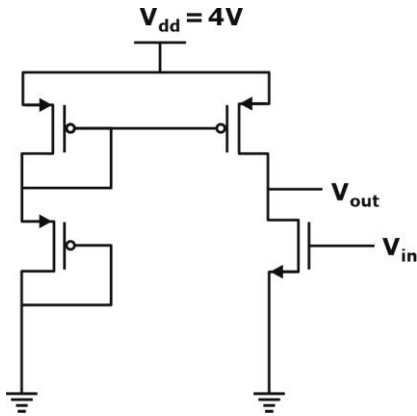μ_n and μ_p are the carrier mobilities, and C_{ox} is the oxide capacitance per unit area. Ignoring the effect of channel length modulation and body bias, the gain of the circuit is _____ (rounded off to 1 decimal place).



32. It is desired to find a three-tap causal filter which gives zero signal as an output to an input of the form

$$x[n] = c_1 \exp\left(-\frac{j\pi n}{2}\right) + c_2 \exp\left(\frac{j\pi n}{2}\right),$$


where c_1 and c_2 are arbitrary real numbers. The desired three-tap filter is given by

$$h[0] = 1, h[1] = a, h[2] = b$$

and

$$h[n] = 0 \text{ for } n < 0 \text{ or } n > 2.$$

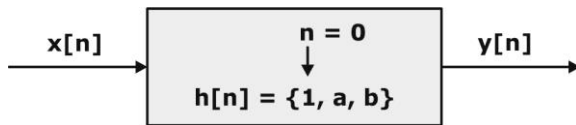What are the values of the filter taps a and b if the output is $y[n] = 0$ for all n , when $x[n]$ is as given above?




- A. $a = 0, b = -1$
- B. $a = 1, b = 1$
- C. $a = -1, b = 1$
- D. $a = 0, b = 1$

33. Consider a long-channel MOSFET with a channel length $1 \mu\text{m}$ and width $10 \mu\text{m}$. The device parameters are acceptor concentration $N_A = 5 \times 10^{16} \text{ cm}^{-3}$, electron mobility $\mu_n = 800 \text{ cm}^2/\text{V-s}$, oxide capacitance/area $C_{ox} = 3.45 \times 10^{-7} \text{ F/cm}^2$, threshold voltage $V_T = 0.7 \text{ V}$. The drain saturation current (I_{Dsat}) for a gate voltage of 5 V is _____ mA (rounded off to two decimal places).

$$[\epsilon_0 = 8.854 \times 10^{-14} \text{ F/cm}, \epsilon_{si} = 11.9]$$

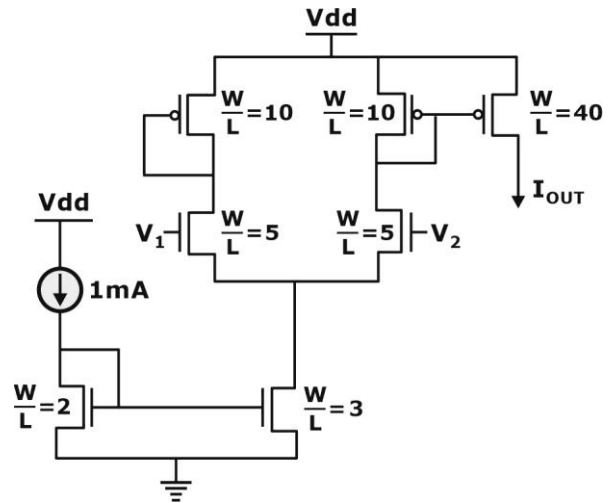
34. In the circuit shown, $V_1 = 0$ and $V_2 = V_{dd}$. The other relevant parameters are mentioned in the figure. Ignoring the effect of channel length modulation and the body effect, the value of I_{out} is _____ mA (rounded off to 1 decimal place).



35. The quantum efficiency (η) and responsivity (R) at wavelength λ (in μm) in a p-i-n photodetector are related by


- A. $R = \frac{1.24 \times \lambda}{\eta}$
- B. $R = \frac{\eta \times \lambda}{1.24}$
- C. $R = \frac{1.24}{\eta \times \lambda}$
- D. $R = \frac{\lambda}{\eta \times 1.24}$

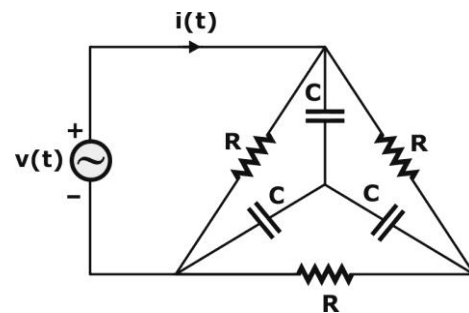36. In the circuit shown, if $v(t) = 2 \sin(1000 t)$ volts, $R = 1 \text{ k}\Omega$ and $C = 1 \mu\text{F}$, then the steady-state current $i(t)$, in milliamperes (mA), is



- A. $\sin(1000 t) + \cos(1000 t)$
- B. $2 \sin(1000 t) + 2 \cos(1000 t)$
- C. $3 \sin(1000 t) + \cos(1000 t)$
- D. $\sin(1000 t) + 3 \cos(1000 t)$

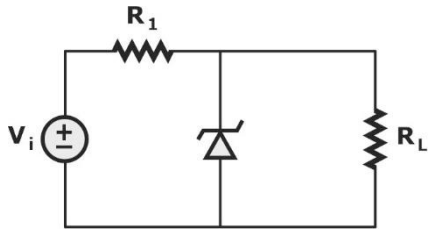37. In the circuit shown, the breakdown voltage and the maximum current of the Zener diode are 20 V and 60 mA , respectively. The values of R_1 and R_L are 200Ω and $1 \text{ k}\Omega$, respectively. What is the range of V_i that will maintain the Zener diode in the 'on' state?




- A. 18 V to 24 V
- B. 20 V to 28 V
- C. 24 V to 36 V
- D. 22 V to 34 V

38. Consider a differentiable function $f(x)$ on the set of real numbers such that $f(-1) = 0$ and $|f'(x)| \leq 2$. Given these conditions, which one of the following inequalities is necessarily true for all $x \in [-2, 2]$?

- A. $f(x) \leq \frac{1}{2}|x|$
- B. $f(x) \leq 2|x+1|$
- C. $f(x) \leq \frac{1}{2}|x+1|$
- D. $f(x) \leq 2|x|$

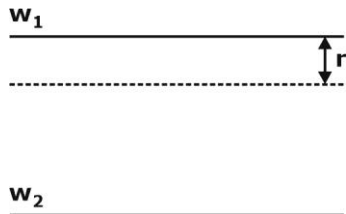39. Two identical copper wires W1 and W2, placed in parallel as shown in the figure, carry currents I and $2I$, respectively, in opposite directions. If the two wires are separated by a distance of $4r$, then the magnitude of the magnetic field \vec{B} between the wires at a distance r from W1 is



- A. $\frac{\mu_0 I}{6\pi r}$
- B. $\frac{\mu_0^2 I^2}{2\pi r^2}$
- C. $\frac{5\mu_0 I}{6\pi r}$
- D. $\frac{6\mu_0 I}{5\pi r}$

40. The dispersion equation of a waveguide, which relates the wavenumber k to the frequency ω , is

$$k(\omega) = (1/c)\sqrt{\omega^2 - \omega_0^2}$$

where the speed of light $c = 3 \times 10^8$ m/s, and ω_0 is a constant. If the group velocity is 2×10^8 m/s, then the phase velocity is

- A. 1.5×10^8 m/s
- B. 2×10^8 m/s
- C. 4.5×10^8 m/s
- D. 3×10^8 m/s

41. Consider a causal second-order system with the transfer function


$$G(s) = \frac{1}{1 + 2s + s^2}$$

with a unit-step $R(s) = \frac{1}{s}$ as an input. Let $C(s)$ be the corresponding output. The time taken by the system output $c(t)$ to reach 94% of its steady-state value $\lim_{t \rightarrow \infty} c(t)$ rounded off to two decimal places, is

- A. 4.50
- B. 2.81
- C. 5.25
- D. 3.89

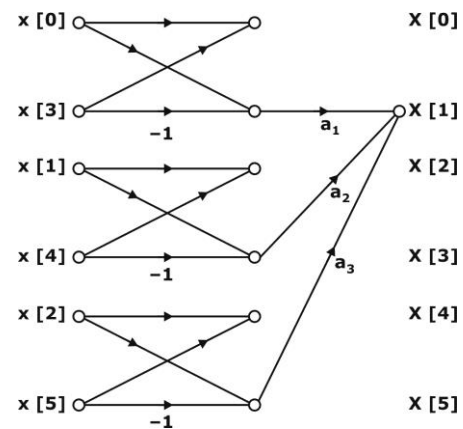42. Consider a six-point decimation-in-time Fast Fourier Transform (FFT) algorithm, for which the signal-flow graph corresponding to $X[1]$ is shown in the figure.

Let $W_6 = \exp\left(-\frac{j2\pi}{6}\right)$. In the figure, what should be the values of the coefficients a_1, a_2, a_3 in terms of W_6 so that $X[1]$ is obtained correctly?



- A. $a_1 = 1, a_2 = W_6, a_3 = W_6^2$
- B. $a_1 = -1, a_2 = W_6, a_3 = W_6^2$
- C. $a_1 = 1, a_2 = W_6^2, a_3 = W_6$
- D. $a_1 = -1, a_2 = W_6^2, a_3 = W_6$

43. Let the state-space representation of an LTI system be $\dot{x}(t) = Ax(t) + Bu(t), y(t) = C x(t) + d u(t)$ where A, B, C are matrices, d is a scalar, $u(t)$ is the input to the system, and $y(t)$ is its output. Let $B = [0 \ 0 \ 1]^T$ and $d = 0$. Which one of the following

options for A and C will ensure that the transfer function of this LTI system is

$$H(s) = \frac{1}{s^3 + 3s^2 + 2s + 1} ?$$

A. $A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -2 & -3 \end{bmatrix}$ and $C = [1 \ 0 \ 0]$

B. $A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -2 & -3 \end{bmatrix}$ and $C = [0 \ 0 \ 1]$

C. $A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -3 & -2 & -1 \end{bmatrix}$ and $C = [0 \ 0 \ 1]$

D. $A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -3 & -2 & -1 \end{bmatrix}$ and $C = [1 \ 0 \ 0]$

44. A CMOS inverter, designed to have a mid-point voltage V_I equal to half of V_{dd} , as shown in the figure, has the following parameters :


$$V_{dd} = 3 \text{ V}$$

$$\mu_n C_{ox} = 100 \text{ } \mu\text{A/V}^2 ; V_{tn} = 0.7 \text{ V for nMOS}$$

$$\mu_p C_{ox} = 40 \text{ } \mu\text{A/V}^2 ; |V_{tp}| = 0.9 \text{ V for pMOS}$$

The ratio of $\left(\frac{W}{L}\right)_n$ to $\left(\frac{W}{L}\right)_p$ is equal to _____


(rounded off to 3 decimal places).

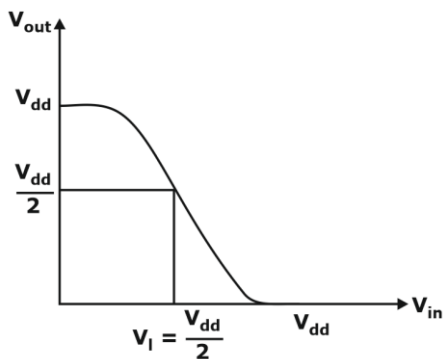

45. A rectangular waveguide of width w and height h has cut-off frequencies for TE_{10} and TE_{11} modes in the ratio 1 : 2. The aspect ratio w/h , rounded off to two decimal places, is _____.

46. Let a random process $Y(t)$ be described as $Y(t) = h(t) * X(t) + Z(t)$, where $X(t)$ is a white noise process with power spectral density $S_X(f) = 5 \text{ W/Hz}$.

The filter $h(t)$ has a magnitude response given by $|H(f)| = 0.5$ for $-5 \leq f \leq 5$, and zero elsewhere. $Z(t)$ is a stationary random process, uncorrelated with $X(t)$, with power spectral density as shown in the figure. The power in $Y(t)$, in watts, is equal to _____ W (rounded off to two decimal places).

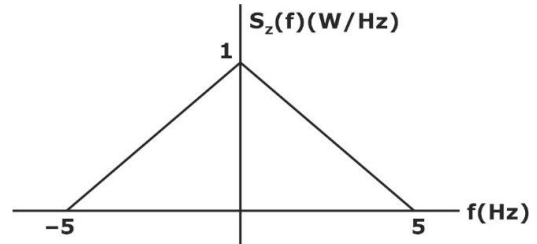

47. Let $h[n]$ be a length-7 discrete-time finite impulse response filter, given by $h[0] = 4, h[1] = 3, h[2] = 2, h[3] = 1, h[-1] = -3, h[-2] = -2, h[-3] = -1$, and $h[n]$ is zero for $[n] \geq 4$. A length-3 finite impulse response approximation $g[n]$ of $h[n]$ has to be obtained such that

$$E(h, g) = \int_{-\pi}^{\pi} |H(e^{j\omega}) - G(e^{j\omega})|^2 d\omega$$

is minimized, where $H(e^{j\omega})$ and $G(e^{j\omega})$ are the discrete-time Fourier transforms of $h[n]$ and $g[n]$, respectively. For the filter that minimizes $E(h, g)$, the value of $10g[-1] + g[1]$, rounded off to 2 decimal places, is _____.

48. In an ideal pn junction with an ideality factor of 1 at $T = 300 \text{ K}$ the magnitude of the reverse-bias voltage required to reach 75% of its reverse saturation current, rounded off to 2 decimal places, is _____ mV.

$$[k = 1.38 \times 10^{-23} \text{ J/K}^{-1}, h = 6.625 \times 10^{-34} \text{ J-s}, q = 1.602 \times 10^{-19} \text{ C}]$$

49. Consider the homogeneous ordinary differential equation


$$x^2 \frac{d^2y}{dx^2} - 3x \frac{dy}{dx} + 3y = 0, x > 0$$

with $y(x)$ as a general solution. Given that $y(1) = 1$ and $y(2) = 14$ the value of $y(1.5)$, rounded off to two decimal places, is _____.

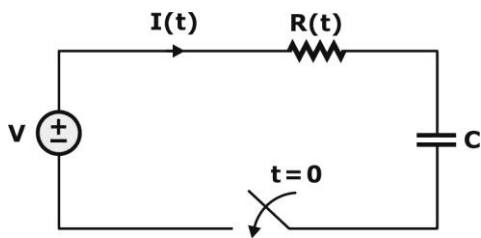
50. The RC circuit shown below has a variable resistance $R(t)$ given by the following expression :

$$R(t) = R_0 \left(1 - \frac{t}{T} \right) \text{ for } 0 \leq t < T$$

where $R_0 = 1 \Omega$, and $C = 1 \text{ F}$. We are also given that $T = 3 R_0 C$ and the source voltage is $V_s = 1 \text{ V}$. If the current at time $t = 0$ is 1 A , then the current $I(t)$, in amperes, at time $t = T/2$ is _____ (rounded off to 2 decimal places).



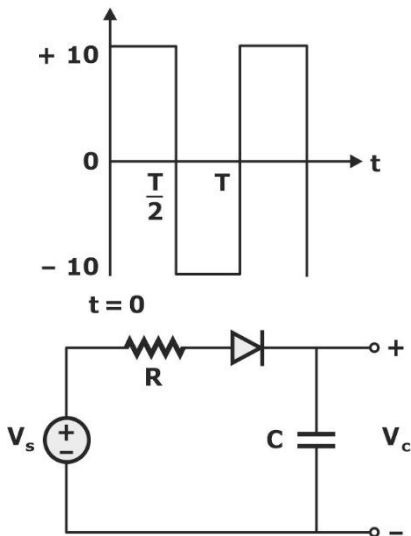51. In the circuit shown, V_s is a 10 V square wave of period, $T = 4 \text{ ms}$ with $R = 500 \Omega$ and $C = 10 \mu\text{F}$. The capacitor is initially uncharged at $t = 0$, and the diode is assumed to be ideal. The voltage across the capacitor (V_c) at 3 ms is equal to _____ volts (rounded off to one decimal place).




52. Consider the line integral

$$\int_C (x dy - y dx)$$

the integral being taken in a counterclock-wise direction over the closed curve C that forms the boundary of the region R shown in figure below. The region R is the area enclosed by the union of a $2 \times$

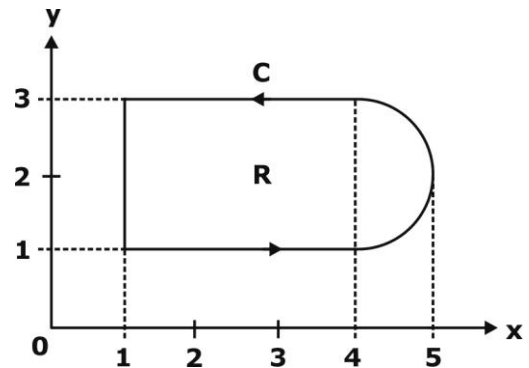3 rectangle and a semi-circle of radius 1. The line integral evaluates to




- A. $16 + 2\pi$
- B. $8 + \pi$
- C. $12 + 8\pi$
- D. $6 + \pi/2$

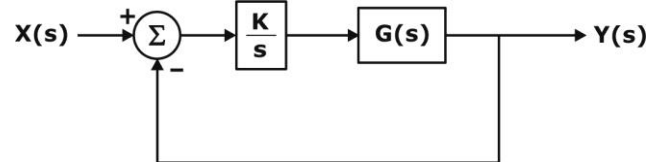53. Consider a unity feedback system, as in the figure shown, with an integral compensator and open-loop transfer function

$$G(s) = \frac{1}{s^2 + 3s + 2}$$

Where $K > 0$. The positive value of K for which there are exactly two poles of the unity feedback system on the $j\omega$ axis is equal to _____ (rounded off to two decimal places).



54. A voice signal $m(t)$ is in the frequency range 5 kHz to 15 kHz . The signal is amplitude-modulated to generate an AM signal $f(t) = A(1 + m(t)) \cos 2\pi f_c t$, where $f_c = 600 \text{ kHz}$. The AM signal $f(t)$ is to be digitized and archived. This is done by first sampling $f(t)$ at 1.2 times the Nyquist frequency, and then quantizing each sample using a 256-level quantizer. Finally, each quantized sample is binary coded using K bits, where K is the minimum number of bits required for the encoding. The rate, in Megabits per second (rounded off to 2 decimal places), of the resulting stream of coded bits is _____ Mbps.

55. A single bit, equally likely to be 0 and 1, is to be sent across an additive white Gaussian noise (AWGN) channel with power spectral density $N_0/2$. Binary signaling, with $0 \rightarrow p(t)$ and $1 \rightarrow q(t)$, is used for the

transmission, along with an optimal receiver that minimizes the bit-error probability.

Let $\phi_1(t)$, $\phi_2(t)$ form an orthonormal signal set.

If we choose $p(t) = \phi_1(t)$ and $q(t) = -\phi_1(t)$, we would obtain a certain bit-error probability P_b .

If we keep $p(t) = \phi_1(t)$, but take $q(t) = \sqrt{E} \phi_2(t)$, for what value of E would we obtain the same bit-error probability P_b ?

- | | |
|------|------|
| A. 3 | B. 2 |
| C. 0 | D. 1 |

Benefits of Online Classroom Program

1. GATE Learning Tablet

› Access high-quality classes at your convenience, anywhere and anytime with the tablet

2. Live Classroom Sessions

› Get Access to Live Classes By India's Leading GATE Faculty

3. Previous Year Question Books

› 20+ Years PYQs with Solutions

4. Workbooks

› Access to 3000+ Practice Questions with solutions

5. Regular Quizzes

› Sample Quizzes for daily practice and regular tests along with live class

6. Doubt Resolution

› Complete Doubt Resolution within 24 hours by Subject Experts

Additional Offerings

- › **Test Series** - Mock Tests based on GATE Exam pattern
- › **Preparation Guidance** - Get a competitive advantage from our Experts
- › **Subject wise formula Notes** - Comprehensive short notes for Revision
- › **Report Card** - Regular performance analysis along with Live Class

