

# Solved Paper 2014

## Electrical Engineering (Paper II)

1. (a) A copper wire has a resistance of  $0.85 \Omega$  at  $20^\circ\text{C}$ . What will be its resistance at  $40^\circ\text{C}$ ? Temperature coefficient of resistance of copper at  $0^\circ\text{C}$  is  $0.004^\circ\text{C}$ . (10)
- (b) In the circuit shown in Figure, what is the value of  $V$ ? (10)

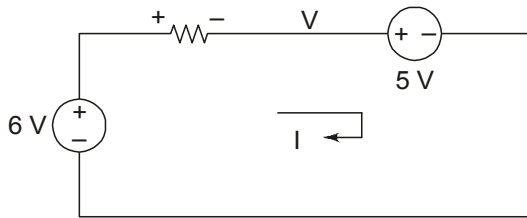


Figure 1

- (c) What is the value of Thevenin voltage  $E_{Th}$  in the given circuit of Figure? (10)

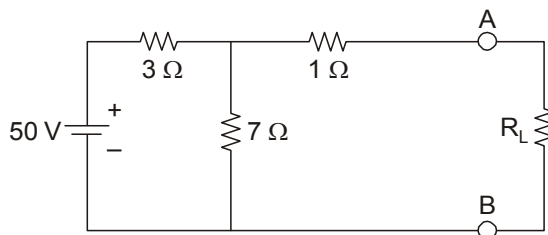


Figure 2

- (d) In Figure, find the value of resistance  $R$ . (30)

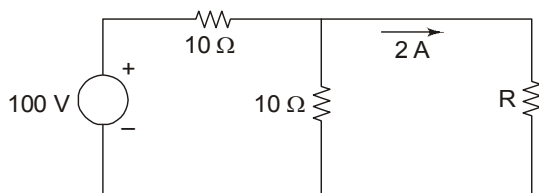


Figure 3

2. (a) Define the following terms: (20)
- Magnetic field intensity
  - Magnetic flux density
  - Magnetomotive force
  - Reluctance

- (b) In a pair of coupled coils, coil 1 has a continuous current of  $2\text{A}$  and the corresponding fluxes  $\phi_{11}$  and  $\phi_{21}$  are  $0.3$  and  $0.6$  mWb respectively. If the turns are  $N_1 = 500$  and  $N_2 = 500$ , find  $L_1$ ,  $L_2$ ,  $M$  and  $K$ . (10)
- (c) An AC voltage of  $50$  Hz has a maximum value of  $50\text{V}$ . What will be its voltage after  $1/600$  second? (10)
- (d) A circuit with a resistor, inductor, and capacitor in series is resonant of  $f_0$  Hz. If all the component values are now doubled. Find the new resonant frequency. (20)

3. (a) A  $100 \mu\text{A}$  ammeter has internal resistance of  $100\Omega$ . For extending its range to measure  $500\mu\text{A}$ , calculate the value of shunt resistance (in  $\Omega$ ). (10)
- (b) A wattmeter is connected as shown in Figure. What will be the wattmeter reading of power consumed either by  $Z_1$  or  $Z_2$ ? (10)

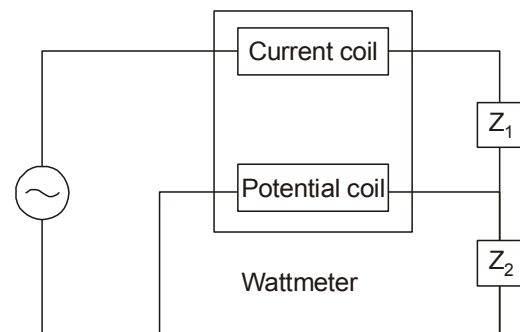


Figure 4

- (c) A CRO screen has ten divisions on the horizontal scale. If a voltage signal  $5 \sin(314t + 45^\circ)$  is examined with a line base setting of  $5$  msec/div, find the number of cycles of signal displayed on the screen. (20)
- (d) Prove that the power in AC circuit is equal to  $VI \cos \phi$ . (20)

**2 SOLVED PAPER 2014**

4. (a) Explain the various losses in DC machines. (20)
- (b) A DC machine induces an EMF of 240 V at 1500 rpm. Find the developed torque for an armature current of 25 A. (10)
- (c) A 3300/300 V single phase transformer gives 0.6 A and 60 W as ammeter and wattmeter reading when supply is given to the low voltage winding and high voltage winding is kept open. What is the power factor of no load current? (15)
- (d) A 3 hp, 3-phase 4-pole, 400V 50Hz induction motor runs at 1440 rpm. What will be the frequency of the rotor-induced EMF? (15)
5. (a) Explain the need for connecting a capacitor in the auxiliary winding of a single phase induction motor. (15)
- (b) Why are two alternators connected in parallel to supply a common load? What are the necessary conditions for parallel connection? (15)
- (c) What are the advantages and disadvantages of AC over DC? (15)
- (d) Overhead power transmission lines are preferred over underground power cables. Discuss. (8)
- (e) What are the main advantages of SF6 circuit breakers? (7)

6. (a) A residential flat has the following average electrical consumptions per day:
- (i) 4 tube lights of 40 watts working for 5 hours per day;
- (ii) 2 filaments of 60 watts working for 8 hours per day;
- (iii) 1 water heater rated 2 kW working for 1 hour per day;
- (iv) 1 water pump of 0.5 kW rating working for 3 hours per day.
- Calculate the cost of energy per month if 1 kWh of energy (i.e., 1 unit of energy) costs ₹3.50. (20)
- (b) Cite the advantages and disadvantages of electric drives. (20)
- (c) A silicon diode is connected across a 3V supply with a series resistance of  $20\Omega$  as shown in Figure. Neglecting diode resistance, find the diode current. (20)

