

# Electronics & Communication Engineering

GATE 100 Most Important Questions with Solutions

Byju's Exam Prep App

https://byjusexamprep.com



# **GATE 100 Most Important Questions with Solutions**

1. Consider the CMOS circuit shown in the figure (substrates are connected to their respective sources). The gate width (W) to gate length (L) ratios (W/L) of the transistors are as shown. Both the transistors have the same gate oxide capacitance per unit area. For the pMOSFET, the threshold voltage is -1 V and the mobility of holes is  $40 \text{cm}^2/\text{Vs}$ . For the nMOSFET, the threshold voltage is 1 V and the mobility of electrons is  $300 \text{cm}^2/\text{Vs}$ . The steady state output voltage V<sub>0</sub> is \_\_\_\_\_.



- A. equal to 0 V
- C. less than 2 V

B. more than 2 VD. equal to 2 V

# Ans. C

Sol. Given,

$$I_{D} = I_{DD} = I_{DD}$$

$$V_{DS} \ge V_{GS} - V_t$$
, always true.

From the given diagram  $V_G = V_D$  hence both MOSFET are in saturation

$$\begin{split} I_{Dn} &= \frac{1}{2} \mu_n C_{OX} \left( \frac{W}{L} \right)_n \left( V_{GS} - V_t \right)^2 \\ I_{Dp} &= \frac{1}{2} \mu_p C_{OX} \left( \frac{W}{L} \right)_p \left( V_{GS} - \left| V_t \right| \right)^2 \\ I_D &= I_{Dn} = I_{Dp} \\ \frac{1}{2} \mu_n C_{OX} \left( \frac{W}{L} \right)_n \left( V_{GS} - V_t \right)^2 = \frac{1}{2} \mu_p C_{OX} \left( \frac{W}{L} \right)_p \left( V_{GS} - \left| V_t \right| \right)^2 \\ \mu_n C_{OX} \left( \frac{W}{L} \right)_n \left( V_0 - V_S - V_t \right)^2 = \mu_p C_{OX} \left( \frac{W}{L} \right)_p \left( V_S - V_0 - \left| V_t \right| \right)^2 \\ 300 \times 1 \left( V_0 - 0 - 1 \right)^2 = 40 \times 5 \left( 4 - V_0 - 1 \right)^2 \end{split}$$



$$3(V_0 - 1)^2 = 2(3 - V_0)^2$$
  

$$3V_0^2 + 3 - 6V_0 = 18 + 2V_0^2 - 12V_0$$
  

$$V_0^2 + 6V_0 - 15 = 0$$
  

$$V_0 = \frac{-6 \pm \sqrt{36 + 60}}{2} = 1.89V, -789V$$

At  $V_0 = 1.89V$ , both MOSFET will be in saturation.

Hence, the correct option is (C).

2. The Fourier transform X(j $\omega$ ) of the signal x(t) =  $\frac{t}{(1+t^2)^2}$  is \_\_\_\_\_.

A. 
$$\frac{\pi}{2j} \omega e^{-|\omega|}$$
  
B.  $\frac{\pi}{2} \omega e^{-|\omega|}$   
C.  $\frac{\pi}{2j} e^{-|\omega|}$   
D.  $\frac{\pi}{2} e^{-|\omega|}$ 

# Ans. A

**Sol.** Consider,  $x(t) = e^{-|t|}$ 

By taking Fourier transform,

$$X(j\omega) = \frac{2}{1+\omega^2}$$
$$e^{-|t|} \longleftrightarrow \frac{F.T.}{1+\omega^2} \xrightarrow{2} \frac{2}{1+\omega^2}$$

By differentiation in frequency domain property,

$$t \mathbf{x}(t) \xleftarrow{F.T.} j \frac{d}{d\omega} X(\omega)$$
$$t e^{-|t|} \xleftarrow{F.T.} j \left[ \frac{d}{d\omega} \left( \frac{2}{1+\omega^2} \right) \right]$$
$$t e^{-|t|} \xleftarrow{F.T.} \frac{-4j\omega}{\left(1+\omega^2\right)^2}$$

Apply duality property,

$$\frac{-4jt}{(1+t^2)^2} \longleftrightarrow \frac{F.T.}{2\pi(-\omega)} 2\pi(-\omega) e^{-|\omega|}$$
$$\frac{t}{(1+t^2)^2} \longleftrightarrow \frac{F.T.}{-4j} \xrightarrow{-2\pi \omega e^{-|\omega|}}{-4j}$$
$$\frac{t}{(1+t^2)^2} \longleftrightarrow \frac{F.T.}{2j} \omega e^{-|\omega|}$$



3.





for what range of  $V_i(t)$  diode in the Breakdown region.

A. 
$$V_i(t) = 10 V$$
B.  $V_i(t) > 12 V$ C.  $V_i(t) > 11 V$ D. None

# Ans. B

**Sol.** From given V-I graph if is clear that diode breakdown voltage is -8 volt.

$$2 k\Omega$$

$$V_{ab} = 8 - 2$$

$$V_{ab} = 6V$$

$$V_{ab} = \frac{V_i(t) \times 2k\Omega}{2k\Omega + 2k\Omega}$$

$$V_{ab} = \frac{V_i(t)}{2}$$

So, diode will go in breakdown if  $V_{i}\left(t\right)$  > 12 V

- **4.** The system with input x(t) and output y(t) described as  $\frac{dy(t)}{dt} + 4t^2y(t) = 2tx(t)$ 
  - A. Linear and non causal
  - B. Non linear and causal
  - C. Linear and causal
  - D. non linear and non causal

Ans. C



#### Sol. Linearity:

For input  $x_1$  (t)

$$x_1(t) \rightarrow \frac{dy_1(t)}{dt} + 4t^2y_1(t) = 2tx_1(t) \dots(1)$$

For input x<sub>2</sub> (t)

$$x_2(t) \rightarrow \frac{dy_2(t)}{dt} + 4t^2y_2(t) = 2tx_2(t) \dots(2)$$

Multiply equ<sup>n</sup> (1) by a and equ<sup>n</sup> (2) by b and then adding

$$\frac{a \, dy_1(t)}{dt} + 4at^2y_1(t) + \frac{b \, dy_2(t)}{dt} + 4b \, t^2y_2(t) = 2at \, x_1(t) + 2b \, tx_2(t)$$

 $\frac{dt}{dt} [ay_1 (t) + by_2(t)] + 4t^2 [ay_1(t) + by_2(t)] = 2t [ax_2(t) + bx_2(t)]$ 

This equ<sup>n</sup> shows that for an input  $ax_1(t) + bx_2(t)$  output is  $ay_1(t) + by_2(t)$ , so system is linear. Causality: The output depends on the present input only therefore the system is causal.

**5.** A magnetic field strength of 10  $\mu$ A/m is required at point on  $\theta = \frac{\pi}{2}$ , 4 Km from an antenna in

air. Neglect ohmic loss. How much power (in Watt) must antenna transmitted if it is  $\frac{\pi}{2}$  dipole?

#### Ans. [2 to 2.5]

Sol.

$$\begin{aligned} \left| H_{68} \right| &= \frac{I_0 \cos\left(\frac{\pi}{2} \cos \theta\right)}{2\pi r \sin \theta} \\ 10 \times 10^{-6} &= \frac{I_0 \cos\left(\frac{\pi}{2} \cos\frac{\pi}{2}\right)}{2\pi \times 4 \times 10^3 \times \sin\frac{\pi}{2}} \\ 10 \times 10^{-6} &= \frac{I_0 \cos(\theta)}{2\pi \times 4 \times 10^3 \times 1} \\ 10 \times 10^{-6} &= \frac{I_0}{8\pi \times 10^3} \\ I_0 &= 80\pi \times 10^{-6} \times 10^3 \\ I_0 &= 80\pi \text{ mA} \\ P_{rad} &= \frac{1}{2} I_0^2 R_{rad} \\ P_{rad} &= \frac{1}{2} (80 \pi)^2 \times 73 \\ P_{rad} &= \frac{4606405.12 \times 10^{-6}}{2} \\ P_{rad} &= 2.3 \text{ w} \end{aligned}$$

**6.** Find value of k under resonance cond<sup>n</sup>.





# Ans. B

Sol. At resonance  $X_{eq} = 15$ 

$$2\pi f \left( M = k \sqrt{L_1 L_2} \right)$$
  

$$X_M = k \sqrt{X_1 X_2}$$
  

$$2\pi f \left( L_{eq} = L_1 + L_2 + 2 M \right)$$
  

$$X_{eq} = X_1 + X_2 + 2 X_M$$
  

$$X_{eq} = X_1 + X_2 + 2 k \sqrt{X_1 X_2}$$
  

$$15 = 6 + 7 + 2 k \sqrt{6 \times 7}$$
  

$$k = \frac{1}{\sqrt{42}}$$

Determine DTFT for given signal $x(n) = \{-4, -1, 0, 1, 4\}$  origin at 0A. 2j (4sin 2 $\Omega$  - sin  $\Omega$ )B. -2j (sin  $\Omega$  - 4 sin 2 $\Omega$ )C. 2j (sin  $\Omega$  + 4 sin 2 $\Omega$ )D. -2j (4sin 2 $\Omega$  + sin  $\Omega$ )

Ans. D

7.

**Sol.** 
$$X(e^{j\Omega}) = -4e^{2j\Omega} - 1.e^{j\Omega} + 0 + e^{-j\Omega} + 4e^{-2j\Omega}$$
  
 $= -4\left[e^{2j\Omega} - e^{-2j\Omega}\right] + (-1)\left[e^{j\Omega} - e^{j\Omega}\right]$   
 $= -4\frac{\left[e^{2j\Omega} - e^{-2j\Omega}\right]}{2j} \times 2j - 1.2j\frac{\left[e^{j\Omega} - e^{-j\Omega}\right]}{2j}$   
 $= -8j \sin 2\Omega - 2j \sin \Omega$   
 $= -2j \left[4 \sin 2\Omega + \sin \Omega\right]$   
**8.**  $Nd = 10^{16}/cm^{3}$   
 $V_{T} = 26mV$   
 $D_{n} = 35.1 cm^{2}/s$   
 $D_{p} = 12.48 cm^{2}/s$   
 $n_{i} = 1.5 \times 10^{10}/cm^{3}$   
 $A = 1 nm^{2}$   
Find the minority carries in N-Type semiconductor in length of semiconductor is 2nm?  
 $A. 10^{10}$   
 $B. 0$ 

C. 10<sup>12</sup> D. 10<sup>-3</sup>

2

# Ans. B



Sol. Total minority carriers

$$= \frac{n_{i}^{2}}{N_{D}} \times V$$

$$= \frac{n_{i}^{2}}{N_{D}} \times A \times L$$

$$= \frac{2.25 \times 10^{20}}{10^{16}} \times 10^{-14} \times 2 \times 10^{-7}$$

$$= 4.5 \times 10^{-17}$$

$$= 0$$
{L = 2 nm ; L = 2 × 10^{-7} cm  
A = 1 nm^{2}; A = 1 × (10^{-7})^{2} cm^{2}
$$A = 10^{-14}$$
Sk0





Find io

A. 1 mA

C. 5 mA

B. 2 mA D. – 2 mA

# Ans. B

Sol. It is a comparator

V+ = 8V

$$V^{-} = \frac{10 \times 5}{5 + 5} = \frac{10}{2} = 5 V$$
  
If, V<sup>+</sup> > V<sup>-</sup>; V<sub>out</sub> = + V<sub>sat</sub> = 10 V  
V<sup>+</sup> < V<sup>-</sup>; V<sub>out</sub> = - V<sub>sat</sub> = -10 V  
Here, V<sup>+</sup> > V<sup>-</sup>

So, 
$$V_{out} = 10 V$$

$$I'_{o} = \frac{10}{5 \text{ k}\Omega} = 2 \text{ mA}$$

**10.** The Laplace transform of a signal x(t) is

$$x(s) = \frac{d^2}{ds^2} \left(\frac{1}{s-8}\right), ROC: R_e(s) > 8$$

The signal  $x(t) = (te^{kt})^2 U(t)$ , where constant k is

- A. 2 B. 6
- C. 4 D. 3

#### Ans. C

## Sol.

$$\frac{1}{s-8} \xleftarrow{L^{-1}}{e^{8t}} U(t)$$

$$\frac{d^2}{ds^2} \left\{ \frac{1}{s-8} \right\} \xleftarrow{L^{-1}}{t^2} e^{8t} U(t)$$

$$\frac{d^2}{ds^2} \left\{ \frac{1}{s-8} \right\} \xleftarrow{L^{-1}}{t^2} \left( t e^{kt} \right)^2 U(t)$$

$$2k = 8$$

$$K = 4$$

11.



**12.** A signal uniformly distributed on [-1, 1] is baseband modulated using PCM with 128 levels. Calculate the resulting SQNR?

A. 36 dB	B. 42 dB
C. 48 dB	D. 30 dB



# Ans. B

**Sol.** The pdf of the signal given will be:

$$f_{x}(x)$$

$$1/2$$

$$-1$$

$$1 \rightarrow x$$

The power of the signal is given by

$$P_{s} = \int_{-\infty}^{\infty} x^{2} f_{X}(x) dx$$
  

$$\Rightarrow P_{s} = \int_{-1}^{1} \frac{1}{2} x^{2} dx = \frac{1}{3}$$
  
n = log<sub>2</sub> 128 = 7 bits  
SQNR = P\_{s}/P\_{N}  
Where  $P_{N} = \frac{\Delta^{2}}{12}$  and  $\Delta = \frac{2A_{m}}{L} = \frac{2}{128} = \frac{1}{64}$   

$$\Rightarrow P_{N} = \frac{1}{64^{2} \times 12}$$
  

$$\Rightarrow SQNR = 16384$$
  

$$\Rightarrow SQNR (dB) = 10log_{10}(SQNR) = 42 dB$$

**13.** Two  $\lambda/4$  transformer lines are used to connect a 50 $\Omega$  line to a 70 $\Omega$  load. Determine characteristic impedance Z<sub>01</sub> if Z<sub>02</sub> = 30 $\Omega$ .

Assume there is no reflection to the t of A.







$$(Z_{01})^2 = Z_{in_1} \times Z_{in_2}$$
  
=  $Z_{in_1} \times \frac{(30)^2}{70}$ 

There is no reflection to left to A so

$$Z_{in_{1}} = Z_{0}$$

$$Z_{in_{1}} = 50$$
So,
$$(Z_{01})^{2} = 50 \times \frac{(30)^{2}}{70}$$

$$Z_{01} = \sqrt{\frac{(30)^{2} \times 50}{70}}$$

$$Z_{01} = 30\sqrt{\frac{50}{70}}$$

$$Z_{01} = 30 \times .85$$

$$Z_{01} = 30 \times .85$$

14. For circuit Diode is ideal plot V<sub>0</sub> versus Vi is



**Sol.** Voltage at cathode terminal =  $\frac{10 \times 2}{4} = 5V$ So, for V<sub>i</sub> (anode) < 5V Diode is open circuit  $V_0 = V_i$ For  $V_i$  (anode)> 5V diode is short circuit So, Circuit will be



2 kΩ **≧1 kΩ** <sup>≦</sup>2 kΩ ٧o 10 V( V. Write KCL,  $\frac{V_{_{0}}}{2K}+\frac{V_{_{0}}-10}{2k\Omega}+\frac{V_{_{0}}-V_{_{i}}}{1k\Omega}=0$  $V_0 + V_0 - 10 + 2V_0 - 2V_i = 0$  $4V_0 - 2V_i = 10$  $4V_0 = 2V_i + 10$  $V_0 = .5 V_i + 2.5$ So, If Vi = 10  $V_0 = 7.5 v$ 15. A sum of money is to be distributed among P, Q, R, and S in the proportion 5 : 2 : 4 : 3, respectively. If R gets ₹ 1000 more than S, what is the share of Q (in ₹)? A. 500 B. 1000 C. 1500 D. 2000 Ans. D **Sol.** P:Q:R:S = 5:2:4:3 Money of P = 5xMoney of Q = 2xMoney of R = 4xMoney of S = 3xMoney of R = 1000 + Money of Si.e. 4x = 1000 + 3xx = 1000Now, Money of Q = 2x= 2000 **16.** If the vectors (1.0, -1.0, 2.0), (7.0, 3.0, x) and (2.0, 3.0, 1.0) in R<sup>3</sup> are linearly dependent the value of x is \_\_\_\_ **Ans.** 8 Sol. Given vectors are  $x_1 = [1 - 1 2]$  $x_2 = [7, 3x]$  $x_3 = [2 3 1]$ are linearly dependent Let,  $\mathbf{A} = \begin{bmatrix} \mathbf{X}_1^{\mathsf{T}} \mathbf{X}_2^{\mathsf{T}} \mathbf{X}_3^{\mathsf{T}} \end{bmatrix}$ 

$$A = \begin{bmatrix} 1 & 7 & 2 \\ -1 & 3 & 3 \\ 2 & x & 1 \end{bmatrix}_{3 \times 3}$$
  
Rank (A) < order of 3  
 $\because$  rank (A) < 3  
 $\Rightarrow$  A should be singular matrix |A| = 0  
 $\Rightarrow \begin{bmatrix} 1 & 7 & 2 \\ -1 & 3 & 3 \\ 2 & x & 1 \end{bmatrix} = 0$   
 $\Rightarrow 1 \times (3 - 3x) - 7x (-1 - 6) + 2 \times (-x - 6) = 0$   
 $\Rightarrow -5x + 40 \Rightarrow x = 8$ 

- 17. A digital transmission system uses a (7,4) systematic linear Hamming code for transmitting data over a noisy channel. If three of the message –codeword pairs in this code (m<sub>i</sub>; c<sub>i</sub>) where c<sub>i</sub> is the codeword corresponding to the i<sup>th</sup> message m<sub>i</sub>, are known to be (1100;0101100), (1110;0011110) and (0110; 1000110), then which of the following is a valid codeword in this code?
  - A. 0110100B. 1011010C. 0001011D. 1101001

# Ans. C

Sol. Given code is systematic linear hamming code of order (7, 4)

Given message and code word pairs are

1100; 0101100

- 1110; 0011110
- 0110; 1000110

The code word is of the form

```
p1 p2 p3 d1 d2 d3 d4
```

```
where P_1 = d_1 \oplus d_2 \oplus d_4
```

 $P_2 = d_2 \oplus d_3 \oplus d_4$ 

 $P_3 = d_1 \oplus d_2 \oplus d_3$ 

The code word which satisfies this pattern is 0001011

- $\therefore$  option 'C' (or) option '3' is answer.
- **18.** Find resp. of  $V_c$  i<sub>c</sub>, &  $V_x$  when initial voltage of cap. Is 3V.



#### Ans. A

#### Sol.



In steady state cap. Without source

 $V_{c} = 0 \text{ (cap. Discharge through R)}$   $V_{c} (0^{-}) = V_{c} (0^{+}) = 3V \text{ (given)}$   $R_{eq} = 8||8 = 4$ Cap. Is without source.  $V_{c} = 3 e^{-t/4 \times .5}$   $\boxed{V_{c} (t) = 3 e^{-\frac{t}{2}}}$   $i_{c} = \frac{C \, dV}{dt} = .5 \times 3 \frac{d}{dt} e^{-t/2}$   $i_{c} = -\frac{1.5}{2} e^{-t/2}$   $\boxed{i_{c} = -.75 e^{-\frac{t}{2}}}$   $V_{x} = \frac{V_{c} \times 2}{6+2}$   $\boxed{V_{x} = \frac{V_{c} \times 2}{6+2}}$ 

**19.** An 8 bit digital data 10101100 is fed to an DAC. The reference voltage is +5V. Analog output voltage will be:

A. 1.05	B. 3.372
C. 4.5	D. 5.15

#### Ans. B

 $i/p = 10101100 = (172)_{10}$  $V_{out} = \frac{V_R}{2^n - 1} \times 172$  $= \frac{5 \times 172}{2^8 - 1} = \frac{5 \times 172}{255}$  $= \frac{860}{255} = 3.372$ 

# B BYJU'S

#### **20.** The state equation Of LTI system is represented by

$$\overset{\circ}{X} = \begin{bmatrix} 0 & 1 \\ -4 & 0 \end{bmatrix} X + \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} U$$

Eigen value are

# Ans. C

```
Sol. For Eigen value,
```

$$|SI - A| = 0$$

$$(SI - 1) = \begin{bmatrix} s & -1 \\ 4 & s \end{bmatrix}$$

$$|SI - A| = S^{2} + 4$$

$$|SI - A| = 0$$

$$S^{2} + 4 = 0$$

$$S^{2} = -4, S = \pm 2j$$
**21.** Given  $L^{-1} \begin{bmatrix} 3s + 4 \\ s^{2} + 4s + (k - 2)s \end{bmatrix}$ 

if  $\lim_{t \to \infty} f(t) = 1$ , then value of k is

- A. 1
- C. 3

Ans. B

```
Sol. \lim_{t\to\infty} f(t) = \lim_{s\to 0} sF(s)
```

$$\lim_{s \to 0} s \cdot \left[ \frac{(3s+4)}{s[s+4+(k-2)]} \right] = 1$$
$$\lim_{s \to 0} \frac{3s+4}{s+4+k-2} = 1$$
$$\frac{4}{4+k-2} = 1$$
$$4 = 4 + k - 2 \Rightarrow k = 2$$

**22.** A ideal long silicon *pn* junction diode is shown in fig. The n-region is doped with  $10^{16}$  organic atoms per cm<sup>3</sup> and the *p* - region is doped with  $5 \times 10^{16}$  boron atoms per cm<sup>3</sup>. The minority carrier lifetime of holes are  $10^{-8}$  seconds and diffusion constant is  $D_n = 23$  cm<sup>2</sup>/s and  $D_p = 8$  cm<sup>2</sup>/s.

B. 2

D. 0

The forward-bias voltage is  $V_a = 0.61V$ 





The excess hole concentration is

A.  $6.8 \times 10^{12} e^{-246x} \text{ cm}^{-3}, x \ge 0$ B.  $6.8 \times 10^{12} e^{246x} \text{ cm}^{-3}, x \ge 0$ 

C.  $3.8 \times 10^{14} e^{-353x} \text{ cm}^{-3}, x \ge 0$  D.  $3.8 \times 10^{14} e^{3534x} \text{ cm}^{-3}, x \ge 0$ 

Ans. D

Sol. 
$$\delta p_n = p_n - p_{no} = p_{no} \left[ e^{\frac{eV_a}{kT}} - 1 \right] \left[ e^{-\left(\frac{x}{L_p}\right)} \right]$$
  
 $p_{no} = \frac{n_i^2}{N_d} = \frac{\left(1.5 \times 10^{10}\right)^2}{10^{16}} = 2.25 \times 10^4 \, cm^{-3}$   
 $L_p = \sqrt{D_p \tau_{po}} = \sqrt{8 \times 10^{-8}} = 2.83 \times 10^{-4} \, cm$   
 $\delta p_n = 2.25 \times 10^4 \left[ e^{\left(\frac{0.61}{0.0259}\right) - 1} \right] \left[ e^{-\left(\frac{x}{2.83 \times 10^{-4}}\right)} \right] = 3.8 \times 10^{14} e^{-3534x} \, cm^{-3}$ 

**23.** The electrical system shown in the figure converts input source current  $i_s(t)$  to output voltage  $v_o(t)$ 



Current  $i_L(t)$  in the inductor and voltage  $v_c(t)$  across the capacitor are taken as the state variables, both assumed to be initially equal to zero, i.e.,  $i_L(0) = 0$  and  $v_0(0) = 0$  The system is A. neither state controllable nor observable

B. completely state controllable but not observable

C. completely observable but not state controllable

D. completely state controllable as well as completely observable

#### Ans. A

Sol. 
$$i_s = i_L + \frac{V_L}{1}$$
  
 $i_s = i_L + L \frac{di_L}{dt} \dots (1)$   
 $i_s = i_C + \frac{V_C}{1}$   
 $i_C = C \frac{d V_C}{dt} \dots (2)$   
Let  $i_L = x_1$   
 $V_C = x_2$   
 $i_s = u = input$   
 $1. \Rightarrow \frac{L \frac{d}{dt} x_1 + x_1 = u}{x_{.1} = \frac{-1}{L} x_1 + \frac{1}{L} u}$ 



$$2. \Rightarrow \frac{C \frac{d}{dt} x_2 + x_2 = u}{\dot{x}_2 = -\frac{1}{C} x_2 + \frac{1}{C} u}$$

Output,  $y(t) = V_{C}(t) = x_{2}(t)$ 

So, we have

$$\dot{\mathbf{x}} = \begin{pmatrix} -\frac{1}{L} & \mathbf{0} \\ \mathbf{0} & -\frac{1}{C} \end{pmatrix} \mathbf{x} + \begin{pmatrix} \mathbf{1}/L \\ \mathbf{1}/C \end{pmatrix} \mathbf{u}$$

$$y = x_2$$

y =(0 1) x

Putting L = 1H and C = 1F we get

$$\dot{x} = \begin{pmatrix} -1 & 0 \\ 0 & -1 \end{pmatrix} x + \begin{pmatrix} 1 \\ 1 \end{pmatrix} u$$

$$y = x_2$$

y = (0 1) x

Controllability Matrix

$$S = \begin{bmatrix} B & AB \end{bmatrix} = \begin{bmatrix} 1 & -1 \\ 1 & -1 \end{bmatrix}$$

 $|S| = 0 \Rightarrow$  uncontrollable

**Observability Matrix** 

$$V = \begin{bmatrix} C \\ CA \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ 0 & -1 \end{bmatrix}$$

 $|V| = 0 \Rightarrow$  unobservable



Ans. C

#### Sol.

at t=0-







at t =  $0^+$ 







25. An air filled rectangular wave guide is operating at 6 GHz with dominant propagating inside it. If the wavelength inside the wave guide is 6cm, then the wave impedance of the mode is given by \_\_\_\_\_\_Ω.

A. 245	5.6	B. 345.6
C. 452	2.4	D. 568.6

# Ans. C

**Sol.** Given, f = 6GHz

$$\lambda = \frac{c}{f} = 5cm$$

$$\lambda_{a} = 6cm$$

Mode =  $TE_{10}$ 

Wave impedance

$$\eta_{\tau \epsilon} = \eta \frac{\lambda_{\epsilon}}{\lambda} = 120\pi \times \frac{6}{5}$$
$$\eta_{\tau \epsilon} = 452.4\Omega$$

**26.** A message signal m(t) and a carrier signal C(t) are applied to an amplitude modulation shown

The message signal m(t) is band-limited to  $f_m$ , where  $f_c \gg 3f_m$ . The BPF has a unity passband gain over a Bandwidth of  $2f_m$  centred at  $f_c$ . The input-output characteristic of non-linear device is y(t) =  $8x(t) + 2x^2(t)$ . If average power of message signal m(t) is 16W, find the % transmission efficiency of resultant AM signal.

- A. 40 B. 60
- C. 80 D. 90

Ans. C

**Sol.**  $x(t) = m(t) + cos2nf_ct$ 

$$y(t) = 8x(t) + 2x^2(t)$$

$$= 8[m(t) + \cos 2\pi f_c t] + 2[m(t) + \cos 2\pi f_c t]^2$$

 $= 8 m(t) + 8\cos 2\pi f_c t + 2m^2(t) + 2\cos^2 2\pi f_c t + 4m(t) \cos 2\pi f_c t$ 

After passing through BPF, we get

$$y(t) = 8\cos 2\pi f_c t + 4m(t) \cos 2\pi f_c t$$

$$=8\left[1+\frac{1m(t)}{2}\right]\cos 2\pi f_{c}t$$

The amplitude sensitivity of resultant AM signal is  $K_a = \frac{1}{2} V^{-1}$ 

The transmission efficiency of resultant AM signal is



$$\%\eta = \left(\frac{K_a^2 P_m}{1 + K_a^2 P_m} \times 100\right)\%$$

 $P_m$  = message signal power = 16W

$$\%\eta = \left(\frac{\left(\frac{1}{2}\right)^2 \times 16}{1 + \left(\frac{1}{2}\right)^2 \times 16}\right) \times 100\% = 80\%$$

27. How many 1's are present in binary representation of

7 × 64 + 5 × 8 + 3 A. 8 B. 9 C. 7 D. 10

Ans. C

```
Sol. (2^2 + 2 + 1) \times 2^6 + (2^2 + 1) \times 2^3 + (2 + 1)

2^8 + 2^7 + 2^6 + 2^5 + 2^3 + 2^1 + 2^0

1 1 1 1 0 1 0 1 1

So, Ans is 7
```

**28.** X is random variable with uniform probability density function in the interval [-2, 10]. For Y = 2X - 6, the conditional probability  $P(Y \le 7 | X \ge 5)$  (rounded off to three decimal places) is .....

**Ans.** 0.3

**Sol.** Given (0.3 to 0.3)

$$f_{x}(x) = \begin{cases} 1/12 & -2 \le x \le 10 \\ 0 & \text{otherwise} \end{cases}$$

As y = 2x - 6

So,

$$f_{y}(y) = \begin{cases} 1/24 & -10 \le x \le 14 \\ 0 & \text{otherwise} \end{cases}$$

If  $x \ge 5$  then  $y \ge 4$ 

So, 
$$P(y \le 7/x \ge 5) = P(Y \le 7/y \ge 4)$$

$$=\frac{P(4 \le y \le 7)}{P(4 \le y \le 14)} = \frac{3}{10} = 0.3$$





**29.** The block diagram of a closed-loop control system is shown in the figure. R(s), Y(s), and D(s) are the Laplace transforms of the time-domain signals r(t), y(t), and d(t), respectively. Let the error signal be defined as e(t) = r(t) - y(t). Assuming the reference input r(t) = 0 for all t, the steady-state error  $e(\infty)$ , due to a unit step disturbance d(t), is \_\_\_\_ (rounded off to two decimal places).







$$G_1(s) = 10, \quad G_2(s) = \frac{1}{s(s+10)}$$

$$\frac{E(s)}{D(s)} = \frac{-G_2(s)}{1 + G_1(s)G_2(s)}$$

$$= \frac{\frac{-1}{s(s+10)}}{1 + \left(10 \times \frac{1}{s(s+10)}\right)}$$
$$= \frac{-1}{s^2 + 10s + 10}$$
$$D(s) = \frac{1}{s}$$
 (Given in the question)
$$e_{ss} = \lim_{t \to \infty} e(t) = \lim_{t \to \infty} E(s)$$

$$e_{ss} = \lim_{s \to 0} \frac{s(\frac{1}{s})(-1)}{s^{2} + 10s + 10}$$
$$e_{ss} = \frac{-1}{10}$$

**30.** The magnetic field of a uniform plane wave in vacuum is given by

$$\vec{H}(x, y, z, t) = (\hat{a}_x + 2\hat{a}_y + b\hat{a}_z)\cos(\omega t + 3x - y - z)$$

The value of b is .....

**Ans.** 1



# Sol. Given,

$$\vec{H}(x, y, z, t) = (\hat{a}_x + 2\hat{a}_y + b + \hat{a}_z) \cdot \cos(\omega t + 3x - y - z)A / m$$

For a uniform wave,

 $\vec{k} \cdot \vec{H}_{o} = 0, \vec{k} \cdot \vec{E}_{o} = 0, \vec{E}_{o} \cdot \vec{H}_{o} = 0$ 

i.e.,  $\vec{E}\,,\,\vec{H}$  and  $\vec{K}$  are mutually perpendicular to each other.

 $(\vec{K}$  is the vector along the direction of wave propagation)

Comparing the given expression of  $\vec{H}$  with the standard expression.

$$k = 3 a_x - a_y - a_z$$

$$\vec{H}_{o} = (\hat{a}_{x} + 2\hat{a}_{y} + b\hat{a}_{z})$$

Then,

$$\vec{k}\cdot\vec{H}_{o}=3-2-b=0$$

- **31.** A sinusoidal message signal having root mean square value of 4 V and frequency of 1 kHz is fed to a phase modulator with phase deviation constant 2 rad/volt. If the carrier signal is  $c(t) = 2 \cos (2\pi 10^6 t)$ , the maximum instantaneous frequency of the phase modulated signal KHz.
- Α

c(c) = 2 cos (2110 c), the maximum instantaneous  
(rounded off to one decimal place) is \_\_\_\_\_ KHz.  
Ans. [1010 to 1013]  
Sol. m(t)<sub>rms</sub>= 4V  

$$\frac{d}{dt}m(t) = 4\sqrt{2} \times 2\pi \times 10^{3} \cos(2\pi \times 10^{3} t)$$
m(t) =  $4\sqrt{2}$   

$$\frac{dm(t)}{dt} = 4\sqrt{2} \times 2\pi \times 10^{3}$$
K<sub>p</sub> = 2 rad / volt  
PM:  $\theta(t) = w_{c} t + k_{p}m(t)$   
 $w_{i}(t) = w_{c} t + k_{p}m(t)$   
 $w_{i}(t) = w_{c} + k_{p} \frac{dm(t)}{dt}$   
 $f_{Maximum} = f_{c} + \frac{K_{p}}{2\pi} \cdot \left[\frac{dm(t)}{dt}\right]$   
 $f_{max} = 1000 \times 10^{3} + \frac{2}{2\pi} \times 4\sqrt{2} \times 2\pi \times 10^{3} Hz$   
 $f_{Maximum} = (1000 + 8\sqrt{2})$ kHz  
 $f_{Maximum} = (1000 + 11.3137)$ kHz  
 $f_{Maximum} = 1011.3137$  kHz



**32.** A germanium sample of dimensions 1 cm  $\times$  1 cm is illuminated with a 20 mW, 600 nm laser light source as shown in the figure. The illuminated sample surface has a 100 nm of loss-less Silicon dioxide layer that reflects one-fourth of the incident light. From the remaining light, one-third of the power is reflected from the Silicon dixodie-Germanium interface, one-third is absorbed in the Germanium layer, and one-third is transmitted through the other side of the sample. If the absorption coefficient of Germanium at 600 nm is 3  $\times$  10<sup>4</sup> cm<sup>-1</sup> and the bandgap is 0.66 eV, the thickness of the Germanium layer, rounded off to 3 decimal places, is \_\_\_\_\_µm.



$$3 \times 10^{-1}$$
  
.: x = 0.231 µm

**33.** Consider the circuit shown with an ideal OPAMP. The output voltage V<sub>0</sub> is \_\_\_\_\_V (rounded off to two decimal places).



**Ans.** [-0.55 to -0.45]

Sol.



B BYJU'S

Now we get,



Hence, the correct answer is - 0.5V.

**34.** Consider a unity feedback system as in the figure shown

$$X(s) + \sum_{k} - K_{k} - G(s) - Y(s)$$

with transfer function as  $G(s) = \frac{1}{s^2 + 3s + 2}$ , where K > 0,

Find the positive value of K for which there are exactly two poles of the unity feedback system on the  $j\omega$  axis is equal to \_\_\_\_\_ (rounded off to two decimal places).

# **Ans.** 6

Sol. Overall

$$G_{C}(s) = \frac{K}{s(s^{2}+3s+2)}$$
  

$$\therefore q(s) = s^{3}+3s^{2}+2s+k = 0$$
  

$$s^{3} \begin{vmatrix} 1 & 2 \\ 3 & k \\ s^{1} & \frac{6-k}{3} \\ s^{0} & k \end{vmatrix}$$

Auxiliary equation is  $3s^2 + k = 0$ And for roots on imaginary axis  $s^1$  row = 0

$$\therefore \frac{6-k}{3} = 0$$
$$\therefore k = 6$$

**35.** The switch in the circuit in the figure is in position P for a long time and moved to position Q at time t = 0





The value of 
$$\frac{dv(t)}{dt}$$
 at t = 0<sup>+</sup> is  
A. - 5 V/s B. 3 V/s  
C. - 3 V/s D. 0 V/s

#### Ans. C

**Sol.** At t = 0<sup>-</sup>



$$20 \begin{array}{c} \downarrow \\ \text{Volt} \end{array} \qquad 20 \begin{array}{c} \downarrow \\ 20 \\ \text{k}_{2} \end{array} \qquad 10 \\ \downarrow \\ i_{c}(0^{+}) + \frac{10}{5} + 1 = 0 \\ \Rightarrow i_{c}(0^{-}) = -3 \\ \text{mA} \end{array}$$

 $\frac{dV_{c}(0^{+})}{dt} = \frac{i_{c}(0^{+})}{C} = \frac{-3mA}{1mF} = -3volt/sec$ 

**36.** A simple closed path *C* in the complex plane is shown in the figure. If

$$\oint_C \frac{2^z}{Z^2 - 1} dz = -i\pi A$$

Where  $i = \sqrt{-1}$ , then the value of A is \_\_\_\_ (rounded off to two decimal places).



1mA

**Ans.** [0.5 to 0.5]



Sol.  $\oint \frac{2^z}{z^2 - 1} dx = -i \pi A$ LHS  $\oint_C \frac{2^z}{z^2 - 1} dz = \frac{1}{2} \oint_C \frac{2^z}{z^2 - 1} dz - \frac{1}{2} \oint_C \frac{2^z}{z^2 - 1} dz$ 

For pole z = 1 does not lie inside the close path counter so apply cauchy's integral theorem  $\frac{1}{2} \oint \frac{2^z}{dz} dz = 0$ 

$$\frac{1}{2}\oint \frac{z}{z-1} dz = 0$$

Z = -1 lie inside the close path C. So,  $-\frac{1}{2}\oint \frac{2^z}{z+1}dz = -\frac{1}{2} \times 2\pi i \times 2^{-1} = \frac{-1}{2}\pi i$ 

$$\oint_C \frac{2^z}{z^2 - 1} dz = \frac{1}{2} \oint_C \frac{2^z}{z^2 - 1} dz - \frac{1}{2} \oint_C \frac{2^z}{z^2 - 1} dz = 0 + \frac{-1}{2} \pi i$$

37. The stack pointer of an 8085 micro-processor is ABCDH. At the end of execution of the sequence of instructions, what will be the content of the stack pointer?PUSH PSW

XTHL

- PUSH D
- JMP FC70H
- A. ABCBH
- C. ABC9H

```
B. ABCAHD. ABC8H
```

```
Ans. C
```

- Sol. Push instruction decreases the stack pointer by 2.
  - $\therefore$  Two push instruction in programme decrement it by 4.
  - $\therefore$  SP = ABCD 4 = ABC9H
- **38.** The Nyquist sampling rate of the signal  $x(t) = 4 \operatorname{Sinc}^2 (10^4 t) \operatorname{sinc}^2 (10^6 t)$  is \_\_\_\_\_ MHz (upto two decimal points)
- **Ans.** [2.01 to 2.09]

# Sol.

 $\sin ct \xleftarrow{CIFT} \operatorname{rect}(f)$   $\sin c(10^{\circ}t) \longleftrightarrow \operatorname{rect}[f/10^{\circ}] \longleftrightarrow \underbrace{-5}_{-5} f(kHz)$   $\sin c^{2}(10^{\circ}t) \xleftarrow{CIFT} \underbrace{-10}_{-10} f(kHz)$   $4\sin c^{2}(10^{\circ}t) \xleftarrow{CIFT} \underbrace{-10}_{-10} f(kHz)$   $\sin c^{2}(10^{\circ}t) \xleftarrow{CIFT} \underbrace{-10}_{-10} f(kHz)$ 



 $f_{max} = 1000 + 10$ = 1010 KHz = 1.01 MHz Nyquist sampling rate  $f_{s(min)} = 2f_{max}$ = 2 (1010) KHz = 2.02 MHz

**39.** The electric field in free space is given by  $E = 100 \cos(10^8 + \frac{1}{3} \cdot X) a_y V/m$ . Calculate the time it

take to travel a distance of  $\lambda/2$ .

A. 30 ns	B. 31 ns
C. 31.42 ns	D. 32 ns

#### Ans. C

**Sol.** Distance =  $\frac{\lambda}{2}$ 

Wave Traveling at speed of light C =  $3 \times 10^8$  m/s. So, Distance = Speed × Time

$$\frac{\lambda}{2} = C \times T$$
  
T -  $\frac{\lambda}{2}$ 

$$\lambda = \frac{2\pi}{\beta}$$

$$E = 100 \cos \left( 10^8 t + \frac{1}{2} x \right) ay$$

So, 
$$\beta = \frac{1}{3}$$
  
 $\lambda = \frac{2\pi}{\frac{1}{3}} = 6\pi$   
 $\lambda = 6\pi$   
 $T = \frac{6\pi}{2 \times (3 \times 10^8)}$ 

$$T = 31.42 \text{ ns}$$

**40.** The state space representation of a control system is given by

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -2 & -3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} u ;$$
$$x(0) = \begin{bmatrix} 1 \\ 1 \end{bmatrix} ;$$
$$y = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

The transfer function of above system will be

A. 
$$\frac{1}{s^2 + 3s + 2}$$
  
B.  $\frac{1}{s^2 + 6s + 4}$   
C.  $\frac{4}{s^2 + 3s + 8}$   
D.  $\frac{6}{s^2 + 6s + 8}$ 



# Ans. A

Sol. Transfer function

$$\frac{Y(s)}{u(s)} = T(s) = c[SI - A]^{-1}B + D$$
  
=  $\begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} s & -1 \\ 2 & s+3 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix}$   
=  $\frac{\begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} s+3 & 1 \\ -2 & s \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix}$   
=  $\frac{1}{(s+1)(s+2)}$   
=  $\frac{1}{s^2 + 3s + 2}$ 

**41.** A silicon NMOS has gate width 95  $\mu$ m length 1.5  $\mu$ m, t<sub>ox</sub> = 0.2  $\mu$ m. Relative permittivity of oxide is 3.9,  $\mu$ n = 0.08 m<sup>2</sup>/v-s. Calculate the trans conductance of device in triode region for drain voltage of 2V.

A. 6.9 × $10^{-4}$ S	B. 6.9 × 10 <sup>-2</sup> S
C. 1.749 × 10 <sup>-3</sup> S	D. 1.45 × 10 <sup>-5</sup> S

# Ans. C

Sol. Given that,

L = 1.5 μm W = 95 μm

t<sub>ox</sub> = 0.2 μm

$$\because C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 \times 8.85 \times 10^{-12}}{0.2 \times 10^{-6}}$$

 $C_{ox} = 1.7265 \times 10^{-4} \text{ F/m}^2$ 

In triode region

$$g = \mu_n C_{ox} \frac{W}{L} \cdot V_{DS}$$

 $= 0.08 \times 1.7265 \times 10^{-4} \times \frac{95}{1.5} \times 2$ 

 $g = 1.749 \times 10^{-3}S$ 

**42.** The value of 
$$\int_{0}^{1} \frac{e^{x}}{e^{2x} + 1} dx$$
 \_\_\_\_\_

Α.	$\tan^{-1}(e) + \frac{\pi}{4}$	в.	$\tan^{-1}(e) - \frac{\pi}{4}$
C.	$\frac{\pi}{4}$	D.	$\tan^{-1}(e) + \frac{\pi}{2}$

#### Ans. B

**Sol.** Put  $e^x = t$  $e^x dx = dt$ limit x = 0, t = 1x = 1, t = e



So, 
$$\int_{1}^{e} \frac{1}{t^2 + 1} dt$$

- $= \left[ \tan^{-1} t \right]_{1}^{e}$
- $= \tan^{-1}(e) \tan^{-1}(1)$
- $= \tan^{-1}(e) \pi/4$
- **43.** In the voltage regulator shown below, V<sub>1</sub> is the unregulated at 15 V. Assume  $V_{BE} = 0.7$  V and the base current is negligible for both the BJTs. If the regulated output V<sub>o</sub> is 9 V, the value of R<sub>2</sub> is .....Ω.



**Ans.** 800

Sol.



Voltage  $V_B = V_z + V_{BE}$ 

$$V_{\rm B} = 4V ...(i)$$

$$\therefore I = \frac{9-4}{1K}$$

I = 5 mA

Since base cement is negligible,

$$V_{B} = 9 \times \frac{R_{2}}{R_{1} + R_{2}}$$
$$4 = \frac{9R_{2}}{1K + R_{2}} \Longrightarrow R_{2} = 800\Omega$$



**44.** Using the incremental low frequency small-signal model of the MOS device, the Norton equivalent resistance of the following circuit is



**45.** A solar cell of area 1.0 cm<sup>2</sup>, operating at 1.0 sun intensity, has a short circuit current of 20 mA, and an open circuit voltage of 0.65 V. Assuming room temperature operation and thermal equivalent voltage of 26 mV, the open circuit voltage (in volts, correct to two decimal places) at 0.2 sun intensity is \_\_\_\_\_.

Ans. [0.59 to 0.63]



Sol. For solar cell open circuit voltage is given by,

$$V_{oc} = V_{\tau} ln \left( \frac{I_{sc}}{I_0} \right)$$

Since, the Current through the solar cell is directly proportional to intensity of light,

$$V_{oc2} - V_{oc1} = V_T ln \left( \frac{I_{SC2}}{I_{SC1}} \right) = V_T ln \left( \frac{0.20}{1.0} \right)$$
$$V_{oc2} = V_{oc1} - 0.026 ln (5)$$
$$= 0.65 - 0.041845 = 0.608 \text{ V}$$

$$V_{OC2} = 0.608 V.$$

**46.** Let  $x_1(t) = e^{-t}u(t)$  and  $x_2(t) = u(t) - u(t - 2)$ , where u(.) denotes the unit step function. If y(t) denotes the convolution of  $x_1(t)$  and  $x_2(t)$ , then  $\lim_{t \to 0} y(t) =$ \_\_\_\_\_. (Rounded off to one

decimal place).

#### **Ans.** [0 to 0]

**Sol.** 
$$x_1(t) = e^{-t}u(t)$$

$$x_{2}(t) = u(t) - u(t - 2)$$

$$y(t) = x_{1}(t) * x_{2}(t)$$

By applying Laplace transform

$$Y(s) = X_1(s) \cdot X_2(s) = \frac{1}{(s+1)} \frac{1 - e^{-2}}{s}$$

By applying final value theorem,

$$\left. y\left(t\right)\right|_{t=\infty} = \lim_{s \to 0} sY\left(s\right) = \lim_{s \to 0} \left(\frac{1 - e^{-2s}}{s+1}\right)$$

= 0

#### **Alternate Method:**

$$\begin{aligned} y(t) &= x_1(t) * x_2(t) \\ &= e^{t}u(t) * [u(t) - u(t - 2)] \\ &= e^{t}u(t) * u(t) - e^{t}u(t) * u(t - 2) \\ &= \int_{-\infty}^{t} e^{-t}u(t)dt - \int_{-\infty}^{t-2} e^{-t}u(t)dt \ [u(t) \text{ is the impulse response of an integrator}] \\ y(t) &= [1 - e^{t}]u(t) - [1 - e^{-(t - 2)}]u(t - 2) \\ y(\infty) &= [1 - 0]1 - [1 - 0]1 = 0 \end{aligned}$$

**47.** In the circuit shown below, the (W/L) value for  $M_2$  is twice that for  $M_1$ . The two NMOS transistors are otherwise identical. The threshold voltage  $V_T$  for both transistors is 1.0 V. Note that  $V_{GS}$  for  $M_2$  must be > 1.0 V.





Current through the nMOS transistors can be modeled as

$$\begin{split} I_{\text{DS}} &= \mu C_{\text{ox}} \left( \frac{W}{L} \right) \! \left( \left( V_{\text{GS}} - V_{\text{T}} \right) V_{\text{DS}} - \frac{1}{2} V_{\text{DS}}^2 \right) \text{ for } V_{\text{DS}} \leq V_{\text{GS}} - V_{\text{T}} \\ I_{\text{DS}} &= \mu C_{\text{ox}} \left( \frac{W}{L} \right) \! \frac{\left( V_{\text{GS}} - V_{\text{T}} \right)}{2} \text{ for } V_{\text{DS}} \geq V_{\text{GS}} - V_{\text{T}} \end{split}$$

The voltage (in volts, accurate to two decimal places) at  $V_{\text{x}}$  is ,

# Ans. [0.3 to 0.5]

**Sol.** The device constant  $K_n$ ,

$$K_n = \frac{\mu_n \, C_{ox}}{2} \left( \frac{W}{L} \right)$$

Given that,

$$\left(\frac{W}{L}\right)_2 = 2\left(\frac{W}{L}\right)_1$$

Then,

 $K_{n2} = 2K_{n1}$ For M<sub>1</sub>  $V_{GS1} - V_7 = 2 - 1 = 1 V$ Now, for M<sub>2</sub>  $V_{GS2} - V_7 = 2 - V_x - 1 = 1 V - V_x < 1 V$  $V_{DS2} = (3.3 - V_x) > (V_{GS2} - V_7)$ 

Here, clearly  $M_1$  will be in linear region and  $M_2$  will be in saturation region. But current across them would be same,

$$\begin{split} I_{D_1} &= I_{D_2} \\ \mathcal{K}_{n1} \Big[ 2 \left( V_{GS1} - V_T \right) V_{DS1} - V_{DS1}^2 \Big] &= \mathcal{K}_{n2} \left( V_{GS2} - V_T \right)^2 \\ \mathcal{K}_{n1} \Big[ 2 (2 - 1) V_x - V_x^2 \Big] &= 2 \mathcal{K}_{n1} (2 - V_x - 1)^2 \\ 2 V_x - V_x^2 &= 2 \left( 1 + V_x^2 - 2 V_x \right) = 2 V_x^2 - 4 V_x + 2 \\ 3 V_x^2 - 6 V_x + 2 &= 0 \quad ; \quad V_x^2 - 2 V_x + \frac{2}{3} = 0 \\ V_x &= 1 \pm \sqrt{\frac{4 - \frac{8}{3}}{43}} = 1 \pm \sqrt{\frac{1}{3}} V \\ V_{GS2} &= (2 - V_x) \ge V_T \implies (1 - V_x) \ge 0 \\ \text{So, the only valid value, } V_x = 1 - \sqrt{\frac{1}{3}} = 0.4226 \text{ V} \end{split}$$



**48.** A sinusoidal input  $x(t) = 2\sin(2t)$  is applied to system with transfer function  $P(s) = \frac{2}{2(s-2)}$ .

Determine steady state o/p.

A. 2 sin(2t + 45°)B. .707 sin(2t - 135°)C. .5 sin(2t - 90°)D. .707 sin(2t - 90°)

Ans. B

- **Sol.** X(t) = A Sin (Wt)
  - W = 2 , A= 2

Calculate magnitude and phase at w = 2 of system

Magnitude = 
$$\frac{2}{2\sqrt{(2)^2 + (2)^2}}$$
  
=  $\frac{1}{\sqrt{8}}$   
Phase = -90° - tan<sup>-1</sup> (2/2)  
= -90° - 45° = -135°  
So, o/p will be  
 $y(t) = 2 \times \frac{1}{\sqrt{8}} \sin(2t - 135°)$ 

**49.** The function  $f(x) = x^2 - x - 2$  the maximum value of f(x) at value of x in closed internal [-2, 2] is

-2 0

A5	В,
C. 2	D.

Ans. B

```
Sol. f(-2) = (-2)^2 - (-2) - 2
```

f(-2) = 4 + 2 - 2

f(-2) = 4

 $f(2) = (2)^2 - 2 - 2$ 

f(2) = 0

So, maximum value of f(x) at value of x = -2

**50.** A causal LTI system described by the difference equation:

 $y\left(n\right)=y\left(n-1\right)+y\left(n-2\right)+x\left(n-1\right)$ 

The impulse response of the system is h(n). Then the value of h(1) =\_\_\_\_\_.

**Ans.** [0.95 to 1.05]

Sol. Given difference equation is:

y(n) = y(n-1) + y(n-2) + x(n-1)

Applying Z-transform to this equation,



$$\Rightarrow Y(z) = z^{-1}Y(z) + z^{-2}Y(z) + z^{-1}X(z)$$
  

$$\Rightarrow H(z) = \frac{Y(z)}{X(z)} = \frac{z^{-1}}{1 - z^{-1} - z^{-2}}$$
  

$$\Rightarrow H(z) = \frac{z}{z^2 - z - 1}$$
  

$$\Rightarrow H(z) = \frac{0.447z}{z - 1.618} - \frac{0.447z}{z + 0.618}$$
  

$$\Rightarrow h(n) = 0.447(1.618)^n u(n) - 0.447(-0.618)^n u(n)$$
  

$$\Rightarrow h(1) = 0.447 * 1.618 - 0.447(-0.618)$$
  

$$h(1) \approx 1$$

**51.** The voltage and current associated with a load is V =  $100 \angle 30^{\circ}$ , I =  $5 \angle -30^{\circ}$ .

Then which of the following are true?

A. the power factor of the load is  $0.5 \mbox{ lag}$ 

B. the power factor of the load is 0.5866 lag

C. the active power of load is 250 W

D. the active power of load is 500 W

# **Ans.** A, C

**Sol.** Given:  $V = 100 \angle 30^{\circ}$ ,  $I = 5 \angle -30^{\circ}$ 

$$\Rightarrow$$
 S = VI<sup>\*</sup>

 $\Rightarrow S = (100 \angle 30^\circ)(5 \angle 30^\circ)$ 

$$\Rightarrow$$
 S = 500 $\angle 60^{\circ}$ 

Here  $\phi = 60^{\circ}$ 

 $\Rightarrow$  pf = cos $\phi$  = cos $60^{\circ}$  = 0.5 lag

Since, current lags the voltage in this load.

The active power of the load is given by:

 $P = Scos\phi = 500 \times 0.5 = 250 W$ 

**52.** An engineer needs to make an RC high pass filter. He has one 10PF capacitor, one 30PF capacitor, one  $1.8K\Omega$  resistor and one  $3.3K\Omega$  resistor available. The greatest cutoff frequency (in MHz) possible is\_\_\_\_\_

#### Ans. [18 to 19]

**Sol.** Cut-off frequency of HP filter is given by:

$$f = \frac{1}{2\pi RC}$$

So, to get the maximum cutoff frequency, the values of R and C should be as low as possible. So the two resistors should be connected in parallel.

$$\Rightarrow$$
 R<sub>eq</sub> =  $\frac{1.8 \times 3.3}{1.8 + 3.3}$  = 1.1647 KΩ

Also, the two capacitors should be connected in series.



$$\Rightarrow C_{eq} = \frac{10 \times 30}{10 + 30} = 7.5 \text{ PF}$$

So, the greatest cutoff frequency is given by:

$$f = \frac{1}{2\pi R_{eq}C_{eq}} = \frac{1}{2\pi * 1.1647 * 10^3 * 7.5 * 10^{-12}}$$
  
$$\Rightarrow f = 18.2 \text{ MHz}$$

**53.** Let  $x(t) = \frac{1}{t} [1 - e^{-t}] u(t)$ . Then the value of Laplace transform of function at s = 1 is\_\_\_\_\_

Sol. Let, 
$$y(t) = [1 - e^{-t}]u(t)$$
  

$$\Rightarrow x(t) = \frac{1}{t}y(t)$$

$$\Rightarrow X(s) = \int_{s}^{\infty} Y(s)ds$$

$$Y(s) = \frac{1}{s} - \frac{1}{s+1}$$

$$\Rightarrow X(s) = \int_{s}^{\infty} \frac{1}{s}ds - \int_{s}^{\infty} \frac{1}{s+1}ds$$

$$\Rightarrow X(s) = -\ln(s) + \ln(s+1)$$

$$X(s) = \ln\left(\frac{s+1}{s}\right)$$

$$\Rightarrow X(s)_{s \to 1} = \ln\left(\frac{2}{1}\right) = \ln(2)$$

$$\Rightarrow X(s = 1) = 0.693$$

54. The value of R for which the circuit resonates is?



# Ans. D

**Sol.** When a circuit resonates at a particular frequency, at that frequency the imaginary part of impedance or admittance of the network is zero.

$$\Rightarrow Y_{AB} = \frac{1}{10 + j10} + \frac{1}{R - j2}$$



RET

$$\begin{split} Y_{AB} &= \frac{10 - j10}{10^2 + 10^2} + \frac{R + j2}{R^2 + 2^2} \\ Y_{AB} &= \frac{10}{200} + \frac{R}{R^2 + 4} - j\left(\frac{10}{200} - \frac{2}{R^2 + 4}\right) \end{split}$$

Now equate the imaginary part to zero.

$$\Rightarrow \frac{10}{200} - \frac{2}{R^2 + 4} = 0$$
$$\Rightarrow R^2 + 4 = 40$$
$$\Rightarrow R^2 = 36$$
$$\Rightarrow R = 6 \Omega$$

**55.** A unity feedback system has open transfer function  $G(s) = \frac{50}{(s+4)(s+5)}$ . A PID controller having

transfer function  $G_{c}(s) = \left(k_{p} + sk_{d} + \frac{k_{i}}{s}\right)$  is introduced to improve the steady state as well as

transient performance. For what value of ki, the steady state error is 10% for unit ramp input?

A.	1			В	. 2

C. 3 D. 4

#### Ans. D

 $\ensuremath{\textbf{Sol.}}$  The open loop transfer function with controller is given by:

$$G(s)_{\text{with compensator}} = \frac{50}{(s+4)(s+5)} * \left(k_{p} + sk_{d} + \frac{k_{i}}{s}\right)$$

$$G(s)_{wc} = \frac{50(s^{2}k_{d} + sk_{p} + k_{i})}{s(s+4)(s+5)}$$

$$\Rightarrow e_{ss} = \frac{A}{K_{v}} = \frac{1}{\frac{50 * k_{i}}{4 * 5}}$$

$$Given \% e_{ss} = 10\%$$

$$\Rightarrow 0.1 = \frac{20}{50k_{i}}$$

$$\Rightarrow 5k_{i} = 20$$

$$\Rightarrow k_{i} = 4$$

**56.** The position of a particle y(t) is described by the differential equation:

 $\frac{d^2y}{dt^2} = -\frac{dy}{dt} - \frac{5y}{4}$ 

The initial conditions are y(0) = 1 and  $\frac{dy}{dt}\Big|_{t=0} 0$ . The position (accurate to two decimal places) of

the particle at  $t = \pi$  is \_\_\_\_.

**Ans.** – 0.21



#### Sol. Given condition,

$$\frac{d^2y}{dt^2} + \frac{dy}{dt} + \frac{5y}{4} = 0$$
$$y(0) = 1$$
$$y'(0) = 0$$

This can be solved easily in laplace domain,

$$s^{2}Y(s) - s(1) + sY(s) - 1 + \frac{5}{4}Y(s) = 0$$
$$Y(s) = \frac{s+1}{s^{2} + s + \frac{5}{4}} = \frac{s+1}{\left(s + \frac{1}{2}\right)^{2} + 1}$$
$$= \frac{\left(s + \frac{1}{2}\right)}{\left(s + \frac{1}{2}\right)^{2} + 1} + \frac{\frac{1}{2}}{\left(s + \frac{1}{2}\right)^{2} + 1}$$

By taking inverse Laplace transform we get y(t),

$$y(t) = e^{-t/2} \left[ \cos(t) \frac{1}{2} \sin(t) \right] ; t > 0$$

Now its value at  $t = \pi$ ,

$$y(t = \pi) = e^{-\pi/2} [(-1) + (0)] = e^{-\pi/2}$$
  
= -0.2078 \approx -0.21

**57.** A curve passes through the point (x = 1, y = 0) and satisfies the differential equation  $\frac{dy}{dx} = \frac{x^2 + y^2}{2y} + \frac{y}{x}$ . The equation that describes the curve is

A. 
$$\ln\left(1 + \frac{y^2}{x^2}\right) = x - 1$$
  
B.  $\frac{1}{2}\ln\left(1 + \frac{y^2}{x^2}\right) = x - 1$   
C.  $\ln\left(1 + \frac{y}{x}\right) = x - 1$   
D.  $\frac{1}{2}\ln\left(1 + \frac{y}{x}\right) = x - 1$ 

Ans. A

Sol. Given Differential equation,

$$\frac{\mathrm{d}y}{\mathrm{d}x} = \frac{x^2 + y^2}{2y} + \frac{y}{x}$$

We need to use suitable substitution here,

Put,  $\frac{y}{x} = t$ 



$$\frac{dy}{dx} = t + x \frac{dt}{dx}$$

$$1 + x \frac{dt}{dx} = \frac{x}{2t} + \frac{tx}{2} + t$$

$$x \frac{dt}{dx} = x \left(\frac{1}{2t} + \frac{t}{2}\right)$$

$$x \frac{dt}{dx} = x \left(\frac{1 + t^2}{2t}\right)$$

$$\int \frac{2t}{1 + t^2} dt = \int dx + C$$

$$ln (1 + t^2) = x + C$$

$$t = \frac{y}{x}$$

After simplification we obtain the following relation,

$$ln\left(1+\frac{y^2}{x^2}\right) = x + C$$

Given that the curve passes through points,

x = 1, y = 0, we can obtain the value of constant C.

$$ln\left(1+\frac{0}{1}\right) = ln(1) = 0 = 1+C$$
  

$$C = -1$$
  
So,  $ln\left(1+\frac{y^{2}}{x^{2}}\right) = x-1$ 

58. Consider a white Gaussian noise process N(t) with two-sided power spectral density

 $S_N(f) = 0.5$  W/Hz as input to a filter with impulse response  $0.5e^{\frac{-t^2}{2}}$  (where t is in seconds) resulting in output Y(t). The power in Y(t) in watts is

A. 0.11	B. 0.22
C. 0.33	D. 0.44

#### Ans. B

Sol. Power Spectral Density of noise input,

$$S_{N}(f) = 0.5 \text{ W/Hz}$$

Power of y(t),

$$P_{y} = \int_{-\infty}^{\infty} S_{N}(f) |H(f)|^{2} df$$
  
= 0.50  $\int_{-\infty}^{\infty} |H(f)|^{2} df = 0.50 \int_{-\infty}^{\infty} |h(f)|^{2} dt$ 

Given the impulse response of the filter being used,



$$h(t) = \frac{1}{2}e^{-t^2/2}$$

So,

$$P_{\gamma} = \frac{1}{2} \int_{-\infty}^{\infty} \left(\frac{1}{2} e^{-t^2/2}\right)^2 dt = \frac{1}{8} \int_{-\infty}^{\infty} e^{-t^2} dt$$
$$= \frac{\sqrt{\pi}}{8} = 0.22 \text{ W}$$

**59.** Let  $c(t) = A_c \cos(2\pi f_c t)$  and  $m(t) = \cos(2\pi f_m t)$ . It is given that  $f_c > > 5f_m$ . The signal c(t) + m(t) is applied to the input of a non-linear device, whose output  $v_0(t)$  is related to the input  $v_i(t)$  as  $v_0(t)av_i(t) + bv_i^2(t)$ , where a and b are positive constants. The output of the non-linear device is passed through an ideal band-pass filter with center frequency  $f_c$  and bandwidth  $3f_m$ , to produce an amplitude modulated (AM) wave. If it is desired to have the sideband power of the AM wave to be half of the carrier power, then a/b is

C. 1 D. 2

# Ans. D

Sol. According to given input signal, we can obtain an output signal as follows,

$$\begin{split} v_i(t) &= A_c \cos(2\pi f_c t) + \cos(2\pi f_m t) \\ v_o(t) &= a v_i(t) + b v_i^2(t) \\ &= \left[ a A_c \cos(2\pi f_c t) + a \cos(2\pi f_m t) \right] + b \\ \left[ A_c^2 \cos^2(2\pi f_c t) + \cos^2(2\pi f_m t) + 2A_c \cos(2\pi f_c t) \cos(2\pi f_m t) \right] \end{split}$$

When the signal is passed through given Band Pass Filter,

$$y(t) = aA_c \cos 2\pi f_c t + 2bA_c \cos (2\pi f_c t)$$
  

$$\cos (2\pi f_m t)$$
  

$$= aA_c \left[ 1 + \frac{2b}{a} \cos (2\pi f_m t) \right] \cos (2\pi f_c t)$$

The Modulation index can be obtained through output of the BPF,

$$\mu = \frac{2b}{a}$$

We have been given in the problem statement that Side Band contains half the carrier power,

$$P_{SB} = \frac{\mu^2}{2} P_c = \frac{1}{2} P_c$$

So, 
$$\mu^2 = 1 \Rightarrow \mu = 1$$

Comparing with the value obtained in form of a and b,

 $\frac{2b}{a} = 1$  $\frac{a}{b} = 2$ 



- **60.** The distance (in meters) a wave has to propagate in a medium having a skin depth of 0.1 m so that the amplitude of the wave attenuates by 20 dB, is
  - A. 0.12 B. 0.23
  - C. 0.46 D. 2.3

# Ans. B

**Sol.** Attenuation constant is related with skin depth as follows, And according to given condition of 20 dB attenuation we can get required depth by following calculation,

$$\alpha = \frac{1}{\text{skin depth}} = 10 \text{ Np/m}$$

$$20 \log_{10} \left( \frac{E_o}{E_x} \right) = 20 \text{ } dB$$

$$\frac{E_o}{E_x} = 10 \Rightarrow (E_x) = \frac{E_o}{10}$$

$$E_x = E_o e^{-\alpha x} = E_o e^{-10x} = \frac{E_o}{10}$$

$$e^{-10x} = \frac{1}{10}$$

$$x = \frac{1}{10} \text{ In}(10) = 0.23 \text{ m}$$

**61.** A circuit and the characteristics of the diode (D) in it are shown. The ratio of the minimum to

the maximum small signal voltage gain  $\frac{\partial V_{out}}{\partial V_{in}}$  in \_\_\_\_\_ (rounded off to two decimal places).



**Ans.** [0.7 to 0.8]

**Sol.** Given circuit is shown below,



And diode characteristics is,





Replacing the circuit in figure (a) with the small signal equivalent



# Case 1: When diode ON

As  $r_d(ON) = 0$ , the  $2k\Omega$  resistor in parallel to the diode becomes short circuit.

$$\begin{array}{ll} \therefore & V_{\text{out}} = \frac{V_{\text{input}} \times 2}{4} = \frac{V_{\text{input}}}{2} \\ \\ \therefore & \frac{\partial V_{\text{out}}}{\partial V_{\text{in}}} \bigg|_{\text{max.}} = \frac{1}{2} \end{array}$$

#### Case 2: When diode OFF

As  $r_d(OFF)$  = infinite, the equivalent resistance will  $2k\Omega + 2k\Omega + 2k\Omega = 6k\Omega$ 

$$\therefore V_{out} = \frac{V_{input} \times 4}{2 + 2 + 2} = \frac{2V_{input}}{3}$$
  
$$\therefore \frac{\partial V_{out}}{\partial V_{in}} \bigg|_{min.} = \frac{2}{3}$$
  
$$\therefore \frac{\partial V_{out}}{\partial V_{in}} \bigg|_{min.} = \frac{1}{2} = \frac{1}{2} \times \frac{3}{2} = 0.$$

Hence, Correct answer is 0.75

**62.** A lossy transmission line has resistance per unit length  $R = 0.05 \Omega/m$ . The line is distortionless and has characteristic impedance of  $50\Omega$ . The attenuation constant (in Np/m, correct to three decimal places) of the line is \_\_\_\_\_.

**Ans.** 0.001

Sol. The following condition is true for a distortion-less transmission line,

75

$$\frac{L}{R} = \frac{C}{G}$$

Propagation constant is given by,

$$\begin{split} \gamma &= \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \\ &= \sqrt{RG} \left(1 + j\omega \frac{L}{R}\right) \end{split}$$



And the attenuation constant, which is real part of the propagation constant,

$$\alpha = \sqrt{RG}$$

Characteristic impedance,

$$Z_{o} = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}} = \sqrt{\frac{R}{G}}$$
$$\sqrt{G} = \frac{\sqrt{R}}{Z}$$

So,

$$\alpha = \sqrt{R} \cdot \frac{\sqrt{R}}{Z_o} = \frac{R}{Z_o} = \frac{0.05}{50} = \frac{0.01}{10}$$
$$= 0.001 \text{ Np/m}$$

**63.** A p-type semiconductor with zero electric field is under illumination (low level injection) in steady state condition. Excess minority carrier density is zero at  $x = \pm 2\ell_n$ , where  $\ell_n = 10^{-4}$  cm is the diffusion length of electrons. Assume electronic charge,  $q = -1.6 \times 10^{-19}$ C. The profiles of photogeneration rate of carriers and the recombination rate of excess minority carriers (R) are shown. Under these conditions, the magnitude of the current density due to the photo-generated electrons at  $x = \pm 2\ell_n$  is \_\_\_\_\_ mA/cm<sup>2</sup> (rounded off to two decimal places).



**Ans.** [0.57 to 0.61] **Sol.** 

$$\delta n(x) = R\tau_n = 10^{20} e^{-|x|/l_n} \tau_n$$

$$\delta n(\ln) = 1020e^{-1}\tau_n ...(1)$$

$$I_n \le x \le 2I_n$$

Continuity equation in steady state,

$$D_{n} \frac{\partial^{2} \delta n}{\delta x^{2}} + G - R = 0$$
  
Since,  $G = 0$   
 $R = 0$   $I_{n} \le x \le 2I_{n}$ 

$$\therefore D_{n} \frac{\partial^{2} \delta n}{\partial x^{2}} = 0$$
Whose solution is,  
 $\delta n(x) = Ax + B$ 
Since at  $x = 2I_{n}$ :  
 $\delta n(2I_{n}) = 0$  (given)  
 $0 = A(2I_{n}) + B$ 

$$A = -\frac{B}{2I_{n}}$$

$$\therefore \delta n(x) = -\frac{B}{2I_{n}} x + B = B\left(1 - \frac{x}{2I_{n}}\right) ...(ii)$$

$$\therefore At x = I_{n}: equation (i) = equation (ii)$$
 $10^{20}e^{-t}\tau_{n} = B\left(1 - \frac{I_{n}}{2I_{n}}\right)$ 

$$\therefore B = 2 \times 10^{20}e^{-t}\tau_{n}$$

$$\therefore \delta n(x) = 2 \times 10^{20}e^{-t}\tau_{n}\left(1 - \frac{x}{2I_{n}}\right) I_{n} \le x \le 2I_{n}$$

$$\therefore Electron diffusion current density:$$
 $|J_{n}|_{aff} = qD_{n}\frac{dn}{dx} = qD_{n} \times 2 \times 10^{20} \times e^{-t} \times \tau_{n}\left(0 - \frac{1}{2I_{n}}\right)$ 
 $= \frac{1.6 \times 10^{-19} \times I_{n}^{2} \times 2 \times 10^{20} \times e^{-t}}{2I_{n}}$ 
 $= 1.6 \times 10^{-19} \times I_{n}^{2} \times 2 \times 10^{20} \times e^{-t}$ 
 $= 1.6 \times 10^{1} \times 1 \times 10^{-4} \times e^{-t} (I_{n} = 10^{-4} \text{ cm})$ 
 $= 0.588 \text{ mA/cm}^{2} = 0.59$ 

**64.** In the circuit shown in figure below, identical transistors with large  $\beta$  value and  $V_{A1} = V_{A2} = 100V$  at a thermal voltage of 26 mV are used. The approximate small signal output resistance of the circuit in K $\Omega$  is \_\_\_\_.



# **Ans.** [8.8 to 9.2]

**Sol.** Apply KCL at node C<sub>1</sub> :

 $\Rightarrow$  I<sub>ref</sub> = I<sub>C1</sub> + I<sub>B1</sub> + I<sub>B2</sub>

But given both transistors are identical,

$$\Rightarrow I_{ref} = I_{C2} + 2I_{B2}$$

$$I_{ref} = I_{C2} \left[ 1 + \frac{2}{\beta} \right]$$

$$I_{ref} \approx I_{C2}$$
Now  $r_{o2} = \frac{V_{A2}}{I_{C2}} = \frac{100}{1m} = 100$ 

$$\Rightarrow R_o = \frac{10K * 100K}{10K + 100K} = 9.09 \text{ K}\Omega$$

- 65. An intrinsic semiconductor is doped with an impurity concentration of 10<sup>16</sup>/cm<sup>3</sup>. Assume the intrinsic carrier concentration  $n_i = 1.5 \times 10^{10}/\text{cm}^3$  and the thermal voltage V<sub>T</sub> = 26 mV. The Fermi level in doped semiconductor
  - A. Goes down by 0.35 eV if the impurity is 3rd group element

KΩ

- B. Goes up by 0.35 eV if the impurity is 3rd group element
- C. Goes up by 0.35 eV if the impurity is 5th group element
- D. Goes down by 0.35 eV if the impurity is 5th group element

Ans. A, C

**Sol.** Shift in Fermi-level is given by:

shift = kTln 
$$\left(\frac{\text{Doping concentration}}{\text{Intrinsic concentration}}\right)$$
  
 $\Rightarrow$  shift = 0.026 ln  $\left(\frac{10^{16}}{1.5 \times 10^{10}}\right)$ 

$$\Rightarrow \operatorname{sinit} = 0.020 \operatorname{III} \left( \frac{1.5 \times 1}{1.5 \times 1} \right)$$

 $\Rightarrow$  shift = 0.35 eV

If the impurity is 3<sup>rd</sup> group element, the resultant is a P-type semiconductor and the Fermi-level shifts downwards.

If the impurity is 5<sup>th</sup> group element, the resultant is an N-type semiconductor and the Fermilevel shifts upwards.

**66.** In the following circuit  $V_c(0^-) = 5V$  and  $V_c(t) = \frac{5}{e}V$  at t = 0.1 sec, then the value of C in







# **Ans.** [2.4 to 2.6]

**Sol.** It is a source free RC circuit; voltage across capacitor is given by:

$$V_{c}(t) = V_{c}(0^{-})e^{-\frac{t}{\tau}}$$
  
Where,  $\tau = CR$   
Given  $V_{c}(0.1) = \frac{5}{e} = 5e^{-\frac{0.1}{RC}}$   
 $\Rightarrow 5e^{-1} = 5e^{-\frac{0.1}{RC}}$   
 $\Rightarrow RC = 0.1$   
 $\Rightarrow C = \frac{0.1}{40K} = 2.5 \,\mu\text{F}$ 

- **67.** A photo diode has a quantum efficiency of 80% when photons of energy  $1.6*10^{-19}$ J are incident upon it. Then the incident optical power in  $\mu$ W required to obtain a photocurrent of  $4\mu$ A is\_\_\_\_\_.
- **Ans.** [5 to 5]
- Sol. Given data is:

$$\eta = 80\% = 0.8$$

$$E = hf = 1.6*10^{-19}J$$

Responsivity of a photo diode is given by:

$$R = \frac{\eta q}{hf}$$
  
$$\Rightarrow R = \frac{0.8 * 1.6 * 10^{-19}}{1.6 * 10^{-19}} = 0.8$$

Responsivity is also given by:

$$R = \frac{I_p}{P} = \frac{\text{photocurrent}}{\text{incident optical power}}$$
$$\Rightarrow P = \frac{4 * 10^{-6}}{0.8} = 5 \,\mu\text{W}$$

**68.** Consider a CMOS inverter fabricate in a  $0.13\mu$ m process for which V<sub>DD</sub> = 1.2V,

$$V_{tn} = -V_{tp} = 0.4$$
,  $\frac{\mu_n}{\mu_p} = 4$  and  $\mu_n C_{ox} = 430 \,\mu\text{A} / V^2$ . If the NMOS and PMOS transistor are matched,

then find the noise margin for high level and noise margin for low level respectively.

- A. 0.55 V and 0.65 V B. 0.55 V and 0.55 V
- C. 0.65 V and 0.55 V D. 0.65 V and 0.65 V

# Ans. B

Sol. Noise margin for high level is given by:

$$NM_{H} = V_{OH} - V_{IH}$$
  
But  $V_{OH} = V_{DD} = 1.2 V$   
Also  $V_{IH} = \frac{1}{8} (5V_{DD} - 2V_{t}) = \frac{1}{8} (5 * 1.2 - 2 * 0.4) = 0.65 V$   
 $\Rightarrow NM_{H} = 1.2 - 0.65 = 0.55 V$ 



Noise margin for high level is given by:

$$NM_{L} = V_{IL} - V_{OL}$$
  
But  $V_{OL} = 0 V$   
Also  $V_{IL} = \frac{1}{8}(3V_{DD} + 2V_{t}) = \frac{1}{8}(3 * 1.2 + 2 * 0.4) = 0.55$ 

 $\Rightarrow NM_{L} = 0.55 - 0 = 0.55 V$ 

Since NMOS and PMOS are matched  $NM_H = NM_L$ 

**69.** The impulse response of a unity feedback control system is  $c(t) = te^{-t}u(t)$ , and then which of the following are correct?

A. 
$$CLTF = \frac{1}{(s+1)^2}$$
 B.  $OLTF = \frac{1}{s(s+2)}$ 

C. Closed loop system is stable

D. Type of closed loop system is zero

**Ans.** A, B, C

**Sol.** CLTF = L[impulse response] = L[te<sup>-t</sup>u(t)] = 
$$\frac{1}{(s+1)^2}$$

As the poles of closed loop system are in the left half of s-plane, it is stable. OLTF can be found as below:

$$CLTF = \frac{C(s)}{R(s)} = \frac{G(s)}{1 + G(s)} = \frac{1}{(s+1)^2} = \frac{1}{s^2 + 2s + 1}$$
  

$$\Rightarrow \frac{1 + G(s)}{G(s)} = s^2 + 2s + 1$$
  

$$\Rightarrow \frac{1}{G(s)} + 1 = s^2 + 2s + 1$$
  

$$\Rightarrow G(s) = \frac{1}{s(s+2)}$$
  

$$\Rightarrow OLTF = \frac{1}{s(s+2)}$$

Only one pole at s=0, so the type of the closed loop system is 1

**70.** For the system shown in figure below, the DC gain due to noise is\_\_\_\_\_



**Ans.** [0.6 to 0.7]

**Sol.** The transfer function is given by:

$$\frac{C}{N} = \frac{\frac{4}{s+2}}{1 - \left[\frac{-1}{s+1} * \frac{4}{s+2}\right]}$$
$$\Rightarrow \frac{C}{N} = \frac{4(s+1)}{(s+1)(s+2)+4}$$



$$\Rightarrow \frac{C}{N} = \frac{4(s+1)}{s^2 + 3s + 6}$$
  
DC gain is obtained by putting s  
$$\Rightarrow DC gain = \frac{4(0+1)}{s^2 + 3s + 6} = \frac{4}{3}$$

= 0 in the TF,

$$\Rightarrow DC gain = \frac{4(0+1)}{0+0+6} = \frac{4}{6}$$
$$\Rightarrow DC gain = 0.67$$

**71.** Given that  $V_T = 1V$ ,  $\mu_n C_{ox} = 60 \,\mu\text{A} / V^2$ ,  $\frac{W}{L} = 40$ , and  $I_D = 0.3\text{mA}$  and  $V_D = 0.4V$ . Then the

value of Rs is?



B. 4.2 kΩ D. 3.8 kΩ

# Ans. A

**Sol.** The transistor is in saturation region, so  $I_D$  is given by:

$$I_{D} = \frac{1}{2} \mu_{n} C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{T})^{2}$$
  

$$\Rightarrow 0.3 * 10^{-3} = \frac{1}{2} * 60 * 10^{-6} * 40 * (V_{GS} - V_{T})^{2}$$
  

$$\Rightarrow V_{GS} - V_{T} = 0.5 V$$
  

$$\Rightarrow V_{GS} = 1.5 V$$
  

$$V_{G} - V_{S} = 1.5 V$$
  
But  $V_{G} = 0 V$   

$$\Rightarrow V_{S} = -1.5 V$$
  

$$\Rightarrow R_{S} = \frac{-1.5 - (-2.5)}{0.3m} = 3.3 \text{ K}\Omega$$

**72.** The real conjugate symmetric part of signal  $x(t) = e^{(5+7j)t}$  is

A. sinh(5t) . sin(7t)	B. sinh(5t) . cos(7t)
C. cosh(5t) . cos(7t)	D. cosh(5t) . sin(7t)

# Ans. C

**Sol.** We know that conjugate symmetric part is given by:

$$x_{cs}(t) = \frac{x(t) + x^{*}(-t)}{2}$$
  
$$\Rightarrow x_{cs}(t) = \frac{e^{(5+7j)t} + e^{-(5-7j)t}}{2}$$



$$\Rightarrow x_{cs}(t) = \frac{e^{5t} (\cos(7t) + j\sin(7t)) + e^{-5t} (\cos(7t) + j\sin(7t))}{2}$$
$$(\cos(7t) + j\sin(7t))(e^{5t} + e^{-5t})$$

$$\Rightarrow x_{cs}(t) = \frac{(\cos(7t) + j\sin(7t))(e^{5t} + e^{-5t})}{2}$$

The real part of conjugate symmetric signal is:

$$\operatorname{Re}(x_{cs}(t)) = \frac{(e^{5t} + e^{-5t})}{2} \cos(7t)$$
$$\Rightarrow \operatorname{Re}(x_{cs}(t)) = \cosh(5t) \cos(7t)$$

73. Let h[n] be the impulse response of a discrete-time linear time invariant (LTI) filter. The impulse response is given by

$$h[0] = \frac{1}{3}; h[1] = \frac{1}{3}; h[2] = \frac{1}{3}; and h[n] = 0 \text{ for } n < 0 \text{ and } n > 2$$

Let  $H(\omega)$  be the discrete-time Fourier system transform (DTFT) of h[n], where  $\omega$  is the normalized angular frequency in radians. Given that  $H(\omega)=0$  and  $0 < \omega_0 < \pi$ , the value of  $\omega_0$ (in radians) is equal to \_\_\_\_\_.

# **Ans.** 2.094

**Sol.** It is given that,

$$h[0] = \frac{1}{3}; h[1] = \frac{1}{3}; h[2] = \frac{1}{3}$$
  

$$h[n] = 0 \text{ for } n < 0 \text{ and } n > 2.$$
  

$$\therefore h[n] = h[0]\delta[n] + h[1]\delta[n-1] + h[2]\delta[n-2]$$

$$\frac{1}{3}[\delta[n] + \delta[n - 1] + \delta[n - 2]]$$

Apply DTFT on both sides,

$$\therefore H(\omega) = \frac{1}{3} [1 + e^{-j\omega} + e^{-2j\omega}]$$

Given that  $H(\omega_0) = 0 \& 0 < \omega_0 < \pi$ 

$$\frac{1}{3} [1 + e^{-j\omega} + e^{-2j\omega}] = 0$$

$$1 + e^{-j\omega}(1 + e^{-j\omega}) = 0$$

$$1 + e^{-j\omega} = -e^{j\omega}$$

$$e^{-j\omega} + e^{j\omega} = -1$$

$$\cos\omega = -\frac{1}{2}$$

$$\therefore \quad \omega_0 = \frac{2\pi}{3}$$

$$\omega_0 = 2.094$$





**74.** A continuous time signal x(t)=4cos(200πt)+8cos(400πt), where t is in seconds, is the input to a linear time invariant (LTI) filter with the impulse response

$$h(t) = \begin{cases} \frac{2\sin(300 \pi t)}{\pi t} & t \neq 0 \\ 600 & t = 0 \end{cases}$$

Let y(t) be the output of this filter. The maximum value of |y(t)| is \_\_\_\_\_\_.

**Sol.** Given: (t) = 
$$\begin{cases} \frac{2\sin(300\,\pi t)}{\pi t} & t \neq 0 \\ 600 & t = 0 \end{cases}$$

Thus  $h(t) = 600 \sin c(300t)$ 

$$\therefore H(f) = 2rect\left(\frac{f}{300}\right)$$

Given  $x(t) = 4\cos 200\pi t + 800\cos 400\pi t$ 

In f-domain

 $X(f)=2[\delta(f-100) + \delta(f+100)] + 4[\delta(f-200) + \delta(f+200)]$ 



For the whole signal =  $4 \times 2 = 8$ 

- **75.** An optical fiber is kept along the  $\hat{z}$  direction. The refractive indices for the electric fields along  $\hat{x}$  and  $\hat{y}$  directions in the fiber are  $n_x = 1.5000$  and  $n_y = 1.5001$ , respectively ( $n_x \neq n_y$  due to the imperfection in the fiber cross-section). The free space wavelength of a light wave propagating in the fiber is 1.5µm. If the light wave is circularly polarized at the input of the fiber, the minimum propagation distance after which it becomes linearly polarized, in centimeter, is \_\_\_\_\_.
- Ans. [0.36 to 0.38]
- Sol. For circular polarization, the phase difference between  $E_x$  and  $E_y$  is  $\pi/2$

The phase difference for linear polarization should be  $\boldsymbol{\pi}$ 

 $\Rightarrow$  So the wave must travel a minimum distance such that the extra phase difference of  $\pi/2$  must occur.

$$\beta_{yI}I_{min} - \beta_{x}I_{min} = \frac{\pi}{2}$$
  
 $\Rightarrow I_{min}$ 



$$\frac{\omega}{c} \left[ n_y - n_x \right] = \frac{\pi}{2} \Rightarrow \frac{2\pi I_{min}}{\lambda_0} \left[ n_y - n_x \right] = \frac{\pi}{2}$$
$$\Rightarrow I_{min} =$$
$$\frac{\lambda_0}{4 \left[ n_y - n_x \right]} = \frac{1.5 \times 10^{-5}}{4 \left[ 0.0001 \right]} = \frac{1.5}{4} \times 10^{-2}$$
$$= 0.375 \times 10^{-2} m = 0.375 \text{ cm}$$

**76.** The band diagram of a p-type semiconductor with a band-gap of 1eV is shown. Using this semiconductor, a MOS capacitor having  $V_{TH}$  of -0.16 V, C'<sub>ox</sub> of 100 nF/cm<sup>2</sup> and a metal work function of 3.87 eV is fabricated. There is no charge within the oxide. If the voltage across the capacitor is  $V_{TH}$ , the magnitude of depletion charge per unit area (in C/cm<sup>2</sup>) is





**77.** Four points P(0, 1), Q(0, -3), R(-2, -1), and S(2, -1) represent the vertices of a quadrilateral. What is the area enclosed by the quadrilateral?

- C. 8 D. 8√2
- Ans. B

Sol.



Area under PQRS =  $(\sqrt{8})^2$ 

Area under PQRS = 8

**78.** If the op-amp is ideal, then the current in amperes through the 90 $\Omega$  resistor is\_\_\_\_\_



**Ans.** [0.02 to 0.02]

**Sol.** Since DC 4V is given and there are no transients, we can do steady state analysis. Under DC: C becomes open circuited and L becomes short circuited The circuit then will be as below:



From superposition theorem:

$$V_{o} = -\frac{90}{100}(4) + \left[1 + \frac{90}{100}\right] \left[\frac{4(2K)}{2K + 2K}\right]$$
  
$$\Rightarrow V_{o} = -3.6 + 3.8 = 0.2 V$$

From the circuit we can write as below:

$$V_{2} = \frac{4(2K)}{2K + 2K} = V_{1}$$
  

$$\Rightarrow V_{1} = 2 V$$
  

$$\Rightarrow I_{90 \Omega} = \frac{V_{1} - V_{0}}{90} = \frac{2 - 0.2}{90} = 0.02 \text{ A}$$

**79.** For a class B amplifier providing a 20V peak signal to a 16ohm load speaker and a power supply of  $V_{CC} = 30V$ . The efficiency is

#### Ans. B

Sol. A 20V peak signal across a  $16\Omega$  load providing a peak load current of:

$$I_{\rm m} = \frac{V_{\rm m}}{R_{\rm L}} = \frac{20}{16} = 1.25 \text{ A}$$
$$I_{\rm dc} = \frac{2I_{\rm m}}{\pi} = \frac{2}{\pi} (1.25) = 0.796 \text{ A}$$

The input power delivered by the supply voltage is:

$$P_{i_{DC}} = V_{cc}I_{dc} = 30 * 0.796 = 23.9 W$$

The output AC power is given by:

$$P_{oAC} = \frac{V_m^2}{2R_L} = \frac{20^2}{2*16} = 12.5 \text{ W}$$

Therefore, efficiency is given by:

$$\eta = \frac{P_{oAC}}{P_{i_{DC}}} * 100\% = \frac{12.5}{23.9} * 100\% = 52.3\%$$

80. An analog signal of BW 20 KHz is sampled at a rate of 40 KHz and quantized into 16 levels resultant signal is transmitted using M-PSK with raised cosine pulse of roll off factor 0.3. Find minimum value of M if channel with a 110 KHz BW is available to transmit data?

C. 8 D. 16

Ans. B

Sol. Number of bits required for 16 levels is:

$$n = \log_2 L = \log_2 16 = 4$$

Bit rate is given by:

$$R_b = nf_s = 4 \times 40 \ K = 160 \ K$$

BW for M-ary PSK is given by:

$$BW = \frac{R_b}{\log_2 M} (1 + \alpha)$$
  

$$\Rightarrow 110 K = \frac{160 K}{\log_2 M} (1 + 0.3)$$
  

$$\Rightarrow M = 2^{1.89} = 3.7$$
  

$$\Rightarrow M = 4$$

Since, M is always an integer.

**81.** A HWR with capacitor filter is to supply 30V to a  $500\Omega$  load. If the ripple factor is 0.02 and frequency of AC supply is 50 Hz, then the value of peak diode current is

A. 2.12 A	B. 1.2 A

C. 1.48 A D. 2.36 A

#### Ans. A

**Sol.** Given values are:

 $V_{DC} = 30 \ V \quad R_c = 500 \ \Omega \quad r = 0.02 \quad f = 50 \ Hz$ 

$$\Rightarrow I_{DC} = \frac{V_{DC}}{R_c} = \frac{30}{500} = 0.06 \text{ A}$$

Ripple factor of HWR is given by:

$$r = \frac{1}{2\sqrt{3}R_{L}fC}$$
  

$$\Rightarrow C = \frac{1}{2\sqrt{3}R_{L}fr} = \frac{1}{2\sqrt{3} * 50 * 0.02 * 500} = 0.58 \text{ mF}$$
  

$$V_{r} = \frac{I_{DC}}{fC} = \frac{0.06}{50 * 0.58 * 10^{-3}} = 2.07 \text{ V}$$
  

$$\Rightarrow V_{m} = V_{DC} + \frac{V_{r}}{2} = 30 + \frac{2.07}{2} = 31.035 \text{ V}$$

The value of peak diode current is given by:

$$\Rightarrow i_{D \text{ peak}} = I_{DC} \sqrt{1 + 2\pi \sqrt{\frac{2V_m}{V_r}}}$$
$$\Rightarrow i_{D \text{ peak}} = 0.06 \sqrt{1 + 2\pi \sqrt{2 * \frac{31.035}{2.07}}} = 2.12 \text{ A}$$

82. A and B play a game where each is asked to select a number from 1 to 25. If the two numbers match both of them win a prize, and then probability that they will not win a prize in single trail is \_\_\_\_\_.

#### **Ans.** [0.95 to 0.97]

**Sol.** No. of ways in which either player can choose a number from 1 to 25 is 25 Total number of ways of choosing numbers is  $25 \times 25 = 625$ There are 25 ways in which the number chosen by both players is the same.



The probability that they will win a prize in single trail is:

$$\mathsf{P} = \frac{25}{625} = \frac{1}{25}$$

The probability that they will not win a prize in single trail is:

$$\Rightarrow P^{c} = 1 - \frac{1}{25} = \frac{24}{25} = 0.96$$

**83.** If the differential equation  $\frac{dy}{dx} = \sqrt{x^2 + y^2}$ , y(1) = 2 is solved using the Eulers method with step size h = 0.1, then y(1.2) =\_\_\_\_.

**Sol.** Let, 
$$f(x, y) = \frac{dy}{dx} = \sqrt{x^2 + y^2}$$

From Euler's method:

$$\Rightarrow y_1 = y(1.1) = y_0 + hf(x_0, y_0)$$

$$\Rightarrow y_1 = 2 + (0.1)f(1,2)$$

$$\Rightarrow y_1 = 2 + (0.1)\left(\sqrt{1+4}\right)$$

$$\Rightarrow y_1 = 2.2236$$

Again from Euler's method:

$$\Rightarrow y_2 = y(1.2) = y_1 + hf(x_1, y_1)$$
  

$$\Rightarrow y_2 = 2.2236 + (0.1)f(1.1, 2.2236)$$
  

$$\Rightarrow y_1 = 2 + (0.1)\left(\sqrt{(1.1)^2 + (2.2236)^2}\right)$$
  

$$\Rightarrow y_1 = 2.4717$$

- 84. A base band signal with f = 4 MHz is uniformly distributed in the range from 4V to 4V. This signal is sent on a channel whose maximum capacity is 32 Mbps using PCM. The best SNR (in dB) that could be achieved is \_\_\_\_\_
- **Ans.** [23.5 to 24.5]
- Sol. Signal power is Mean Square Value (MSV) of Uniform random variable

$$\Rightarrow S = \int_{-4}^{4} x^2 f(x) dx = \int_{-4}^{4} x^2 \times \frac{1}{8} dx = \frac{16}{3} W$$

Ideal sampling frequency is given by

$$f_s = 2f_m$$
  

$$\Rightarrow f_s = 2 \times 4 M = 8 MHz$$

For error free transmission through a channel, using PCM:

$$C \ge BW = nf_s$$

 $\Rightarrow$  32 *Mbps*  $\geq$  *n*  $\times$  8 *MHz* 

$$\Rightarrow n \leq 4$$



Hence maximum value of n = 4 bits/sample

For best SNR, Noise power N =  $\frac{\Delta^2}{12}$  should be small. So, step size  $\Delta = \frac{V_{max} - V_{min}}{2^n}$  should be small.

 $\Rightarrow$  'n' Should be considered the maximum value

$$\Rightarrow \Delta = \frac{4 - (-4)}{2^4} = \frac{8}{16} = \frac{1}{2}$$

$$N = \frac{1}{4 \times 12} = \frac{1}{48} W$$

$$SNR = \frac{S}{N} = \frac{16}{3} \times 48 = 256$$

$$\Rightarrow SNR(in \, dB) = 10 \log(256) = 24.08 \, dB$$

- **85.** The transmitting and receiving antennas are separated by a distance of  $200\lambda$  and having directive gain of 25 and 18 dB respectively. If 5mW of power is to be received, the minimum transmitted power in watts is\_\_\_\_\_
- Ans. [1.57 to 1.59]

**Sol.** Given that 
$$G_t(dB) = 25 dB = 10 \log(G_t)$$

$$\Rightarrow G_t = 10^{2.5} = 316.23$$

Also given that  $G_r(dB) = 18 dB = 10 \log(G_r)$ 

$$\Rightarrow G_r = 10^{1.8} = 63.1$$

Using the Friis equation, we have:

$$P_r = G_t G_r \left[\frac{\lambda}{4\pi R}\right]^2 P_t$$
  

$$\Rightarrow P_t = P_r \left[\frac{4\pi R}{\lambda}\right]^2 \frac{1}{G_t G_r}$$
  

$$\Rightarrow P_t = 5 * 10^{-3} \times \left[\frac{4\pi * 200\lambda}{\lambda}\right]^2 \times \frac{1}{316.23 * 63.1}$$
  

$$\Rightarrow P_t = 1.583 W$$

**86.** A finite state machine (FSM) is implemented using the D flip-flops A and B, and logic gates, as shown in the figure below. The four possible states of the FSM are  $Q_AQ_B = 00,01,10$  and 11.



Assume that  $X_{1N}$  is is held at a constant logic level throughout the operation of the FSM. When the FSM is initialized to the state  $Q_A Q_B = 00$  and clocked, after a few clock cycles, it starts cycling through

A. all of the four possible states if  $X_{1N} = 1$ 

- B. three of the four possible states if  $X_{1N} = 0$
- C. only two of the four possible states if  $X_{1N} = 1$
- D. only two of the four possible states if  $X_{IN} = 0$



#### Ans. D

**Sol.** In given diagram

Brocont					$X_a = 0 N$	ext State	X <sub>a</sub> = 1 Nex	t State
State	DA	D <sub>B</sub>	X <sub>a</sub>	Xa	θ* <u>,</u>	θ <b>*</b> Β	θ*,	θ*в
00	0	1	0	1	0	1	0	1
01	1	1	0	1	1	1	1	1
11	0	1	0	1	0	1	0	0
01	1	1	0	1	1	1	1	1

When  $X_{in} = 0.2$  States

When  $X_{in} = 1$  3 States

**87.** Consider the D-Latch shown in the figure, which is transparent when its clock input CK is high and has zero propagation delay. In the figure, the clock signal CLK1 has a 50% duty cycle and CLK2 is a one-fifth period delayed version of CLK1. The duty cycle at the output latch in percentage is \_\_\_\_\_.



Ans. [29.9 to 30.1]

Sol.



$$\Rightarrow \text{Duty-cycle of output} = \frac{\frac{T_{CLK}}{2} - \frac{T_{CLK}}{5}}{T_{CLK}} \times 100 = 30\%$$

**88.** In a non-degenerate bulk semiconductor with electron density  $n = 10^{16} \text{ cm}^{-3}$ , the value of  $E_C - E_{Fn} = 200 \text{ meV}$ , where  $E_C$  and  $E_{Fn}$  denote the bottom of the conduction band energy and electron<br/>Fermi level energy, respectively. Assume thermal voltage as 26 mV and the intrinsic carrier<br/>concentration is  $10^{10} \text{ cm}^{-3}$ . For  $n = 0.5 \times 10^{16} \text{ cm}^{-3}$ , the closest approximation of the value of<br/>( $E_C - E_{Fn}$ ), among the given options, is \_\_\_\_\_\_.<br/>A. 226 meV<br/>C. 218 meVB. 174 meV<br/>D. 182 meV



# Ans. C

Sol.



#### n-type

Given,  $E_C - E_{fn} = 200 \text{ meV} = 0.2 \text{ eV}$ 

We know that,  $E_{_{\rm C}} - E_{_{\rm F}} = KT \ln \frac{N_{_{\rm C}}}{N_{_{\rm D}}}$ 

#### Case 1:

$$n\cong N_{_{D1}}=10^{16}\ /\ cm^3$$

$$E_{c} - E_{Fn1} = KT \ln \frac{N_{c}}{N_{D_{1}}} = 0.2 eV = 200 meV$$

$$\frac{N_{c}}{N_{D_{1}}} = 2191.43 \Rightarrow N_{c} = 2191.43 \times 10^{10}$$

# Case 2:

 $n\cong N_{_{D2}}=0.5\!\times\!10^{_{16}}$  /  $cm^3$ 

$$E_{c} - E_{Fn2} = kT \ln \frac{N_{c}}{N_{D_{2}}}$$
$$= kT \ln \frac{2191.43 \times 10^{14}}{0.5 \times 10^{16}}$$
$$= 26 \ln (\frac{2191.43}{0.5})$$
$$= 218 \text{ meV}$$

Other Method:

Let, 
$$E_{c} - E_{Fn1} = kT \ln \frac{N_{c}}{N_{D_{1}}}$$
 ...(i)

$$E_{c} - E_{Fn_{2}} = kT \ln \frac{N_{c}}{N_{D_{2}}}$$
 ...(ii)

$$\left( E_{c} - E_{F_{n_{2}}} \right) - \left( E_{c} - E_{F_{n_{1}}} \right) = kT ln \frac{N_{c}}{N_{D_{1}}} \cdot \frac{N_{D_{1}}}{N_{c}}$$

$$E_{c} - E_{F_{n_{2}}} - 200 = kT ln \frac{10^{16}}{0.5 \times 10^{16}}$$



$$E_{c} - E_{Fn_{2}} = 200 + kT \ln 2$$

 $= 200 + 26 \times \ln(2)$ 

≅218 meV

**89.** Consider the homogeneous ordinary differential equation  $x^2 \frac{d^2y}{dx^2} - 3x \frac{dy}{dx} + 3y = 0$ , x > 0 with

y(x) as a general solution. Given that y(1) = 1 and y(2) = 14 the value of y(1.5), rounded off to two decimal places, is \_\_\_\_\_.

**Ans.** [5.24 to 5.26]

**Sol.** Given differential equation is of Cauchy – Euler differential equation type.

So let  $x = e^z \therefore z = \ln x$ 

The differential equation can be written as,

D (D -1) - 3D + 3 = 0  

$$\therefore$$
 D<sup>2</sup> - 4 D + 3 = 0  
 $\therefore$  D = 1, 3  
 $\therefore$  y = C<sub>1</sub>e<sup>z</sup> + C<sub>2</sub>e<sup>3z</sup>  
 $\therefore$  y = C<sub>1</sub>x + C<sub>2</sub>x<sup>3</sup>  
Now y (1) = 1  
 $\therefore$  C<sub>1</sub> + C<sub>2</sub> = 1 ...(i)  
And y(2) = 14  
 $\therefore$  2C<sub>1</sub> + 8C<sub>2</sub> = 14 ...(ii)  
From (i) and (ii)  
C<sub>1</sub> = -1, C<sub>2</sub> = 2  
 $\therefore$  y = -x + 2x<sup>3</sup>  
 $\therefore$  y(1.5) = -1.5 + 2(1.5)<sup>3</sup>  
 $\therefore$  y(1.5) = 5.25

**90.** Consider the DE given below with y(0) = 1. Then y(3) = ?

$$(x^{2} + 1)\frac{dy}{dx} + 4xy = \frac{1}{x^{2} + 1}$$
  
A. 0.01 B. 0.02  
C. 0.03 D. 0.04

# Ans. D

**Sol.** Given DE can be rearranged as below:

$$\frac{dy}{dx} + \frac{4x}{1+x^2} \cdot y = \frac{1}{\left(1+x^2\right)^2}$$

This is a standard Bernoulli's equation, whose integrating factor is given by:

$$IF = e^{\int \frac{4x}{1+x^2} dx}$$



$$\Rightarrow IF = e^{\int 2\frac{2x}{1+x^2}dx} = e^{2\ln(1+x^2)} = (1+x^2)^2$$

The general solution is given by:

$$y(IF) = \int (IF) \cdot \frac{1}{(1+x^2)^2} dx$$
  

$$\Rightarrow y(1+x^2)^2 = \int (1+x^2)^2 \cdot \frac{1}{(1+x^2)^2} dx$$
  

$$\Rightarrow y(1+x^2)^2 = x + c$$
  

$$\Rightarrow y(x) = \frac{x}{(1+x^2)^2} + \frac{c}{(1+x^2)^2}$$
  
Given,  $y(0) = 1$ ,  

$$\Rightarrow y(0) = 1 = 0 + c$$
  

$$\Rightarrow c = 1$$
  

$$\Rightarrow y(x) = \frac{x+1}{(1+x^2)^2}$$
  

$$\Rightarrow y(3) = \frac{4}{100} = 0.04$$

**91.** If f(z) = x - 2ay + i(bx - cy) is an analytic function, then  $\left(\frac{ac}{b}\right) = ?$ 

A. - 0.5 C. 0.5 B. - 1 D. 1

Ans. A

**Sol.** Let, 
$$f(z) = x - 2ay + i(bx - cy) = u + iv$$

$$\Rightarrow u = x - 2ay \& v = bx - cy$$
$$\Rightarrow u_x = 1 \& u_y = -2a$$
$$\Rightarrow v_x = b \& v_y = -c$$

For a function to be analytic, it should satisfy CR equations

$$\Rightarrow u_x = v_y \& u_y = -v_x$$
$$\Rightarrow 1 = -c \& -2a = -b$$
$$\Rightarrow c = -1$$
$$\Rightarrow b = 2a$$
$$\Rightarrow \left(\frac{ac}{b}\right) = \frac{a(-1)}{2a} = -0.5$$

**92.** For a MOD-28 ripple counter, each flip flop has a propagation delay of 50 ns and the NAND gate has a propagation delay of 30 ns . The maximum frequency of clock that can be applied to the counter is

A. 9.2 MHz	B. 2.5 MHz
C. 3.57 MHz	D. 4.34 MHz



# Ans. C

**Sol.** We know that:  $MOD \le 2^n$   $\Rightarrow 28 \le 2^n$   $\Rightarrow n = 5$ Total delay in the flip flops is given by:  $T_D = nt_{pd}$   $T_D = 5 \times 50 \text{ ns} = 250 \text{ ns}$ So, the total propagation delay is:  $\Rightarrow T = 250 + 30 = 280 \text{ ns}$  $\Rightarrow f_{max} = \frac{1}{T} = \frac{1}{280 \text{ ns}} = 3.57 \text{ MHz}$ 

**93.** The logic levels used in a 6-bit R-2R ladder type DAC are 1 = 5V and 0 = 0V. Find the output voltage for input 1 0 1 0 1 1. Consider R =  $1k\Omega$ .

A. 
$$\frac{55}{32}$$
V
 B.  $\frac{13}{8}$ V

 C.  $\frac{215}{64}$ V
 D.  $\frac{97}{4}$ V

#### Ans. C

**Sol.** Output voltage of R-2R ladder is given by:

$$V_o = -I_F R$$
  

$$\Rightarrow V_o = -\left[\frac{5}{2R} + 0 + \frac{5}{8R} + 0 + \frac{5}{32R} + \frac{5}{64R}\right]$$
  

$$\Rightarrow V_o = -\left[\frac{160 + 40 + 10 + 5}{64R}\right]$$
  

$$V_o = -\frac{215}{64} V$$

Here, negative sign only shows that input is given to inverting pin of op-amp or output is 180° phase reversed input.

$$\Rightarrow V_0 = \frac{215}{60} V$$

**94.** The following program is executed on 8085 microprocessor. After execution the contents of stack pointer is

LXI H, 0100H DCX H SPHL PUSH H PUSH PSW CALL SUBI POP H RET A. 0100 H C. 00FF H

B. 00FD H

D. 00FB H

# Ans. C

- Sol. LXI H, 0100H HL = 0100 H DCX H HL = 0100 H - 1=00FF H SPHL SP = HL =00FF H PUSH H SP = 00FF H - 2=00FD H PUSH PSW SP = 00FD H - 2=00FB H CALL SUBI SP = 00FB H -2 +2 =00FB H POP H SP = 00FB H + 2=00FD H RET SP = 00FD H + 2=00FF H So, the contents of SP is 00FF H
- **95.** The approximate delay in LOOP2 that the below 8085 microprocessor program with clock frequency of 2MHz produces in milliseconds is?

MVI B, 38H

LOOP2: MVI C, FFH

- LOOP1: DCR C
- JNZ LOOP1

DCR B

JNZ LOOP2

- Options:
- A. 50
- C. 100

B. 75 D. 125

# Ans. C

**Sol.** Instruction with corresponding T-states is given as:

MVI C, FFH 7 T-states DCR C 4 T-states JNZ LOOP1 10/7 T-states DCR B 4 T-states JNZ LOOP2 10/7 T-states So, the delay in LOOP1 is given by:  $T_{D1} = (T_{clk} \times Loop T \ states \ \times N_{10}) - (correction)$ 

 $T_{D1} = (0.5 \times 14 \times 255) - (0.5 \times 3) = 1783.5 \mu s$ 

And the delay in LOOP2 is given by:

 $T_{D2} = (0.5 \times 21 + T_{D1}) \times 56 - (0.5 \times 3)$ 

$$\Rightarrow T_{D2} \approx 100 ms$$

**96.** A parallel plate capacitor with plate area of 5 cm<sup>2</sup> and plate separation of 3 mm has a voltage  $50\sin(10^{3}t)V$  applied to its plates. The displacement current assuming  $\varepsilon = 2\varepsilon_{0}$  is?

A. 147.4 sin(10 <sup>3</sup> t) nA	B. 274.1 cos(10 <sup>3</sup> t) nA
C. 147.4 cos(10 <sup>3</sup> t) nA	D. 274.1 sin(10 <sup>3</sup> t) nA





# Ans. C

Sol. From the below equations:

$$D = \varepsilon E = \frac{\varepsilon V}{d}$$
$$\Rightarrow J_d = \frac{\partial D}{\partial t} = \frac{\varepsilon}{d} \frac{dV}{dt}$$

Displacement current is thus given by:

$$I_{d} = J_{d} \cdot S = \frac{\varepsilon S}{d} \frac{dV}{dt} = C \frac{dV}{dt}$$
  

$$\Rightarrow I_{d} = \frac{2 * 10^{-9}}{36\pi} \times \frac{5 * 10^{-4}}{3 * 10^{-3}} \times 10^{3} \times 50 \cos(10^{3}t) A$$
  

$$\Rightarrow I_{d} = 147.4 \cos(10^{3}t) nA$$

**97.** Consider a super heterodyne receiver tuned to 600 kHz. If the local oscillator feeds a 1000 kHz signal to the mixer, the image frequency (in integer) is \_\_\_\_\_ kHz.

#### **Ans.** 1400

# Sol.

$$F_{L_0} > F_{R_F}$$

$$\mathbf{F}_{L_0} = \mathbf{F}_{R_F} + \mathbf{F}_{I_F}$$

 $1000 = 600 + {}^{F_{I_{F}}} \Rightarrow {}^{F_{I_{F}}} = 400 \text{ kHz}$ 

 $F_{Image} = F_{fs} + 2^{F_{I_F}}$ 

 $F_{Image} = 600 + 2(400) = 1400 \text{ kHz}$ 

98. For a unit step input u[n], a discrete-time LTI system produces an output signal ( $2\delta$ [n +1] +

 $\delta[n] + \delta[n-1]$ ). Let y[n] be the output of the system for an input  $\left(\left(\frac{1}{2}\right)^n u[n]\right)$ . The value of y[0]

**Ans.** 0

**Sol.**  $u[n] \longrightarrow h[n] \longrightarrow 2\delta[n+1] + \delta[n] + \delta[n-1]$ 

$$\begin{split} u[n] &\longleftrightarrow \frac{z_{T.}}{z-1} \\ 2\delta[n+1] + \delta[n] + \delta[n-1] &\longleftrightarrow 2z + 1 + z^{-1} \\ &= 2z + 1 + \frac{1}{z} \\ &= \left(\frac{2z^2 + z + 1}{z}\right) \end{split}$$

Now,

$$H(z) = \left(\frac{2z^2 + z + 1}{z}\right) / \left(\frac{z}{z - 1}\right)$$



$$\begin{aligned} H(z) &= \frac{(z-1)(2z^2+z+1)}{z^2} \\ H(z) &= \frac{2z^3-z^2-1}{z^2} \\ H(z) &= 2z-1-z^{-2} \\ h[n] &= 2\delta[n+1] - \delta[n] - \delta[n-2] \\ \textbf{x}[n] & \textbf{h}[n] \\ \textbf{x}[n] &= \left(\frac{1}{2}\right)^n .u[n] \\ , h[n] &= 2\delta[n+1] - \delta[n] - \delta[n-2] \\ y[n] &= x[n] * h[n] \\ y[n] &= x[n] * [2\delta[n+1] - \delta[n] - \delta[n-1]] \\ y[n] &= 2x[n+1] - x[n] - x[n-2] \\ y[n] &= 2\left(\frac{1}{2}\right)^{n+1} .u[n+1] - \left(\frac{1}{2}\right)^n .u[n] - \left(\frac{1}{2}\right)^{n-2} .u[n-2] \\ y[0] &= 2\left(\frac{1}{2}\right)^1 .u[1] - \left(\frac{1}{2}\right)^0 .u[0] - \left(\frac{1}{2}\right)^{-2} .u[-2] \\ y[0] &= 1 - 1 - 0 \\ y[0] &= 0 \end{aligned}$$

**99.** The transfer function of a linear time invariant system is given by  $H(s) = 2s^4 - 5s^3 + 5s - 2$ . The number of zeros in the right half of the s-plane is \_\_\_\_\_.

**Ans.** 3

**Sol.** Since, Routh Hurwitz gives information about location of roots about imaginary axis. So, the roots i.e. zeroes of H(s) can be found by Routh Hurwitz.

We can proceed here by taking this polynomial as characteristic equation and conclusion can be draw by using RH criterion. As we are interested to know how many roots are lying on right half of s plane.

S <sup>4</sup>	2	0	-2
	-5	+5	0
		-2	$\begin{cases} Since row of zero \\ occurs the \\ auxiliary equation \\ is \\ A.\varepsilon: 2s^2 - 2 \\ \frac{d}{ds}(At) = 4 \end{cases}$
	4	0	
S	-2		

 $\rightarrow$  The number of roots i.e. the number of zeros in this case in right half of plane is number of sign changes

 $\rightarrow$  Number of sign changes = 3



**100.** The open-loop transfer function of a unity-feedback control system is

$$G(s) = \frac{K}{s^2 + 5s + 5}$$

The positive value of K at the breakaway point of the feedback control system's root-locus plot is

# **Ans.** 1.25

**Sol.** In this first we need to find the break point by finding the root of  $\frac{dk}{ds} = 0$  and then by using magnitude condition value of k can be obtained.

$$G(s) = \frac{k}{s^2 + 5s + 5}$$

$$k = (s^2 + 5s + 5)$$

$$\frac{dk}{ds} = 0$$

$$\Rightarrow 2s + 5 = 0 \Rightarrow s = -2.5$$
Applying magnitude condition  $|G(s)| = 1$ 

$$\left|\frac{K}{s^2 + 5s + 5}\right|_{s=-2.5} = 1$$

$$\Rightarrow \left[\frac{k}{(-2.5^2)[5x(-2.5)] + 5}\right] = 1$$

$$\Rightarrow \left[\frac{k}{6.25 - 12.5 + 5}\right] = 1$$

$$\Rightarrow \left|\frac{k}{-1.25}\right| = 1$$

$$\Rightarrow k = 1.25$$
\*\*\*\*