

Electrical Engineering

Basic of Power
Electronics

SHORT NOTES



1. Basics of power electronics

Important Fourier series representations:

S. No	Signal	Fourier series expansion
1.		$V_0 = \sum_{n=1,3,5} \frac{4A}{n\pi} \text{Sin}n\omega t$
2.		$V_0 = \sum_{n=1,3,5} \frac{4A}{n\pi} \text{Sin}(n\omega t - n\alpha)$
3.		$V_0 = \sum_{n=1,3,5} \frac{4A}{n\pi} \text{Cos}\left(\frac{n\alpha}{2}\right) \text{Sin}\left(n\omega t - \frac{n\alpha}{2}\right)$
4.		$V_0 = \sum_{n=1,5,7} \frac{6A}{n\pi} \text{Sin}n\omega t :$ Each pulse width of 60° Duration

- For output of half wave uncontrolled rectifier Fourier series expression is


$$V_0 = \frac{A}{\pi} + \frac{A}{2} \sin \omega t + \sum_{n=2,4,6} \frac{2A}{\pi(1-n^2)} \cos n\omega t \quad ; \text{ Where } A = \text{Amplitude of signal}$$

- For output of Full wave uncontrolled rectifier Fourier series expression is

$$V_0 = \frac{2A}{\pi} + (\text{fundamental} = 0) + 2 \sum_{n=2,4,6} \frac{2A}{\pi(1-n^2)} \cos n\omega t$$

- Two switching quarter per cycle (topic of inverters):

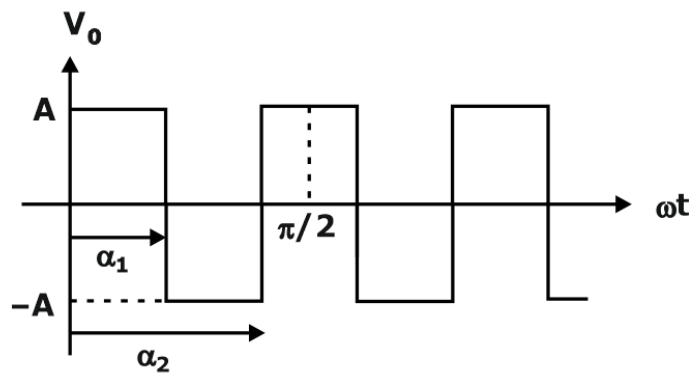Fourier series expansion is $V_0 = \frac{4A}{n\pi} (1 - 2 \cos n\alpha_1 + 2 \cos n\alpha_2)$




2. Power semiconductor devices

S.No	Device	Features
1	Diode	<ul style="list-style-type: none"> • Uncontrolled device • Unipolar and unidirectional
2	BJT/MOSFET/IGBT	<ul style="list-style-type: none"> • Fully controlled • Unipolar and unidirectional (Without body diodes)
3	SCR and GTO	<ul style="list-style-type: none"> • SCR-Semi controlled • GTO- Fully controlled • Both are Bipolar and unidirectional
4	TRIAC	<ul style="list-style-type: none"> • Semi controlled device • Bipolar and Bidirectional

- Conduction losses in BJT is less than MOSFET.
- Switching time in MOSFET is less than BJT.
- Majority carrier devices: MOSFET and Schottky diode are having positive temperature coefficient property.
- Minority carrier devices: SCR, BJT, GTO, IGBT, Power diode and having Negative Temperature Coefficient property.
- IGBT was developed in 1988 by combining the advantage of both BJT and MOSFET. IGBT possesses high input impedance like a MOSFET and has low on-state voltage as in a BJT. It does not suffer from secondary breakdown problems. The turn-on speed can be controlled by the rate of change of gate-source voltage.
- The turn-off time of IGBT consists of three intervals: (i) delay time, (ii) initial fall time (iii) final fall time.
- SIT is a high-power high-frequency solid-state semiconductor device. It is basically $n^+ n^- n$ device with a buried grid-like p^+ gate structure
- The SIT has been used in audio, VHF/UHF and microwave amplifiers. The reliability, noise, switching speed and radiation hardness of SIT are claimed to be superior to MOSFET. It has lower gate-to-source capacitance and resistance.
- SCR is a four-layer, three junctions, p-n-p-n switching device. It has three terminals namely anode, cathode, and gate. It is called SCR because silicon is used for construction and its operation is similar to a rectifier i.e., very low resistance in forward conduction and very high resistance in a reverse direction.
- SCR is a unidirectional device as the current can be low only from anode to cathode and it is a bilateral switch which means it can block the voltage of either direction. SCR does not allow conduction in forward direction until its gate terminal gets a proper triggering signal.
- SCR has three modes of operations:
 - i. Forward blocking mode
 - ii. Forward conduction mode
 - iii. Reverse blocking mode

- SCR can be turned-on by following methods:
 - i. Forward voltage triggering
 - ii. $\frac{dv}{dt}$ triggering
 - iii. gate triggering
 - iv. light triggering
- SCR turn-off means that it has changed from on to off state. SCR turn-off contains two steps:
 - (a) Reducing the anode current below holding current
 - (b) Removal of stored charges from the semiconductor layer
- Circuit turn-off time (t_c) is defined as the time between the instant anode current becomes zero and the instant reverse voltage due to the practical circuit reaches zero.
- For reliable turn-off t_c should be greater than t_{cr} , otherwise the device may turn on at an undesired instant, a process called commutation failure.
- For reliable and satisfactory operation of SCR, it must be protected against all abnormal conditions. These conditions are over voltages, over currents, high $\frac{di}{dt}$, false triggering due to high value of $\frac{dv}{dt}$ and spurious signal across gate-cathode terminal may lead to unwanted turn-on.
- By using a small inductor called a limiting inductor in series with the anode circuit can be used for $\frac{di}{dt}$ protection.
- If the rate of rise of the suddenly applied voltage across the thyristor is high the device may get turned on. Such phenomena of turning on a thyristor called $\frac{dv}{dt}$ turn-on, it must be avoided as it leads to false operation. False turn-on of an SCR by large change of voltage even without application of gate signal can be prevented by using a snubber circuit in parallel with the device.
- To suppress these over voltages, voltage clamping device is used. a voltage clamping device is a non-linear resistor connected across SCR. Voltage clamping device has falling resistance characteristic with increasing voltage. Under normal conditions the device has a high resistance and draws only a small leakage current. When a voltage surge appears, the voltage clamping device operates in lower assistance region and produces a short circuit across SCR.
- To protect SCR from overcurrent we can use two devices namely fast acting current limiting fuse (FACLIF), circuit Breakers.
- During conduction power loss occurs in SCR due to
 - i) Forward conduction loss
 - ii) gate triggering loss
 - iii) Switching loss
 - iv) loss due to leakage current


1. Static V-I characteristics of SCR:

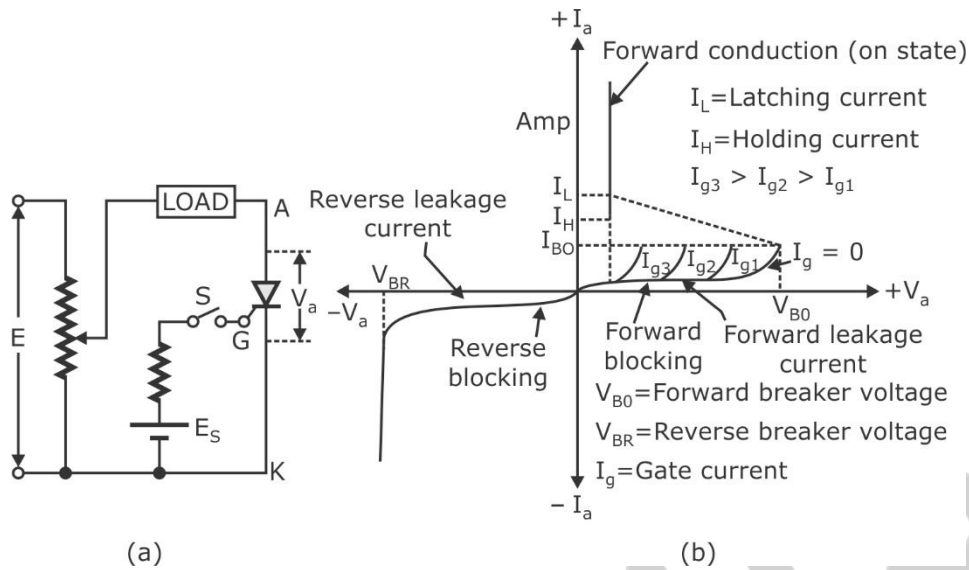

- Latching Current: Minimum current required for conduction even after the gate pulse is removed.
- Holding Current: Minimum Current below which SCR is turned off
- Usually Latching current is 1.5 to 3 times of Holding current

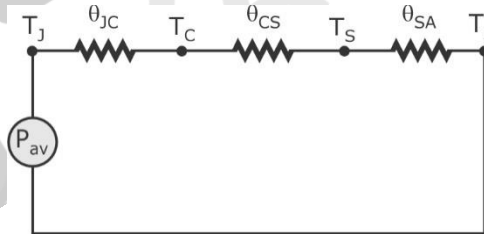2. Thermal equivalent circuit:

θ_{JC} is the thermal resistance between the junction and case
 θ_{CS} is the thermal resistance between the case and sink
 θ_{SA} is the thermal resistance between the sink and ambience



$$P_{avg} = \frac{T_J - T_C}{\theta_{JC}} = \frac{T_C - T_S}{\theta_{CS}} = \frac{T_S - T_A}{\theta_{SA}}$$

Rating of thyristor $\propto \sqrt{P_{avg}}$

3. Charge stored in depletion region:

Let Q_R be the charge stored in depletion region of power diode.

$$Q_R = \frac{1}{2} \cdot I_{RM} \cdot t_{rr}$$

$$I_{RM} = \frac{2Q_R}{t_{rr}} = t_a \cdot \frac{di}{dt}$$

$$\text{If } t_a \approx t_{rr}, t_{rr} = \sqrt{\frac{2Q_R}{di/dt}}$$

$$I_{RM} = t_{rr} \cdot \frac{di}{dt} = \sqrt{2Q_R \left(\frac{di}{dt}\right)}$$


$$t_{rr} \propto \sqrt{Q_R}$$

$$Q_R \propto I_f$$

$$t_{rr} \propto \sqrt{I_f}$$

$$I_{RM} \propto \sqrt{I_f}$$

4. Design of Snubber circuit:

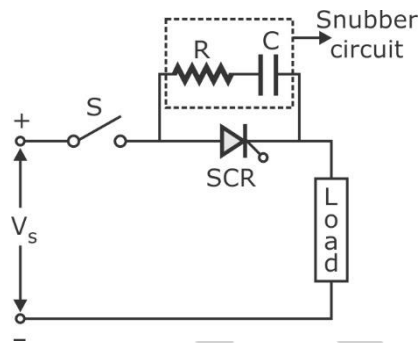

For Inductor (L):

$$\left(\frac{di}{dt}\right)_{\max} = \frac{V_s}{L}$$

$$L = \frac{V_s}{(di/dt)_{\max}}$$

For resistor (R):

$$\left(\frac{dv_s}{dt}\right)_{\max} = R \left(\frac{di}{dt}\right)_{\max}$$

$$\text{or } R = \frac{L}{V_s} \left(\frac{dv_s}{dt}\right)_{\max}$$

For Capacitor (C):

$$C = \left(\frac{2\xi}{R}\right)^2 L \quad \text{where } 0.5 < \xi < 1$$


5. Series and parallel operation of SCR:

- String efficiency = $\frac{\text{Actual voltage/current rating of string.}}{n \times \text{individual voltage/current rating of SCR}}$

Where n is the number of SCR in string.

Derating factor, DRF=1- string efficiency.

- Series operation:

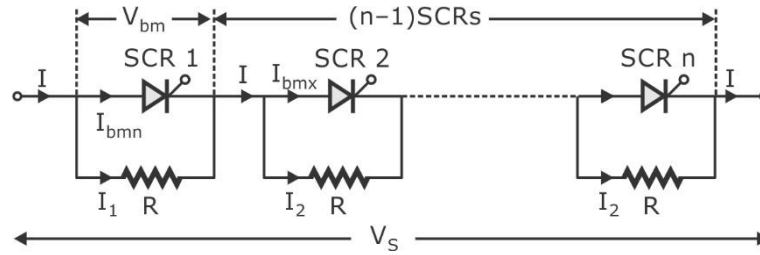


$$\text{Static equalizing resistance } R = \frac{nV_{bm} - V_s}{(n-1)\Delta I_b} \Omega$$


$$\text{Dynamic equalizing capacitance } C = \frac{(n-1)\Delta Q}{nV_{bm} - V_s} \text{ F}$$

- Parallel operation.

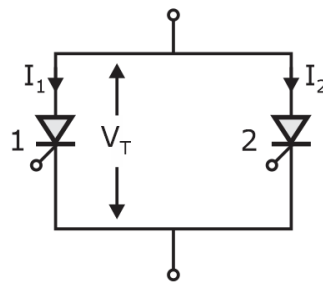When current required by the load is more than the rated current of a single thyristor, SCRs are connected in parallel.



(a)

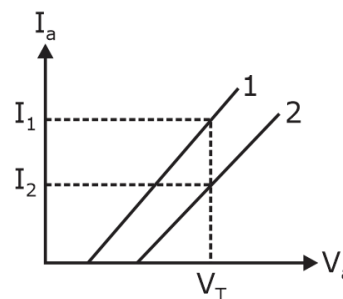

(b)

$$\text{String efficiency} = \frac{I_1 + I_2}{2I_1} = \frac{1}{2} \left(1 + \frac{I_2}{I_1} \right)$$

6. Ratings of Thyristors:

- 1) I_{Trms} Rating: The actual Thyristor rms in a converter must always be less than thyristor RMS ratings.

I_{Trms} value in a converter < I_{frms} rating.

- 2) I_{Tavg} Rating: (average on-state current ratings)

$$(I_{Tavg}) \text{ rating} = \frac{(I_T)_{rms} \text{ Rating}}{\text{Form Factor of thyristor current waveform}}$$

Average rating of a thyristor depends on:

- Conduction angle of thyristor increases which decrease the form factor and then increase the average thyristor rating.
- Type of load: Smoothness of thyristor current waveform increase the FF decreases and therefore $(I_{Tavg})_{Rating}$ increases.
- Type of converter: because FF of thyristor waveform depends on average value of converter.

3) I²t Rating of thyristor: specified to select a proper fuse for overcurrent protection.

I²t current Rating of thyristor > I²t current Rating of Fuse.

4) Surge current rating of thyristor:

General values

$$(I_T)_{rms} = 35A$$


$$(I_S)_{rms} = 2000A \text{ for one cycle and } 3000A \text{ for } 2MW$$

N-cycle surge current rating: (I_m): It is the surge current that the SCR can withstand for n-cycles.

$$(I_{Sn})^2 \left(\frac{nT}{2} \right) = I^2t \text{ rating of thy}$$
 from the equation, we can find the value of 'I_{sn}'

One-cycle surge current rating (I_s): It is the surge current that the SCR can withstand for a cycle. $I_{s1}^2 = (I_{sn})^2$ $I_{s1} = \sqrt{n} I_{sn}$

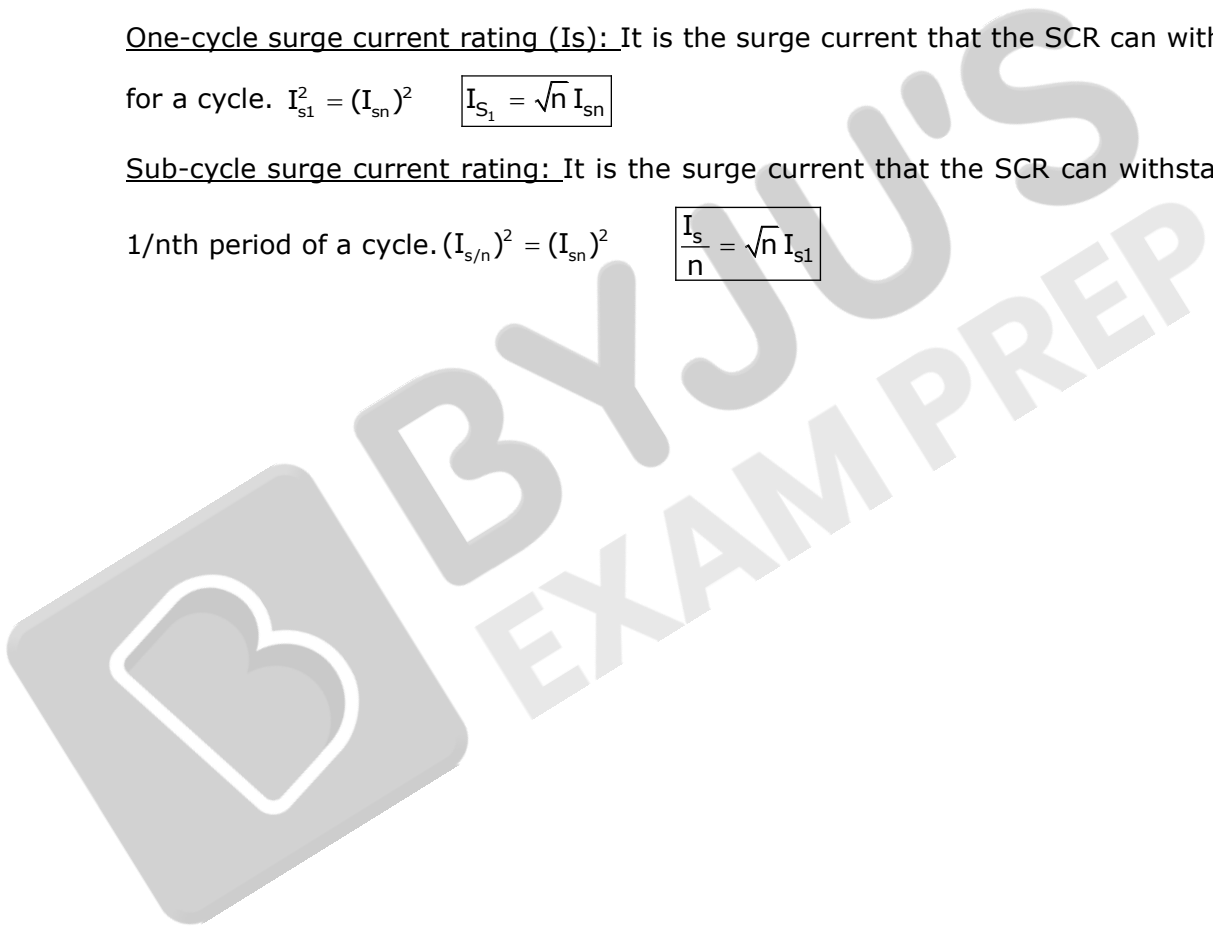Sub-cycle surge current rating: It is the surge current that the SCR can withstand for 1/nth period of a cycle. $(I_{s/n})^2 = (I_{sn})^2$ $\frac{I_s}{n} = \sqrt{n} I_{s1}$



3. RECTIFIERS

- For n-pulse converter:
 - Source current has $nk \pm 1$ Harmonics $k=1,2,3,\dots$
 - Output voltage has nk Harmonics.

1.Single Phase Half Wave controlled rectifier:

R-load:

Average output voltage $V_{o,avg} = \frac{V_m}{2\pi} (1 + \cos \alpha)$

RMS output voltage $V_{o,rms} = \sqrt{\frac{V_m^2}{4\pi} \left((\pi - \alpha) + \frac{\sin 2\alpha}{2} \right)}$

RL-Load:

Average output voltage $V_{o,avg} = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$

RMS output voltage $V_{o,avg} = \frac{V_m}{2\sqrt{\pi}} \left(\sqrt{(\beta - \alpha) + \frac{1}{2}(\sin 2\alpha - \sin 2\beta)} \right)$

Circuit Turnoff time: $t_c = \frac{2\pi - \beta}{\omega}$

For a constant output current refer below table:

	1- ϕ Full conv.	3 ϕ Full conv.	1 ϕ Semi conv.	3 ϕ semi conv.
Output voltage	$\frac{2V_m}{\pi} \cos \alpha$	$\frac{3V_{m,line}}{\pi} \cos \alpha$	$\frac{V_m}{\pi} (1 + \cos \alpha)$	$\frac{3V_{m,line}}{2\pi} (1 + \cos \alpha)$
Fundamental source current RMS (I_{s1})	$\frac{2\sqrt{2}}{\pi} I_0$	$\frac{\sqrt{6}}{\pi} I_0$	$\frac{2\sqrt{2}}{\pi} I_0 \cos\left(\frac{\alpha}{2}\right)$	$\frac{\sqrt{6}}{\pi} I_0 \cos\left(\frac{\alpha}{2}\right)$
Source current RMS (I_s)	I_0	$\sqrt{\frac{2}{3}} I_0$	$I_0 \sqrt{\frac{\pi - \alpha}{\pi}}$	$\alpha \leq 60^\circ \rightarrow I_0 \sqrt{\frac{2}{3}}$ $\alpha > 60^\circ \rightarrow I_0 \sqrt{\frac{\pi - \alpha}{\pi}}$
Displacement power factor (DPF)	$\cos \alpha$	$\cos \alpha$	$\cos\left(\frac{\alpha}{2}\right)$	$\cos\left(\frac{\alpha}{2}\right)$



- Distortion factor (DF) = $\frac{I_{s1}}{I_s}$
- Input power Factor= DF*DPF
- Total Harmonic distortion = $\sqrt{\left(\frac{1}{DF}\right)^2 - 1}$

For R-Load refer below table:

	3 φ Half wave rectifier	3 φ full wave rectifier
Continuous	$\alpha < 30^\circ$ $\frac{3V_{m,line}}{2\pi} \cos \alpha$ Hint: Integrate from $30+\alpha$ to $150+\alpha$ and Time period $T=120^\circ$ and function take in phase, you will get above formula Like this $\frac{1}{\left(\frac{2\pi}{3}\right)} \int_{30+\alpha}^{150+\alpha} V_{m,phase} \sin \omega t \, d\omega t$	$\alpha < 60^\circ$ $\frac{3V_{m,line}}{\pi} \cos \alpha$ Hint: Integrate from $60+\alpha$ to $120+\alpha$ and Time period $T=60^\circ$ and function take in line, you will get above formula
Discontinuous	$\alpha \geq 30^\circ$ $V_0 = \frac{3V_{m,phase}}{2\pi} \left(1 + \cos\left(\alpha + \frac{\pi}{6}\right)\right)$ Hint: Integrate from $30+\alpha$ to 180° and Time period $T=120^\circ$ and function take in phase, you will get above formula	$\alpha \geq 60^\circ$ $V_0 = \frac{3V_{m,line}}{\pi} \left(1 + \cos\left(\alpha + \frac{\pi}{3}\right)\right)$ Hint: Integrate from $60+\alpha$ to 180° and Time period $T=60^\circ$ and function take in line, you will get above formula

Effect of Source Inductance:

- 1 φ Half wave:

$$V_0 = \frac{V_m}{2\pi} (1 + \cos \alpha) - fL_s I_0$$

$$I_0 = \frac{V_m}{\omega L_s} (\cos \alpha - \cos(\alpha + \mu))$$

- 1 φ Full wave:

$$V_0 = \frac{2V_m}{\pi} \cos \alpha - 4fL_s I_0$$

$$I_0 = \frac{V_m}{2\omega L_s} (\cos \alpha - \cos(\alpha + \mu))$$

$$\text{Regulation} = \frac{\cos \alpha - \cos(\alpha + \mu)}{2 \cos \alpha}$$

Displacement power factor: $\cos\left(\alpha + \frac{\mu}{2}\right)$


➤ 3φ Full Wave:

$$V_0 = \frac{3V_{m,line}}{\pi} \cos \alpha - 6fL_S I_0$$

$$I_0 = \frac{V_{m,line}}{2\omega L_S} (\cos \alpha - \cos(\alpha + \mu))$$

Single Phase Full converter:


Source current waveform:

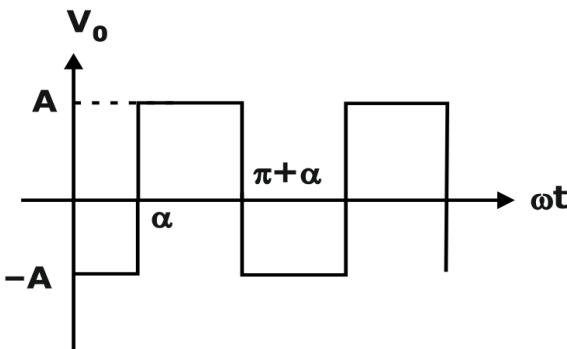

Fundamental source current is $i_{s1} = \frac{2\sqrt{2}}{\pi} I_0$

Single phase half controlled or Semi converter:

Source current waveform:

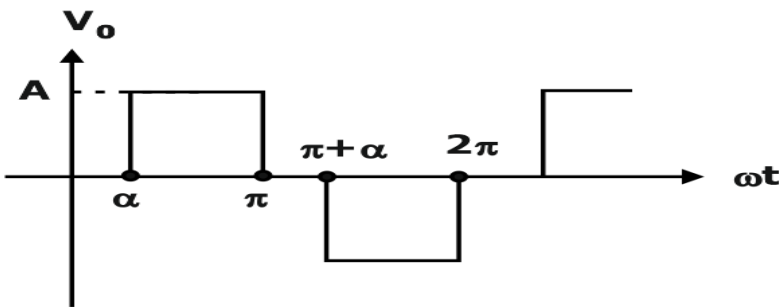

- In this there are two configurations:

Symmetrical configuration: On one leg one thyristor and one diode

Unsymmetrical configuration: on one leg two thyristors or two diodes

γ represents conduction in below table

D- Diode, T-Thyristor, α -Firing angle

Symmetrical configuration	Unsymmetrical configuration	Full converter with Freewheeling diode
$\gamma_T = \pi$	$\gamma_T = \pi - \alpha$	$\gamma_T = \pi - \alpha$

$\gamma_D = \pi$	$\gamma_D = \pi + \alpha$	$\gamma_D = 2\alpha$
------------------	---------------------------	----------------------

3-Phase:

3Phase half wave-controlled rectifiers:

- Take phase voltage reference in the integration function for the below mentioned limits for calculations
- For R-Load $\alpha < 30^\circ$
 $\alpha < 30^\circ$: Continuous conduction: $30 + \alpha$ to $150 + \alpha$
 $\alpha \geq 30^\circ$: Discontinuous conduction: $30 + \alpha$ to 180°
- For current stiff load:
 Without Freewheeling diode: $30 + \alpha$ to $150 + \alpha$
 With Freewheeling diode: $\alpha < 30^\circ$: $30 + \alpha$ to $150 + \alpha$
 $\alpha \geq 30^\circ$: $30 + \alpha$ to 180°
- Mentioned limits are useful while calculating output voltage average or RMS values for those particular conditions. Use phase as reference while doing calculations of average and RMS

3Phase full wave-controlled Rectifiers:

- Take Line voltage reference in the integration function for the below mentioned limits for calculations
- Limits are $60 + \alpha$ to $120 + \alpha$ for calculating output voltage average or RMS value
- Circuit Turnoff time:

$$\alpha \leq 60^\circ, t_c = \frac{240^\circ - \alpha}{\omega}$$


$$\alpha > 60^\circ, t_c = \frac{180^\circ - \alpha}{\omega}$$

3Phase semi converter:

- $\alpha < 60^\circ$ it is 6 Pulse converter
- $\alpha \geq 60^\circ$ it is 3 Pulse converter
- Freewheeling Action Duration:
 $\alpha < 60^\circ$, Duration = zero (No freewheeling action)
 $\alpha \geq 60^\circ$, Duration = $3\left(\alpha - \frac{\pi}{3}\right)$
- Limits for calculating output voltage average or RMS values (Line voltages are reference)
 $\alpha < 60^\circ$: $60^\circ + \alpha$ to $120^\circ \rightarrow V_{AB}$ reference
 : 120° to $180^\circ + \alpha \rightarrow V_{AC}$ reference
 $\alpha \geq 60^\circ$: $60^\circ + \alpha$ to $240^\circ \rightarrow V_{AC}$ reference

4. Commutation Techniques

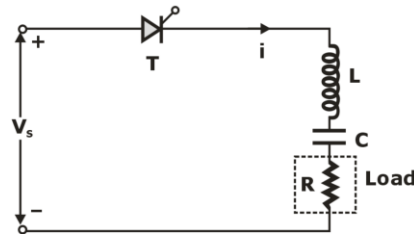1) Class A Commutation (Load Commutation/self-commutation)




- For successful Load commutation, circuit must be under damped
- For under damped $I = I_p e^{-\alpha t} \sin \omega_r t$

$$I_p = \frac{V_s}{\omega_r L}, \alpha = \text{Damping factor} = \frac{R}{2L}, \omega_r^2 = \omega_0^2 - \alpha^2$$

$$\omega_r \text{ is ringing frequency, } \omega_0 = \text{Natural frequency} = \frac{1}{\sqrt{LC}}$$

- Conduction time of thyristor, $t_c = \frac{\pi}{\omega_r}$

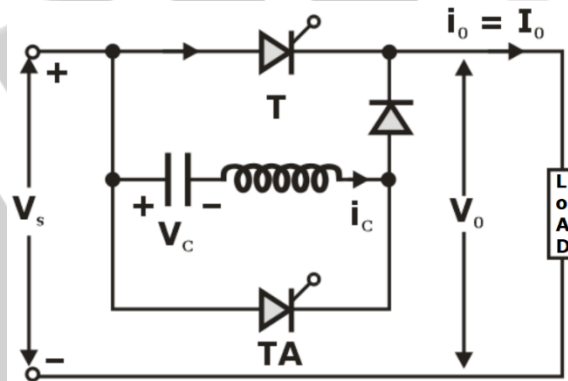2) Class B Commutation/Current Commutation/Resonant pulse commutation:



- Voltage across capacitor $V_c = V_s \cos \omega t$
- Circuit turn-off time for the main thyristor (T_1); $t_c = C \frac{V_{ab}}{I_0}$

$$V_{ab} = V_s \cos \omega_0(t_3 - t_2)$$

Where t_3 = time when the main thyristor is turned off

t_2 = time when auxiliary thyristor is turned off

$$\omega_0(t_3 - t_2) = \sin^{-1} \left(\frac{I_0}{I_p} \right)$$

- Main thyristor peak current = I_0
- Auxiliary Thyristor peak current = $V_s \sqrt{\frac{C}{L}}$
- Conduction time of auxiliary thyristor = $\pi \sqrt{LC}$


- Conduction time of main thyristor = $\pi\sqrt{LC} + \sqrt{LC} \sin^{-1}\left(\frac{I_0}{I_p}\right)$

Minimum Conduction time of main thyristor = $\pi\sqrt{LC}$

Maximum Conduction time of main thyristor = $\frac{3}{2}\pi\sqrt{LC}$

- Time for which capacitor current exists = $\frac{C}{I_0}(V_{ab} + V_s)$

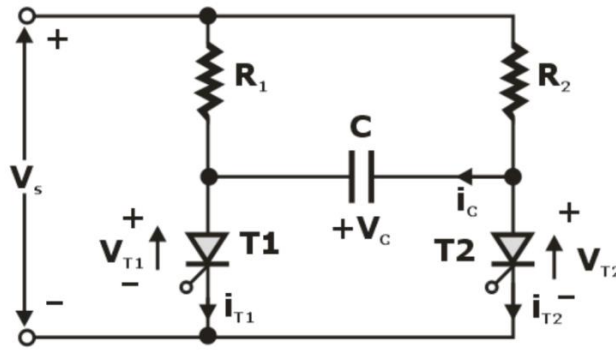3) Class C Commutation (Impulse/Complementary commutation):



When T_1 is turned on at $t=0$

- The charging current $I_s = \frac{V_s}{R_2} \cdot e^{-t/R_2 C}$

- Voltage across capacitor

$$V_c(t) = V_s(1 - e^{-t/R_2 C})$$

When T_1 is to be turned-off, T_2 is turned-on at T_1

- The charging current $I_c(t) = -\frac{2V_s}{R_1} \cdot e^{-t/R_1 C}$

- The Voltage across capacitor

$$V_c(t) = V_s[2e^{-t/R_1 C} - 1]$$

- Maximum current though thyristor T_1

$$I_{T_1(max)} = V_s \left[\frac{1}{R_1} + \frac{2}{R_2} \right]$$

- Maximum current though thyristor T_2 ,

$$I_{T_2(max)} = V_s \left[\frac{2}{R_1} + \frac{1}{R_2} \right]$$


Circuit turn-off time t_{c_1} for thyristor T_1

$$t_{c_1} = R_1 C \ln(2)$$

Circuit turn-off time t_{c_2} for thyristor T_2

$$t_{c_2} = R_2 C \ln(2)$$

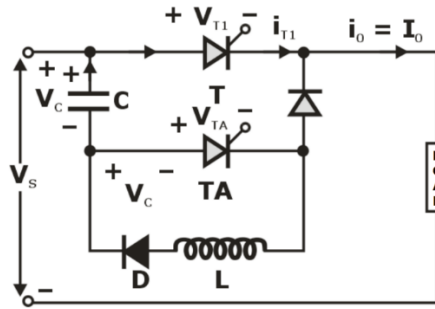4) Class D Commutation (Voltage commutation):




- Maximum thyristor current Peak = $I_o + V_s \sqrt{\frac{C}{L}}$
 - Auxiliary Thyristor peak current = I_o
 - Capacitor peak current = $V_s \sqrt{\frac{C}{L}}$
 - Circuit turn-off time for main thyristor T1 is $t_c = C \frac{V_s}{I_o}$
- For R-load: $t_c = RC \ln 2$
- Circuit turn-off time for main thyristor (TA)

$$t_{c1} = \frac{\pi}{2\omega_0}$$

5. DC-DC Converters

Buck Converter:

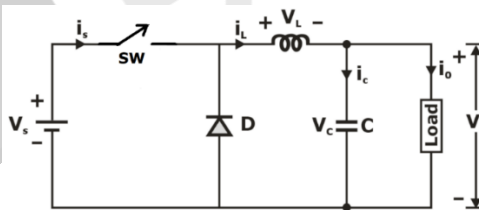

In Buck regulator, the average output voltage V_o is less than the input voltage V_s .

$$\Delta I = \frac{(V_s - V_o) T_{ON}}{L}$$

$$\Delta I = \frac{V_o T_{OFF}}{L}$$

$$V_o = V_s \frac{T_{ON}}{T} = V_s \alpha$$

Where $\Delta I = I_2 - I_1$ is the peak-to-peak current ripple of the inductor L.

The peak-to-peak ripple current is
$$\Delta I = \frac{V_s \alpha (1 - \alpha)}{fL}$$

The peak to ripple voltage of the capacitor is $\Delta V_C = \frac{V_S \alpha (1 - \alpha)}{8LCf^2}$

Condition for continuous inductor current and capacitor voltage:


If I_L is average inductor current, the inductor ripple current $\Delta I = 2I_L$, which gives the

critical value of the inductor L_c as $L_c = L = \frac{(1 - \alpha)R}{2f}$

If V_C is the average capacitor voltage, the capacitor ripple voltage $\Delta V_C = 2V_0$, which gives

the critical value of capacitor C_c as $C_c = C = \frac{1 - \alpha}{16Lf^2}$

Boost Converter:

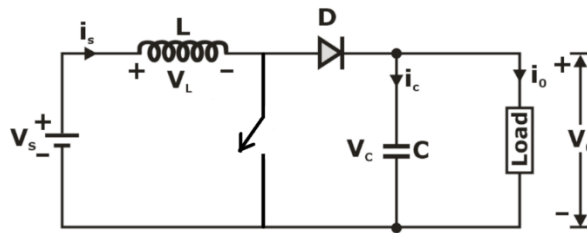

$$\Delta I = \frac{V_S T_{ON}}{L} = \frac{(V_0 - V_S) T_{OFF}}{L}$$

where $\Delta I = I_2 - I_1$ is peak to peak ripple current of the inductor L.

The average output voltage,

$$V_0 = V_S \frac{T}{T_{OFF}} = \left(\frac{1}{1 - \alpha} \right) V_S$$

The peak to peak current ripple is, $\Delta I = \frac{V_S \alpha}{fL}$

The peak to peak ripple voltage of capacitor, $\Delta V_C = \frac{I_0 \alpha}{fC}$

Condition of continuous inductor current and capacitor voltage:


If V_C is the average capacitor voltage, the capacitor ripple voltage $\Delta V_C = 2V_0$, which gives

the critical value of the capacitor C_c as $C_c = \frac{\alpha}{2fR}$

If I_L is average inductor current, the inductor ripple current $\Delta I = 2I_L$, which gives the

critical value of the inductor L_c as $L_c = L = \frac{\alpha(1 - \alpha)^2 R}{2f}$

Buck Boost Converter:

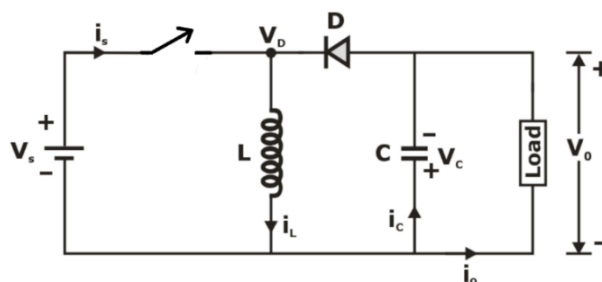

$$\Delta I = \frac{V_s T_{ON}}{L} = \frac{-V_0 T_{OFF}}{L}$$

where $\Delta I = I_2 - I_1$ is the peak to peak ripple current of inductor L.

The average output voltage is, $V_0 = -\frac{V_s \alpha}{1 - \alpha}$

The peak to peak current ripple is, $\Delta I = \frac{V_s \alpha}{fL}$

peak to peak ripple voltage of the capacitor is, $\Delta V_c = \frac{I_0 \alpha}{fC}$


Condition of continuous inductor current and capacitor voltage:

If V_c is the average capacitor voltage, the capacitor ripple voltage, $\Delta V_c = 2V_0$, which gives the critical value of the capacitor C_c as $C_c = \frac{\alpha}{2fR}$.

If I_L is average inductor current, the inductor ripple current $\Delta I = 2I_L$, which gives the critical value of the inductor L_c as $L_c = L = \frac{(1 - \alpha)^2 R}{2f}$

Expression for V_0	BUCK	BOOST	BUCK BOOST
In CCM	$V_0 = \alpha V_s$	$V_0 = \frac{V_s}{1 - \alpha}$	$V_0 = -\frac{\alpha V_s}{1 - \alpha}$
In DCM	$V_0 = \frac{\alpha}{\beta} V_s$	$V_0 = \frac{\beta V_s}{\beta - \alpha}$	$V_0 = -\frac{\alpha V_s}{\beta - \alpha}$

Steady State analysis of Type A Chopper:

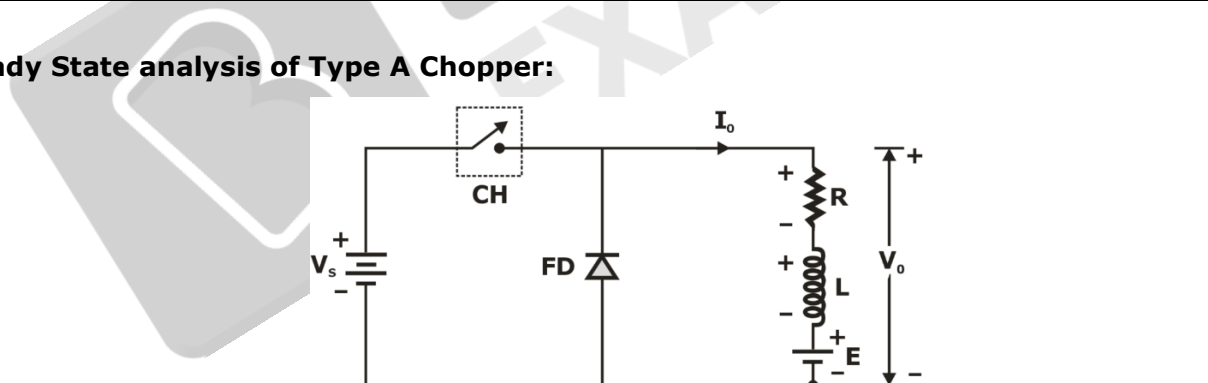

Average output voltage

$$V_0 = \alpha V_s$$

$$V_{or} = \sqrt{\alpha} V_s \text{ (Rms value of output voltage)}$$

$$I_{max} = \frac{V_s}{R} \left[\frac{1 - e^{-T_{on}/T_a}}{1 - e^{-T/T_a}} \right] - \frac{E}{R}$$

$$I_{min} = \frac{V_s}{R} \left[\frac{e^{T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right] - \frac{E}{R}$$


Where, $T_a =$ load time constant

$$T_a = \frac{L}{R}$$

Current ripple,

$$(\Delta I) = I_{\max} - I_{\min}$$
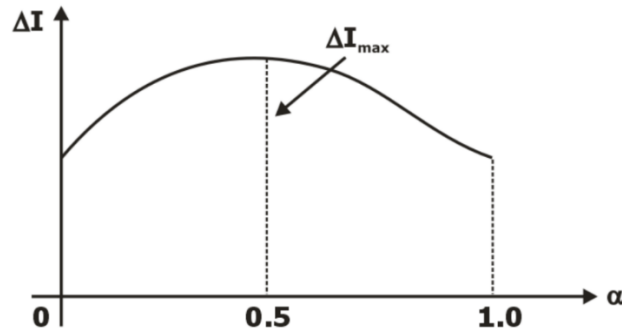
$$\Delta I = \frac{V_s}{R} \left[\frac{(1 - e^{-T_{on}/T_a})(1 - e^{-T_{off}/T_a})}{(1 - e^{-T/T_a})} \right]$$



$$T_{on} = \alpha T$$

$$T_{off} = (1 - \alpha) T$$

Per unit ripple (or) Ripple is a function of duty cycle ' α '. Ripple is minimum at $\alpha = 0$, increases maximum at $\alpha = 0.5$ and decrease at $\alpha = 1.0$. For $\alpha = 0.5$, ripple would be maximum.

$$(\Delta I)_{\max} = \frac{V_s}{R} \left(\frac{(1 - e^{-0.5x})(1 - e^{-0.5x})}{1 - e^{-x}} \right) \quad \left(\text{Let, } \frac{T}{T_a} = x \right)$$

$$(\Delta I)_{\max} = \frac{V_s}{R} \tanh\left(\frac{R}{4fL}\right)$$

6. Inverters

Series Inverters: In a series inverter, the commutating elements L and C are connected in series with the load resistance R. The load resistance R can also be in parallel with C. The value of L and C are such that those form an underdamped circuit i.e.

$$R^2 < \frac{4L}{C}$$

$$f = \left[\frac{1}{2\left(\frac{T}{2} + T_{off}\right)} \right]$$
 is the frequency of output voltage.

Where, $\frac{T}{2}$ is the time period of oscillations.

T_{off} is the time gap between turn-off one thyristor and turn-on of the second thyristor.

$$\frac{T}{2} = \frac{\pi}{\sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)}}$$

The period of oscillation

Bridge Inverter: Bridge circuits are commonly used in DC-AC conversion. Moreover, an output transformer is not essential in a bridge circuit.

1φ Half Bridge Inverter - The output voltage volt $V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin n\omega t$

1 φ Full Bridge Inverter- The output voltage

$$V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t$$

Where, n = order of harmonic

$\omega = 2\pi f$, is frequency of the output voltage in red/sec

Key points:

- The load impedance (Z_n) is

$$Z_n = \left[R^2 + \left(n\omega L - \frac{1}{n\omega C} \right)^2 \right]^{1/2}$$

- Phase angle, $\phi_n = \tan^{-1} \left[\frac{n\omega L - \frac{1}{n\omega C}}{R} \right]$

3phase Full Bridge VSI:

	180° Conduction	120° Conduction
Line Voltage RMS	$V_s \sqrt{\frac{2}{3}}$	$V_s \frac{1}{\sqrt{2}}$
Phase voltage RMS	$V_s \frac{\sqrt{2}}{3}$	$V_s \frac{1}{\sqrt{6}}$
Fundamental line voltage RMS	$V_s \frac{\sqrt{6}}{\pi}$	$V_s \frac{3}{\pi\sqrt{2}}$
Fundamental phase voltage RMS	$V_s \frac{\sqrt{2}}{\pi}$	$V_s \frac{1}{\pi} \sqrt{\frac{3}{2}}$

180° Conduction:

1) Pole Voltages = $V_{A0} = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin n\omega t$

2) Line Voltages = $\sum_{n=1,3,5} \left(\frac{4V_s}{n\pi} \cos\left(n\frac{\pi}{6}\right) \right) \sin(n(\omega t + 30^\circ))$

When n=3, 9, 15 Line voltage= 0, So Line voltages are free from Triplet harmonics

3) Phase Voltage = $\sum_{n=6k\pm 1} \frac{2V_{dc}}{n\pi} \sin n\omega t$

$n = 6k \pm 1$ is due to stepped waveform

120° Conduction:

- 1) Pole and Phase Voltage are of same waveform
- 2) Triplet harmonics are absent in Phase and pole voltages
- 3) Line voltage contains $n = 6k \pm 1$ Harmonics

Pulse Width Modulation:

Let N= number of pulses per half cycle

Each pulse width = $\frac{2d}{N}$

Then Output voltage Expression is

$$V_0 = \sum_{n=1,3,5} \left(N \frac{4V_s}{n\pi} \sin n\gamma \sin \frac{nd}{N} \right) \sin n\omega t$$

Where $\gamma = \frac{\pi - 2d}{N + 1} + \frac{d}{N}$

- Number of pulses per half cycle $N = \frac{f_c}{2f}$

f= reference input frequency

f_c = Carrier input frequency

- Modulation Index $m_a = \frac{V_{Ref}}{V_{carrier}}$
- Relation between Pulse width and modulation index

$$\frac{2d}{N} = \frac{\pi}{N} (1 - m_a)$$

Amplitude Modulation Depth:

$$m_0 = \frac{\hat{V}_m}{\hat{V}_c}$$

Where V_m, V_c are the modulating and carrier signal voltage peak values

For sinusoidal PWM, the amplitude modulation depth must be less than 1.0

Output Voltages by Sinusoidal PWM:

- In single phase half bridge VSI

Fundamental peak output voltage = $\hat{V}_{Ao1} = m_a \frac{V_s}{2}$

- In single phase Full bridge VSI

Fundamental peak output voltage = $\hat{V}_{Ao1} = m_a V_s$

- In Three phase Full bridge VSI

Peak Fundamental Phase voltage $\hat{V}_{an1} = m_a \frac{V_{DC}}{2}$

The fundamental line-line rms voltage is given by

$$V_{LLO1} = \frac{\sqrt{3}}{2\sqrt{2}} m_a V_{DC}$$

- If peak value of carrier input and zero crossing of reference sinusoidal coincidence then,

Number of Pulses per half cycle will be $N = \frac{f_c}{2f}$

If Zero Crossing of carrier input and reference sinusoidal coincidence then, Number of Pulses

per half cycle will be $N = \frac{f_c}{2f} - 1$

If N is the number of pulses per half cycle then the predominant harmonics in the output is

$2N \pm 1$